

EUROPEAN EDITION

# EDN<sup>®</sup>

ELECTRONIC TECHNOLOGY FOR ENGINEERS AND ENGINEERING MANAGERS WORLDWIDE

NEW! Use EDN's  
postage-paid reader-service  
cards for free product info

21 JUN 1993

A CAHNERS PUBLICATION

**April 29, 1993**

**Special Report:**  
**Mix ASIC models to win**  
**the simulation game pg 74**

## SPECIAL REPORT

**Multilevel ASIC  
modeling**  
pg 74

## DESIGN FEATURES

**ICs provide  
control for  
sensorless dc  
motors**  
pg 85

**Use Spice  
to analyze  
component  
variations in  
circuit designs**  
pg 109

**Fixed-point DSP  
chip generates  
real-time random  
noise**  
pg 119


## TECHNOLOGY UPDATE

**Low-power  $\mu$ Ps  
simplify design  
of portable  
computers**  
pg 39

**Product Updates**  
pg 51

**Processor Updates**  
pg 65

**Design Ideas**  
pg 127

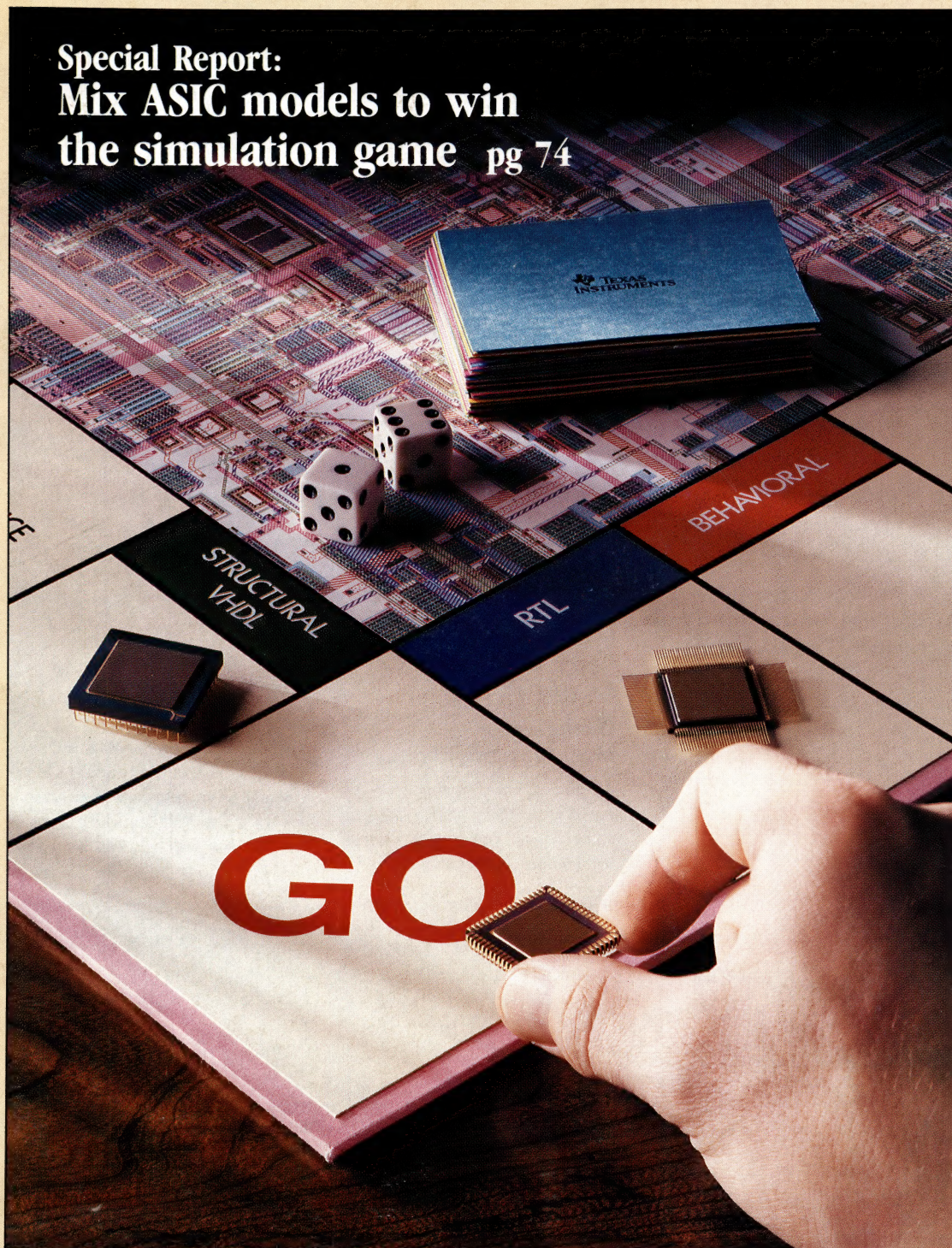





**On the cover:** Playing the multilevel ASIC modeling game requires finesse. Once you start off, you'll encounter ASICs with more than 20,000 gates, vendors with simulation secrets, and some closely held intellectual property. Instead of rolling the dice, read the Special Report for ways to make multilevel modeling easier. (Photo courtesy Texas Instruments Inc; art direction, Ken Martin; photography, Cece Cox) . . . . . **PAGE 74**

### Foldout Contents

Turn to the last information-retrieval service card in the back of this magazine and you'll find a foldout table of contents. Now, instead of flipping back and forth from this table of contents to the articles you want to read, you can have the convenient foldout open at all times while you're reading EDN. Use the foldout contents to mark off articles you'd like your colleagues to read or to remind yourself to copy stories for your files.



### SPECIAL REPORT

## Multilevel ASIC modeling

**74**

Model accuracy and speed, intellectual-property concerns, and the lack of standard model formats will force you to mix gate- and higher-level models to simulate complex ASICs.—*John C Napier, Technical Editor, with Julie Anne Schofield, Senior Associate Editor*

### DESIGN FEATURES

## ICs provide control for sensorless dc motors

**85**

The need for low-cost, highly reliable, miniature, brushless dc motors has given rise to a new class of devices—sensorless dc motors.—*Dave Peters and Jeff Harth, Silicon Systems Inc*

## Use Spice to analyze component variations in circuit designs

**109**

If you already use Spice to simulate circuits, you can easily use Monte Carlo methods to investigate the effects of component variation on circuit performance.—*George Ellis, Kaydon Corp*

## Fixed-point DSP chip can generate real-time random noise

**119**

An inexpensive, 16-bit, fixed-point DSP chip can generate real-time pseudorandom noise signals for testing the performance of telephony systems in the presence of noise.—*Bill Salibrici, TeleSciences Co Systems*

### TECHNOLOGY UPDATE


## Low-power $\mu$ Ps simplify design of portable computers

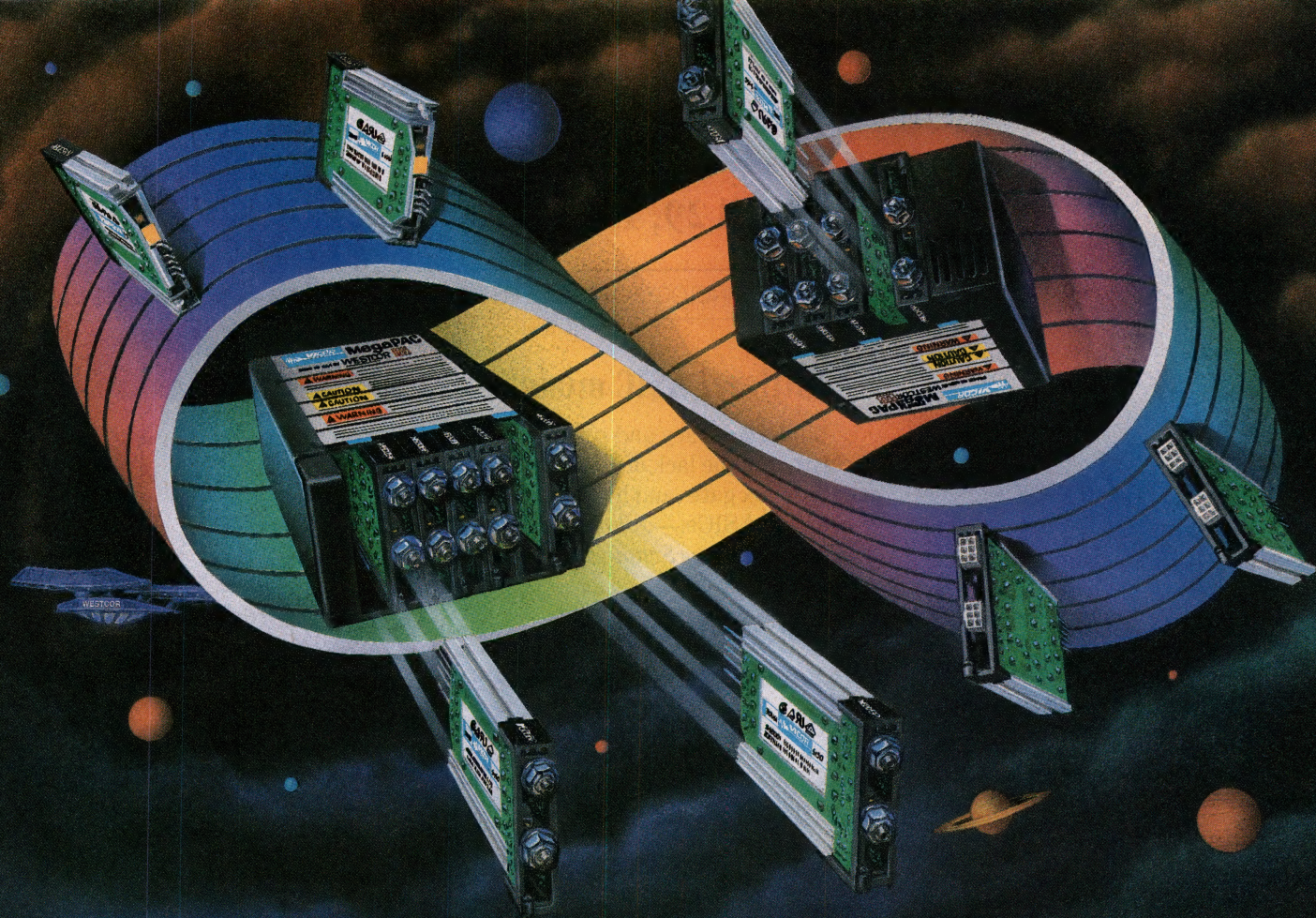**39**

At the heart of portable computers are  $\mu$ Ps with sophisticated power-management features that conserve battery life.—*John Gallant, Technical Editor*

EDN® (ISSN 0012-7515, GST Reg. #123397457) is published 48 times a year (twice monthly with 2 additional issues a month, except for March and October, which have 3 additional issues and July and December which have 1 additional issue) by Cahners Publishing Company, A Division of Reed Publishing USA, 275 Washington Street, Newton, MA 02158-1630. Frank J Sibley, Executive Vice President/Business Publishing; Jerry D Neth, Executive Vice President/Publishing Operations; Michael Wisner, Senior Vice President/General Manager, Boston Division; J J Walsh, Senior Vice President/Finance; Thomas J Dellamaria, Senior Vice President/Production and Manufacturing; Ralph Knupp, Senior Vice President/Human Resources; Steve Thompson, Senior Vice President/Corporate Marketing; Daryl Otte, Vice President/Planning. EDN® is a registered trademark of Reed Properties Inc., used under license. Circulation records are maintained at Cahners Publishing Company, 44 Cook Street, Denver, CO 80206-5800. Telephone: (303) 388-4511. Second-class postage paid at Denver, CO 80206-5800 and additional mailing offices. **POSTMASTER: Send address changes to EDN®, PO Box 173377, Denver, CO 80217-3377.** Rates for non-qualified subscriptions: US, \$159.95 one year, \$271.95 two year; Canada, \$240.70 one year, \$408.95 two year (includes 7% GST, GST# 123397457); Mexico, \$224.95 one year, \$381.95 two year; Foreign surface \$265.95 one year, \$451.95 two year; Foreign air expedited surcharge add \$192.00 one year, \$384.00 two year. Except for special issues where price changes are indicated, single copies are available for \$20.00 US and \$25.00 foreign. Please address all subscription mail to Ellen Porter, EDN Circulation Manager, 44 Cook Street, Denver, CO 80206-5800. (Printed in U.S.A.)





# Endless Power Options

## Field-Configurable MegaPAC™ Switching Power Supplies

Your opportunities are endless to mix and match MegaPAC options. And with so many possible power solutions available, you can define one precisely to fit *your* needs.

But MegaPAC flexibility doesn't end there. If your needs change, so can your switcher ...which gives you another reason to choose MegaPAC power supplies: they're *the only field-configurable power supplies* on the market. To alter voltage or power levels on site, just loosen a screw, slide out a ModuPAC converter assembly, and slide in a new one. It's that simple.

Take a look at our new additions to the MegaPAC family, highlighted at right.

For details about MegaPAC switching power supplies, call Vicor Express at 800-735-6200 or Vicor's Westcor Division at 408-395-7050 (FAX 408-395-1518).

### Size Options

- **MegaPAC**—8 ModuPAC slots  
11.8"L x 6.0"W x 3.4"H
- **Mini MegaPAC**—5 ModuPAC slots  
9.4"L x 6.0"W x 3.4"H **NEW smaller size!**

### Input Options

- 120/240 VAC strappable
- 120/240 autostrapping universal input  
**NEW! Automatically senses line voltage and straps power supply accordingly.**
- 85-264 VAC universal input with power factor correction **NEW! Meets IEC 555.**

### Output Options

- Up to 1600 watts total
- Up to 100 or up to 200 watts per output
- 1-16 outputs, isolated & fully regulated
- 1 to 95 VDC

### ModuPAC slide-in converter assemblies:

- Standard—one output, up to 200 watts
- **NEW DualPAC™**—two outputs, up to 100 watts each
- **NEW TachoPAC™**—for fast transient response to high-speed load changes
- **NEW RamPAC™**—for very low noise
- **NEW VXI Option**—for low noise and low ripple to meet instrumentation standard VXI

### Family Options

- DC OK (Power Good)—TTL signal high when output is  $\geq 90\%$  of nominal
- Trim range  $\pm 10\%$  or 40-110% of nominal
- Industrial or military grade modules
- Hardwired local sense
- Enable/Disable—TTL signals inhibit or enable each output; includes one-pin global shutdown

## Component Solutions For Your Power System

Vicor Corporation • 23 Frontage Rd., Andover, MA. 01810 USA • TEL: (508) 470-2900 • FAX: (508) 475-6715


Vicor GmbH • Tel: +49-89-329-2763 • Fax: +49-89-329-2767 • Vicor Far East • Tel: +886-2-9188240 • Fax: +886-2-9132982

CIRCLE NO. 121






# UNITED WE SERVE

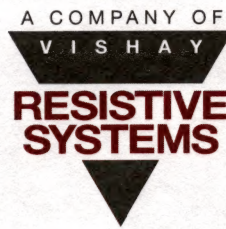


In recent years, four respected organizations have evolved into a united, service-oriented source for passives. You already know us as Dale®, Roederstein, Sprague® and Vishay Resistive Systems. But, you'll come to know us better as partners within Vishay Electronic Components. Better, because the time is right to strategically utilize a single, coordinated passives source in meeting the challenges of global marketing. And we are that source. With unmatched depth and versatility in resistors, tantalum and film capacitors, and magnetic components, plus trimmers, potentiometers, thermistors, EMI/RFI filters, oscillators, connectors and displays. To find out more about Vishay Electronic Components: (1) Write for your copy of a management presentation outlining how we're structured to help you be more competitive and; (2) Make us prove it. Fax 1-800-835-4272 or write c/o Management Report, Vishay Electronic Components, U.S., P.O. Box 609, Columbus, Nebraska 68602-0609.

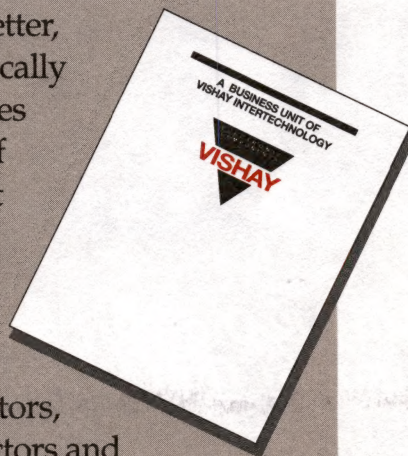



**RC TOKO**  
TOKO AMERICA, INC.

**FOR ALL YOUR  
DESIGN NEEDS**

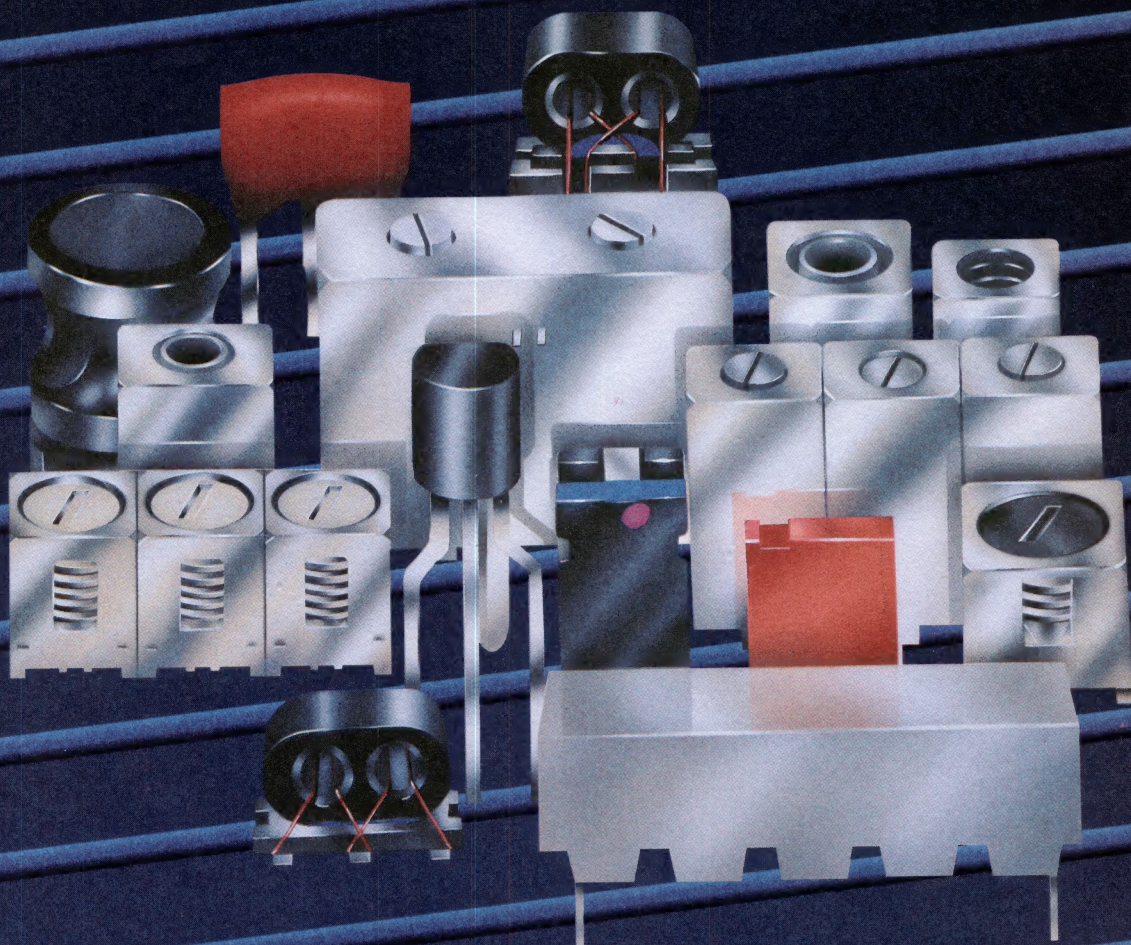

**Toko Quality & Digi-Key Service**  
**A Combination That Works For You**

- Coils, Molded Coils
- Fixed Inductors
- Surface Mount Inductors
- AM/FM Ceramic Filters
- Helical Filters
- Active Filters
- Ceramic Resonators
- Delay Lines
- DC-DC Converters
- Balun Transformers
- Voltage Regulators
- Switching Power Supplies

**Call, write or fax for  
YOUR FREE catalog today!**

**Digi-Key<sup>®</sup>**  
CORPORATION

701 Brooks Ave. South, Thief River Falls, MN 56701  
Toll Free: 1-800-344-4539, Fax: 218-681-3380



## Home Office

275 Washington St, Newton, MA 02158  
EDN Bulletin Board: (617) 558-4241  
MCI: EDNBOS  
Phone (617) 558- plus 4-digit extension below  
Fax (617) 558-4470

To send a message to an EDN editor via Internet, add "@MCIMAIL.COM" to his or her MCI address.

## Vice President/Publisher

Roy Forsberg -4367

## VP/Editorial Director

Jonathan Titus -4573

## Editor

Steven H Leibson -4214

## Managing Editor

Joan Morrow Lynch -4215

## Assistant Managing Editor

Anne Connors -4653

Gary Legg, Senior Technical Editor -4404

Tom Ormond, Senior Technical Editor -4414

Charles Small, Senior Technical Editor -4556

MCI: EDNSMALL; Compuserve: 70324, 3270

Dan Strassberg, Senior Technical Editor -4205

MCI: EDNSTRASSBERG

John A Gallant, Technical Editor -4666

Julie Schofield, Senior Associate Editor -4619

James P Leonard, Associate Editor -4324

Susan Rose, Associate Editor -4738

Gillian A Caulfield, Production Editor -4263

Erin Heffernan, Production Editor -4333

Doug Conner, Technical Editor  
Atascadero, CA: (805) 461-9669  
MCI: EDNDCONNER

Richard A Quinnell, Technical Editor  
Aptos, CA: (408) 685-8028  
MCI: EDNQUINNELL

David Shear, Technical Editor  
Corvallis, OR: (503) 754-9310  
MCI: EDNSHEAR

Anne Watson Swager, Technical Editor  
Wynnewood, PA: (215) 645-0544  
MCI: EDNSWAGER

Ray Weiss, Technical Editor  
Woodland Hills, CA: (818) 704-9454  
MCI: EDNWEISS

Brian Kerridge, Technical Editor  
22 Mill Rd, Loddon  
Norwich, NR14 6DR, UK  
(508) 28435  
MCI: EDNKERRIDGE

EDN Asia, Mike Markowitz, Editor  
Cahners Asia Limited  
19th Floor, Centre Point  
181-185 Gloucester Rd, Wanchai, Hong Kong  
Phone (852) 838-2666; fax (852) 575-1690

## Contributing Technical Editors

Robert Pease, Don Powers, Dave Pryce,  
Bill Travis

## Editorial Coordinator

Kathy Leonard -4405

## Editorial Services

Helen Benedict -4681

Bobby Cooper -4603

## Art Staff

Robert L Fernandez, Art Department Director  
Ken Racicot, Senior Art Director -4708  
Chinsoo Chung, Associate Art Director -4446  
Ana Murdock, Staff Artist -4695

## Marketing & Business Director

Deborah Virtue -4779

## Marketing Communications

Kathy Calderini, Manager -4526

Pam Wilson, Promotion Specialist -4660

## PRODUCT UPDATES

Firms reduce the cost of color in DSO displays	51
Mathcad 4.0 for Windows 3.1	57
14- and 16-bit ADCs speed past 1-MHz	58
Video op-amp prices drop to new depths	60

## PROCESSOR UPDATES

68360 comm controller moves to 32 bits	65
24-bit DSP chip drops to 165 mW at 40 MHz	66
TMS370C moves up to 32 kbytes of ROM/EPROM	66
Drive an 8-bit PIC $\mu$ C with Basic	68

## DESIGN IDEAS

Software extends ac current probe's range	127
Solid-state fuse resets itself	128
Address latch increases $\mu$ P's data width	130
Reset trap locates system errors	132


## NEW PRODUCTS

Integrated Circuits. . . . .	135
Components & Power Supplies. . . . .	139
Computers & Peripherals. . . . .	145
Test & Measurement Instruments. . . . .	148
CAE & Software Development Tools. . . . .	155


## DEPARTMENTS

Inside EDN. . . . .	9
News Breaks. . . . .	17
Ask EDN. . . . .	25
Editorial. . . . .	31
Career Opportunities. . . . .	168
EDN's International Advertisers Index. . . . .	172
Hands On!. . . . .	175



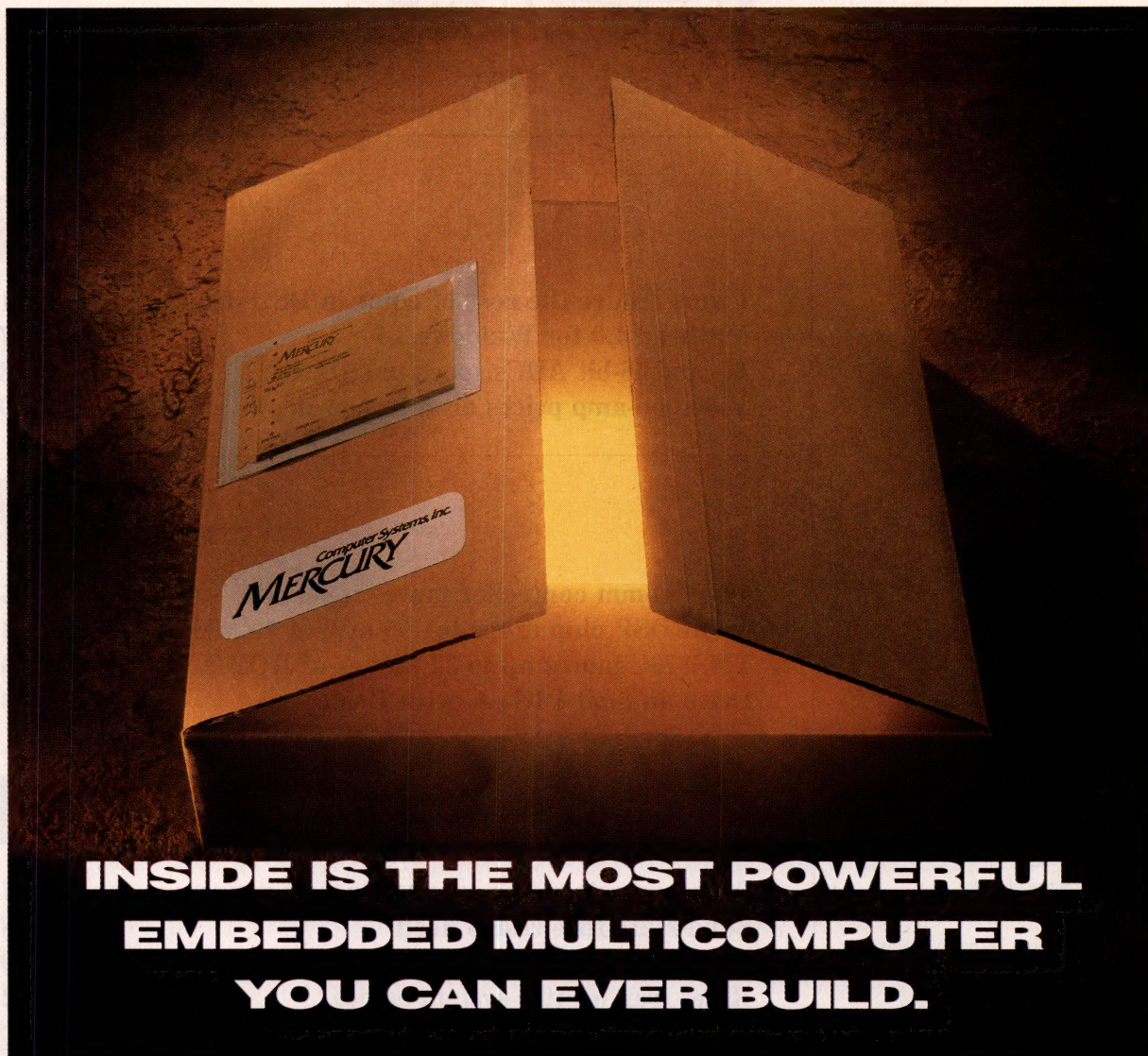

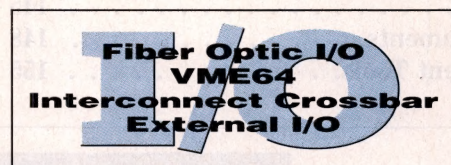Open up to Mercury's embedded realtime multicomputer solutions. Because of a balanced architecture, our multicomputers deliver scalable performance into the tens of GFLOPS, with GBytes of I/O to match. With interboard and interchassis communications, you can build a solu-



tion to satisfy even the most demanding applications within your constraints of cost, space, and power consumption.

Mercury's commercial and ruggedized multicomputers are supported by our standards-based realtime operating system software, including advanced multicomputing development tools that enable you to harness the power of hundreds of processors.

For more information on our commercial off-the-shelf (COTS) products and to receive our White Paper:

**Balancing I/O and Computation, call Mercury toll free today at 1-800-229-2006 or (508) 256-1300.**

Computer Systems, Inc.  
**MERCURY**

**The Ultimate Performance Machine.**  
199 Riverneck Rd., Chelmsford, MA 01824-2820



## A summary and analysis of articles in this issue

Sooner or later, improvements and advances in technology are going to affect you and your products. The articles in this issue of EDN concentrate on some of those developments that may not affect you today, but that you may soon need to consider. Many of those developments are the same story: Some things get bigger so that everything else can get smaller and cheaper. Of course, that doesn't always make your life easier right away.

In the Special Report on **Multi-level ASIC modeling**, John Napier and Julie Anne Schofield explore the problems you'll encounter if you decide to put a  $\mu$ P on your ASIC. Gate counts on ASICs are growing rapidly. Although you may not use an ASIC with more than 20,000 gates today, chances are you will by the end of the year. So, now that there is room to stick a  $\mu$ P on an ASIC, you have to figure out how to model the ASIC to make sure it works.

Sounds simple, but as John reveals on this issue, "capitalism collides with engineering." Semiconductor vendors won't give you detailed simulation models of their chips because they don't want you to reverse engineer them. But they will give you higher-level models. That leaves you with the problem of how to perform multilevel modeling. John explores some of the techniques that make multilevel modeling easier as well as tackling the issue of intellectual property.

John Gallant's Technology Update on **low-power  $\mu$ Ps** looks at the power-management ICs that help you extend battery life in your portable application. "In the late 80s and early 90s, a trend emerged toward putting power equivalent to a desktop PC in portable applications. To do that, you have to be very clever about how you conserve power," says John. "Handheld communicators that keep you in constant contact with home and office

is just right around the corner." With that in mind, John gives a survey of popular low-power processors for battery applications and the power-management techniques that will help make personal communicators a reality.


In our Design Features, EDN looks to experts in the field to give insight into other trends. Dave Peters and Jeff Harth of Silicon Systems Inc discuss how **ICs provide control for sensorless dc motors**. Sensorless dc motors are replacing the Hall-effect sensors normally used for motor control. These small, inexpensive, and reliable motors particularly suit rotating-memory, process-control, VCR, fan-motor, heat-pump, environmental-control, robotics, automotive, and toy applications.

Bill Salibrici of TeleSciences Co Systems explores **more uses for DSP chips** in his article. He discusses how you can use a 16-bit fixed-point DSP chip to generate real-time, pseudorandom uniform- or Gaussian-distributed noise signals. These signals can be useful in testing digital filters, in implementing tone detection, in spectral estimation, or for speech-synthesis functions, as well as many other DSP applications.

As the industry changes, so does EDN. EDN is always open to the suggestions of its readers. When we hear an idea we think makes sense, we are happy to implement it. And, if several people suggest something, we figure it's definitely a good idea. Many of you requested reader-service numbers on News Breaks. You've got it. By circling the appropriate number and returning your postage-paid reader-service card to EDN, you will receive free information about the products, trends, and technologies covered in the News Breaks section. Keep the good ideas coming.

Susan Rose  
Associate Editor

## ULTRA-MINIATURE SURFACE MOUNT

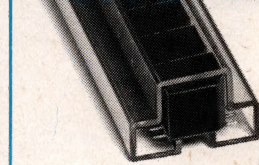

Actual Size

## DC-DC Converter Transformers and Power Inductors

All PICO surface mount units utilize materials and methods to withstand extreme temperature (220°C) of vapor phase, IR, and other reflow procedures without degradation of electrical or mechanical characteristics.

These units have gull wing construction and are packaged in shipping tubes, which is compatible with tube fed automatic placement equipment or pick and place manufacturing techniques. Transformers can be used for self-saturating or linear switching applications. The Inductors are ideal for noise, spike and power filtering applications in Power Supplies, DC-DC Converters and Switching Regulators.

- Transformers have input voltages of 5V, 12V, 24V and 48V. Output voltages to 300V.
- Transformers can be used for self-saturating or linear switching applications
- Schematics and parts list provided with transformers
- Inductors to 20mH with DC currents to 23 amps
- Inductors have split windings

Delivery—  
stock to one week

See EEM  
or send direct for  
FREE PICO Catalog

## PICO Electronics, Inc.

453 N. MacQuesten Pkwy. Mt. Vernon, N.Y. 10552

Call Toll Free **800-431-1064**


IN NEW YORK CALL **914-699-5514**

FAX **914-699-5565**

CIRCLE NO. 76

EDN April 29, 1993 • 9



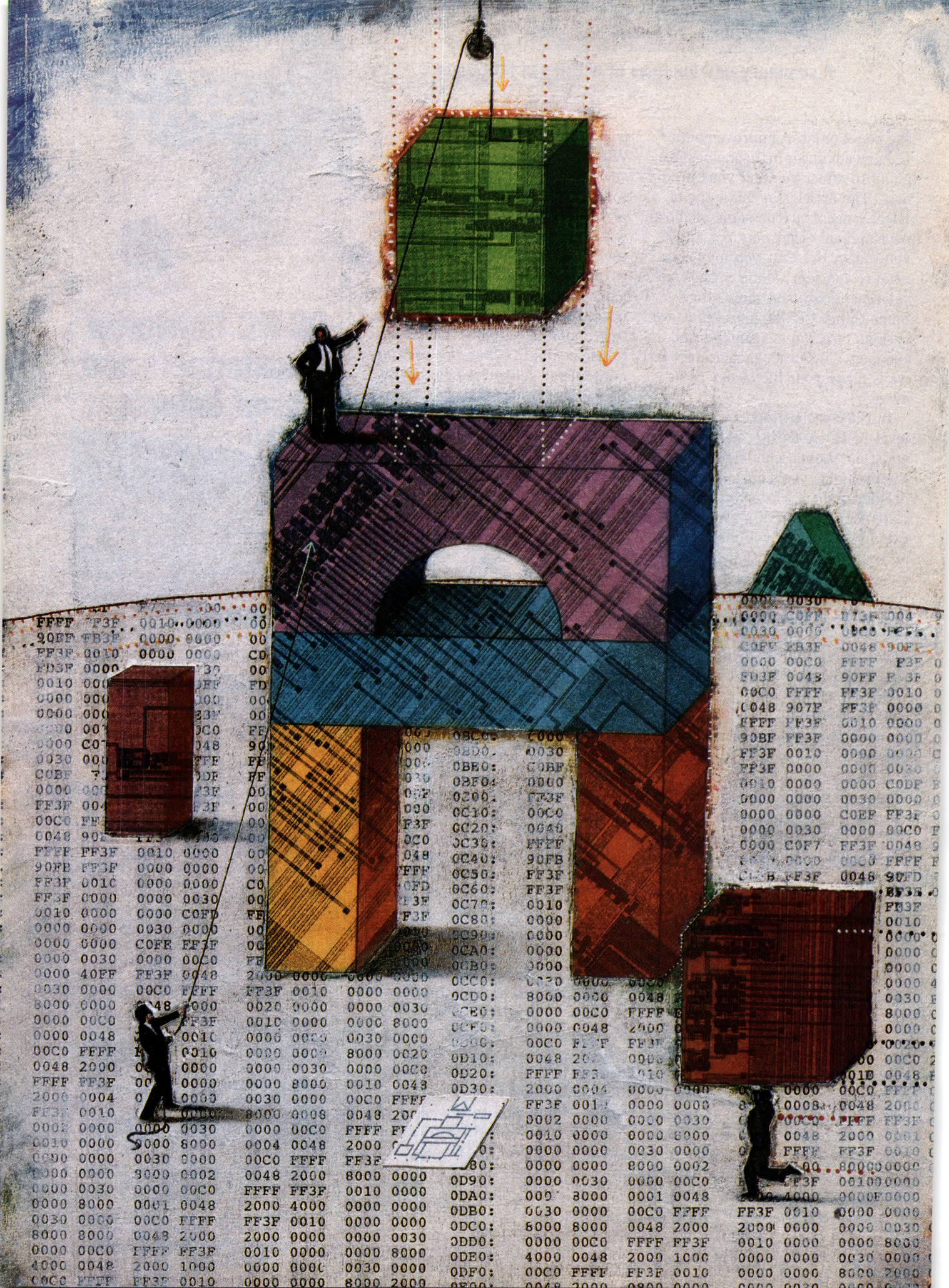



# Advanced tools that help you build upon what you've already built. That's Total Integration.

Moving quickly from concept to silicon requires the right development tools. That's why providing you with powerful but user-friendly tools is a part of our Total Integration™ commit-

ment. It's why we're committed to the establishment of open, industry-standard hardware and soft-

ware tools that are compatible with those you already have. And — just as we have developed reusable silicon methodologies — so we maintain the same philosophy when it comes to creating powerful customer tools. When you need to combine your functions with ours, it's an approach that will save you time and money.


You need core tools for core functions. Our hardware and software development tools enable you to adapt our advanced core functions to your system quickly and easily.

For example, our DSPs are world-class, so we provide a development environment to match. It includes high-level-language optimising compilers, multitasking operating systems, real-time emulation and more than 100 third-party developers for additional support. It's as comprehensive and easy to work with as your general-purpose microprocessor environment. But that's not all.

**Opening the door to open tools.** To help you move to your next level of integration we've



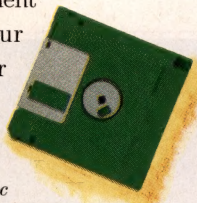*Working closely with Cadence Design Systems, we will install the ASIC WorkBench™ in all world-wide TI design centres.*



*Our Logic Integration Software Tool™ provides a simple analysis tool to help you determine what complexity of product is optimal for your design: PLDs, FPGAs or gate arrays.*

defined new commercial flows with leading software and hardware vendors like Mentor Graphics and Cadence Design Systems. After all, the faster you complete your product design, the faster you get to market.

As a result of our combined efforts with Mentor, we are defining an open, industry-integrated tool set for combining complex mixed-signal functions.

*Our DSP starter kit is the lowest cost tool available for first-time DSP users who want to begin the evaluation process.*



This allows for on-chip integration of linear, power, micro-controller and logic functions. Our team-


work with Cadence is resulting in a next-generation, beginning-to-end design environment for ASIC solutions. Then, with early simulation and testing, TI can help you avoid time-consuming alterations and begin the process of designing complex silicon.

**Tools that simulate and test.** To help compress your design cycle, and make your life easier, we work with Logic Modeling Corporation to provide one of the industry's most extensive libraries of simulation and behavioural models. And we offer a broad family of devices specially designed for rapid implementation of testability within systems.

Assisting you to build the bridge to silicon integration with tools that enable you to get to market faster — that's just one part of Total Integration. Because Total Integration from Texas Instruments unites our best technologies, tools, information, people and services to help you extend your reach.

Texas Instruments, BP 5, MS 94, 06271  
Villeneuve Loubet cedex, France.

## EXTENDING YOUR REACH WITH TOTAL INTEGRATION™

 **TEXAS  
INSTRUMENTS**



As the FIRST at 60 ns, they're  
*The* FASTEST  
2-MEG VRAMs.

[We suspect you'll also be *quick* to USE them.]

Available in production quantities right now, Samsung's 60 ns, 2-meg VRAM is the fastest in the world. And it's making us one of the leaders in video products.

But it will also do some remarkable things for you. Which

means you may want to start putting this extremely fleet VRAM to use in a hurry.

You'll have all the low-parts-count, low-power and low-capacitance advantages of a 2-meg. But you'll also have the advantages of

speed—with a 40 ns cycle time for Fast Page Mode, and an 18 ns tRSCC. Which will result in faster image creation, and will also make it easier to drive high resolution and high refresh rates.

Those things, in turn, will



*Samsung's broad line of VRAMS.*

PART	ORG.	FASTEST SPEED
KM428C256	256K x 8	60 ns
KM428CI28	128K x 8	60 ns
KM424C257	256K x 4	60 ns
KM424C64	64K x 4	100 ns

*All parts in production quantities now.*



enhance the image-making powers of the video products you use them in. And improve your own image as well.

At Samsung, our extremely fast VRAMS are further advancing our leadership position in memory

products. And, like our cutting-edge static RAMs, they build on our remarkable achievement in building the world's first 16-meg DRAM.

To learn more about video RAMs with Mercury-like speed, please contact us at 1-800-446-2760 or


408-954-7229 today.

Or write to VRAM Marketing, Samsung Semiconductor Inc., 3655 North First St., San Jose, CA 95134.



*A Generation AHEAD.*



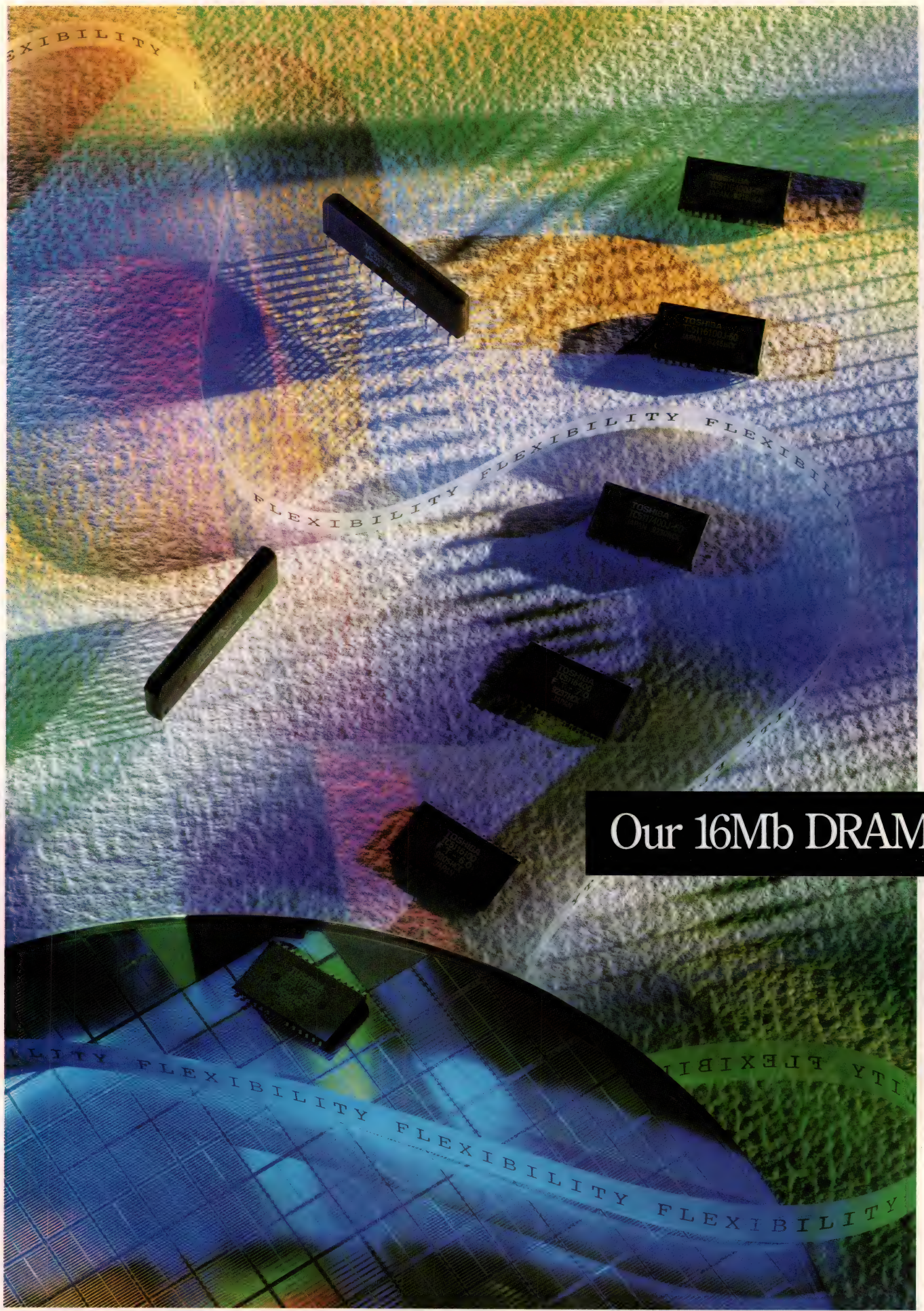

Our 16Mb DRAMs



When's the right time to cross over from 4Mb to 16Mb DRAMs?

When you can get access times as quick as 60ns, a greater than four-fold drop in power consumption and greatly increased design flexibility with byte-wide and word-wide organizations—and not a nanosecond sooner.

Or, to put that another way, when you can get a second-generation 16Mb DRAM from that dynamic dynamo, Toshiba. We've combined a 0.55  $\mu$ m die shrink with optimized row and column architectures. The result: some very compelling reasons to make the move to 16Mb now.

To start with, there's substantial reduction in board

Our 2Mx8 organizations also give you the cleverest solution for providing 8Mb of base memory in your next generation of portables. And today's higher


performance systems can boost system throughput with the wider data paths of 2Mx8, 1Mx16 and 1Mx18 parts.

Combine all this with backward compatibility with the 4Mb generation, access times of 60, 70 and 80ns

and wide variety of SOJ and TSOP package options and you end up with maximum design flexibility.

Toshiba is committed to staying at the forefront of memory technology and to keeping you at the forefront of your competitive

Organization	Refresh Rate	Access Time(ns)	Package
1M X 16	1K, 4K	70/80	SOJ, TSOP
1M X 18	1K	70/80	SOJ, TSOP
2M X 8	2K	60/70/80	SOJ, TSOP
4M X 4	2K, 4K	60/70	SOJ, TSOP
16M X 1	4K	60/70	SOJ, TSOP

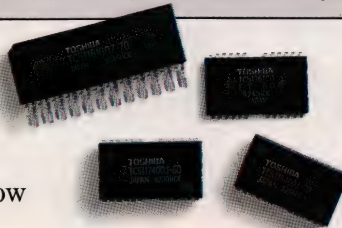

## go to great widths to offer you design flexibility.

real estate when you replace four 1Mx4 parts with one 1Mx16 part. And SIMM modules in 1Mx36 and 2Mx36 configurations, utilizing the 1Mx18 DRAM in place of 4Mb DRAMs, provide elegant solutions in today's power conscious systems.

markets. And we go to great lengths—and widths—to stay on top.

Please call 1-800-879-4963 for our DRAM Product Specification Guide.

In Touch with Tomorrow  
**TOSHIBA**

TOSHIBA AMERICA ELECTRONIC COMPONENTS, INC.





With HP, the biggest news  
in motor control

is also the smallest.

Miniature in size, but a giant when it comes to performance, HP's new HCPL-7800 high common mode rejection isolation amplifier is nothing short of revolutionary.

We've used our leading optocoupler technology to create the world's smallest high CMR isolation amplifiers—so small they fit in a standard 8-pin DIP or SMT package. Giving you a revolutionary alternative to Hall-effect sensors that provides the competitive advantage you need to meet today's demand for smaller design solutions.

Our new isolation amplifier also delivers unequalled CMR performance

and excellent drift characteristics in high-noise environments, far outclassing standard current transformers and bulky Hall-effect sensors for current sensing.

Its small price may surprise you, too. But that's not all. HP also offers isolated power transistor drivers that deliver high output currents and a wide range of output voltages. Team them up with our new isolation amplifiers, and you'll have a complete motor control solution from one reliable source.

All of which gives HP a big advantage when it comes to serving your motor control needs. Because now you can

get the smallest solutions at smaller prices, all with one little call to HP. **In the U.S., call 1 (800) 227-1817, ext. 7251**, today, for an information packet and to request a designer's kit including a free sample. **In Europe, fax us at (31) 20-691-5701.**

There is a better way.



**HEWLETT  
PACKARD**

In Canada, call 1 (800) 387-3867, ext. 7251.  
CG08301



## FPGA Update

**Programmable-logic performance benchmarks.** The Programmable Electronics Performance (Prep) Corp has made the data from its first benchmark suite (version 1.2) of nine circuits available. The benchmarks include data on devices from Actel, Altera, AMD, Cypress, Intel, Quicklogic, Texas Instruments, and Xilinx. The benchmarks show how different field-programmable gate arrays (FPGAs) and complex PLDs compare in speed and capacity for a variety of circuit types. The benchmarks provide a considerable amount of information that should prove helpful to engineers deciding which PLDs are suitable candidates for an application. Certified Prep benchmark results, including background material, cost \$25. Prep Corp, Los Gatos, CA, (408) 356-2169, Fax (408) 356-0195. **Circle No. 509**

**FPGA software is free and almost free.** If you've put off using FPGAs because the high cost of software prevents you from evaluating the devices, your excuses are gone. Intel is now offering the PLDshell Plus 3.0 software for its iFX780 Flexlogic family for free—it previously cost \$249. If you currently use Data I/O's Abel or Minc's PLDesigner-XL V3.1, you can obtain free FPGA support by calling (800) 323-3753. Logical Devices CUPL Total Designer V4.4 and Orcad's V2.0 environment also include support for the Intel FPGAs. Intel Corp, Santa Clara, CA, (408) 765-8080. **Circle No. 510**

**Quicklogic lets you try out its FPGA design software** with a 30-day license and 30-day hotline support for \$99. The software includes Windows-based schematic entry, place and route, and full timing analysis. You can view the physical layout of your design and interactively cross-probe between the layout and schematic. The \$99 can be applied to the purchase of an unrestricted user license. **Circle No. 511**

**FPGA gets faster, cheaper, smaller.** Quicklogic has also released a new version of its 1000-gate QL8x12A that is 30% faster, 30% less expensive, and is available now in a 1.4-mm thin quad flatpack (TQFP). The speed increase reduces the logic-cell delays on the fastest versions to 2.4 nsec. You can obtain internal data-path operating speeds of 120 MHz. The price reduction results from a 20% die-size reduction due to a new layout and a move to a high-volume manufacturing facility. The QL8x12A-2 is the fastest version and costs \$37.60 in a 68-pin PLCC; the QL8x12A-0 standard-speed version costs \$23.20 (1000). The 2000-gate QL12x16 is also available in a TQFP. Quicklogic, Santa Clara, CA, (408) 987-2000, Fax (408) 987-2012. **Circle No. 512**

**Ultralow-power FPGA.** The Zero+ FPGA family from Xilinx has a 20- $\mu$ A quiescent current and 5- $\mu$ A standby current at 3.3V. The XC2014L is available in a 1.1-mm-thick, 64-pin, very thin quad flatpack (VQFP) for \$13. The XC3042L, in a 100-pin TQFP, costs \$25 (1000).—by Doug Conner. Xilinx Corp, San Jose, CA, (408) 559-7778, Fax (408) 559-7114. **Circle No. 513**

## 64-Mbit DRAMs arrive

NEC Electronics is now making samples of its 64-Mbit dynamic RAMs (DRAMs) available to de-

signers. The devices are available in 16M $\times$ 4-bit ( $\mu$ PD42S64400), 8M $\times$ 8-bit ( $\mu$ PD42S64800), and 4M $\times$ 16-bit ( $\mu$ PD42S64160) configurations with access times as fast as 50 nsec. The devices use a 3.3V supply

and offer a JEDEC-compatible low-voltage TTL (LVTTTL) I/O interface.

Other features include a self-refresh option and fast page-mode operation. All three configurations are available in thin small-outline packages (TSOP); the  $\mu$ PD42S64400 and  $\mu$ PD42S64800 parts are also available in small-outline J-lead (SOJ) packages. Samples are available, and volume production is scheduled to begin in 1994. High-volume (10,000) pricing starts at \$600. —by Richard A. Quinnell. NEC Electronics, Mountain View, CA, (415) 965-6000, Fax (415) 965-6130. **Circle No. 514**

## PC chip set works with Pentium processor

Designers wanting to turn the Pentium processor into an ISA bus PC now have a chip set available to simplify their task. The 3-chip set includes a bus controller (82C596), a system controller (82C597), and an integrated peripheral controller (82C296). The bus controller serves as a buffer to steer data between the CPU and memory buses, adds parity generation and detection logic, and translates commands between the ISA bus and the VESA local bus. The system controller handles CPU-interface, secondary-cache, and DRAM control. It also interprets and translates bus cycles from the CPU, local-bus master, ISA bus master, and DMA to the host memory, local-bus slave, and ISA bus devices. You can use a system clock as fast as 66 MHz (1 $\times$ ).

The set will work with SRAM to provide a secondary cache for the Pentium. The secondary cache has a direct-mapped, write-back architecture, and its size

*Continued on pg 18*

## SHORTS

**Slide rules, anyone?** If you're interested in the history of slide rules, or in collecting and preserving them, there's a society just for you. Members receive a semiannual newsletter and swap lists. Membership is \$20/year in the US, \$25 elsewhere. Osborne Price, 8338 Colombard Ct, San Jose, CA 95135.—JT. **Circle No. 524**

**For EE instructors only.** Dr David Middlebrook of California Institute of Technology in Pasadena, CA, offers a summer workshop for instructors that trains them how to teach students design-oriented analysis. (If you're not an instructor, there are seminars for you, too.) The Design-oriented Analysis workshop for instructors costs \$200 and takes place June 14 to 16 at the Kellogg Center for Continuing Education in Pomona, CA. If you're a circuit designer, ask about the 3-day seminars set for September. Dr Middlebrook, (818) 356-4822—JT. **Circle No. 516**

**Guide for PC chip sets.** The \$139 *Personal Computer Design Guide: A Survey of Integrated Solutions*, by Scott Hopkinson provides an approach to understanding PC design and the technical factors that drive a design. The guide covers 255 chip sets from 30 manufacturers.—RW. Annabooks, San Diego, CA, (619) 673-0870. **Circle No. 517**

**HP offers symposium.** HP's 1993 High-Speed Digital Symposium addresses clock-distribution networks, timing-margin verification, and managing signal-integrity effects. The symposium is free and runs in various cities from April 20 to June 8. Phone HP for scheduling and registration information.—JL. Hewlett-Packard Co, Palo Alto, CA, (800) 765-9200. **Circle No. 518**




Continued from pg 17  
ranges from 64 kbytes to 2 Mbytes. The set also has a built-in DRAM controller for as many as four banks of 64-bit-wide page-mode DRAM. The DRAM density can range from 256 kbytes to 8 Mbytes in configurations as large as 128 Mbytes. Sample chip sets, design kits, and technical support are available now. The chip set costs \$75 (1000); volume production is scheduled for mid-year. —by Richard A. Quinnell. Opti Inc, Santa Clara, CA, (408) 980-8178, Fax (408) 980-8860.

Circle No. 515
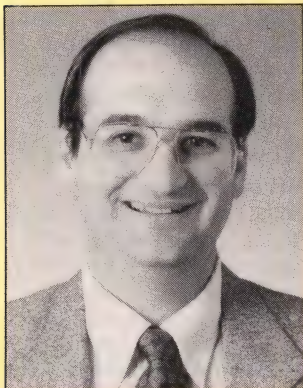
## Steven H Leibson becomes EDN's Chief Editor

Steven H Leibson has been promoted to Chief Editor of EDN Magazine. Jon Titus, who has held the dual title of Chief Editor and Editorial Director since 1989, will now concentrate solely on his Editorial Director duties. "Steve has done an outstanding job as executive editor during the last year and half. It's a pleasure to have him take over, and both of us look forward to continuing our work together," said Titus. Leibson is now in charge of the day-



Steven H Leibson, EDN's new Chief Editor

to-day operations of the magazine edition, freeing Titus to oversee the operations of all of EDN's proper-

ties (EDN Magazine, Products and Careers, and EDN Asia) as well as working on other EDN ventures. —by Susan Rose

## New fuzzy-logic processor costs \$2

The anticipated movement of fuzzy logic into consumer products may soon become a reality. American Neuralogix Inc is developing a fuzzy-logic processor that will sell for only \$2 (100,000). Slated for delivery in September, the NLX-220 processor is suited for products and applications including motor controllers, AGC controllers, power and battery management, smart appliances, security systems, and industrial control.

The chip does not need a host processor or peripheral chips. It has four analog input pins and four analog output pins; other pins provide power, ground, reset/standby, and frequency control for an on-chip oscillator circuit. The device can process 100 input terms and 50 rules. It provides six selectable membership functions in mask ROM. Parameters for fuzzy-logic rules that you specify also go into mask ROM. Smaller quantities of the chip will be available but will include a mask-ROM charge. In quantities of 1000, for example, you'll pay \$5.25 per chip plus a mask fee of \$7000.

—by Gary Legg. American Neuralogix Inc, Sanford, FL, (407) 322-5608.

Circle No. 519

## Templates speed power-electronics designs

Power Express from Analogy is a power-electronics design and analysis package that speeds design by offer-

ing topology templates. The templates are part schematic and part system models of popular power-electronic topologies used in power supplies, motor-drive circuits, and power-factor-correction circuits. The models are predefined and presimulated, which lets you quickly evaluate multiple configurations to determine the best one to meet your design requirements. Templates offered in the initial release include buck, boost, buck-boost, cuk, sepic, zeta, forward flyback, push-pull, full bridge, and half bridge. The package will be available as a \$5000 option to Saber. Bundled with Saber, prices start at \$30,000. The software runs on Sun and HP workstations. —by Doug Conner. Analogy, Beaverton, OR, (503) 626-9700, Fax (503) 643-3361.

Circle No. 520

## Circuit board emulates ASICs

A field-programmable circuit board from Aptix works in conjunction with software from Pie Design Systems to emulate ASICs with up to 30,000 gates. The FPCB-AP4 has sockets to accommodate up to 16 Xilinx 4010 FPGAs and four field-programmable interconnect devices from Aptix. A 320-pin prototyping area lets you add RAM and other hardware to expand the system's capacity beyond 30,000 gates. Although speed depends on the application, the company expects most applications to run at clock speeds of 10 to 20 MHz. Pie Design Systems provides the Mars compiler software necessary to automatically partition and map designs into the board.

A fully configured system costs \$60,000, including software and a fully populated programmable circuit board. Once you've finalized a design, you can purchase

replicate boards that have all configuration data stored in nonvolatile memory. The replicate boards are useful for hardware and software development after you've finalized the design and before you have working ASICs from your foundry. Replicate boards cost \$25,000. The field-programmable circuit boards are available now; the Mars compiler software will be available in the third quarter of 1993. —by Doug Conner. Aptix Corp, San Jose, CA, (408) 428-6200, Fax (408) 944-0646. **Circle No. 521**  
Pie Design Systems, Sunnyvale, CA, (408) 738-8899, Fax (408) 738-8853. **Circle No. 522**

## Placement drives ASIC logic synthesis

To meet high-density ASIC needs, Cadence Design Systems has added placement-based synthesis to its Synergy PBS (Placement-Based Synthesis) design tool. The package makes a preplacement pass on the finished netlist before the silicon layout/verification phase. The tool rearranges the netlist to reduce interconnect. Additionally, it resizes gates and buffers based on layout and inserts new gates as needed to reduce overall timing delays. The resulting optimized netlist is then passed to standard ASIC place-and-route tools to finalize the ASIC's silicon. The company claims that by including preplacement in the design cycle, timing performance improves 10 to 30%, depending on the design.

Enhanced Synergy, with placement-based logic synthesis, will be available this quarter; it costs \$55,000 and includes a VHDL or Verilog Synthesizer/Optimizer. The Synergy PBS option is available for \$25,000. —by Ray Weiss. Cadence Design Systems Inc, San Jose, CA, (408) 943-1234. **Circle No. 523**





## HOW TO SAVE 6 MONTHS, 30 ns & 50 PARTS ON YOUR NEXT DRAM DESIGN.

It's as simple as assigning a mere 7.8 square inches of board space for the Cypress DRAM Accelerator. You'll save months of design time for single- or multi-processor applications — and transfer data between DRAM and cache at cache speeds — error-corrected. The Cypress DRAM Accelerator provides four high-level functions that combine to maximize system-to-DRAM interface, allow more processors to share the bus, and enhance cache-level transactions. Its system bus interface supports 40 MHz 32- or 64-bit buses, so it won't slow down hot processors such as SPARC®, R4000, 486 or Pentium™. It's the first DRAM subsystem to integrate both address and data path in a single part. And our DRAM Accelerator's 128-bit DRAM look-up, error detection/correction, and transaction control features enable it to do the work of up to 35-50 22V10 PLDs...plus EDC chips and FIFOs. It also saves money by allowing use of cheaper, 80 ns DRAMs. At Cypress, great things come in small packages. **For further proof, call the Cypress DRAM Accelerator hotline for an informative, free datapack. Europe: (32) 2-652-0270, ext. 119\*. Ask for Dept. C4Z.**



Or contact us via Europe fax and Asia telephone numbers listed below.

\*The international operator can give you your country's specific access code. Europe: Fax (32) 2-652-1504. Telephone Hong Kong:

(852) 3-880-629. India: (812) 566-630 x-3808. Japan: (81) 423-69-82-11. Korea: (82) 2-516-1144. Singapore: (65) 28-00-200. Taiwan: (886) 2-820-53-53. © 1993 Cypress

Semiconductor, 3901 North First Street, San Jose CA 95134. Phone 1 (408) 943-2600, Telex: 821032 CYPRESS SNJ UD, TWX: 910-997-0753. SPARC is a registered trademark of SPARC International, Inc. Products bearing the SPARC trademark are based on an architecture developed by Sun Microsystems, Inc. Pentium is a trademark of Intel Corp. All other trademarks and registered trademarks are the property of their respective companies.






# POWER SPLITTERS/ COMBINERS

the world's largest selection  
2KHz to 10GHz from \$2<sup>95</sup>

With over 300 standard models, from 2-way to 48-way, 0°, 90° and 180°, 50- and 75-ohms, covering 2KHz to 10GHz, Mini-Circuits offers the world's largest selection of off-the-shelf power splitter/combiners. And, with rapid turnaround time, we'll also supply "special" needs, such as wider bandwidth, higher isolation, lower insertion loss and phase matched ports.

Available for use in military and commercial requirements, models include plug-in, flat-pack, surface-mount, connectorized standard and custom designs. New ultra-miniature surface mount units provide excellent solutions in cellular communications, GPS receivers, Satcom receivers, wireless communications, and cable systems.

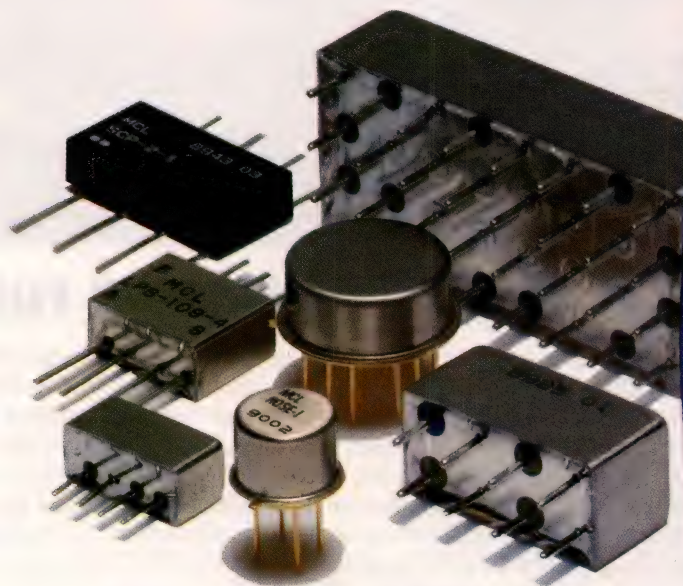All units come with a one-year guarantee and unprecedented "skinny" sigma unit-to-unit and production run-to-production run repeatability. All catalog models guaranteed to ship in one week. Mini-Circuits...dedicated to exceed our customers' expectations.



finding new ways ...  
setting higher standards



**Mini-Circuits**™

WE ACCEPT AMERICAN EXPRESS AND VISA

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718) 332-4661

Distribution Centers/NORTH AMERICA 800-654-7949 • 417-335-5935 Fax 417-335-5945 EUROPE 44-252-835094 Fax 44-252-837010







## THE WORLD'S FIRST 2-CHIP SOLUTION.

Today's desktop machine market is screaming for more bandwidth – a full 100Mbps. And National is providing market-ready solutions for both fiber



and copper connectivity *today*.

Our extensive networking experience, proven product portfolio and active involvement with the ANSI FDDI standards committee will help drive your FDDI application all the way to the desktop. Our highly integrated 2-chip solution reduces time to market and lowers adoption costs. It



is comprised of the MACSI™ (media access controller and systems interface) and PLAYER+™ (physical layer device). Together they incorporate receive and transmit buffering and integrated clock recovery. And for copper connectivity, our CDL™ (copper data link) solution is the first integrated



# FDDI TO DESK





transceiver for FDDI across shielded twisted pair that conforms to SDDI specifications.

## **SOLID CUSTOMER SUPPORT.**

Our FDDI support is designed to minimize your risks and total development costs, ensuring rapid market entry with truly unique designs. In addition to providing a full range of software including SMT and drivers, we offer the finest application support worldwide: a design hotline staffed by experienced applications engineers, detailed technical documentation, a complete line of evaluation boards, and both router and concentrator design examples. Everything you need for FDDI is here now. For more information call 1-800-NAT-SEMI, Ext. 229.

**NATIONAL KNOWS NETWORKING.**



# **TOPS NOW!**

©1993 National Semiconductor Corporation. MACSI, PLAYER+ and CDL are trademarks of National Semiconductor Corporation.



# Synergy. Out Front Again... And Again.

## The New Dual '040 VME SBC: Faster, More Efficient and Lower Cost Than Any Multi-board Solution

Get on-board multiprocessing and an astounding **40 MIPS** throughput, when you power your system with Synergy's new SV420 single-slot SBC. The SV420's dual-CPU design means you'll need fewer boards in your VME chassis, with no VMEbus bandwidth bottlenecks between the '040s, and system-wide cost saving of more than 40%.



And even if you don't need multiprocessing right now, the SV420 still puts you out front. Use the second '040 as a super-smart DMA controller. When combined with the SV420's **66 MByte/sec VME64<sup>®</sup>** circuitry, nothing communicates faster over the VMEbus.

Add even more on-board power by selecting from Synergy's big list of

high-performance, intelligent plug-on I/O modules – such as our latest Super-VSB module offering 40+ MB/sec over the VSB bus. Or choose another module, from a T1/E1 controller to a super-fast graphics engine, that plugs onto any Synergy SBC.

Better yet, just tell us what you need. We're the company you can talk to about your VME system design problems. You'll find that we listen *and deliver* (every Synergy I/O module on our list started as a customer request). We mean business when we say customer support is our most important mission.

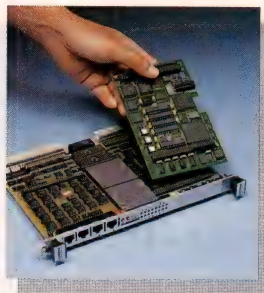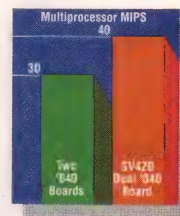So if you want to be out front in system performance, just be up front with Synergy. Call us today.



Over a dozen smart, powerful I/O modules fit Synergy's '020, '030, '040 and Dual '040 SBC's.



**SYNERGY**  
microsystems

Synergy Microsystems, Inc.  
179 Calle Magdalena, Encinitas, CA 92024  
(619) 753-2191 FAX: 619-753-0903

CIRCLE NO. 66



## Reader needs EPROM, contents, or firmware program

My company is searching for the firmware program listing, EPROM contents, or actual 2708 EPROMs for the National Semiconductor BLC 8229/8228 CRT/keyboard controller. These devices were also part of the company's Starplex development system. National no longer supports the Starplex system, nor could it recommend a company that does. Is there anyone out there from whom we can beg, borrow, or buy any of these devices?

*L Mente  
Software Engineer  
Amparts Electric  
South Holland, IL*

Let's find out.

## Zero-crossing detector may not be the problem

I am in dire need for quick information on using a zero-crossing or peak detector with the minimum amount of parts to interface with a Z-World Z180 microcontroller in an embedded system. "The Computer Applications Journal" (February 1993) suggested the ac power line as an excellent time base. You derive that time base using an optoisolator and a 74LS14 as a zero-crossing detector. We're swamped with putting our resources into coding and don't have a lot of time for this circuit. We tried sampling the 10-bit ADC more frequently than we did in an earlier project, but this tack took about 25% of our processor time to get the accuracy (100ths of the power-line frequency) we need. We catch the volts and amps at the crossing and use the timestamps to calculate power factor and frequency. I am under the gun and responsible for both the hardware microcontroller interface to our machine as well as the bulk of the coding. Could you drop me a hint or two and help pull off an eleventh-hour miracle?

*Mike Raffesberger  
Intelligen  
San Marcos, CA*

The Cahners CAPS (Computer-Aided Product Selection) System from Cahners Technical Information Services

(Newton, MA) coughed up only one "zero-crossing" chip: Siemens's IL426. That chip is a 600V 2A power triac—probably not what you want. You can call Siemens Components (Santa Clara, CA) at (408) 980-4518, or fax them your request at (408) 980-0319.

A scan of the Design Idea files yielded the following DIs that feature zero-crossing detectors, as well as the EDN issues they appeared in: "Power controller switches cycles" (3/15/90, pg 179), "VFC rejects common-mode noise" (1/21/91, pg 166), "Current loop controls SCRs" (2/4/91, pg 106), "Phase shifter adapts to frequency changes" (6/6/91, pg 184), and "Single-chip  $\mu$ P suppresses unwanted tone" (12/5/91, pg 196). For other zero-crossing circuits, see the *IC Op-Amp Cookbook*, by Walter Jung (Howard W Sams & Co, Indianapolis, IN) and *The Art of Electronics*, by Paul Horowitz and Winfield Hill (Cambridge University Press, New York, NY).

Frankly, we don't understand how you could be chewing up 25% of your  $\mu$ C's time measuring something that happens 120 times/sec. How about letting a counter run free at whatever rate will give you the resolution you need? You could use the output from the zero-crossing detector as an interrupt to store the current counter value into a register or memory location. Some simple math that accounts for counter overflow should yield the difference between two successive readings. In other words, perhaps your computational algorithm is your real problem, not a zero-crossing detector circuit. If you're out of internal counters, try using an external one.

## Data-analysis software is a bargain compared with stand-alone instrument

I've been searching for data-analysis-type software that would write all data both passed by modem and running in a program to the screen, so I could watch data flowing in both directions via a split window. I have heard of such programs but don't remember a program or author name. Can you help?

*Howard Lukenbill  
HSL Inc  
Pueblo, CO*

Try the program Microtap (formerly Datascope). It costs \$299, including the special cabling you'll need. Serial-data analyzers start at \$10,000 as stand-

alone instruments, so the software is quite inexpensive.

Paladin Software Inc  
3945 Kenosha Ave  
San Diego, CA 92117  
(619) 490-0368  
Fax (619) 490-0177

## Spice source code not available in Fortran

I need a point of contact for Berkeley Spice Fortran source code. Our government customer wants to upgrade a mainframe-based Spice front end to a microprocessor-based tool. I understand that Spice is available to the government in source form for a nominal price, but I need a phone number to call.

*Bill Hensley  
TRW  
Midwest City, OK*

Bad news, Bill. The folks at Berkeley gave up on Fortran and recoded Spice in C. Hope you have a C compiler. Berkeley sells Spice to anybody—not just institutions—for a media fee. Contact

Industrial Liaison Program  
Software Distribution Office  
Department of Electrical Engineering and Computer Science  
Electronics Research Lab  
205 Cory Hall  
University of California, Berkeley  
Berkeley, CA 94726  
(510) 643-6687.

Also, it wouldn't hurt to get yourself a postprocessor to turn number-stuffed Spice files into graphs and to do things like Fourier transforms. Look on the EDN BBS's /SPICE Special Interest Group for the TRSpice postings.

Ask EDN solves nagging design problems and provides the answers to difficult questions. Address your letters to Ask EDN, 275 Washington St, Newton, MA 02158. Fax (617) 558-4470; MCI: EDNPRIME. Or, send us a letter on EDN's bulletin-board system at (617) 558-4241, 300/1200/2400 8,N,1. From the Main System Menu, enter ss/ask\_edn and select W to write us a letter.



# ***FILTERS***





# dc to 3GHz from \$11.45


## lowpass, highpass, bandpass

- less than 1dB insertion loss • greater than 40dB stopband rejection • surface-mount • BNC, Type N, SMA available
- 5-section, 30dB/octave rolloff • VSWR less than 1.7 (typ) • rugged hermetically-sealed pin models • constant phase
- meets MIL-STD-202 tests • over 100 off-the-shelf models • immediate delivery

### low pass, Plug-in, dc to 1200MHz

Model No.	Passband MHz	Stopband, MHz	loss < 1dB	loss > 20dB	loss > 40dB	Model No.	Passband MHz	Stopband, MHz	loss < 1dB	loss > 20dB	loss > 40dB
★LP-5	DC-5	8-10			10-200	★LP-250	DC-225	320-400		400-1200	
★LP-10.7	DC-11	19-24			24-200	★LP-300	DC-270	410-550		550-1200	
★LP-21.4	DC-22	32-41			41-200	★LP-450	DC-400	580-750		750-1800	
★LP-30	DC-32	47-61			61-200	★LP-550	DC-520	750-920		920-2000	
★LP-50	DC-48	70-90			90-200	★LP-600	DC-680	840-1120		1120-2000	
★LP-70	DC-60	90-117			117-300	★LP-750	DC-700	1000-1300		1300-2000	
★P-90	DC-81	121-137			167-400	★LP-800	DC-720	1080-1400		1400-2000	
★LP-100	DC-98	146-189			189-400	★LP-850	DC-760	1100-1400		1400-2000	
★LP-150	DC-140	210-300			300-600	★LP-1000	DC-900	1340-1750		1750-2000	
★LP-200	DC-190	290-390			390-800	★LP-1200	DC-1000	1620-2100		2100-2500	

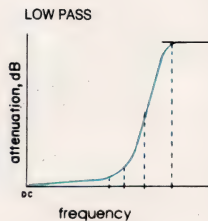Price, (1-9 qty), all models: plug-in \$14.95, BNC \$32.95, SMA \$34.95, Type N \$35.95



### Surface-mount, dc to 570MHz

Model No.	Passband MHz	Stopband, MHz	loss < 1dB	loss > 20dB	loss > 40dB
SCLF-21.4	DC-22	32-41			41-200
SCLF-30	DC-30	47-61			61-200
SCLF-45	DC-45	70-90			90-200
SCLF-135	DC-135	210-300			300-600
SCLF-190	DC-190	290-390			390-800
SCLF-380	DC-380	580-750			750-1800
SCLF-420	DC-420	750-920			920-2000


Price, (1-9 qty), all models: \$11.45

### Flat Time Delay, dc to 1870MHz

Model No.	Passband MHz	Stopband, MHz	loss < 1.2dB	loss > 10dB	loss > 20dB	VSWR	Group Delay Variations, ns
★BLP-39	DC-23	78-117			117	1.3:1	0.7
★BLP-117	DC-65	234-312			312	1.3:1	0.35
★BLP-156	DC-94	312-416			416	1.3:1	0.3
★BLP-200	DC-120	400-534			534	1.6:1	0.4
★BLP-300	DC-180	600-801			801	1.25:1	0.2
★BLP-467	DC-280	934-1246			1246	1.25:1	0.15
▲BLP-933	DC-560	1866-2490			2490	1.3:1	0.09
▲BLP-1870	DC-850	3740-6000			5000	1.45:1	0.05

Price, (1-9 qty), all models: plug-in \$19.95, BNC \$36.95, SMA \$38.95, Type N \$39.95

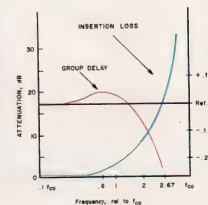
NOTE: ▲ -933 and -1870 only with connectors, at additional \$2 above other connector models.



### high pass, Plug-in, 27.5 to 2200MHz

Model No.	Stopband MHz	Passband, MHz	VSWR	Model No.	Stopband MHz	Passband, MHz	VSWR
★HP-25	DC-13	13-19	27.5-200	★HP-400	DC-210	210-290	395-1600
★HP-50	DC-20	20-26	41-200	★HP-500	DC-280	280-365	500-1600
★HP-100	DC-40	40-55	90-400	★HP-600	DC-350	350-440	600-1600
★HP-150	DC-70	70-95	133-600	★HP-700	DC-400	400-520	700-1800
★HP-175	DC-70	70-105	160-800	★HP-800	DC-445	445-570	780-2000
★HP-200	DC-90	90-116	185-800	★HP-900	DC-520	520-660	910-2100
★HP-250	DC-100	100-150	225-1200	★HP-1000	DC-550	550-720	1000-2200
★HP-300	DC-145	145-170	290-1200				

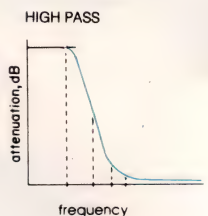
Price, (1-9 qty), all models: plug-in \$14.95, BNC \$36.95, SMA \$38.95, Type N \$39.95



### bandpass, Elliptic Response, 10.7 to 70MHz

Model No.	Center Freq. (MHz)	Passband I.L. 1.5 dB Max. (MHz)	3 dB Bandwidth Typ. (MHz)	Stopbands I.L. > 20dB at MHz	Stopbands I.L. > 35dB at MHz
★BP-10.7	10.7	9.6-11.5	8.9-12.7	7.5 & 15	0.6 & 50-1000
★BP-21.4	21.4	19.2-23.3	17.9-25.3	15.5 & 29	3.0 & 80-1000
★BP-30	30.0	27.0-33.0	25-35	22 & 40	3.2 & 99-1000
★BP-60	60.0	55.0-67.0	49.5-70.5	44 & 79	4.6 & 190-1000
★BP-70	70.0	63.0-77.0	68.0-82.0	51 & 94	6.0 & 193-1000

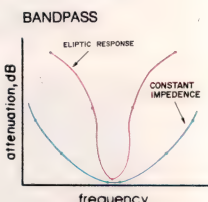Price, (1-9 qty), all models: plug-in \$18.95, BNC \$40.95, SMA \$42.95, Type N \$43.95



### Constant Impedance, 21.4 to 70MHz

Model No.	Center Freq. MHz	Passband MHz loss < 1dB	Stopband loss > 20dB at MHz	VSWR 1.3:1 Total Band MHz
★IF-21.4	21.4	18-25	1.3 & 150	DC-220
★IF-30	30	25-35	1.9 & 210	DC-330
★IF-40	42	35-49	2.6 & 300	DC-400
★IF-50	50	41-58	3.1 & 350	DC-440
★IF-60	60	50-70	3.8 & 400	DC-500
★IF-70	70	58-82	4.4 & 490	DC-550

Price, (1-9 qty), all models: plug-in \$14.95, BNC \$36.95, SMA \$38.95, Type N \$39.95

NOTE: ★Add Prefix P, B, N, or S for Pin, BNC, N, or SMA connector requirement.

finding new ways ...  
setting higher standards

**Mini-Circuits™**

WE ACCEPT AMERICAN EXPRESS AND VISA

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718) 332-4661  
Distribution Centers / NORTH AMERICA 800-654-7949 • 417-335-5935 Fax 417-335-5945 EUROPE 44-252-835094 Fax 44-252-837010


F132 REV. C



*.050 centerline stackers.  
Close, closer, closest.*




***THIS IS AMP TODAY.***

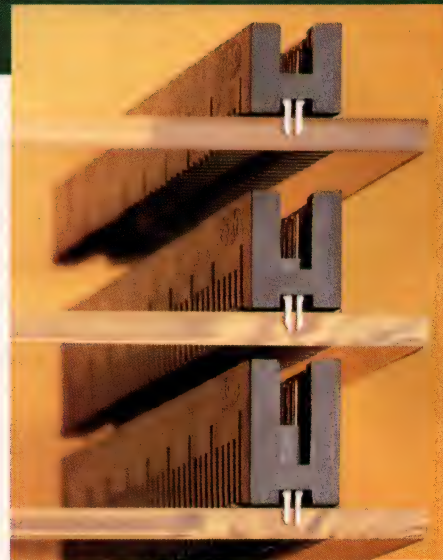

*Surface-mount stack heights: .250" / .320" / .390"*





AMPMODU 50/50 Grid Connectors give you a choice of parallel pcb stack heights: .390", .320", and a very close .250" (the tightest in the industry). So you can squeeze everything possible out of (or into) your design.

This surface-mount system utilizes a .050" contact grid in double row, polarized shrouded headers and receptacles, and offers our exclusive plated copper alloy holddowns. On standard .062" thick boards, the barbed holddowns do their job without

protruding through, allowing surface mounting on both sides. And holddowns are soldered during reflow, providing long-term strain relief.

Dual-beam receptacle contacts and duplex gold plating provide high reliability, in selected sizes from 10 to 100 positions. Dimensional tolerances, reference datums, holddown characteristics, and packaging support robotic application; materials are fully compatible with IR and vapor phase reflow processing.

Call the AMP Information Center near you:

Scandinavia:

Sweden 0758-104 00 (fax 0758-194 70)

Central Europe:

Holland 073-200 911 (fax 073-212 365)

Germany 06103-709 659

(fax 06103-709 619)

Great Britain: 081-954 2356

(fax 081-954 6234)

Southern Europe:

France 1-34 43 27 20 (fax 1-3030 4550)

Italy 011-71731 (fax 011-773 1116)

Spain 03-200 84 66 (fax 03-201 78 79).

**AMP**



# The benchmark of silicon technology.

*Pride...  
craftsmanship...  
a continuing dedication  
to excellence...  
value driven service...  
products designed for the  
customer's need, not the  
supplier's convenience...  
leadership...  
a long term commitment...  
a vision in every aspect  
of our field...*

All of this combined has made NCR Microelectronic Products the industry's benchmark for silicon technology. Our quest is to constantly challenge ourselves... our industry. For over three decades, NCR has balanced these traditional values with the latest technology. To see the results — take a look at the products that are setting industry standards.

Call today for a  
free copy of our  
latest catalog.  
1-800-334-5454





# No policy is good policy



Now that the US has a Democratic administration, we again face the debate about whether we need a national industrial policy. It's interesting that many of our high-tech corporate executives are lining up to tout the virtues of industrial policy. Many of these same people would be peddling potato chips if the US had put an industrial policy in place years ago. Past industrial policies might have included statements such as, "The future is in mainframes, no one will want their own small computers." Or how about, "Microprocessors are toys, the future belongs to minicomputers." Of course, these policies never existed, but they might have. Luckily, the bureaucrats were kept out of policy making for the electronics industry. As the US again debates the need for an industrial policy, here are a few things to consider:

In the 1960s, many European countries and companies, alarmed at the growing military-industrial complex in the US, demanded industrial policies and joint industrial-government ventures. What they got were large bureaucratic money pits that continue to lose technology, market share, and market battles. A European consortium continues to spend billions of dollars on an obsolete HDTV proposal.

Japan's Ministry of International Trade and Industry (MITI) continues to scare US electronics industries. For example, MITI sponsored millions of dollars of research into the fifth-generation computer, and a cry went out in the US that we must have a similar project, too. But today that approach is uncompetitive, and even US supercomputer companies are having a difficult time. That's what competition is supposed to be all about. Now, name a MITI success. You can't; there aren't any that count.

The US already has many government policies. For example, we have a farm policy that subsidizes unprofitable, uncompetitive farms. We hear cries that we must preserve the small family farms. Why? Did we preserve the small neighborhood bakeries and candlemakers? No, and with good reason—they couldn't compete.

The US pays people to not produce food. When they produce too much, the US government buys it and stores it, thus keeping food costs artificially high. The stored food usually doesn't go to people who could use it. Instead, it spoils. We subsidize our dairy industry with over \$400 million per year, and dairy farmers must kill cattle to keep dairy production down. In addition, our farm policy keeps prices for oranges, peanuts, and sugar above what they should be. We subsidize industries to the detriment of consumers.

We have a military policy, too. It means that the US Congress often forces our Department of Defense to buy weapons it doesn't want or need. The policy also means that we maintain military bases that no longer have a purpose.

We have a land-use policy that lets companies "lease" 500 million acres of government land for mining, timbering, or grazing. Leasing rates are far below those for privately owned land. In addition, our wetlands policy jails a landowner who fills in a small damp area on his property, yet it lets municipalities and farmers make profligate use of precious and irreplaceable water resources elsewhere.

The US had an alternative-energy policy that spent billions for research into clean fuels, solar energy, energy conservation, wind power, and synthetic fuels. While the goals were admirable, the program was a boondoggle that tried to predict future energy needs and trends. Today we simply import more oil than ever, and conservation is voluntarily undertaken by those who want to pay less for energy. The hidden hand of the market governs what energy we buy and what we conserve.

And, the US has a space and science policy that continues to sink billions of dollars into a space station that has no clear mission and a super-conducting collider that stands to benefit a handful of academic physicists out for Nobel prizes.

I agree, my examples are short and simplistic. But, what was it you wanted to tell me about needing an industrial policy?

Jon Titus  
Editor



Jesse H. Neal  
Editorial Achievement Awards  
1990 Certificate, Best Editorial  
1990 Certificate, Best Series  
1987, 1981 (2), 1978 (2),  
1977, 1976, 1975

American Society of  
Business Press Editors Award  
1988, 1983, 1981

Send me your comments via FAX at (617) 558-4470, or on the EDN Bulletin Board System at (617) 558-4241 300/1200/2400 8, N, 1.




# Improve yo


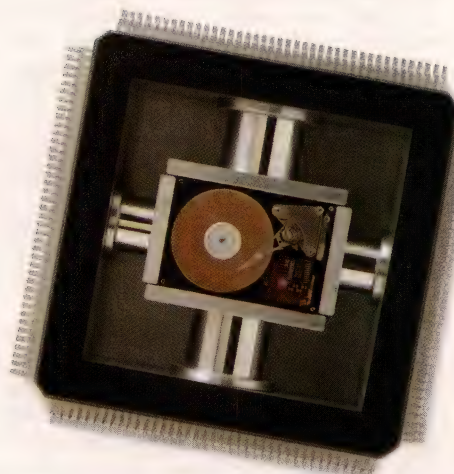
## VGA GRAPHICS CONTROLLERS.

As the industry's leading supplier of VGA controllers for color and monochrome notebook computers, we've set the standard for LCD

display quality. For desktop PCs, set your sights on integrated, 24-bit true color capability...without putting your price-point in the red. We've also included the RAMDAC and frequency synthesizer on all our VGA chips to save additional space and money. Our highly integrated controllers feature industry-standard Super VGA, direct CPU-local bus connection, graphical user interface (GUI) acceleration, and full BIOS and driver support.



## MASS STORAGE.

We're putting the storage world into a compactor, with controllers that make 2.5", 1.8" and even 1.3" hard drives possible. For proof, check out our extended family of AT, SCSI and PCMCIA controllers. They have advanced error correction, power management capabilities, and full firmware support for speedy design-in.

Our "little" advances will similarly fit the form factor of notebooks, pen-based, and even palmtop computers.



So you've got the hottest processor around for your new PC or notebook design...so what? So does your competition. What will set your design apart from all its rivals are the *other* computers inside: Cirrus Logic *FeatureChips*™ controllers. *FeatureChips* controllers bring leading-edge capabilities and performance to critical areas like storage, graphics, communications, multimedia and more. They give your CPU the support it needs for maximum system performance with minimum size and power. Get the most out of your CPU investment; surround it with the best controllers you can buy...Cirrus Logic *FeatureChips* controllers.

\*In Japan (81) 3-5389-5300. Singapore (65) 3532122. Taiwan (886) 2-718-4533. Germany (49) 8152-2030. United Kingdom (44) 0727-872424. ©1992 Cirrus Logic, Inc. 3100 West Warren Avenue, Fremont, CA 94538 (510) 623-8300. Cirrus Logic, the Cirrus Logic logo and FeatureChips are trademarks of Cirrus Logic, Inc. Crystal Semiconductor and SmartAnalog are trademarks of Crystal Semiconductor Corp. "The computer inside" may be claimed to be a trademark of Intel Corporation. Futuristic car scene: Alias Research, Inc.



# ur features.



## COMMUNICATION PRODUCTS.

For innovation, call on our broad line of datacom and telecom products...all of them complete with full software support to ease your design-in effort.

For example, our recently announced highly integrated fax/data modem chip set brings high-quality voice answering machine capabilities to your PCs. For data networking, we feature serial I/O and LAN controllers. And our SmartAnalog™ interface circuits from Crystal Semiconductor help

your designs tap into the vast telecommunications world at a price/performance point that's just right.



## MULTIMEDIA VIDEO & AUDIO ICS.

Inspire encore performances on your PC with real-time video and CD-quality stereo sound. Multimedia and teleconferencing capabilities position any PC for lasting marketability. With capabilities like video editing and multiple video windows, our video chips are ideal for everything from multimedia to video-conferencing. For pro-quality 16-bit stereo audio, our Crystal Semiconductor™ subsidiary has the chips you need to make sound come alive.

## PCMCIA ICS.

Prepare for the upcoming boom in credit card-sized PCMCIA add-in cards. Our single-slot and dual-slot PCMCIA 2.0 host adapters are the fastest, smallest, most power-frugal and feature-filled adapters you can buy. Complementing these host adapters, today we also offer PCMCIA disk interface controllers. Tomorrow, we'll bring PCMCIA capabilities to an even broader set of peripheral functions.

Get the complete 'inside' story: your FREE Cirrus Logic brochure. Learn how our broad *FeatureChips* product line can make your investment in leading CPUs pay off in unparalleled performance and functionality. Seize the competitive advantage. All starting with a single, toll free phone call.

Free *FeatureChips* Literature Hotline:


1-800-858-0487\* Ask for dept. L22



**CIRRUS LOGIC**  
*FEATURECHIPS.™*


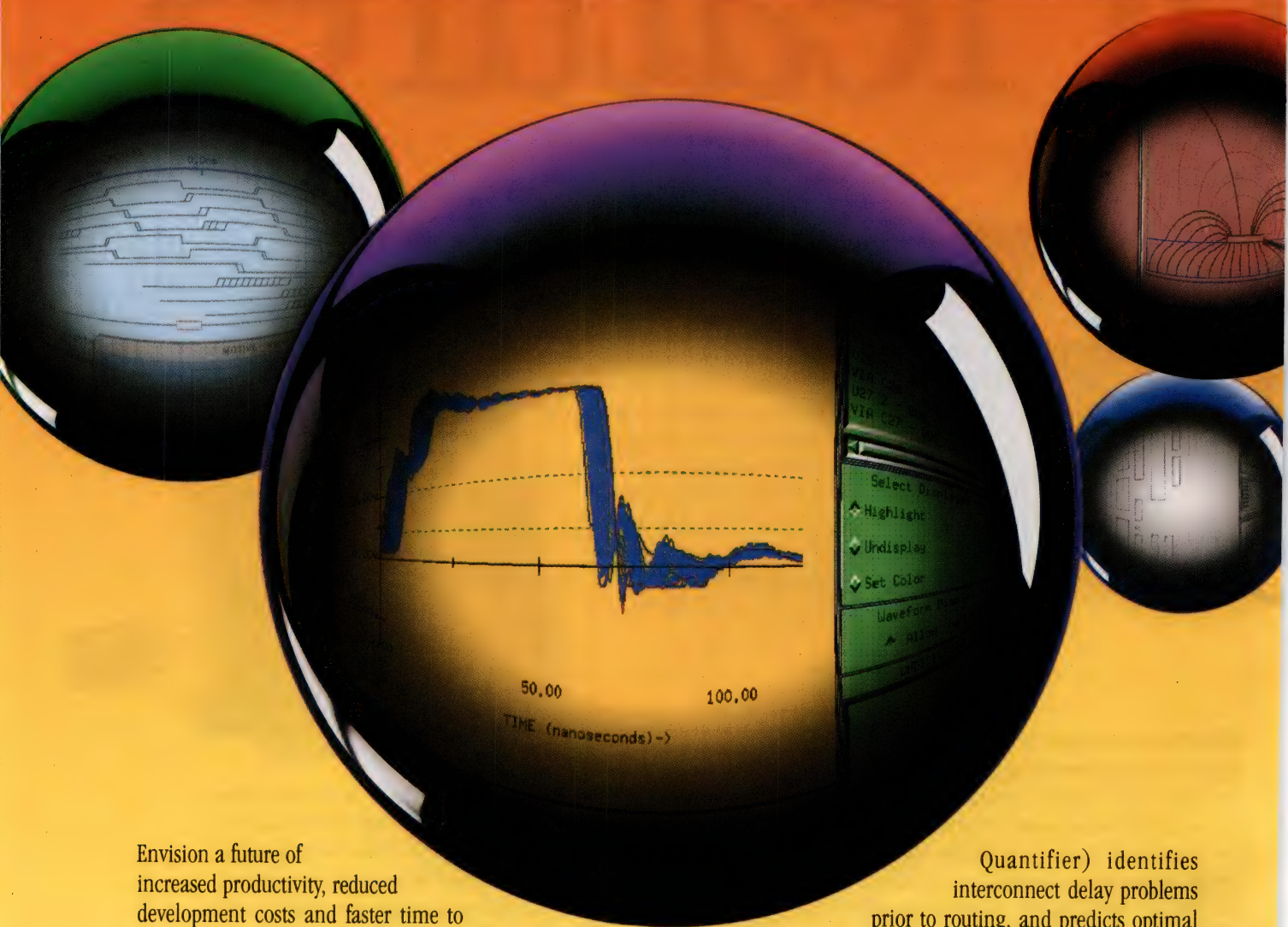
# Look into your digital design future with Quad Design.



Envision a future of increased productivity, reduced development costs and faster time to market... a future enriched by predictive tools that identify and help you correct circuit and system timing and signal integrity errors during the design process.

How? With Quad Design as your crystal ball.

## ***Correct advanced digital design timing errors before prototyping.***

Your brighter future begins with MOTIVE (Modular Timing Verifier). This is our high performance analysis

tool that interactively identifies all critical timing paths on board level and ASIC designs, accelerating your correction of timing problems. Quad Design's XTK (Crosstalk Tool Kit) software suite improves your fortune

by extracting parameters in minutes and simulating PCB interconnect networks in seconds. PDQ (Pre-route Delay

Quantifier) identifies interconnect delay problems prior to routing, and predicts optimal component placement. And TLC (Transmission Line Calculator), an advanced system signal integrity simulation tool, can accurately foresee entire PCB design signal waveforms.

Contact Quad Design at (805) 988-8250 for our free brochure, and watch your digital design future take shape. 1385 Del Norte Road, Camarillo, CA 93010... FAX (805) 988-8259.



Quad Design software can be used independently or together on a broad spectrum of industry-standard engineering workstations, and automatically interfaces with a host of popular CAE/CAD environments.



# Circulating designs throughout Europe for over 80 years

Every month Electronics World focuses on the world of electronics design and PC-based engineering tools. The magazine has a depth of coverage that gives the reader the clearest view of new products and an absolute understanding of the latest technology in design, applications and software.

Electronics World is published by Reed Business Publishing, part of the same company that publishes EDN, so we are able to offer you an exclusive discount on a subscription of as much as 40% off the normal price.

And don't forget the satisfaction guarantee – if you decide at any time you don't like Electronics World write and tell us and we will refund the unused portion of you're subscription!



**ELECTRONICS  
WORLD**  
+ WIRELESS WORLD

**YES, I WOULD LIKE TO SUBSCRIBE TO**

Name..... Job title..... Address.....  
..... Telephone number.....

At a cost of: **SURFACE MAIL** **AIR MAIL**

**1 YEAR**

**£29**

**£42**

**2 YEARS**

**£46**

**£68**

**25% OFF** OR

**40% OFF**

☐ I enclose a Bankers Draft or International Money order for £..... OR

☐ Please debit my credit card for £.....

☐ AMEX

☐ ACCESS

☐ VISA

☐ DINERS CLUB

Account number

Expires.....

Signature..... Date.....

Please return to: Electronics World + Wireless World  
Subscriptions, Reed Business Publishing, Stuart House, Perrymount Road, Haywards Heath, Sussex RH16 3DH, England



EDN

**Priority  
Subscription  
Offer**





# Solid Building Blocks

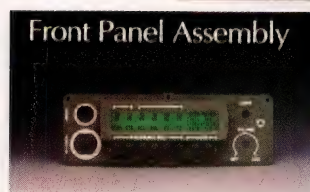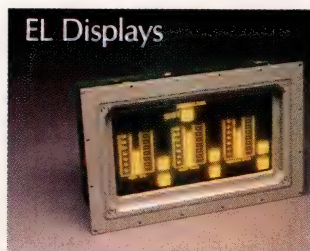

## for Man-Machine Interface Without Equal

The Planar Products Division of IEE provides military and ruggedized keyboard and display technology encompassing a complete line of standard and custom engineered man-machine interface products.

As a qualified supplier of military hardware, IEE designs and manufactures to meet such diverse requirements as **MIL-E-5400**, **MIL-E-16400**, **MIL-T-28800**, **MIL-STD-454** electronics, **MIL-STD-2000** soldering and **MIL-STD-810** environmentals.

Our commitment to quality extends beyond merely meeting **MIL-Q-9858** to include a Total Quality Management Program that ensures the highest quality focus throughout all aspects of our company.

For over 45 years, IEE has been an industry leader in keyboard and display technology and we are more committed than ever to provide man-machine interface without equal.

I n d u s t r i a l   E l e c t r o n i c   E n g i n e e r s ,   I n c .

7740 Lemona Avenue Van Nuys California 91409 Tel 818-787-0311 Fax 818-781-9795


Circle #36 For Reference

Circle #37 For Immediate



# Low-power $\mu$ Ps simplify design of portable computers

JOHN GALLANT, Technical Editor

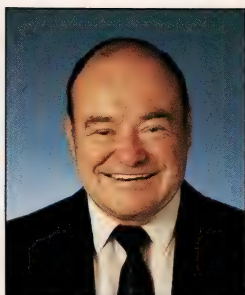


**Portable computers are changing the way people do business. At the heart of these compact mobile units are  $\mu$ Ps with sophisticated power-management features that conserve battery life.**

Designers of first-generation portable computers quickly recognized the need for conserving as much energy as possible from batteries. Because normal operating conditions create battery discharge times of less than 1 hour, portable-computer designers were forced to implement innovative power-savings schemes. In response, microprocessor ( $\mu$ P) vendors have developed a host of  $\mu$ Ps for low-power applications using sophisticated power-management techniques. These techniques extend battery life between charges to four hours—or more.

One of the first  $\mu$ Ps for low-power applications is the i386 SL, which Intel

introduced in 1990 (5V, 25-MHz version, \$66 (1000)). The  $\mu$ P features a 16-, 20-, or 25-MHz i386 core and a power-savings method, called system management mode (SMM), which is transparent to normal operating conditions. To implement SMM, the i386 SL adds two new pins to the i386 CPU. A non-maskable hardware interrupt, called system management interrupt (SMI), and a CPU acknowledge signal, called SUS-STAT. SMI has a higher priority than the standard nonmaskable interrupt (NMI) for the i386  $\mu$ P.

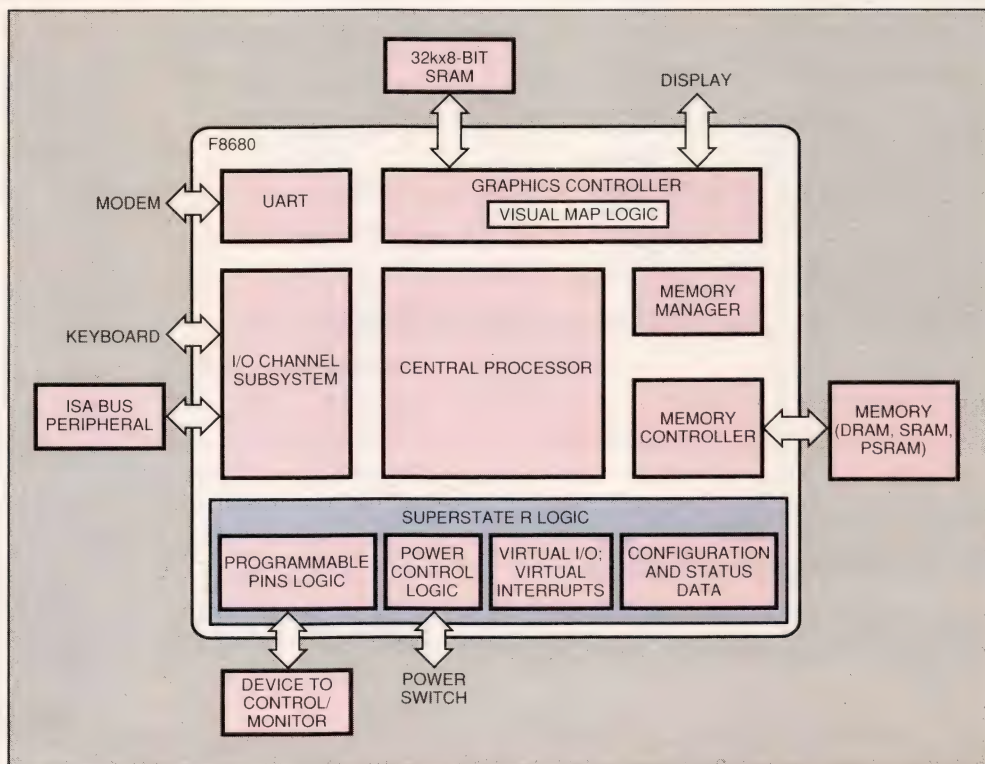Quick on Intel's heels, AMD introduced the 25- and 33-MHz Am386SXLV  $\mu$ P (25-MHz version, \$37 (1000)). This




The Chips and Technologies F8680 PC/Chip runs 8086 opcode, but delivers 80286 performance figures. A SuperState R mode lets you implement transparent power-saving states.



# 3.3 Volt Fast 256K SRAM

Available Today from IDT

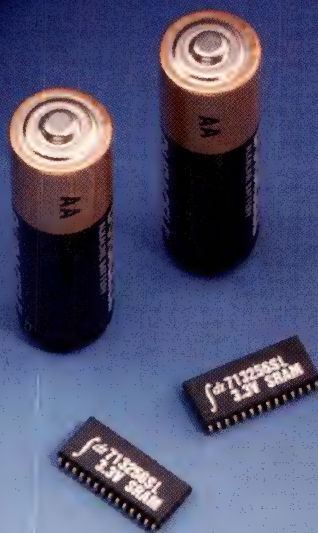

## A Fast 3.3V 256K SRAM

Our new IDT713256SL 3.3V 32K x 8 SRAM lowers power consumption by 57% and operates at speeds as fast as 20ns for zero-wait-state operation in 40MHz applications.

Packaged in a small-footprint 28-pin SOJ, the IDT713256SL meets the new JEDEC LVTTTL 3.3V standard, providing the only fast true 3.3V solution for low-power notebook cache and portable instrument data buffering.

## Good News for Notebooks/Instruments

The IDT713256SL is optimized for noise immunity, low power, and high speed to extend battery life in notebook computers and other portable equipment. And it features a 2V data retention mode and a low 500 $\mu$ A (max.) full standby current—up to a 20x improvement over recharacterized fast 5V SRAMs.

## Start Designing Today

Best of all, IDT's new 3.3V SRAM is available now at very competitive prices! So you don't have to wait to make your 3.3V design a reality.

## Win a Free 3.3V Notebook Computer

Call or FAX us today to receive a copy of the **Desktop & Notebook PC**

**Cache Solutions** booklet, **2 free**

**samples** of IDT's 3.3V 256K

SRAM, and an

entry form for a

drawing to win one of three 3.3V notebook computers.



Integrated Device  
Technology, Inc.

**(800) 345-7015 • FAX: 408-492-8674**

**ASK FOR KIT CODE 8081**



LOW-POWER  $\mu$ Ps

$\mu$ P is a clone of Intel's i386SX core and has a variation of SMM. In 1992, Cyrix introduced the Cx486SLC and Cx486DLC  $\mu$ Ps. Both  $\mu$ Ps run Intel's i486SX instruction set and feature another variation of SMM. At the end of 1992, Cyrix announced a 33-MHz enhanced version of the Cx486SL, called the Cx486SLC/e (25-MHz version, \$99 (1000)). Intel also introduced a new low-power  $\mu$ P, the i486 SL (low-voltage, 25-MHz version, \$227 (1000)) in the fourth quarter of 1992.

Because the Cx486SLC/e and i486 SL are recent introductions and carry the powerful 486 nomenclature, you can draw some logical comparisons. First, neither processor is simply a low-power version of the i486DX  $\mu$ P. Intel integrated a dynamic RAM


(DRAM) controller, a 16-bit ISA bus controller, and a 16-bit parallel interface (PI) bus controller on the i486 SL. The i486 SL runs object code for all 80x86  $\mu$ Ps and comes in a 196-pin plastic quad flatpack (PQFP), 208-pin shrink QFP (SQFP), or 227-pin LGA.

The 25- or 33-MHz i486 SL has a fully static 32-bit i486DX core and an i386 SL-compatible SMM. The core has an enhanced version of the i387 coprocessor and a 4-way, set-associative, 8-kbyte cache. Static registers let you stop the clock to conserve power without losing data. Static designs, which require a minimum clock rate to maintain data, are new to Intel, who previously used dynamic registers in 80x86 designs.

In contrast, the 20-, 25-, or 33-MHz Cx486SLC/e comes in a 100-

pin PQFP that has the same footprint as an i386SX  $\mu$ P, which is used in first-generation designs, but executes the i486SX instruction set. Internally, the chip is considerably different compared with the i486 SL. It has a 1-kbyte direct-mapped, or 2-way set-associative instruction and data cache. Instead of an FPU, the chip has a 16-bit hardware multiplier to accelerate graphics or handwriting-recognition algorithms.

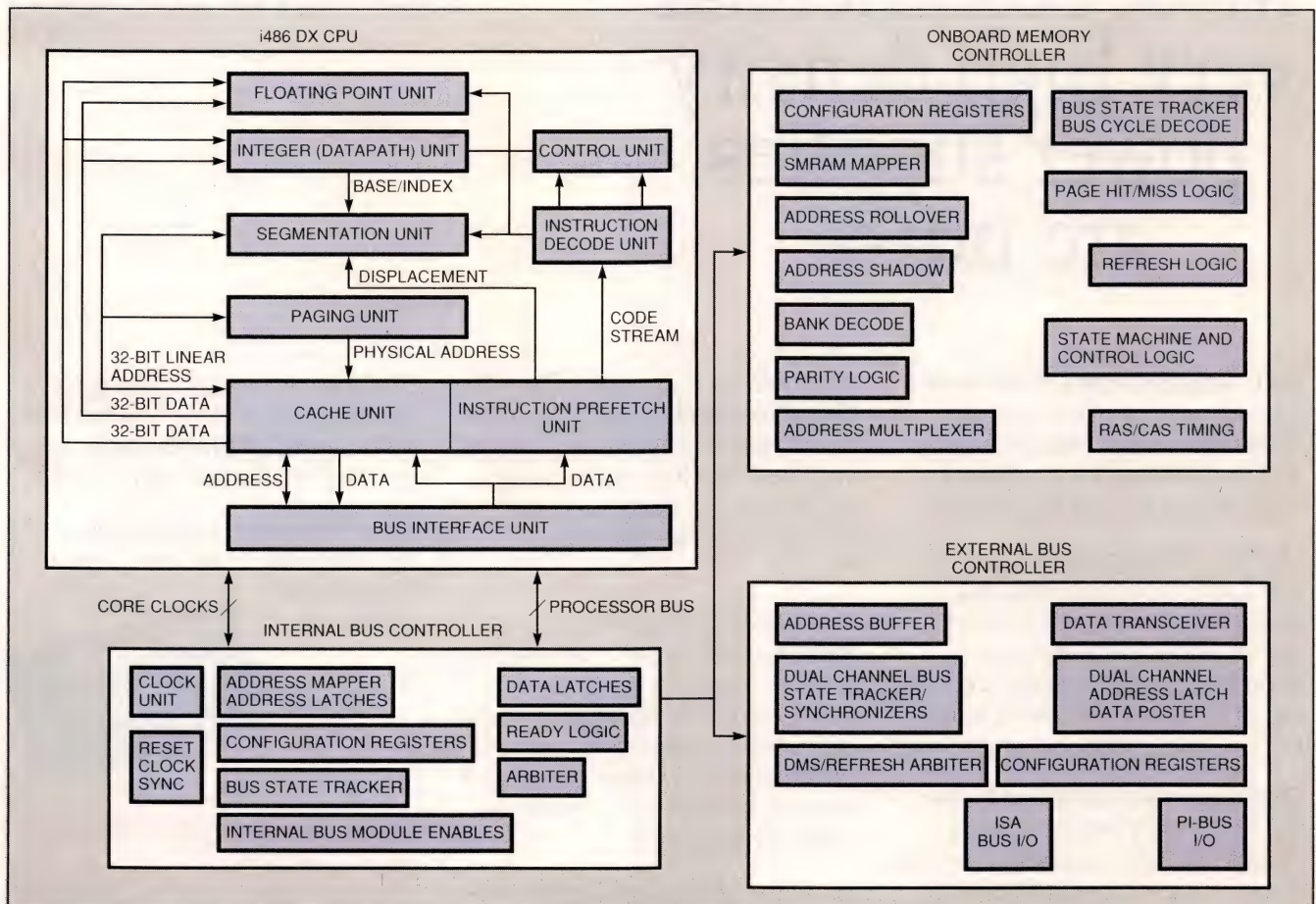
The Cx486SLC/e execution unit consists of a 5-stage pipeline, which overlaps code fetches, instruction decoding, microcode ROM accesses, execution, and writes back to memory or register. The RISC-like architecture permits most instructions to run in a single cycle. Although the Cyrix SMM is functionally equivalent to the Intel




The Intel i486 SL  $\mu$ P features a static 3.3V i486DX core and an i386 SL-compatible SMM. A DRAM controller and an ISA and PI bus controller are also on chip.



#### VARIABLE FREQUENCY SUPPLIES

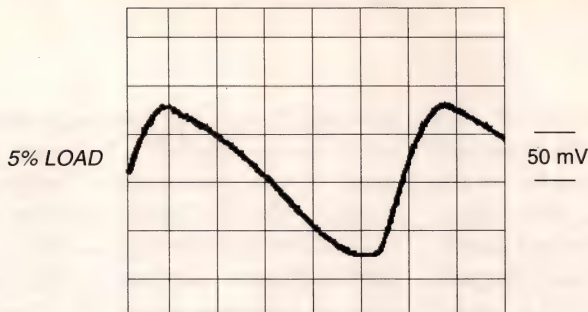


OUTPUT RIPPLE VS. LOAD

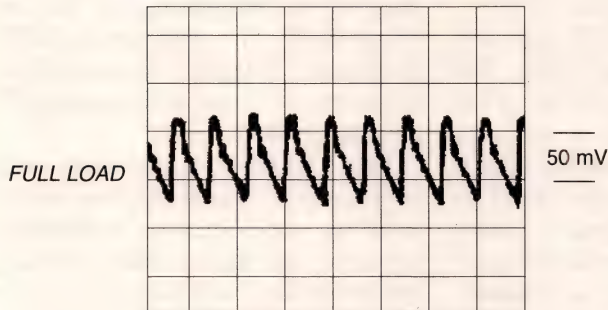

OUTPUT RIPPLE VS. LOAD

#### ABBOTT FIXED FREQUENCY SUPPLIES

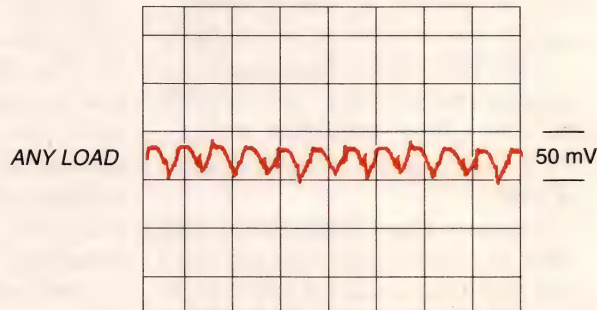

OUTPUT RIPPLE VS. LOAD

Most commercial  
very high density  
power supplies  
are noisy.

We said most.

With Abbott's new CP200 very high density (VHD) DC-DC converter, you won't need to design a filter the size of a shoebox to smooth output and input ripple.

Unlike variable frequency VHD units which change frequency every time the output current varies, the CP200 employs a fixed frequency topology, operating at a constant 400kHz switching rate. No matter what the load.

Offering power densities better than 50 Watts per cubic inch, Abbott CP200 converters provide rated outputs from 200 to 280 Watts at 5 to 28 Volts, including

5.2 VDC for ECL logic. They are board mountable using an industry standard footprint and height, with features that make designing advanced distributed and VMEbus power systems a breeze.

And CP200 converters provide reliability second to none in commercial applications from -20° to +85°C. With full input and output overvoltage protection, output current limiting, short circuit and thermal protection — for a surprisingly low price.

So when you're looking to minimize noise problems in your

VHD power system design, or eliminate them in a system that you already have in production, call Abbott for the new CP200.

The only noise you will have to deal with is the roar of your customers cheering.



Actual size:  
2.4" x 4.6" x 0.5"

**abbott**  
When reliability is imperative®



LOW-POWER  $\mu$ Ps

SMM, the differences provide some power-saving alternatives.

Implementing Intel's SMM also requires its companion, the 82360SL peripheral I/O chip. The chip has a host of on-chip peripherals that are common to an ISA bus computer design, such as DMA, communication, interrupt controllers, and timer counters. The chip generates the SMI to the CPU in response to external system events.

Similar to the i486-based architecture, both i486 SL and Cx486SLC/e  $\mu$ Ps have the same general-purpose, segment, instruction, and flag-pointer registers. The chips also have registers that let you access additional features. In the i486 SL  $\mu$ P you access these registers by enabling one of six different configuration spaces. Each configuration space is protected from accidental or unauthorized writes because each access can only occur when the configuration space is enabled.

You can enable a configuration space by writing a bit to a CPUPWR-MODE register, which in turn makes a host of configuration regis-


ters visible for the selected space. Because the configuration registers for Intel's SMM reside in the 82360SL chip, you must use this chip to implement SMM. Once the 82360SL configuration space is enabled, you write bits to the SM-REQ-CNTRL register using an index to initialize SMM or 00H to disable SMM features. Clock control registers let you control the speed or stop the clock to the CPU, DMA controller, keyboard controller, and math coprocessor depending on the power-management state.

SMM provides three power-management states: local standby, global standby, and suspend. Suspend is the lowest power state, which basically only powers the memory. A software HALT instruction, or the occurrence of an SMI triggered by a system event, enables SMM. When SMM is enabled, the CPU maps a special memory, called system-management RAM (SM-RAM), into the main memory space between 30000H and 3FFFFH. SM-RAM overlays the existing main memory in this region. The CPU saves the current CPU state in SM-

RAM starting at 3FFFFH and stops at 3FFA7H after 22 32-bit transfers.

The CPU then executes a user-written SMM handler code located at system address 38000H to implement power management. A resume (RSM) instruction placed at the end of the SMM handler returns the saved CPU state back to the interrupted application program. If there's an I/O instruction to a powered-down device, an I/O trap can initiate an SMI and cause the SMM handler to power-up the peripheral. The I/O instruction automatically reexecutes upon RSM-instruction execution.

The Cyrix SMM basically functions the same way, but variations can provide other design alternatives. The CPU has a bidirectional SMI pin and a separate address strobe pin (SMADS) to implement SMM. In addition, two separate pins, called suspend request (SUSP) and suspend acknowledge (SUSPA) can place the CPU into a suspend mode while the CPU is executing application software or SMM handler code. Because the SMM configuration registers are lo-

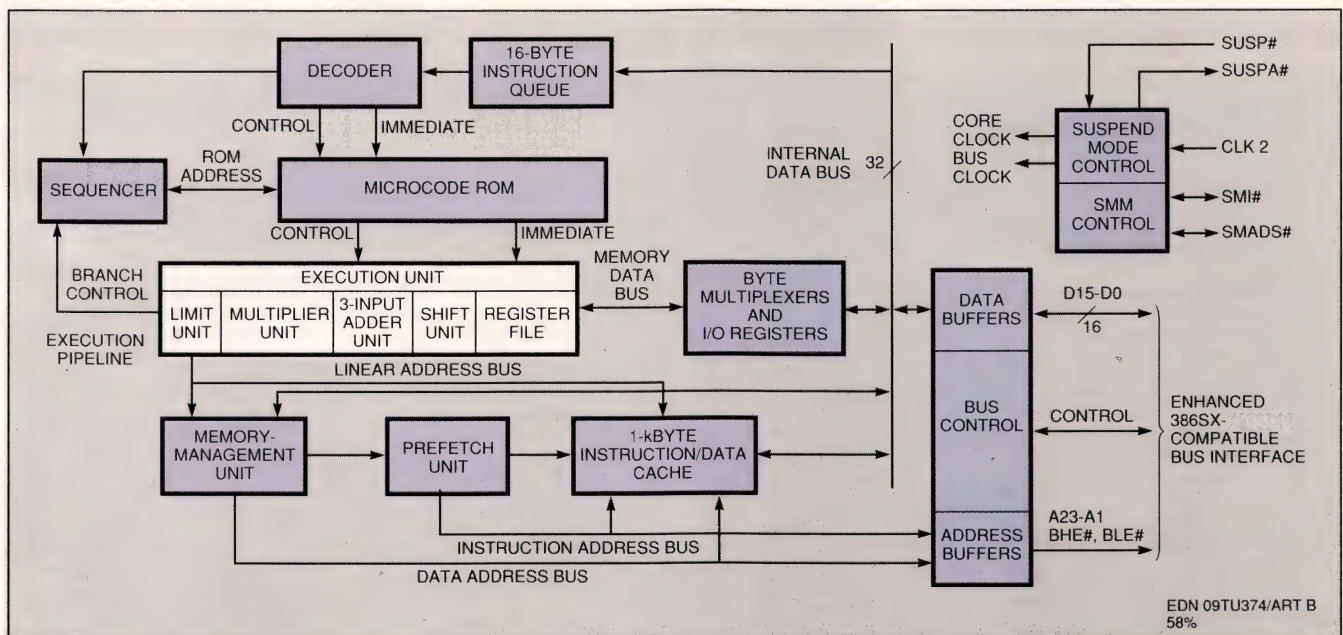

The Cyrix Cx486SLC/e  $\mu$ P features an i386SX bus-compatible interface, a 5-stage pipeline, and a hardware multiplier. A SUSP pin lets you enter a suspend state without using SMM.



LOW-POWER  $\mu$ Ps

cated on the CPU chip, SMM is not tethered to a particular peripheral I/O chip. Third-party core-logic chips, such as Headland's HT25 and VLSI's SCAMP II chip set, generate all of the necessary signals to implement the Cyrix SMM.

When an SMI occurs, the Cyrix CPU saves only a subset of the CPU state to SMM memory, which allows rapid entry and exit into SMM. Cyrix added a number of save and restore instructions, which leave you the option of implementing a complete or partial CPU state store. The SMM memory space can range from 4 kbytes to 16 Mbytes, and the base address is programmable to be a multiple of the memory space size. Execution of a resume instruction returns the CPU to the interrupted application program.

The SUSP and SUSPA pins provide a simple method for placing the CPU in the suspend state without having an SMI issued. Some designers, such as Bob Patti, president of ASIC Design Inc (Chicago, IL), finds managing register bits and flags in Intel's SMM "a software nightmare" and finds the extra two pins on the Cyrix chip an expedient alternative to implement the sus-

pend state. A software HALT instruction can also trigger the suspend state.

The AMD's version of SMM for the Am386DXLV and Am386-SXLV  $\mu$ Ps gives you additional options. AMD uses an SMI pin and two additional pins, called SMIADS and SMIRDY, to initiate and terminate bus cycles. When an SMI occurs it takes 61 32-bit transfers to save the entire CPU state into SM-RAM. Both INTR and NMI are disabled upon entry into AMD's SMM, whereas the Intel and Cyrix versions respond to these interrupts when executing SMM handler code.

AMD added a number of move instructions, called UMOVs, that let you move byte, word, or double-word register operands to or from main system memory while executing an SMM routine. In addition, the AMD chips have an I/O instruction break enable (IIBEN) input pin that lets system logic implement an I/O trap when an I/O instruction occurs to a powered-down peripheral.

Assertion of the IIBEN pin causes the CPU to drive the bidirectional SMI pin active and then execute handler code to power-up the pe-

ripheral. To reexecute the instruction, the handler code must copy the I/O instruction pointer over a default pointer. Both Headland and VLSI core logic chips have the necessary features to handle AMD's SMM.

Of course, all of these low-power  $\mu$ Ps utilize 3V power supplies in one fashion or another. Albeit slower, 3V logic can reap as much as 56% power savings over 5V logic. The Cx486SLC/e comes in 3 or 5V versions. AMD  $\mu$ Ps operate on a power supply ranging from 3 to 5.5V. Intel  $\mu$ Ps have a voltage-tuned 3V core and a flexible memory bus, PI bus, and ISA bus interface that operates from 3 or 5V.

Flexibility has been a watchword in early 3V designs. Many early designs have been plagued by promised—but still unavailable—3V system components. In fact, some horror stories tell of designers' needing to tweak a power-supply potentiometer to voltage-tune some early 3V components to meet specifications. In addition, some system peripherals on the ISA bus, such as floppy-disk drives, don't employ 3V power supplies. To accommodate these mixed-voltage conditions, designers must use ex-

## For more information . . .

For more information on the low-power  $\mu$ Ps discussed in this article, circle the appropriate numbers on the Information Retrieval Service card or use EDN's Express Request service. When you contact any of the following manufacturers directly, please let them know you read about their products in EDN.

**Advanced Micro Devices Inc**

901 Thompson Pl  
Sunnyvale, CA 94088  
(408) 732-2400  
TWX 910-339-9280

Circle No. 356

**AT&T Microelectronics**

Dept AL-500404200  
555 Union Blvd  
Allentown, PA 18103  
(800) 372-2447  
Fax (215) 778-4106

Circle No. 357

**Chips & Technologies**

3050 Zanker Rd  
San Jose, CA 95134  
(408) 434-0600  
Fax (408) 434-6452

Circle No. 358

**Cyrix Corp**

2703 N Central Expressway  
Richardson, TX 75080  
(214) 234-8387  
Fax (214) 699-9857

Circle No. 359

**Intel Corp**

2200 Mission College Blvd  
Santa Clara, CA 95052  
(408) 765-8080

Circle No. 360

**Motorola Inc**

Microprocessor & Memory  
Technologies Group  
6501 William Canon Dr W  
Austin, TX 78735  
(512) 891-3465

Circle No. 361

**VLSI Technology Inc**

1109 McKay Dr  
San Jose, CA 95131  
(408) 434-3000  
Fax (408) 263-2511

Circle No. 362

## VOTE . . .

Please also use the Information Retrieval Service card to rate this article (circle one):


High Interest 500 Medium Interest 501 Low Interest 502


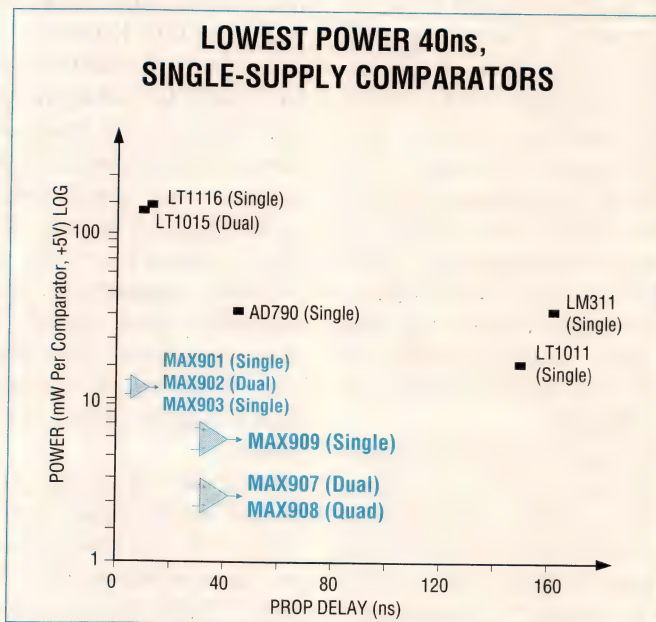
# LOWEST POWER, 40ns DUAL COMPARATOR IN 8-PIN SOIC!

5V Single-Supply Operation, 700 $\mu$ A Supply Current (3.5mW)

- ◆ +5V Operation
  - $\pm$ 5V Supply (MAX909)
- ◆ Quad Comparator in 14-pin Narrow SOIC
- ◆ Clean Output Switching
- ◆ Latched, Complementary Outputs (MAX909)
- ◆ No External Pull-Ups Required



These new single-supply comparators offer the highest speed at the lowest power. Supply current is only 700 $\mu$ A per comparator while propagation delay is a blazing 40ns (5mV overdrive). Internal hysteresis ensures clean output switching when driven by slow moving signals. The MAX907 is the only 40ns dual comparator in an 8-pin small outline package designed to operate from a single 5V supply.

## Choose the Fastest, Low-Power Comparators For Your Application

	Comparators Per Package	Prop Delay (ns)	Supply Current Per Comparator	Latched Outputs	Single Supply Operation	Package	Price†
NEW	MAX909*	Single	40	1.2mA	✓	8-pin DIP/SO	\$1.50
NEW	MAX907	Dual	40	700 $\mu$ A	✓	8-pin DIP/SO	\$1.70
NEW	MAX908	Quad	40	700 $\mu$ A	✓	14-pin DIP/SO	\$2.95
	MAX901	Quad	8	2.5mA	✓	16-pin DIP/SO	\$5.95
	MAX902	Dual	8	2.5mA	✓	14-pin DIP/SO	\$4.00
	MAX903	Single	8	2.5mA	✓	8-pin DIP/SO	\$3.15



**FREE Op Amp/Comparator Design Guide – Sent Within 24 Hrs!**

**Includes: Data Sheets and Cards for Free Samples**

**Call Toll Free 1-800-998-8800**

**For a Design Guide or Free Sample**

MasterCard® and Visa® are accepted for Evaluation Kits or small quantity orders.



Maxim Integrated Products, 120 San Gabriel, Sunnyvale, CA 94086, (408) 737-7600, FAX (408) 737-7194.

**Distributed by Arrow, Bell, Elmo, and Hall-Mark.** Authorized Maxim Representatives: **AL**, M2i Montgomery Marketing, Inc.; **AZ**, Techni Source Inc.; **CA**, Mesa, Pro Associates, Inc.; **CO**, Centaur Corporation; **CT**, NRG Limited; **DE**, TAI Corporation; **FL**, Sales Engineering Concepts; **GA**, M2i Montgomery Marketing, Inc.; **ID**, E.S. Chase; **IL**, Heartland Technical Marketing Inc.; **IN**, Technology Marketing Group; **IA**, JR Sales Engineering, Inc.; **KS**, Delltron; **LA**, BP Sales; **MD**, Micro-Comp, Inc.; **MA**, Comp Rep Associates; **MI**, Micro Tech Sales; **MN**, Mel Foster Technical Sales, Inc.; **MS**, M2i Montgomery Marketing, Inc.; **MO**, Delltron; **MT**, E.S. Chase; **NE**, Delltron; **NV** (Reno, Tahoe area only) Pro Associates, Inc.; **NH**, Comp Rep Associates; **NJ**, Parallax, TAI Corporation; **NM**, Techni Source Inc.; **NY**, Parallax, Reagan/Compar; **NC**, M2i Montgomery Marketing, Inc.; **OH**, Lyons Corporation; **OK**, BP Sales; **OR**, E.S. Chase; **PA** (Pittsburgh area) Lyons Corporation, (Philadelphia area) TAI Corporation; **SC**, M2i Montgomery Marketing, Inc.; **TN**, M2i Montgomery Marketing, Inc.; **TX**, BP Sales; **VA**, Micro-Comp, Inc.; **WA**, E.S. Chase.

**Distributed in Canada by Arrow. Authorized Maxim Representative in Canada: Tech Trek.**

† 1000up Recommended Resale FOB, USA. \* MAX909 with Complementary Outputs, Available After April 1993.



LOW-POWER  $\mu$ Ps

ternal voltage translators. The problem seems to be dissipating, however, as more 3V components with firm specifications are becoming available in 1993.

Not all designs require the computational power of a 386- or 486-compatible CPU. Many handheld units perform their duties using 8086 code. The 20-oz PC-Lite from Two Technologies (Horsham, PA), and the 2<sup>3</sup>/<sub>4</sub>-lb Handbook from Gateway 2000 (North Sioux City, SD) use Chips and Technologies' (C&T) F8680 PC/Chip. PC/Chip (\$47.50 for 8-MHz 3V version (1000)) runs 8086 opcodes, but a 4-stage pipeline and a 14-MHz clock deliver 80286 performance figures.

To implement power-management techniques, C&T introduced a supervisory mode, called SuperState R. SuperState R has its own hidden memory area, and an event such as an access to an I/O port,

an elapsed timer, or an external interrupt can automatically enter the mode. Ill-behaved code in the BIOS or application and terminate-and-stay-resident (TSR) programs cannot disable code written to execute in SuperState R mode.

Instead of slowing or stopping the clock to conserve power, the PC/Chip lets you insert a delay between instructions. SuperState R software can insert delays from 1 to 128 clocks. The delay lets instruction, memory-access, and data-transfer transactions occur at the specified clock speed. The technique eliminates stretching an active state, which is liable to consume power when clocks slow down.

A review of all the  $\mu$ Ps for low-power applications is not possible here, but two more processors are worth mentioning. The AT&T Hobbit ATT9200 chip set consists of five

devices: the Hobbit  $\mu$ P (\$35 (10,000)), system-management controller, PCMCIA (Personal Computer Memory Card International Association) controller, video-display controller, and an optional peripheral controller. The 3.3V chip set runs Go Corp's (Foster City, CA) Penpoint operating system, and EO Inc (Mountain View, CA) employs the chip set in its 440 and 880 personal communicators.

The Hobbit  $\mu$ P employs a 3-stage pipelined RISC architecture that has static branch prediction to minimize pipeline breaks. Instead of general-purpose registers, the  $\mu$ P has a 256-byte stack cache, which eliminates the need to save registers to external memory during procedure calls. The architecture is optimized for running C-language code and features fast interrupt response and context switching. A power-management mode can im-

## TCP/IP NETWORKING PROTOCOLS

### FUSION Developers Kit

#### ... for Embedded Systems

- Fusion TCP/IP protocol suite
- Flexible architecture - Csource code
- Used in hundreds of process control, embedded systems, and end-user designs
- Full support with consulting and porting services

#### ... for Windows

- Binary TCP/IP transport
- PDS for DOS
- Windows Sockets API

**PLEASE CALL US**



*Pacific Softworks*


*We accept Visa and Mastercard*

**1-800-541-9508** within the U.S.  
**1-805-484-2128** outside the U.S.  
**1-805-484-3929** FAX




# COMPLETE 1.44W TO 3W POWER-SUPPLY MODULES ARE NOW 6 TIMES SMALLER!

## FLASH MEMORY PROGRAMMING SUPPLY

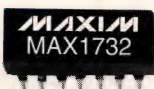

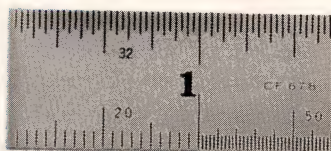14-Pin DIP Only 0.29" High  
0.27" x 0.77" x 0.29"




### MAX1732

- ◆ 12V, 120mA Output
- ◆ 14-Pin DIP Only 0.29" High:  
0.27" x 0.77" x 0.29"  
(6.86mm x 19.57mm x 7.37mm)
- ◆ 4V to 6V Input Range
- ◆ 85% Efficient
- ◆ 1.7mA I<sub>SUPPLY</sub>  
(70μA in Shutdown Mode)
- ◆ Reference Output
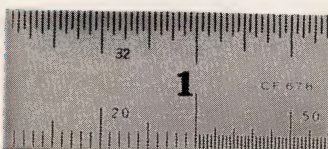
## STEPDOWN TO +5V



14-Pin DIP Only 0.29" High  
0.27" x 0.77" x 0.29"



### MAX1738

- ◆ +5V, 500mA Output
- ◆ 14-Pin DIP Only 0.29" High:  
0.27" x 0.77" x 0.29"  
(6.86mm x 19.57mm x 7.37mm)
- ◆ 6.6V to 16V Input Range
- ◆ 86% Efficient
- ◆ 1.7mA I<sub>SUPPLY</sub>  
(60μA in Shutdown Mode)
- ◆ Reference Output

## DUAL ±12V OR ±15V OUTPUTS



24-Pin Wide DIP Only 0.345" High  
0.57" x 1.27" x 0.345"



### MAX1743

- ◆ ±12V at 125mA or ±15V at 100mA Outputs
- ◆ 24-Pin Wide DIP Only  
0.345" High:  
0.57" x 1.27" x 0.345"  
(14.42mm x 32.32mm x 8.75mm)
- ◆ +5V Input
- ◆ 82% Efficient
- ◆ 20mA I<sub>SUPPLY</sub>  
(2.2mA in Shutdown Mode)
- ◆ Reference Output



**FREE Power Supply Design Guide – Sent Within 24 Hrs!**

Includes: Data Sheets

CALL TOLL FREE 1-800-998-8800

For a Design Guide or Free Sample

MasterCard® and Visa® are accepted for Evaluation Kits or small quantity orders.



Maxim Integrated Products, 120 San Gabriel, Sunnyvale, CA 94086, (408) 737-7600, FAX (408) 737-7194.

**Distributed by Arrow, Bell, Elmo, and Hall-Mark.** Authorized Maxim Representatives: **AL**, M2i Montgomery Marketing, Inc.; **AZ**, Techni Source Inc.; **CA**, Mesa, Pro Associates, Inc.; Centaur Corporation; **CO**, Component Sales; **CT**, NRG Limited; **DE**, TAI Corporation; **FL**, Sales Engineering Concepts; **GA**, M2i Montgomery Marketing, Inc.; **ID**, E.S. Chase; **IL**, Heartland Technical Marketing Inc.; **IN**, Technology Marketing Group; **IA**, JR Sales Engineering, Inc.; **KS**, Delltron; **LA**, BP Sales; **MD**, Micro-Comp, Inc.; **MA**, Comp Rep Associates; **MI**, Micro Tech Sales; **MN**, Mel Foster Technical Sales, Inc.; **MS**, M2i Montgomery Marketing, Inc.; **MO**, Delltron; **MT**, E.S. Chase; **NE**, Delltron; **NV** (Reno, Tahoe area only) Pro Associates, Inc.; **NH**, Comp Rep Associates; **NJ**, Parallax, TAI Corporation; **NM**, Techni Source Inc.; **NY**, Parallax, Reagan/Compar; **NC**, M2i Montgomery Marketing, Inc.; **OH**, Lyons Corporation; **OK**, BP Sales; **OR**, E.S. Chase; **PA** (Pittsburgh area) Lyons Corporation, (Philadelphia area) TAI Corporation; **SC**, M2i Montgomery Marketing, Inc.; **TN**, M2i Montgomery Marketing, Inc.; **TX**, BP Sales; **VA**, Micro-Comp, Inc.; **WA**, E.S. Chase.

**Distributed in Canada by Arrow. Authorized Maxim Representative in Canada: Tech Trek.**

Maxim is a registered trademark of Maxim Integrated Products. © 1993 Maxim Integrated Products

CIRCLE NO. 97

EDN April 29, 1993 • 47



# WE GO BEYOND OUR OWN APPROVAL

All too often when you buy a DC/DC converter, the manufacturers "test OK" stamp is the only approval you're going to get. Not so at Conversion Devices. Most of our products are approved to the latest revisions of UL 1950 and CSA 22.2 safety specifications.



We also subject every production unit to our rigorous reliability screening program that includes 72 hours of burn-in, power cycling and load switching. This level of stress testing virtually eliminates "infant mortality" considerably lowering your cost of ownership.

Our six hundred standard DC/DC converters range in power from 0.5W to 60 watts. Features include ultra-wide input voltage ranges, input/output isolation as high as 2.5kV, low profile cases and high MTBF's.

Based in Brockton MA, the Conversion Devices staff is available to provide the depth of ongoing engineering support, delivery service and cost savings required in today's competitive environment.

Ultimately, we strive for your approval and satisfaction.



**CONVERSION  
DEVICES, INC.**

EXCELLENCE IN POWER CONVERSION TECHNOLOGY

15 Jonathan Drive, Brockton, MA 02401  
Tel. (508) 559-0880 Fax (508) 559-9288

Call or Write  
For Your FREE  
Copy of Our  
Product Data

## EDN-TECHNOLOGY UPDATE

### LOW-POWER $\mu$ Ps

plement four states: full power, idle power, standby, and no power. The mode can also stop any system clock under software control.

Apple Computer chose the ARM (Advanced RISC Machine) 610  $\mu$ P for the heart of its Newton family of Personal Digital Assistants. Acorn and VLSI Technology codeveloped the ARM family and VLSI distributes it. ARM  $\mu$ Ps consist of functional system blocks (FSBs) surrounding a 32-bit ARM 6 RISC core.

The FSBs in the ARM 610 consist of a 4-kbyte instruction and data cache, a write buffer, a memory-management unit, and boundary-scan circuitry. The \$46.49 (1000) ARM 610 conserves battery power by having a low-transistor-count design. The chip draws less than 4.5 mA/MHz and operates as fast as 25 MHz.

Not all portable designs require the power of a CISC or RISC  $\mu$ P, however. Mark Freeman, staff engineer at Stratus Inc, a contract house in Seattle, WA, says that a Motorola MC68HC05  $\mu$ C is good enough for most of his portable designs. The chip is resplendent with on-chip peripherals and an instruction set that's adequate for embedded tasks.

The MC68HC05 has a WAIT instruction that disables CPU processing while the internal clock remains active. A STOP instruction turns off the internal clock. However, the designer must implement power management in external system logic to control power to external peripherals and to manage the system clock rate. High on Freeman's wish list is a  $\mu$ C having an MC68HC05 core and an internal programmable logic block, which could implement these power-saving features. Perhaps one of the  $\mu$ P vendors is listening. **EDN**

Article Interest Quotient  
(Circle One)

High 500 Medium 501 Low 502




# TRY TO DO THIS WITH ANY OTHER 275MHz AMPLIFIER

## Needs **NO** Feedback – Simple to Use

The MAX435 and MAX436's unique architecture provides accurate gain without feedback, eliminating loop-transmission phase shift—a primary cause of parasitic oscillations. And, unlike current feedback amplifiers, the MAX435/MAX436 are easier to use since their inputs are fully symmetric, high-impedance, and tolerate wide differential input voltages without saturation.

- ◆ High CMRR: 53dB at 10MHz
- ◆ 850V/ $\mu$ s Slew Rate
- ◆ 18ns Settling Time
- ◆ Symmetric, Differential Inputs
- ◆ Low Wideband Noise:  $7nV/\sqrt{Hz}$
- ◆ Single Ended Output (MAX436)  
– Differential Output (MAX435)

### Difference Amp with Gain & Filtering

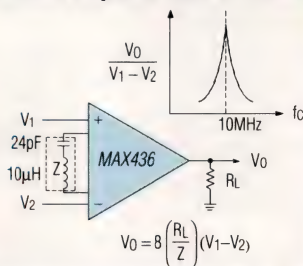


### Wideband Transconductance Amplifier is So Simple to Use
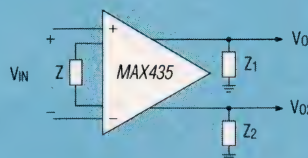
#### TWO EQUATIONS:

$$V_{O1} = K \left( \frac{Z_1}{Z} \right) V_{IN}$$


$$V_{O2} = -K \left( \frac{Z_2}{Z} \right) V_{IN}$$




\*  $K = 4 \pm 2.5\%$  (MAX435),  $8 \pm 2.5\%$  (MAX436)

GAIN IS SET BY A RATIO OF TWO IMPEDANCES AND AN INTERNAL CURRENT-GAIN FACTOR (K).


### Difference/Sum of Differences

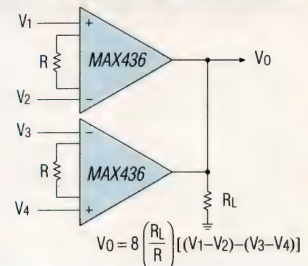

### Differential Line Driver

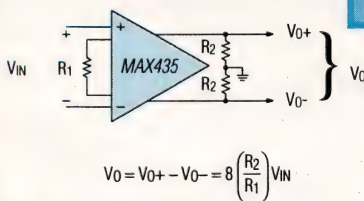

### Phase Splitter

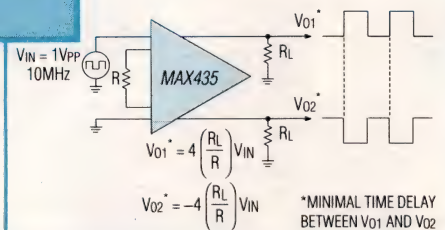

**Free Op Amps, Video & Comparators Design Guide – Sent Within 24 Hrs!**

**CALL TOLL FREE 1-800-998-8800**

**For a Design Guide or Free Sample**

Master Card® and Visa® are accepted for Evaluation Kits or small quantity orders.

# MAXIM

Maxim Integrated Products, 120 San Gabriel, Sunnyvale, CA 94086, (408) 737-7600, FAX (408) 737-7194.

**Distributed by Arrow, Bell, Elmo, Hall-Mark, and Nu Horizons.** Authorized Maxim Representatives: **AL**, M2i Montgomery Marketing, Inc.; **AZ**, Techni Source Inc.; **CA**, Mesa, Pro Associates, Inc.; Centaur Corporation; **CO**, Component Sales; **CT**, NRG Limited; **DE**, TAI Corporation; **FL**, Sales Engineering Concepts; **GA**, M2i Montgomery Marketing, Inc.; **ID**, E.S. Chase; **IL**, Heartland Technical Marketing Inc.; **IN**, Technology Marketing Group; **IA**, JR Sales Engineering, Inc.; **KS**, Delltron; **LA**, BP Sales; **MD**, Micro-Comp, Inc.; **MA**, Comp Rep Associates; **MI**, Micro Tech Sales; **MN**, Mel Foster Technical Sales, Inc.; **MS**, M2i Montgomery Marketing, Inc.; **MO**, Delltron; **MT**, E.S. Chase; **NE**, Delltron; **NV** (Reno, Tahoe area only) Pro Associates, Inc.; **NH**, Comp Rep Associates; **NJ**, Parallax, TAI Corporation; **NM**, Techni Source Inc.; **NY**, Parallax, Reagan/Compar; **NC**, M2i Montgomery Marketing, Inc.; **OH**, Lyons Corporation; **OK**, BP Sales; **OR**, E.S. Chase; **PA** (Pittsburgh area) Lyons Corporation, (Philadelphia area) TAI Corporation; **SC**, M2i Montgomery Marketing, Inc.; **TN**, M2i Montgomery Marketing, Inc.; **TX**, BP Sales; **VA**, Micro-Comp, Inc.; **WA**, E.S. Chase.

**Distributed in Canada by Arrow. Authorized Maxim Representative in Canada: Tech Trek.**

Maxim is a registered trademark of Maxim Integrated Products. © 1993 Maxim Integrated Products.

CIRCLE NO. 98



# POWER-ONE

## D.C. POWER SUPPLIES

### Not Only The Best...The Best Selection, Too



#### SWITCHERS

POWER-ONE'S International Switcher Series incorporates the latest state-of-the-art switching technology while providing POWER-ONE's traditional high quality at low prices. With certification to the world's toughest safety agency requirements, the series is especially suited for products sold not only domestically, but internationally as well. • 85 models... 40 watts to 400 watts • Efficient... reliable... economical • VDE construction • Up to 5 fully regulated outputs • Full international safety and EMI approvals

#### LINEARS

POWER-ONE'S International Linear Series is the world's undisputed leader in versatile, cost-effective linear power supply products. A long-time favorite of designers and engineers worldwide, the series is the most widely purchased power supply line through distribution in the industry. The most popular voltage and current combinations are available in a wide variety of off-the-shelf standard models. • Popular industry standard packages • 77 models... 6 watts to 280 watts •  $\pm 0.05\%$  regulation • Up to 4 fully regulated outputs • Worldwide safety approvals



#### HIGH POWER



POWER-ONE'S International High Power Series is a true fully-modular high power product line. Specify a power system that meets your exact requirements from a wide selection of single, dual and triple output plug-in power modules. Virtually any combination of output voltage and current rating can be delivered from stock. • 500 watts to 2,000 watts • Fully modular construction • Up to 15 fully regulated outputs • UPS battery backup option • Parallelable outputs with current sharing • Power Factor Correction optional

**TOLL FREE  
LITERATURE  
HOT-LINE:  
(800) 678-9445**



POWER-ONE offers one of the largest selections of switcher, linear, and high power standard models in the world. Most models available off the shelf from authorized distributors. So, whatever your D.C. power supply requirement, make POWER-ONE your first choice and be sure you're getting the best—quality, selection, value and quick delivery. Call today for our new Reference Guide and the location of our closest authorized distributor.

"Innovators in Power Supply Technology"  
**POWER-ONE**  
**D.C. POWER SUPPLIES**

POWER-ONE, INC.  
740 Calle Plano • Camarillo, CA 93012-8583  
Phone: (805) 987-8741 • FAX: (805) 388-0476





## Two firms reduce the cost of adding color to DSO displays

Scopes with color displays offer obvious advantages, but until now, those advantages commanded a high price. When you view several waveforms at once, color makes them easy to tell apart. Depending on how a scope implements color, a multihued display can supply information that is missing from most monochrome DSOs' raster displays, but is inherently present in an analog scope's gray scale. A color scope can also ease the task of telling when two waveforms do and don't coincide. In the past, the problem with color-display scopes was that most were expensive; some cost well over \$30,000; others cost close to \$60,000. Now however, Gould and Tektronix have altered the cost picture for scopes with color displays.

Thanks to new technology, both firms are offering color-display DSOs for about \$500 more than the closest equivalent monochrome models. Gould's Datasys 700 series uses an active matrix LCD. You may ask what's new about that; laptop PCs have had active-matrix


color displays for at least two years. But the Gould scopes' double-diode-and-reset technology is quite different from that of PCs' thin-film-transistor active-matrix displays. Liquid-crystal technology is also at the heart of the Tek displays. The TDS 544A and 644A do use CRTs, however. The color results from combining a liquid-crystal shutter with a CRT that uses a 180-Hz field-sequential raster scan.

Both techniques produce stunningly bright, clear traces. On a pure pixel-count basis, Tektronix leads Gould by a wide margin. The resolution of the Tek displays is equivalent to the 640×480 pixels of a PC's VGA (video graphics array) adapter. Because the scopes' 7-in. diagonal screens are much smaller than those of most PCs' color monitors, the effect is exceptional. Gould's pixel counts are lower—256×230. But you have to see the Gould display to believe it. Your first impression will be that the 6-in. (diagonal) screen *must* be a CRT. The tiny white text characters are more readable than those

on many displays that have 10× as many pixels.

Despite the technological achievements embodied in the displays, the vendors like to mention the color feature almost in passing. What they most want you to hear about are the scopes' other advanced capabilities.


Whereas all of these scopes offer color at a modest premium over monochrome, the Gould and Tektronix units really don't compete. The \$7500 Gould unit has 150-MHz bandwidth and can take 100M samples/sec/channel. To make full use of its bandwidth, you must operate it in the random-repetitive sampling mode where it acquires the necessary samples from multiple waveform occurrences. The \$16,750 Tek TDS 544A has four 250M-sample/sec ADCs and a bandwidth of 500 MHz. With one channel active, the scope can combine all four ADCs to take 1G samples/sec, just enough to acquire a 500-MHz signal in real time. The \$21,490 4-channel TDS 644A always samples in real time. It has a 500-MHz band-

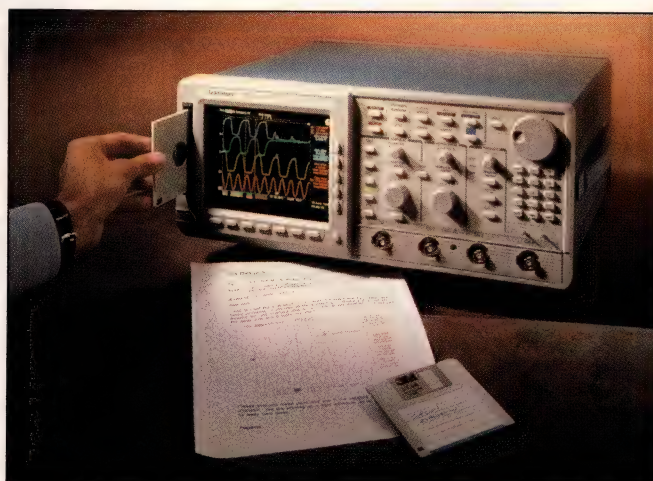

In addition to color, the Gould Datasys 740 (left) offers on-screen readout in user-defined engineering units and a "learn" mode that makes short work of using the front panel to create scope-control programs. The Tektronix TDS 544A (right) and 644A include 3½-in. MS-DOS-compatible floppy-disk drives.


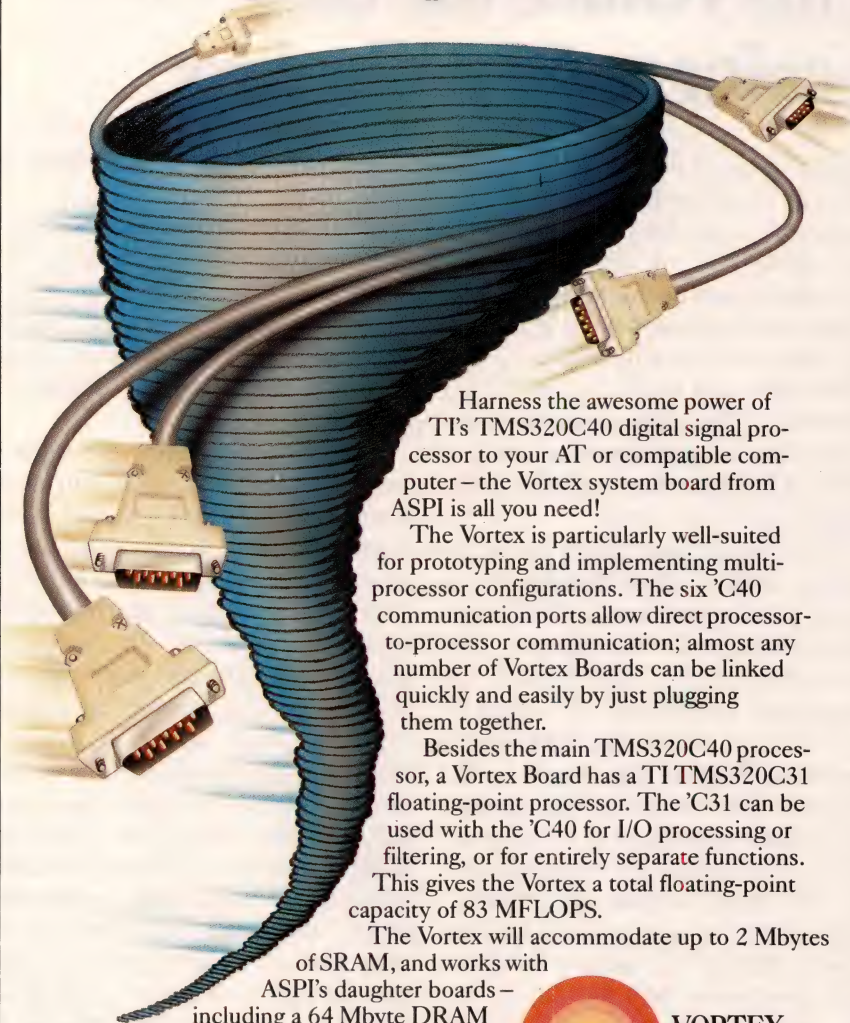
# VORTEX™ Concentrates I/O for top 'C40 performance



Harness the awesome power of TI's TMS320C40 digital signal processor to your AT or compatible computer – the Vortex system board from ASPI is all you need!

The Vortex is particularly well-suited for prototyping and implementing multi-processor configurations. The six 'C40 communication ports allow direct processor-to-processor communication; almost any number of Vortex Boards can be linked quickly and easily by just plugging them together.


Besides the main TMS320C40 processor, a Vortex Board has a TI TMS320C31 floating-point processor. The 'C31 can be used with the 'C40 for I/O processing or filtering, or for entirely separate functions. This gives the Vortex a total floating-point capacity of 83 MFLOPS.

The Vortex will accommodate up to 2 Mbytes of SRAM, and works with ASPI's daughter boards – including a 64 Mbyte DRAM board, digital audio interface and general A-D/D-A systems.

Ask today for full details on this remarkable new DSP system.



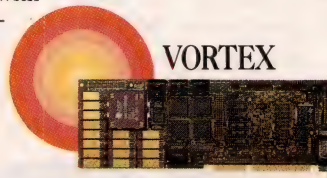Atlanta Signal Processors, Inc. • 770 Spring Street  
Atlanta, GA 30308 USA  
(404) 892-7265 • FAX: (404) 892-2512



CIRCLE NO. 70

## DID YOU KNOW?

EDN serves  
electronic engineers and  
engineering managers in more than  
100 countries worldwide.

**EDN**

width and can take 2G samples/sec/channel.

The Gould products have several features that are unusual in scopes at the \$7500 price. One is a 50k-sample memory. A zoom capability lets you expand a waveform segment by as much as 1000× and display it beneath the original. The scope also offers a roll (strip-chart) mode that is useful for observing slow phenomena. A host of mathematical operations includes low-pass filtering, "live" multiplication of waveforms, and FFTs. When you work with transducers, the scopes can suppress offsets and scale readings in the engineering units of your choice.

The Tektronix scopes, though similar to the monochrome TDS 540 and 640 that were announced in 1991, incorporate several improvements besides color. One feature not shared by the monochrome units is a 1.44-Mbyte, 3½-in. MS-DOS-compatible floppy-disk drive. Both color scopes also offer a \$1495 video-triggering option that lets them trigger on a variety of currently used video-broadcast formats as well as several proposed HDTV formats. In addition, a FlexFormat capability permits triggering on user-defined HDTV formats and on specific color fields.

The TDS 544A also lets you segment its memory (15,000 points/channel standard; 50,000 optional) and use the different segments to store successive single-shot events at rates to 50,000 events/sec. With a 50,000-point memory, the scope can store 910 waveforms.

—Dan Strassberg

Gould Inc, 8333 Rockside Rd,  
Valley View, OH 44125. Phone  
(216) 328-7000. FAX (216) 328-7400.

Circle No. 387

Tektronix Inc, Box 1520,  
Pittsfield, MA 01202. Phone (800)  
426-2200.

Circle No. 388



## 10-BIT ANALOG-TO-DIGITAL CONVERTER

So easy-to-use, it opens a new window of software programmability.

### ■ Dynamic Reconfiguration

A: >reconfig ADC10158\01011010

### ■ Software-Programmable Functions

#### Conversion speed/resolution

- 4.4  $\mu$ s max at 10-bit plus sign
- 3.2  $\mu$ s max at 8-bit plus sign

#### Multiplexer

- Single-ended
- Differential
- Pseudo-differential



#### Output Data Format

- Left or right justified

### ■ Key Features

- Single +5V or  $\pm$ 5V operation
- 33mW power consumption at 5V
- 166KHz sampling rate (10-bit plus sign)
- On-board 2.5V voltage reference
- Sample-and-hold
- 0-5V input with 5V supply
- -5V to +5V input with  $\pm$ 5V supply
- Ratiometric or absolute voltage measurements
- $\pm$ 1.5LSB total unadjusted error
- Guaranteed no missing codes over temperature
- ADC10154 - four input channels
- ADC10158 - eight input channels

### ■ ADC10158 Block Diagram

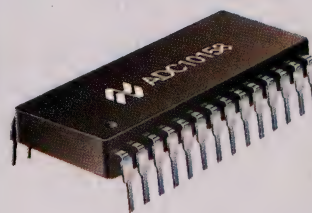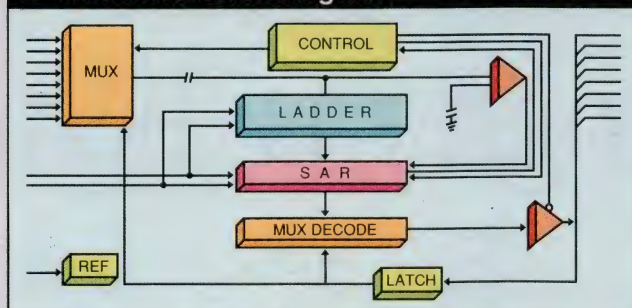

Introducing the industry's first software-programmable 10-bit ADC.

Simply put, our latest ADCreation — the ADC10158 — is open to suggestions.

Now you can change your conversion speed, reconfigure your mux, or adjust your out-

put data format. All with just a few easy keystrokes. However and whenever you'd like.

Which means you get "on-the-fly" optimized system performance, while consuming just 33mW of power.

It also means that — now — you can put design flexibility at your fingertips.

Our lines are open.

For free samples and datasheets, call: 1-800-NAT-SEMI, Ext 145.  
Or, fax: 1-800-888-5113.

**National**  
Semiconductor



**NEW!**  
PCMCIA memory  
card support!



# Prototyping to production – UniSite programs them all.

Whether you want to program devices one at a time or eight at a time, UniSite™ Universal Programmer is the programmer of choice for both design engineers and production personnel. UniSite is the most widely used programmer in the world, because it's the most flexible programmer ever built.

For designers, UniSite is the premier universal programmer. It supports



more devices than any other programmer including FPGAs, PLDs, memory devices, and micro-controllers, all from a single site. It supports more types of packages—including an expanding array of high-pin-count devices—from QFPs, TSOPs, and SOICs to DIPs, PGAs, QUIPs, and PC memory cards. And UniSite is always first to support new devices.

In production, no programmer is easier to set up and operate than

UniSite. This single, compact, rugged system gives you everything you need for reliable gang programming. Manufacturer-certified algorithms ensure high yields. Automatic yield tally and either manual or computer remote control give you all the features and flexibility you need.

For more programming flexibility, start and finish with UniSite. For more information, or a demonstration, call:

**1-800-3-DataIO**  
(1-800-332-8246)

Outside North America contact your local Data I/O representative.

**Austria**  
0222 253626

**Belgium**  
02 252 3690

**Denmark**  
042 458320

**Eastern Europe**  
49 089 858580

**Finland**  
90 8036211

**France**  
013 9568131

**Germany**  
089 858580

**Greece**  
172 49511

**Ireland**  
031 953000

**Italy**  
02 618 1893

**Netherlands**  
040 582911

**Norway**  
02 901190

**Portugal**  
01 410 3420

**Spain**  
01 2425204

**Sweden**  
08 380370

**Switzerland**  
49 089 858580

**United Kingdom**  
0734 440011

# DATA I/O



# Mathcad 4.0 enhances computations under Windows 3.1

Mathcad 4.0, the latest upgrade to Mathsoft's Mathcad, features a rule-based processor, called Smartmath, which simplifies numeric and symbolic computations. Smartmath reduces symbolic expressions, including integrals and derivatives, before Mathcad computes them. Just like Mathcad's numerical calculations, Smartmath recomputes a symbolic result whenever any of the equations it depends on change.


Mathcad 4.0 runs under Windows 3.1 as a 32-bit application using WIN32S libraries. The software requires a 386- or 486-based PC that runs DOS 3.1 or later and has a minimum of 4 Mbytes of RAM. The company recommends a math coprocessor and 8 Mbytes of virtual memory. Mathcad 4.0 runs twice as fast as previous versions and lets you manipulate virtually unlimited data arrays at one time.

As an alternative to the calculator, Mathcad 4.0 features a toolbar of icons for executing numeric and symbolic calculations; cut-and-paste numbers, which enable you to move data to and from Mathcad to a spreadsheet; and autoscrolling, which lets you scroll through a Mathcad document with a single mouse click. The Auto-equation feature lets you enter equations and text anywhere and then aligns the elements vertically and horizontally; drag and drop lets you highlight part of an equation and move it anywhere. The upgrade also includes extensive new mathematics and graphing features, such as polar and contour plotting, trailing zeros, and  $n$ th derivative operators.

Mathcad 4.0 supports Microsoft's Object Linking and Embedding (OLE) software for both client and server, which lets you transfer data and graphics between Mathcad and

other OLE-compliant software, such as Lotus 1-2-3, Microsoft Word, and Excel. Mathcad 4.0 also provides Dynamic Data Exchange (DDE), which lets other Windows-based applications use Mathcad as a server for complex calculations.

*calculus, Calculus, and Differential Equations.* The Educational Library targets students, as well as secondary- and college-level educators. These tools allow users to work with "live" mathematics and explore math concepts without do-

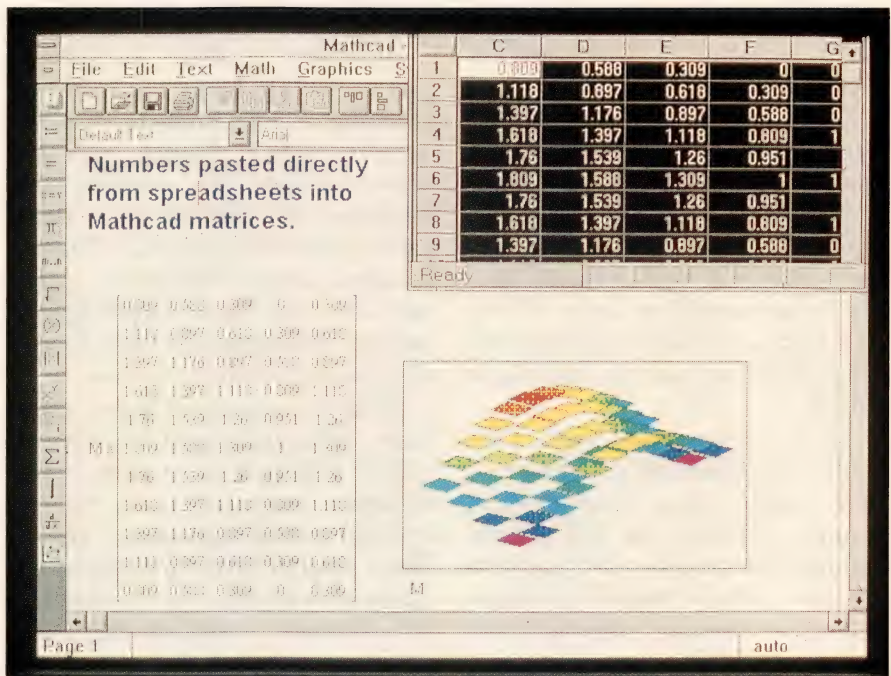

Mathcad 4.0 for Windows 3.1 lets you cut and paste data from a spreadsheet into Mathcad matrices.

Mathsoft also introduced three electronic handbooks, which provide Mathcad 3.1 (or later) users with interactive, accessible technical data. The handbooks are *Theory and Problems of Electric Circuits* from Schaums' Outline Series, Mathsoft's *Topics in Mathcad: Advanced Math*, and *Electrical Engineering*. Schaums' handbook costs \$69; the other two handbooks cost \$99 (all three require Mathcad 3.1 or later and 1 to 3 Mbytes of hard-disk space).

In addition, five new handbooks for the Mathcad Education Library include *Algebra I*, *Algebra II*, *Pre-*

ing routine, repetitive work. The handbooks, which cost \$69, require Mathcad 3.1 or later. Mathcad 4.0 requires 4 Mbytes of memory and costs \$495 (upgrades cost \$49.99).

—John Gallant

Mathsoft Inc, 201 Broadway, Cambridge, MA 02139. Phone (617) 577-1017. FAX (617) 577-8829.

Circle No. 389



# 14- and 16-bit ADCs speed past the 1-MHz mark

High-speed and high-resolution A/D converters are reaching new performance levels. Analogic Corp introduces a 16-bit, 2-MHz device, and start-up Edge Technology announces a deluge of new products, including a series of 16-bit, 1- to 3-MHz converters and higher-speed 14-bit converters and data-acquisition systems.

Edge Technology's ET1663 is the first 3-MHz, 16-bit ADC. And, along with the specifications listed in Table 1, the ET1663 boasts less than 1 LSB of noise. In designing the 2-MHz ADC4344, Analogic doubled the sampling rate of the ADC4322, a 1-MHz predecessor and reduced the package size to a 46-pin hybrid.

All of the converters listed in the table are sampling converters—they include either front-end S/H (sample-and-hold) or T/H (track-and-hold) amplifiers. The converters also include precision voltage references, timing circuitry, and some sort of 16-bit quantizer.

The ADC4322 uses a 2-pass, subranging architecture that includes a very stable 16-bit linear

reference DAC. This converter's S/H amplifier provides low noise (28 nV/√Hz), jitter of 5 psec, and a full-scale step response of 250 nsec for time-domain applications. Noise is typically 90  $\mu$ V rms for a 10V p-p full-scale range. The part requires  $\pm 15$  and 5V supplies.

Designers at Edge Technology use monolithic parts and a unique trimming scheme to produce its converters, which require  $\pm 15$  and  $\pm 5$ V supplies. The company also packages the converters in metal cases, which combined with the converters' power consumption, eliminate the need for an external heat sink and minimizes electrostatic and electromagnetic interference.

All of the converters have a maximum differential nonlinearity of  $\pm 0.75$  LSB and no missing codes. However, comparing these converters' dynamic specifications is tricky. Even though both manufacturers quote an S/N ratio, each uses different methods to specify distortion. Analogic uses peak distortion, total harmonic distortion (THD), and THD plus noise. These specs are -92 dB max, -86 dB max, and

83 dB min, respectively, for 100-kHz, 0-dB inputs. For the ET1663 family, Edge Technology quotes a spurious-free dynamic range of 92 dB min and SINAD (S/N ratio and distortion) of 83 dB min with 100-kHz, -0.5-dB inputs. The spurious-free dynamic range is typically 100 dB for 5-kHz inputs.

Edge Technology's DAS4504 and DAS4808 are 4-channel, 5-MHz, and 8-channel, 8-MHz data-acquisition systems, respectively. These systems have all the components of the company's 14-bit tracking converters in addition to input multiplexers and buffer amplifiers.

—Anne Watson Swager

Analogic Corp, 360 Audubon Rd, Wakefield, MA 01880. Phone (508) 977-3000, ext 2089. Fax (617) 245-1274.

Circle No. 385

Edge Technology, 15 Pine St, Lynnfield, MA 01940. Phone (617) 334-3330. Fax (617) 334-3539.

Circle No. 386

**Table 1—High-speed, 14- and 16-bit sampling ADCs and data-acquisition systems**

Vendor	Part no.	Resolution (bits)	Sampling rate (MHz, max)	S/N ratio (dB)	Package type	Power dissipation (typical W)	Price (100)
Analogic Corp	ADC4322	16	2	86 min, 90 typ (100-kHz, 0-dB input)	1.5 x 2.38 x 0.225-in. hybrid	2.6	\$995
Edge Technology	ET1663	16	3	90 min, 92 typ (100-kHz, -0.5-dB input)	3 x 4 x 0.4-in. module	3.8	\$1795 or \$1995
	ET1662		2				\$950 or \$1295
	ET1661		1				\$499 or \$599
	ET1465	14	5	80 min, 82 typ (100-kHz, -0.5-dB input)	3 x 4 x 0.4-in. module	1.8	\$495 or \$795
	ET1471	14	10	80 min, 82 typ (500-kHz, -0.5-dB input)	3 x 4 x 0.4-in. module	4.2	\$1250 or \$1495
	DAS4504	14	5	80 min, 82 typ (100-kHz, -0.5-dB input)	3 x 4 x 0.4-in. module	2	\$821 or \$971
	DAS4888		8			4.7	\$1688 or \$2021

Note: Edge Technology offers two versions of its products; the lower price is for industrial versions.



# Micron SRAMs

**FASTER**

Speeds

**Wider**

Configurations

**smaller**  
Packages

**LOWER**

Power and Voltage

## Smarter solutions.

Today your design challenges require smart choices.

At Micron, we offer a wide variety of SRAM solutions for virtually any design requirement. This includes low-power, 3.3-volt, high-speed SRAMs for faster program execution. And smaller packaging and wider configurations to save board space and reduce cost.

Plus we provide engineering support and design

materials that help you work smarter and keep your competitive edge.

So when your requirements call for faster, wider, smaller, lower-power or lower-voltage SRAMs, think Micron. Phone 208-368-3900 now for your free copy of Micron's 1993 SRAM Data Book. And make the smart choice.



**MICRON**  
SEMICONDUCTOR, INC.




Micron Europe Limited, Centennial Court, Easthampstead Road, Bracknell, Berkshire RG12 1JA, U.K. Tel: 44 344 360055, Fax: 44 344 869504  
Micron Semiconductor (Deutschland) GmbH, Marsstrasse 3, D-8011 Aschheim, Germany Tel: 49 89 9030021, Fax: 49 89 9043114

© 1993, Micron Semiconductor, Inc.

CIRCLE NO. 91

EDN April 29, 1993 • 59



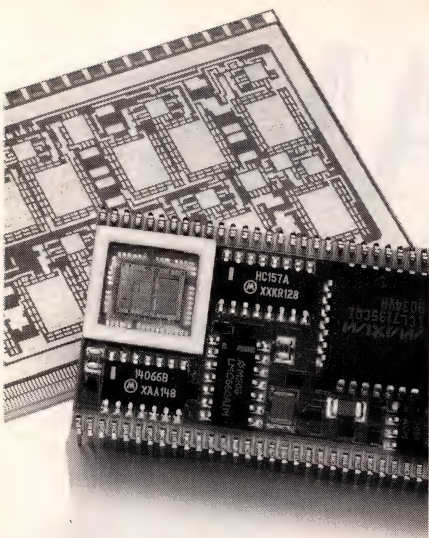


## THICK FILM SUBSTRATES & HIGH DENSITY HYBRIDS

When your designs are long on circuitry and short on real estate, we have your solution. Consider our cost effective Thick Film Multilayer Substrates and High Density Hybrids. We can offer 100% tested Multilayer Substrates as the base for your high density hybrid applications. **And, we can populate them for you, too!**
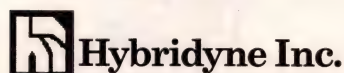
### Our Capabilities Include:

- CAD System Design
- Extensive Engineering Design Services
- In-House Screen Production
- 3 mil Lines & Spaces
- Double Sided Multilayers
- Printed Through Holes
- Resistors on Dielectric
- SMT and/or Chip-And-Wire
- CO2 Laser—Scribe & Drill
- YAG Laser—Active/Passive Trim
- Automated Isolation/Continuity Testing
- And, more. Much more.

From simple one or two layer commercial parts to the most complex designs, we build in quality, performance, and reliability to meet the most demanding applications. Call us with your requirements. *We'd like to talk with you.*



**Hybridyne Inc.**

2155 North Forbes Blvd., Tucson, AZ 85745  
(602) 629-0001 FAX (602) 791-3899

CIRCLE NO. 79

60 • EDN April 29, 1993

## Video op-amp prices drop to new depths

Almost unbelievably, you can now buy some video op amps for under \$2 in 100-piece quantities. Prices for larger quantities drop much lower. Amplifiers in dual and quad packages, which sometimes have less impressive specs than the single versions, are as low as \$1.12 per amp.

The products in **Table 1** join high-speed amplifiers from Analog Devices, Elantec, and Linear Technology, as well as from Burr-Brown, Comlinear, Harris Semiconductor, Maxim Integrated Products, National Semiconductor, and SGS-Thomson. The competition between these vendors seems most intense with current-feedback devices, but many high-speed amplifiers use the voltage-feedback topology.

In addition to 3-dB bandwidth, other specifications that differentiate high-speed amplifiers—especially those tailored for video applications—are output current, differential gain and phase, and gain flatness.

The LT1252 current-feedback op amp features differential gain of 0.01% and phase of 0.09°. The dual and quad versions feature 0.03°

and 0.28° differential gain and phase, respectively. The AD818 voltage-feedback device features 0.05° and 0.01% differential phase and gain. Differential gain and phase for the EL2x44 family are 0.04% and 0.15°, respectively. The EL2x60 devices specifications are 0.04% and 0.1°.

For a video amplifier, 100 mA is a high output drive. The EL2x60 has a minimum and typical output current of 60 and 100 mA, respectively. The LT1252 has a minimum output current of 30 mA; the AD818, 50 mA; and the EL2044 minimum is 50 mA. The 0.1-dB bandwidth of the AD818 is 55 MHz, compared to the LT1252's 30 MHz. —**Anne Watson Swager**

Analog Devices Inc, 181 Ballardvale St, Wilmington, MA, 01887. Phone (617) 937-1428. Fax (617) 821-4273.

**Circle No. 382**

Elantec, 1996 Tarob Ct, Milpitas, CA, 95035. Phone (408) 945-1323. Fax (408) 945-9305.

**Circle No. 383**

Linear Technology Corp, 1630 McCarthy Blvd, Milpitas, CA, 95035. Phone (408) 432-1900. Fax (408) 434-0507.

**Circle No. 384**

**Table 1—Recently introduced low-cost, high-speed op amps**

Vendor	Part no.	Characteristics	Price (100)
Analog Devices Circle No. 382	AD818	100-MHz bandwidth at gain of -1. 50-mA output current. 7.5-mA supply current. (Higher-speed version of company's '817.)	\$1.99
	AD826/828	Dual versions of '817 and '818.	\$2.99/\$3.99
Elantec Circle No. 383	EL2044/2244/2444	Singles, duals, and quads at 60-MHz, unity-gain-stable bandwidth. 5.2-mA supply current.	\$1.80/\$2.95/\$3.95
	EL2260/2460	Dual and quad 100-MHz bandwidth.	\$5.20/\$8.40
Linear Technology Circle No. 384	LT1252/3/4	90- to 100-MHz bandwidth. 0.1-dB flatness to 30 MHz.	\$1.75/\$2.49/\$4.49



# MI GR

# 8

*Migrate with the  
leader to a whole  
new level of 8-bit  
performance, more  
easily than you  
ever imagined.  
Starting May 10.*



**MOTOROLA**



EDN MAGAZINE PRESENTS:

# MOBILE EXPO '93

"THE ELECTRONICS TRADE SHOW ON WHEELS"

## This travelling showcase of electronic products is coming your way!

Check the schedule on the opposite page for the date and time we will be visiting your company. Take a few minutes while the exhibit is on-site to see and learn about the latest product innovations from the leading group of electronic suppliers listed below. Exhibitor representatives will be available to explain and demonstrate products and answer your questions.

Just stop by the large display trailer during the posted show times and climb aboard!



ELCO CORPORATION  
PADS SOFTWARE, INC.  
HEWLETT-PACKARD COMPANY  
HARRIS SEMICONDUCTOR, INC.  
VISHAY RESISTIVE SYSTEMS  
DALE ELECTRONICS, INC.  
OHMTEK – A VISHAY COMPANY  
SPRAGUE – A VISHAY COMPANY  
LeCROY CORPORATION  
NATIONAL INSTRUMENTS CORPORATION  
McKENZIE TECHNOLOGY  
POWERCUBE CORPORATION  
BASLER ELECTRIC COMPANY  
INDUSTRIAL ELECTRONIC ENGINEERS, INC.



# MOBILE EXPO '93

## Tentative Site Itinerary May 10 to June 23 (2nd Half)

DATE	TIME	LOCATION	DATE	TIME	LOCATION
5/10 Monday	9:00-11:00 AM	RAYTHEON ELECTRO-MAGNETIC SYSTEMS 6380 Hollister Avenue, Goleta, CA	5/28 Friday	2:30-4:00 PM	INTEL CORPORATION (Jones Farm) 2111 N.W. 25th Ave., Hillsboro, OR
5/10 Monday	12:00-3:00 PM	DELCO SYSTEMS OPERATIONS 6767 Hollister Avenue, Goleta, CA	6/1 Tuesday	9:30-12:00 AM	PARAMAX CORPORATION, A UNISYS COMPANY 640 North 2200 West, Salt Lake City, UT
5/11 Tuesday	8:30-10:30 AM	HUGHES MISSILE SYSTEMS COMPANY 8433 Fallbrook Avenue, Canoga Park, CA	6/1 Tuesday	1:00-3:00 PM	E-SYSTEMS INC., Montek Div. 2268 South 3270 West, Salt Lake City, UT
5/11 Tuesday	11:30-1:30 AM-PM	LITTON GUIDANCE & CONTROL SYSTEMS 5500 Canoga Avenue, Woodland Hills, CA	6/3 Thursday	9:00-12:00 AM	STORAGE TECHNOLOGY CORPORATION 2345 Clover Basin Dr., Longmont, CO
5/12 Wednesday	9:30-1:00 AM-PM	JET PROPULSION LABORATORIES 4800 Oak Grove Drive, Pasadena, CA	6/3 Thursday	1:00-4:00 PM	STORAGE TECHNOLOGY CORPORATION 2270 South 88th Street, Louisville, CO
5/12 Wednesday	2:15-4:15 PM	LORAL LIBRASCOPE CORPORATION 833 Sonora Avenue, Glendale, CA	6/4 Friday	8:30-11:00 AM	AT&T BELL LABORATORIES 11900 N. Pecos Street, Denver, CO
5/13 Thursday	10:00-2:00 AM-PM	LAWRENCE LIVERMORE LABORATORIES 7000 East Avenue, Livermore, CA	6/4 Friday	12:00-3:00 PM	MARTIN MARIETTA CORPORATION 12257 Colo. State Hwy. 121, Littleton, CO
5/14 Friday	8:30-10:30 AM	WATKINS-JOHNSON COMPANY 3333 Hillview Avenue, Palo Alto, CA	6/7 Monday	9:00-11:30 AM	DIGITAL EQUIPMENT CORPORATION 301 Rockrimmon Blvd. S., Colorado Springs, CO
5/14 Friday	11:30-2:30 AM-PM	LOCKHEED MISSILES & SPACE COMPANY 1111 Lockheed Way, Sunnyvale, CA	6/8 Tuesday	12:00-3:00 PM	BOEING COMMERCIAL AIRPLANE CO. 3801 So. Oliver, Wichita, KS
5/17 Monday	9:00-11:30 AM	SUN MICROSYSTEMS, INC. 2550 Garcia Avenue, Mountain View, CA	6/9 Wednesday	9:00-11:30 AM	ALLIED SIGNAL AEROSPACE, BENDIX/KING 400 North Rogers Road, Olathe, KS
5/17 Monday	1:00-4:00 PM	SILICON GRAPHICS 2011 N. Shoreline Blvd., Mountain View, CA	6/9 Wednesday	1:00-3:00 PM	WILCOX ELECTRIC 2001 N.E. 46th Street, Kansas City, MO
5/18 Tuesday	8:30-11:00 AM	APPLE COMPUTER, INC. 20650 Valley Green, Cupertino, CA	6/10 Thursday	9:00-12:00 AM	ALLIED SIGNAL AEROSPACE 2000 East 95th Street, Kansas City, MO
5/18 Tuesday	1:00-3:30 PM	APPLIED SIGNAL TECHNOLOGY 160 Sobrante Way, Sunnyvale, CA	6/11 Friday	9:00-12:00 AM	McDONNELL DOUGLAS CORPORATION Lindbergh & McDonnell Blvd., St. Louis, MO
5/19 Wednesday	8:30-11:00 AM	3COM CORPORATION 5400 Bayfront Plaza, Santa Clara, CA	6/14 Monday	9:00-12:00 AM	ROCKWELL INTERNATIONAL, COMML' AVIONICS 400 Collins Road N.E., Cedar Rapids, IA
5/19 Wednesday	11:45-1:30 AM-PM	STANFORD TELECOM, INC. 2421 Mission College Blvd., Santa Clara, CA	6/14 Monday	1:00-2:30 PM	ROCKWELL INTL', COLLINS DEFENSE 855 5th Street N.E., Cedar Rapids, IA
5/19 Wednesday	2:15-4:15 PM	SCHLUMBERGER TECHNOLOGIES 1601 Technology Drive, San Jose, CA	6/15 Tuesday	9:00-1:00 AM-PM	IBM CORPORATION Hwy 52 & Northwest 37th St., Rochester, MN
5/20 Thursday	8:30-10:00 AM	WATKINS-JOHNSON COMPANY 2525 North First Street, San Jose, CA	6/16 Wednesday	10:00-12:30 AM-PM	HONEYWELL INC., MILITARY AVIONICS 1625 Zarthan Avenue, St. Louis Park, MN
5/20 Thursday	11:00-1:00 AM-PM	LORAL WESTERN DEVELOPMENT LABS 3200 Zanker Road, San Jose, CA	6/16 Wednesday	1:30-3:30 PM	HONEYWELL INC., COMML' FLIGHT SYSTEMS 8840 Evergreen Blvd., Coon Rapids, MN
5/20 Thursday	2:00-4:00 PM	CONNER PERIPHERALS INC. 3061 Zanker Road, San Jose, CA	6/17 Thursday	8:30-10:00 AM	ADC TELECOMMUNICATIONS 5900 Clearwater Ave., Minnetonka, MN
5/21 Friday	9:30-12:00 AM	UNISYS CORPORATION 2700 North First Street, San Jose, CA	6/17 Thursday	10:30-12:00 AM	ADC TELECOMMUNICATIONS 11311 K-Tel Dr., Minnetonka, MN
5/24 Monday	9:00-12:00 AM	BOEING COMMERCIAL AIRPLANE (Main Campus) 3003 West Casino Road, Everett, WA	6/17 Thursday	1:00-3:00 PM	PARAMAX SYSTEMS, A UNISYS COMPANY 3333 Pilot Knob Road, Eagan, MN
5/24 Monday	1:00-4:00 PM	BOEING COMMERCIAL AIRPLANE (Everett Mall) 906-1010 S.E. Everett Mall Way, Everett, WA	6/18 Friday	9:00-11:00 AM	JOHNSON CONTROLS, INC. 507 E. Michigan Ave., Milwaukee, WI
5/25 Tuesday	10:00-2:00 AM-PM	BOEING MILITARY AIRPLANE CO. 9725 East Marginal Way, Seattle, WA	6/18 Friday	12:00-2:00 PM	ALLEN-BRADLEY COMPANY 1201 South 2nd Street, Milwaukee, WI
5/26 Wednesday	8:00-12:00 AM	BOEING KENT SPACE CENTER South 212th Street, Kent, WA	6/21 Monday	10:00-1:00 AM-PM	SUNDSTRAND ADVANCED TECHNOLOGY 4747 Harrison Avenue, Rockford, IL
5/26 Wednesday	1:30-4:00 PM	BOEING KENT SPACE CENTER EAST 68th Avenue So., Kent, WA	6/22 Tuesday	9:00-11:00 AM	HONEYWELL INC. 1500 W. Dundee Road, Arlington Heights, IL
5/27 Thursday	8:30-11:00 AM	BOEING COMMERCIAL AIRPLANE 8th & Park Streets, Renton, WA	6/22 Tuesday	12:00-2:30 PM	MOTOROLA RADIO-TELEPHONE SYSTEMS 1421 W. Shure Drive, Arlington Heights, IL
5/27 Thursday	12:00-2:30 PM	SUNDSTRAND DATA CONTROL 15001 N.E. 36th Street, Redmond, WA	6/23 Wednesday	9:30-12:00 AM	AT&T BELL LABORATORIES (Indian Hill Main) 2000 N. Naperville Rd., Naperville, IL
5/28 Friday	8:30-10:30 AM	INTEL CORPORATION (Hawthorne Farms) 5200 Elam Young Pkwy., Hillsboro, OR	6/23 Wednesday	1:00-3:00 PM	AT&T/NCR CORPORATION (Indian Hill West) 1100 E. Warrenville Rd., Naperville, IL
5/28 Friday	11:30-1:30 AM-PM	INTEL CORPORATION (Cornell Oaks) 15201 N.W. Greenbrier Pkwy., Beaverton, OR			

**Check the site itinerary above for the date and time we visit your company.  
Make a point to attend this unique mobile exhibit and see the very latest in new  
products and services from this year's exhibitors.**



# The idea.



# The genius.



## FREE

**70 page  
Application Notebook**

**1-800-4-LeCroy**

**(1-800-453-2769)**

---

### 9300 Series Digital Oscilloscopes

---

The Idea is simple. Catch signals with your oscilloscope, then get them onto paper, into your lab notebook, or professional-looking reports. Or maybe you want to analyze them on your PC.

That used to mean instant photos, or printer interfaces, plug-in cards, cables and "utility" software. And lots of wasted effort.

The Genius is LeCroy's 9300 series oscilloscopes. With built-in Printers and DOS-compatible floppy drives, they let you concentrate on your circuit. While we look after the paperwork.



## Motorola's 68360 communications controller moves to 32 bits

There are two ways to do higher-bandwidth communications processing: go to a faster CPU or use built-in hardware to handle specialized protocol processing. Motorola took the second route with its 68302, combining a 68K CPU with dedicated communications hardware, including a microprogrammed line processor. Now, to meet rising bandwidth needs, the company has extended the 302 architecture to a full 32 bits of processing (a more powerful CPU). Running with a 25-MHz clock, the 68360 Quad Integrated Communications Controller (QUICC) can run four channels and/or protocols concurrently, with data rates up to 2.048 Mbps/channel.

Instead of the 68302's 68000 16-/32-bit CPU, the 68360 relies on the CPU32+, a stripped-down 68020 (less MMU and cache-management instructions). At 25 MHz, the CPU delivers approximately 4.5 native MIPS peak. The company sped up internal operations with a 32-bit, on-chip intermodule bus. This bus, a variation of the 683xx family bus, serves as the on-chip system bus, as well as a mechanism for integrating new modules onto the chip.

The 68360 uses the same basic microprogrammed communications processor as the 68302 to process data on to and off of the serial I/O lines. And, like the 68302, the 68360 relies on dual-ported RAM to move data between the CPU32+ and the communications controller. However, the 68360's static RAM (SRAM) is 2.5 kbytes, compared with the 68302's 1152 bytes.


The 68360 also features four SCCs (serial communication channels), each of which can automatically handle (with the communications processor) eight standard

communications protocols. Additionally, the  $\mu$ P has four general-purpose, 16-bit timers (you can cascade two to a 32-bit timer), two IDMA (independent DMA) channels for high speed, 32-bit data transfers, buffer chaining, and independent request/acknowledge logic.

Each SCC can handle multiple protocols through a combination of dedicated hardware and microprogram support. The built-in communications protocols are HDLC/SDLC, HDLC bus, UART, Bi-Synch, Signaling System 7, Local-Talk, Transparent Mode, and Ethernet (68EN360 on the first serial channel). Communications hardware includes two serial management controllers (SMC), a SPI

(serial peripheral interface), and an optional parallel port. Also, a dedicated Time-Slot Assigner (TSA) integrates the serial channels to the single Time-Domain Multiplexed (TDM) bus. The TSA makes it easy to implement TDM interfaces to T1, CEPT, IDL, GCI, ISDN, or Primary Rate protocols. The TSA multiplexes a channel into or from each time division slot. It handles two TDM lines simultaneously.

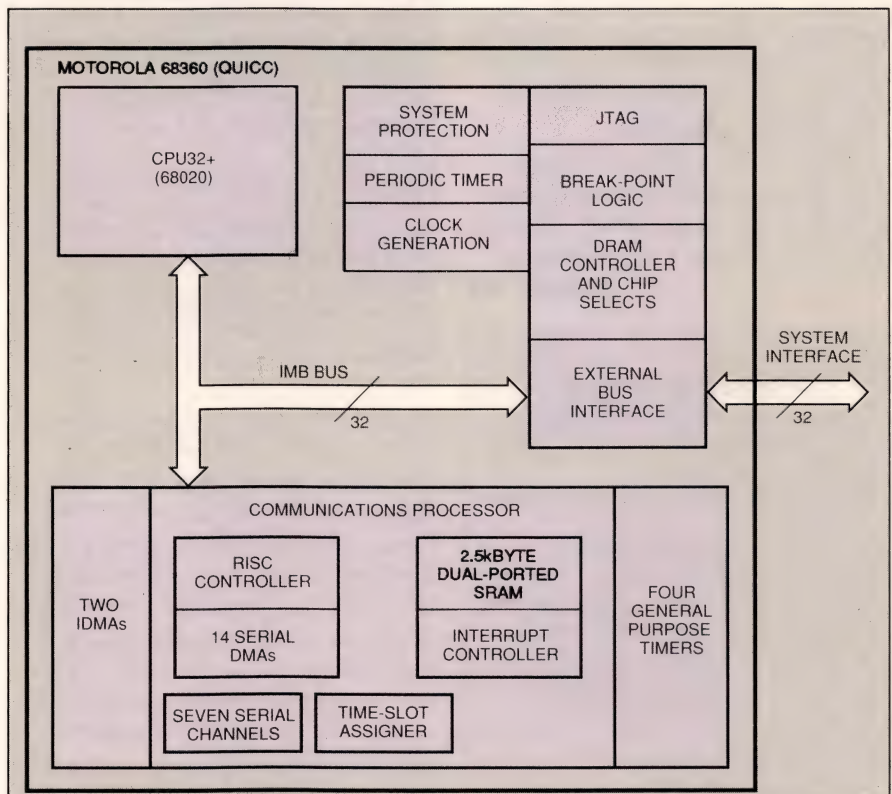Also, for the first time, Ethernet is built into a 683xx communications controller. The 68EN360, a version due in September, implements the Ethernet MAC (media access) layer in hardware and microcode. Thus, with this controller on your mother board, you can easily build a bridge



**Built around a 68020, the 68360 can simultaneously process four complex communications protocols. It features dedicated communications hardware, including a microprogrammed processor.**



between a WAN and a local Ethernet LAN on any desktop.

For more processing power, you can run the 68360 slaved to a 68040. In Slave Mode, the 68360's processor is locked up, and the chip functions as a peripheral chip to the external processor. If the processor is sufficient, but you need more channels, you can slave one 68360 to another.

Additionally, the 68360 requires a minimum of support logic. You can just add memory and start the 68360 running. An on-chip memory controller interfaces to SRAM, DRAM, Flash, and EEPROM. The 68360 handles up to eight memory banks, with up to 15 programmable wait states.

For evaluation and debugging code, Motorola supplies a QUICC Application Development System (QUADS), which includes a board with a 68360 for evaluation. You can also use it as a low-cost ICE by plugging it into a target board and relying on the 68360's background debug mode for control. QUADS costs \$1995.—**Ray Weiss**

*Motorola Inc, Microprocessor and Memory Technologies Group, 6501 William Canon Dr W, Austin, TX 78735. Phone (512) 891-2000.*

**Circle No. 393**

#### Motorola 683xx

##### communications controller

- 25-MHz clock
- CPU32+ (68020 core)
- Microprogrammed communication CPU
- 2.5-kbyte dual-ported SRAM
- 32-bit IMB internal-chip bus
- Glueless memory interface, memory controller—SRAM, DRAM, EEPROM
- External bus: dynamic sizing (8, 16, 32 bits); 28- to 32-bit address
- On-chip hardware breakpoints
- 4 SCCs
- 7 external interrupts
- 240-lead PQFP, PGA
- \$49.90 (10,000) sample qty
- Ethernet, \$59.90 (10,000)

## 24-bit DSP chip drops power to 165 mW at 40 MHz

Many designers equate DSP chips with high-throughput, math-oriented processing, but not low-power operation. Not true. As DSP  $\mu$ Ps move into mainstream embedded processing, they're taking on many properties of the microcontrollers they're competing with. Motorola's 24-bit 56002 DSP family is easing down the power-dissipation curve: The 3V DSP56L002 dissipates 165 mW (typ) while running at 40 MHz.

The DSP56002/1 24-bit processor family fills the gap between low-end

unlike earlier family members. In addition, peripherals—including memories—that the chip does not use or address are switched off to save additional power.

Because the DSP56L002 is a static chip, you can put it to sleep and then stop the clock entirely to really cut power. The on-chip PLL lets you adjust the clock rate to run no faster than needed for a given application. The PLL's 12-bit divider lets you select a clock rate from 10 kHz to 40 MHz.

A classic DSP architecture, the DSP56L002 has automatic hardware loop control, two data-address generators, and multiple internal address and data buses for high-speed, parallel operations. The external interface comprises a 16-bit data bus and 24-bit address bus. The three separate address spaces (X data, Y data, and P program) let you fetch the next instruction, retrieve the next X and Y parameters, and execute the instruction all within the 3-stage pipeline.

—**Ray Weiss**

*Motorola Inc, Microprocessor and Memory Technologies Group, 6501 William Cannon Dr W, Austin, TX 78735. Phone (512) 891-2030. Fax (512) 891-3874.*

**Circle No. 396**

#### Motorola DSP56L002 24-bit DSP $\mu$ P

- 40-MHz clock (static); programmable PLL, 10 kHz to 40 MHz
- 24-bit ALU fed by internal data paths; 2 56-bit accumulators
- 3-stage pipeline, 50-nsec/stage
- 3 data RAMs (256, 256, and 512 24-bit words)
- 2 256-word, 24-bit program ROMs
- External bus: 24-bit addr, 16-bit data
- On-chip emulation-support circuitry
- 3 external interrupts
- 3.3V, 165 mW (typ)
- \$47 (1000) in 132-pin plastic QFP

16-bit DSP chips and the faster, more expensive 32-bit DSP  $\mu$ Ps. Twenty-four bits provide a large data word for digital audio, telecommunications, and consumer applications. Like most DSP chips, the 56002/1 is pipelined and delivers apparent single-cycle execution for most instructions. Its peak performance approaches 25 native MIPS.

The low-power DSP56L002 is fully pin and instruction compatible with earlier 56001/2 DSP chips. Motorola engineers reworked the chip only to reduce power. The new chip is fully static and entirely CMOS,

## TMS370C 8-bit $\mu$ C moves up to 32 kbytes of ROM/EPROM

Today's 8-bit  $\mu$ Cs can take on more and more work. Yesterday's 4- and 8-kbyte memory sizes are no longer large enough for today's more complex applications. Now, TI's TMS370C series 8-bit  $\mu$ Cs can handle applications that need up to 32 kbytes of on-chip program memory.

The TMS370 family of 8-bit  $\mu$ Cs



# SIGNAL PROCESSING. GRIZZLY?


Designing a signal processing system can be a bear of a problem—immense, mean, and unforgiving. Engineers grappling with conventional analog or digital technologies face risk and unpredictability at every turn, with no guarantee of success. Designers invest months of development time in a brutal design process that's as lengthy as it is frustrating. Productivity and time to market are devoured in the struggle!

## SPROC Technology Tames The Task

At the core of STAR Semiconductor's unique signal processing solution is the SPROC™ chip, the first-ever programmable signal processor using the "Sketch and Realize™" design approach. With a single SPROC chip and a SPROClab development system, signal processing becomes a tame task.

Why wrestle with circuit breadboards crawling with sensitive analog components? Or agonize over line after line of assembly code? One SPROC chip integrates the functionality of hundreds of analog and passive components to cut system costs. And SPROClab employs system-level graphical programming so you can capture designs as signal flow block diagrams. You gain all the benefits of a digital solution—**without writing software!**

Stop laboring with trial-and-error debug methods, cumbersome logic analyzers, or software simulators to debug a design! Engineers using SPROC technology download designs **directly** onto actual silicon and interactively debug systems as they execute in **real time!** Using the SPROC chip's unique built-in probe feature, you can easily modify design specifications to tune system performance during execution.

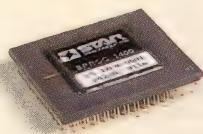

With SPROC technology, engineers focus on designing to create better products in less time.

If you can't bear to see your productivity mauled by the problems of signal processing design, call STAR Semiconductor at **908/647-9400**. We'll send you a brochure and demo disk telling how to tame your next signal processing project.

STAR Semiconductor Corporation  
25 Independence Boulevard, Warren, NJ 07059  
Telephone: (908) 647-9400 FAX: (908) 647-4755

## SPROC Users Slash Development Time

APPLICATION	PREVIOUS TECHNOLOGY	PREVIOUS DEV. CYCLE	SPROC DEV. CYCLE	\$ SAVINGS (1st YEAR)
Secure FSK modem	analog	6 months	<b>3 weeks</b>	<b>\$50,000†</b>
Adaptive noise canceler	DSP	6 months	<b>1 week</b>	<b>\$57,500*</b>
Power supply controller	analog	6 months	<b>1 day</b>	<b>\$60,000*</b>
Closed-loop vibration controller	analog	3 months	<b>2 weeks</b>	<b>\$240,000†</b>

†Total system savings including project overhead, engineering resource, and system hardware costs.  
\*Estimated savings in engineering resource based on cost of \$10,000 per man month.



The Signal Processing Company

CIRCLE NO. 65



FINALIST

**50MHz SPROC  
Now Available!**



is designed for low-end and automotive applications. The TMS370Cx58 controller combines 32 kbytes of ROM/EPROM with 1 kbyte of static RAM (SRAM) and 256 bytes of EEPROM.

The TMS370 8-bit  $\mu$ C family has a surprisingly full set of peripherals, including an A/D converter, a watchdog timer, a serial communications interface (SCI), a serial peripheral interface (SPI), and complex timers.—**Ray Weiss**

*Texas Instruments Inc, Semiconductor Group, Box 809066, Dallas, TX 75380. Phone (800) 336-5236, ext 3990.*

**Circle No. 397**

#### TMS370Cx58 8-bit $\mu$ C

- 2- to 20-MHz clock (internal div-by-4)
- 256 registers in RAM
- 32-kbyte ROM/EPROM, 1-kbyte SRAM
- 256-byte data EEPROM
- 55 I/O pins
- 24-bit watchdog timer
- 2 16-bit timers with 4 compare registers or PWM outputs
- 8-channel, 8-bit ADC
- SCI, SPI
- 3 external interrupts
- In 68-lead PLCC, \$10 (25,000 qty/year)

## Drive an 8-bit PIC $\mu$ C with Basic

If you're performing simple control functions, you don't have to use the hard-to-maintain assembly language to run  $\mu$ C applications. Believe it or not, many engineers use Basic to drive 8051s and 68HC11s, and also the low-cost Microchip Technologies' PIC  $\mu$ C. Now from Parallax comes Basic Stamp—a packaged Basic development and prototyping system that includes the PIC  $\mu$ C with Basic in ROM.


The Basic Stamp development package consists of

- Software—a Basic editor, tokenizer, and downloader that run on a PC;
- A 1x2-in. prototyping board—a processor, a 256-kbyte serial EEPROM to hold the Basic tokens, a prototyping area, and a power supply;
- A  $\mu$ C—the 8-bit Basic PIC16C56, running at 4 MHz with the Basic token interpreter in OTP (one-time-programmable) EPROM. Eight I/O pins are available for application I/O.

When Parallax designers integrated Basic with the PIC  $\mu$ C, they placed the Basic token interpreter in fixed, on-chip program memory. The development software, however, converts the Basic program into tokens and downloads the program into a serial EEPROM on the Basic Stamp board, rather than placing it in on-chip memory. The CPU executes the program by reading the tokens from the EEPROM.

The serial EEPROM holds roughly 80 to 120 Basic instructions; it can also hold application parameters. The Basic Stamp CPU executes about 2000 Basic instructions per second, which is adequate for a range of low-level applications.

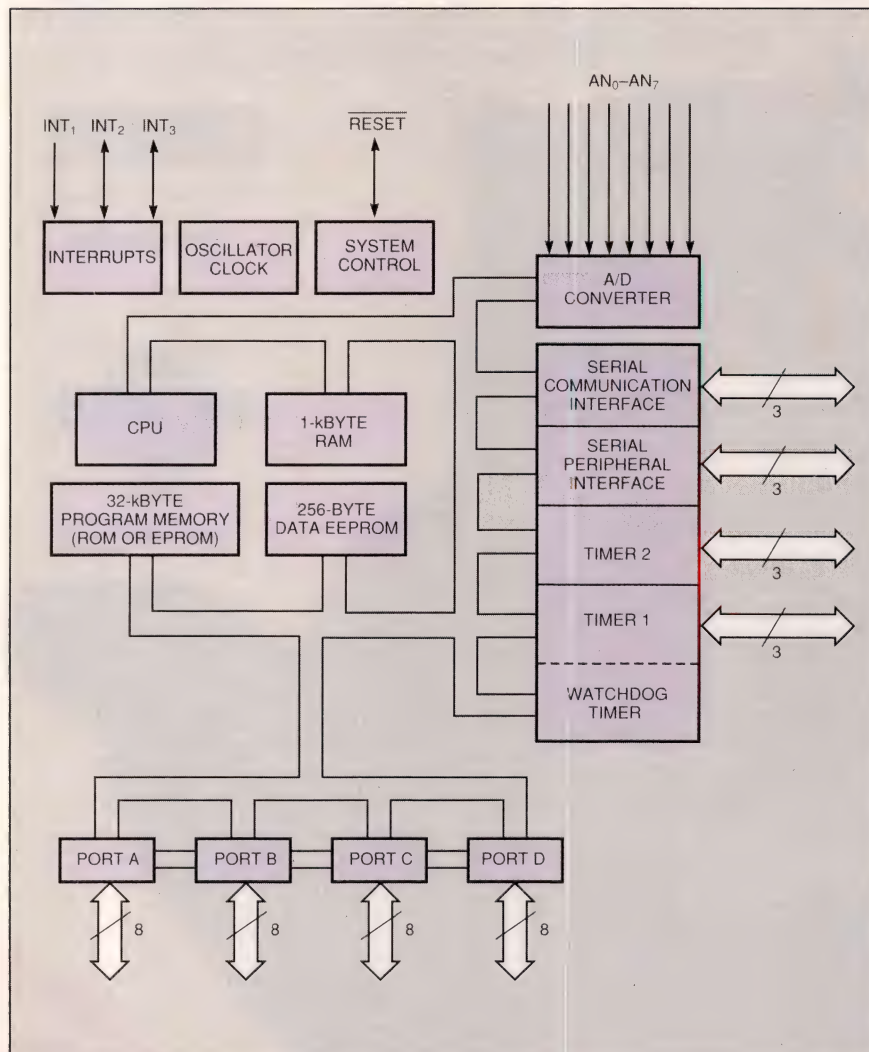The system uses a subset of Basic that Parallax has extended for real-time control. The operations include



The Texas Instruments' TMS370 8-bit  $\mu$ C has a register-oriented architecture with 256 registers held in RAM. The  $\mu$ C handles register-to-register operations and has 14 addressing options.



# 68300 68HC16

**EMUL300, Nohau Corp.**

**File View/Edit Run Breakpoints Config Registers Window Help**

**READY F1 Help F2 Reset F7 Step F9 Go F10 Trace Beg**

**Program**

**Disassembler, in-line assembler Window**

**Shadow RAM**

**Registers**

**Shadow RAM**

**Data**

**Trace stopped: 2729 frames recorded (-2,2727)**

**Instruction**

**Watch**

**Stack**

**Context sensitive Help Line**

**Trace Buffer Window**

**C Call Stack**

**On-line help**

**Speed bar (point and click)**

**Source Window**

**Data Window**

**Watch Window for High Level variables**

**Register Window**

## FEATURES

- Supports both the 683xx and 68HC16 families.
- User Interface under Microsoft Windows.
- Modular approach: From low cost to full feature.
- Real-time emulation at maximum chip speed.
- High-Level C support with in-depth support for Intermetrics, Introl, Microtec, Sierra and more. In-line assembler and disassembler.
- Hardware and software breakpoints.
- Up to 4 Mbytes of emulation RAM
- Trace board, up to 512k records deep, 104 bits wide, 40 bit timestamp.
- Triggering and filtering, with full pipeline decoding.
- Code Coverage. Program Performance Analysis.
- Memory Contents available in real-time (Shadow RAM).
- DDE support to transfer Shadow Ram to other Windows applications.

## 8051 68HC11

Full support for all derivatives.  
Call for FREE demo disk.

**To learn more, please call (408) 866-1820 for a FREE Demo Disk. Or call our 24-hour Information Center at (408) 378-2912 for information via your fax.**

**NOHAU CORPORATION**

51 E. Campbell Avenue  
Campbell, CA 95008  
Tel (408) 866-1820  
Fax (408) 378-7869

Australia (02) 654 1873, Austria 0277 20-0, Benelux (01858) 16133, Brazil (011)-458-8755, Canada 1-514 689-5889, Czechoslovakia 0202-2683, Denmark 43 44 60 10, Finland 90-4526-21, France (1) 69 41 28 01, Germany 08131-25083, Great Britain 0962-733140, Greece (01) 862 9901, Hungary (1) 163 7461, India (0212) 422164, Israel (03) 491202, Italy (011) 771 00 10, Korea (032) 860-5470, New Zealand 09-3092464, Norway 02-67 40 20, Portugal 01-80 95 18, Romania 961-30078, Singapore +65 749-0870, Slovenia 061-445-526, S. Africa (021) 23-4943, Spain (93) 217 23 40, Sweden 040-92 24 25, Switzerland 01-740 41 05, Taiwan 02 7640215, Thailand (02) 281-9596.




## Parallax Basic Stamp (PIC16C56)

- Development package includes software, prototyping board, and PIC16C56 with Basic in ROM. Software runs on IBM PC/XT/AT, DOS 2.0+. \$139
- Basic Stamp board includes  $\mu$ C, EEPROM and power supply. Powered by 5 to 12V dc (or 9V battery), 2 mA (typ). \$39
- Basic ROMed PIC16C56, \$6 (500)

outputting a PWM signal, reading a potentiometer, inputting or outputting a serial I/O data stream, performing digital output or input, reading EEPROM, pausing, controlling power (NAP, SLEEP, END), and sending variables to the PC for debugging. —**Ray Weiss**


*Parallax Inc, 6359 Auburn Blvd, Suite C, Citrus Heights, CA 95621. Phone (916) 721-8217. Fax (916) 721-1905.*

Circle No. 398

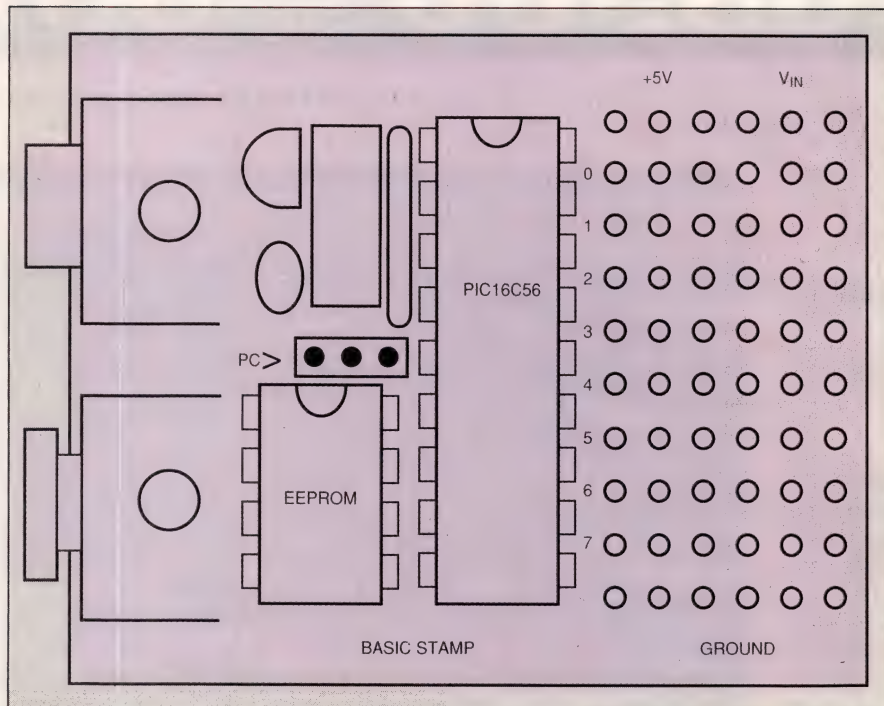

Using Basic to run an 8-bit PIC  $\mu$ C, you can monitor push buttons, potentiometers, and I/O pins. You can also drive audio, PWM, serial, digital I/O-pin outputs.

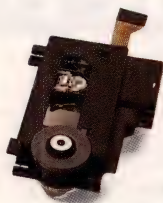**IF YOU WANT A PIECE OF THE CD PIE, TALK TO  
THE COMPANY WITH ALL THE KEY INGREDIENTS.**



The key to cooking up great Compact Disc systems is starting with great CD products. Philips, the inventor of CD technology, offers the key modules you need to design and manufacture your own CD ROM, CD Recorder, CD Games and CD Audio products.

Philips offers a complete family of CD mechanisms and related system ICs, plus a well-defined device interface and ongoing customer support. This flexibility provides the total freedom you need to create the optimized solution for your multimedia application.

CD ROM  
CD RECORDER  
CD GAMES  
CD AUDIO

Only Philips delivers: • low maintenance radial-linear assemblies for reliability and tracking accuracy • 3-beam holographic transports featuring a low mass, low power actuator • 2X transfer rates • fast access times • Photo CD, MPC compliance.



Get your just desserts. Call today to learn how you can partner with Philips to get your piece of the CD pie.



**PHILIPS**

It's Time

1 - 8 0 0 - 2 3 5 - 7 3 7 3

P H I L I P S   K E Y   M O D U L E S   G R O U P

CIRCLE NO. 16



**SIMPLE SWITCHER™ POWER CONVERTER**

# Hook it up. Check it out. Simple.



OUR NEWEST SIMPLE SWITCHER POWER CONVERTER

DELIVERS 500mA.

The **LM2574** lets you design an efficient DC-to-DC converter—with guaranteed system performance—using just four external, off-the-shelf components.

**FEATURES**

- Guaranteed 500mA output current
- 3.3V, 5V, 12V, 15V and adjustable versions
- Input voltage range up to 40V (up to 60V for HV version)
- Guaranteed system performance
- Typical  $I_Q < 200\mu A$  in shutdown mode
- Thermal shutdown and current limit protection
- In 8-pin DIP and 14-pin SO

All in less than five minutes. For about a quarter the cost of a DC-to-DC module.

Now you can get a complete design kit (including a demo board) with one simple phone call.

We'll even include "Switchers Made Simple," our free design software you can use with National's entire **SIMPLE SWITCHER**

Power Converter family.

So pick up the phone and dial **1-800-NAT-SEMI, Ext. 215.**

Because when it comes to switchers it doesn't get any simpler than this.



**National**  
Semiconductor

SIMPLE SWITCHER is a trademark of National Semiconductor Corporation.





```
Architecture A of E is  
signal S: Integer;  
begin  
  process  
  begin  
    S <= transport 1 after  
    S <= transport 2 after  
    S <= transport 3;  
    wait; end process;  
end A;
```





# Multilevel ASIC modeling

**John C Napier, Technical Editor,  
with Julie Anne Schofield, Senior Associate Editor**

Capitalism collides with engineering when you ask semiconductor vendors for detailed simulation models of complex standard cells or cores. Beyond issues of model accuracy and speed, intellectual-property concerns and the lack of standard model formats will force you to mix gate- and higher-level models to simulate complex ASICs.

You can't put a complex microprocessor on today's typical 20,000-gate ASIC. But as gate counts rise into the hundreds of thousands this year, you'll soon be able to use complex LSI (large-scale integration) functions as the core of your designs.

Like most ASIC designers, you probably rely on gate-level design and simulation to verify functions and timing. But you'll hit a brick wall when you ask for gate-level models of complex parts. By giving you such a model, a part maker would also be giving you the ability to clone the part (see **box**, "The risks of creating models"). Instead, you'll get a higher-level model, which will eliminate the option of flattening your whole design to the gate level for simulation.

---

Microprocessor vendors don't want to give away the store, so you'll have to mix their high-level models with gate-level models to simulate complex ASICs. (Photo courtesy Logic Modeling Inc)



## Multilevel ASIC modeling

Unfortunately, there are no standards for passing timing and function information between gate- and higher-level models (see **box**, "VITAL team pursues VHDL timing standards"). Until standards emerge, you'll have these options for modeling complex ASICs: You can use the available high-level models; you can use a hardware modeler to connect existing ICs to a simulation of your new peripheral and application-specific circuitry; or you can reuse your own designs as cores.

Hardware description languages such as VHDL (VHSIC HDL) and Verilog serve as the most common vehicles for describing and modeling multilevel designs. One common approach for using the available models

is to run nonsynthesizable behavioral VHDL models with gate-synthesizable peripheral models. You link the binary files supplied by the part maker with your design's binary files compiled from your source code.

Part makers block the use of logic synthesis as a reverse-engineering tool by distributing only object code and bus-functional behavioral models. Bus-functional models mimic only bus activity (read-write cycles) for a processor, and so run faster than behavioral models that handle all instructions and processor I/O. (It's rare to find a full-function model for complex microprocessors because the work involved in writing such a model is comparable to that of designing the

### The risks of creating models

No matter who employs them, model writers generally don't get access to information that could let others reverse-engineer the chip. In an ideal world, the chip designer would write the model. In practice, several layers of information laundering separate the model writer from the hardware design team. From the part maker's point of view, a model should reveal no more of a design than what shows up in data books.

A short definition of a complete and accurate model is that it represents all hardware registers by a model variable and includes full timing information. However, many storage-element models don't model timing. Thus, the more incompletely modeled storage registers you have in your design, the more accuracy problems you'll have. Parts that present the greatest modeling challenges include high-speed pipelined microprocessors and asynchronous logic such as disk-drive and SCSI controllers.

Because all storage elements consist of groups of gates, a gate-level model that includes timing is completely accurate. That's great for you as a designer—you can use the detailed functional information a gate-level model provides to extract greater speed and performance from a part. But that's bad for the part maker.

Beyond the possibility that you'll clone the part, the part maker acquires greater liability by releasing gate-level models and can inadvertently reveal future strategies for part development. For example, one company reports building a model for a disk driver from the hardware schematics. Simulations showed that the driver's maximum speed was twice the speed rating that its manufacturer published.

Because model accuracy and confidentiality hinges on how storage elements are represented, higher-level models can still pose a security risk to the part maker. Even behavioral models can disclose proprietary design information. Synthesis tools can automatically generate at least partial gate-level designs from behavioral models, says Bill vanCleemput, president of the Delos Research Group (Mountain View, CA), a company that specializes in intellectual-property work. Also—contrary to popular belief—VHDL can model at the gate level and handle hardware timing. It's entirely possible to make a VHDL model complete and accurate enough to reveal proprietary information.

Part makers usually restrict proprietary information by releasing only compiled, or object, code for complex models. The modeling team constructs the model to con-

form to data-book specifications, and the manufacturer does not release the model's source code.

Logic Modeling Inc.'s recent release of its VHDL Sourcemodel Libraries gives an example of the dividing line between proprietary and nonproprietary information. The library includes VHDL source code for 600 SSI and MSI parts and 1400 simple memory devices but has no source code for LSI parts. The company released its Smart-model Library only in object code. This library contains models for 6500 components including microprocessors, FPGAs, DSP  $\mu$ Ps, and complex VLSI parts from leading semiconductor manufacturers.


In addition to the gate-level design, models can give away timing information. Foundries try to keep equations for timing calculations in-house because accurate equations reveal the strengths and weakness of a silicon process. If you push timing limits by using incomplete information, you may cause timing problems in your circuit. The accuracy limits of complex-part models often show up when an advanced user uncovers a problem by pushing a model's published limits. Foundries do help large-volume customers with such problems by giving them the information they need—as long as the customer agrees to sign a nondisclosure agreement.



chip itself. See EDN's Hands-On VHDL Project "Secrets of the Lost Architecture," which began in the January 7, 1993, issue.)

An example of currently available models for core-based design is LSI Logic's Coreware program for its 500,000-gate technology. The models include SPARC and Mips microprocessors, the MIL-standard 1750A CPU and IEEE-754-compliant FPUs, several ALUs and multipliers, and JPEG and MPEG chips. The company doesn't provide gate-level models. Instead, it makes fast C-language models that are functionally and timing equivalent to gate-level models. A C shell plugs these models into source code running on VHDL simulators from Vantage Analysis Systems and Synopsys as well as Verilog simulators from Vantage and Chronology Corp. You get only the compiled-code forms of these models.

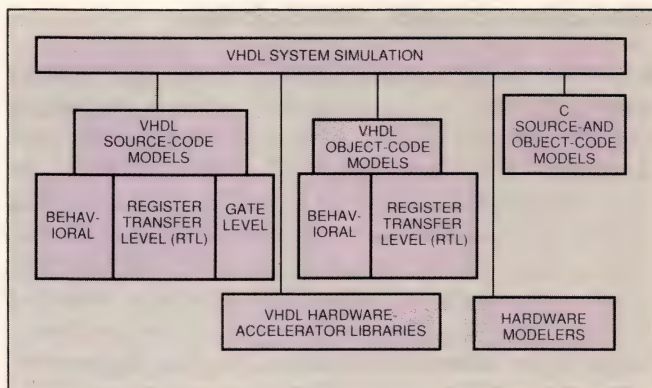The models Synopsys makes available for its VHDL System Simulator are another example of current practices. Under one of many agreements that Synopsys



The modeling levels used in VHDL system simulation span the full range of design abstraction. VHDL source models are available for SSI and MSI components. VHDL object models are sometimes available for LSI components, but they usually model only bus activity rather than all I/O. Hardware modelers are tools that interface working silicon with software simulators. Hardware-accelerator libraries group VHDL primitives to speed simulations. And the C language links VHDL simulators to user-built models and models for proprietary EDA toolsets.

## VITAL team pursues VHDL timing standards

At last year's Design Automation Conference, Cadence Design Systems Inc initiated VITAL—the VHDL Initiative Toward ASIC Libraries. The group's goal is to create uniform formats for gate-level timing in VHDL. Such a standard would replace the dozens of approaches now used by semiconductor and EDA-tool vendors. Steve Schulz, North American coordinator for VITAL, says the effort now involves 40 companies worldwide representing a broad cross section of semiconductor vendors, EDA-tool suppliers, and ASIC designers.

The problem with VHDL is that the language isn't efficient at expressing pin-to-pin delays and performing setup and hold checks, says Stephen Caplow, director of marketing for VHDL at Cadence. The language's designers sought independence from specific silicon technologies, so they didn't define VHDL's timing primitives in such a way that they would map efficiently to a layout.

VHDL can represent any gate as text, thus making a large ASIC look like thousands of primitives. Each

primitive generates a software process in VHDL, which consumes host-machine resources and makes simulations run slowly. VHDL accelerators—whether hardware or software—recognize a predefined set of primitives above the gate level. In other words, accelerators group gates together and run them as one process. Verilog includes such timing primitives, which gives it advantages over VHDL in gate-level simulation, timing checks, and carrying logical design to layout.

To standardize VHDL gate-level timing, VITAL plans to use the IEEE 1164 standard for defining signal strength and is considering using Cadence's Standard Delay File (SDF) format for timing information. Multiple tools, such as those for static timing and synthesis, could read an SDF. Existing foundry tools for calculating timing delays could store their results in the SDF. VHDL simulators could access this timing information during linking, or "elaboration."

Although VITAL's work began with gate-level timing, the group is also proposing a standard VHDL

description for megafunction cells. Such a standard would make timing semantics portable across toolsets. Whether this proposal blossoms into a full treatment of multilevel-modeling issues remains to be seen. Fred Cohen, director of the ASIC vendor group at Mentor Graphics (Beaverton, OR), suggests that business issues outweigh technology issues when it comes to developing standards for ASIC multilevel modeling. But he encourages VITAL and VHDL International to accept the challenge, even though it's somewhat beyond the charter of either organization.

### VITAL

Steve Schulz  
North American Coordinator  
Texas Instruments  
Automation Systems Div  
Box 869305, MS 8420  
Plano, TX 75086  
(214) 575-2720  
FAX (214) 575-6807  
**Circle No. 301**

### VHDL International Inc

407 Chester St  
Menlo Park, CA 94025  
(800) 554-2550  
(415) 329-0578  
FAX (415) 324-3150  
**Circle No. 302**



## Multilevel ASIC modeling


has with ASIC manufacturers, Texas Instruments makes available to Synopsys four types of models for the TMS320 line of DSP  $\mu$ Ps: a fast functional model for design validation; one that's timing accurate for cycle boundaries; a third for signoff by TI for building silicon; and the fourth, a synthesis timing shell that uses a subset of the signoff model with additions that cover drive-signal strength. The Synopsys simulator lets you view simulations as traditional low-level waveforms or as higher-level information. The higher-level simulations give you the information in the part data book, including instruction-level data and register and pipeline contents.

The hardware modeler is another aid to simulating systems before standards emerge for multilevel modeling. Combined with SSI and MSI (small- and medium-scale integration) models in source code and LSI models in object code, the hardware modeler lets you simulate boards or systems. The tool lets complex parts run at close to full hardware speeds within the much slower software simulation of a complete system.

Some complex ICs can't run in single-step mode, and

therefore require you to use hardware modelers to connect the parts to software simulations. An example of a hardware modeler is the LM-1200 from Logic Modeling Inc. The product includes a blank cardrack, pattern memory, and software to interface parts to workstation-based simulators. You purchase cards and some peripheral circuitry to hold your part, and you write some driver code to interface your part to the modeler. The pattern memory saves data required to let the part run at speed and yet interface to the much slower software simulator.

If you want to build your own inventory of core models by reusing your previous work, look into Synopsys' Designware. The toolset provides structured methods for managing designs. The methods help you organize libraries of your own work and can compile reports on design characteristics. A companion product, Synthetic Designs, consists of synthesis and simulation models for advanced MSI logic, math, and sequential-processing designs in VHDL or Verilog. The combination of tools lets you focus on such issues as throughput and latency of an FIR

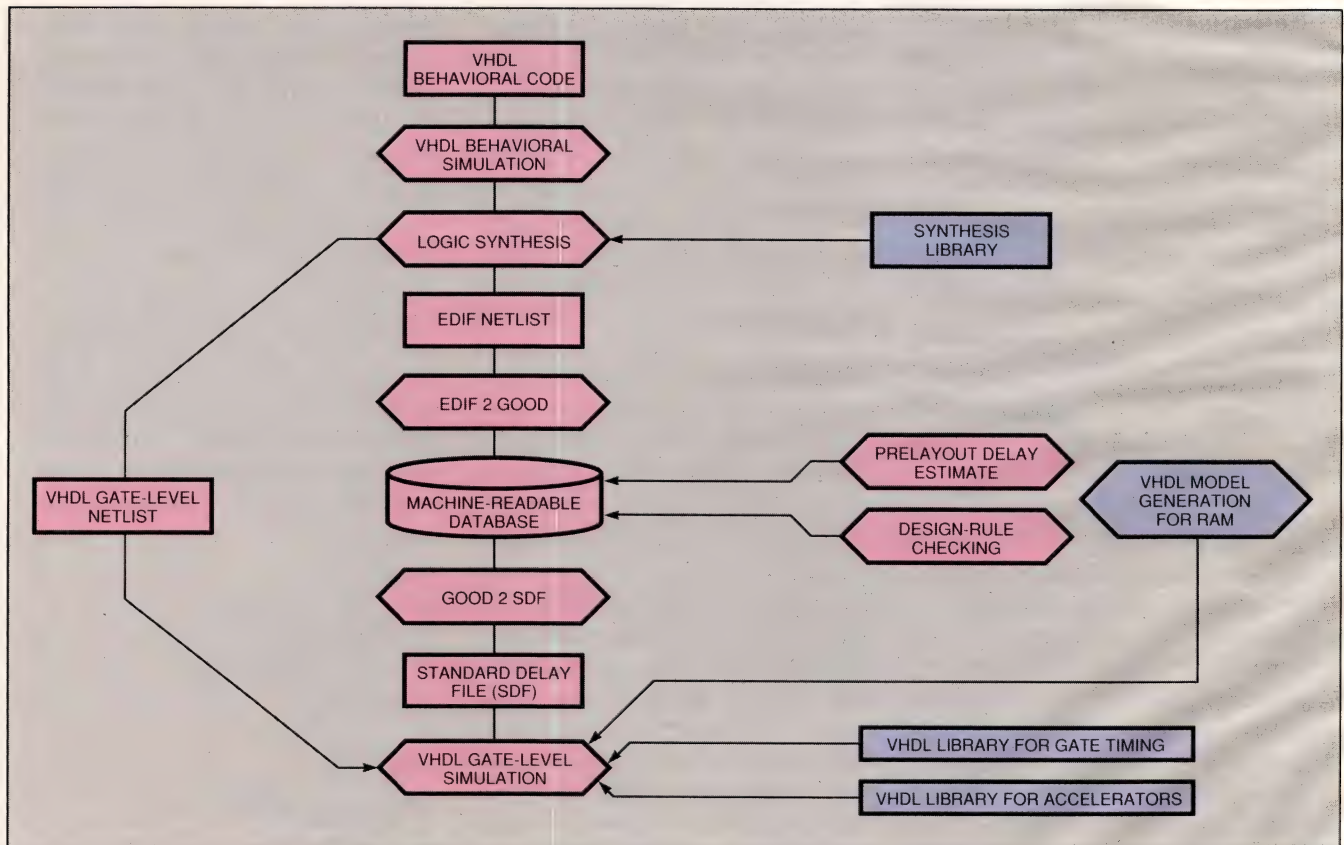

The burden of compensating for lack of VHDL timing information for multilevel modeling falls mostly on semiconductor vendors, as this synthesis-based VHDL design flow from Texas Instruments' Military Products Div shows. (Rectangular blocks show libraries and models; pointed blocks show tools.) The flowchart includes three TI-written libraries: a synthesis library that maps ASIC design components via a VHDL netlist to TI-specific gate; a second library passes the gates' timing characteristics to the VHDL simulator; and a third provides timing information for other primitives for hardware acceleration. A TI tool that generates models for RAM directly translates behavioral information into timing-capable simulation models.





"We chose HSPICE and Cadence to develop our very high performance SRAM products because it's a proven combination. With HSPICE, we get the accuracy and strong technical support that we need, and Cadence has the most flexibility of any open software CAD tool. A lot of people in the IC industry are using this combination because it works!"

Nearly three years ago, when Sony established its semiconductor design and R&D center in San Jose, the company chose HSPICE to work within their Cadence environment because HSPICE is the simulator of choice in the industry. No matter which Cadence framework you're using, Meta's six interfaces offer users a complete Cadence connection for circuit simulation. And, HSPICE can also be used as a stand-alone product. With a full range of advanced analysis capabilities, HSPICE and Cadence make a winning design combination. If you're a Cadence user, call Meta to find out how well HSPICE and Cadence work together.

Call today for an evaluation.

(800) 346-5953, ext. A4

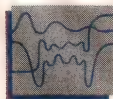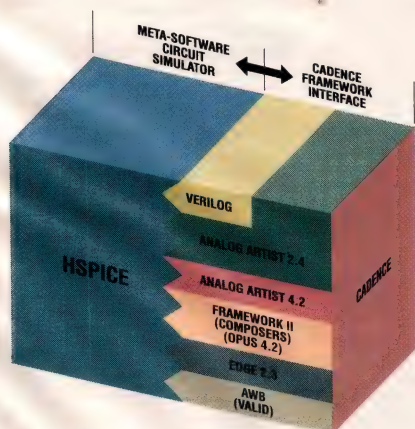

**META-SOFTWARE**

## CADENCE USERS KNOW A GOOD THING WHEN THEY SEE IT.

Pradip Banerjee,  
Design Operations Manager  
Sony Microelectronics



## Multilevel ASIC modeling

filter rather than designing the multiplier/adder for it.

Calls to semiconductor vendors revealed this general rule: More and better models become available the tighter you lock your design into a particular fab. Texas Instruments doesn't supply VHDL behavioral models. The company regards such models as its customer's responsibility, per Claude Huffer, military ASIC design engineering manager, and Dan Jensen, ASIC strategic marketing manager. The company does offer VHDL models for gate-level primitives and has the relationship with Synopsys Corp that facilitates core-based design with the TMS320 line.

Motorola made an MC68000 core model available last year for gate arrays. The Verilog model is proprietary, and Motorola judged the language's encryption techniques as too weak to protect the company's intellectual property. Motorola therefore teamed with a third party to make a C model for simulators. The Verilog C model comes in Verilog object format. It models function only; a Verilog "wrapper" file provides timing information. The 68000 model is not synthesizable, so you can't reduce an entire design to the gate level. The company has an effort underway to produce models for other parts in this family, but so far only the MC68000 core model is available.

VLSI Technology offers core models for the Z80, the ARM RISC processor 600 series, and a fuzzy-logic processor. The semiconductor vendor also has an agreement with Intel to supply 80386 microprocessor core models. You're required to make royalty payments to use any of these models.

Lastly, Fujitsu Microelectronics is looking into core-based design and expects in 12 to 18 months to have models available for some SPARC cores, SCSI controllers, and RAM and data-communications parts. The models will remain Fujitsu's intellectual property for use of its customers only, so you will not be legally able to take a netlist to make silicon at another fab.

A common industry belief is that models will eventually become a byproduct of hardware development. That's unlikely to happen for two reasons. First, the part maker needs to protect design ownership and limit liability. Second, making models is labor-intensive software-development work and represents overhead to the main business of making chips.

You also can't count on the aging of patents to put complex parts in the public domain anytime soon. Patents last for 17 years, and trade secrets last as long as a company protects them. Models are readily available for MSI parts because many of these parts are so simple that they're not patentable. Others have been around so long that they're in the public domain. Today's complex LSI parts will probably become technically obsolete long before their 17 years are up. **EDN**

### References

1. *VHDL Design Guide*, Cadence Design Systems Inc, 1992.
2. *Handbook of Hardware Modeling*, Logic Modeling Inc, 1991.

Article Interest Quotient (Circle One)  
High 497 Medium 498 Low 499

## Manufacturers of simulation tools and models

For more information from suppliers of tools and models such as those mentioned in this article, circle the appropriate numbers on the Information Retrieval Service card or use EDN's Express Request service. When you contact any of the following manufacturers directly, please let them know you read about their products in EDN.

### Cadence Design Systems Inc

555 River Oaks Pkwy  
San Jose, CA 95134  
(408) 943-1234  
FAX (408) 943-0513  
**Circle No. 303**

### Chronology Corp

17411 NE Union Hill Rd  
Suite 100  
Redmond, WA 98052  
(206) 869-4227  
FAX (206) 869-4229  
**Circle No. 304**

### Fujitsu Microelectronics Inc

3545 N First St  
San Jose, CA 95134  
(408) 922-9000  
FAX (408) 432-9034  
**Circle No. 305**

### Logic Modeling Inc

19500 NW Gibbs Dr  
Beaverton, OR 97075  
(503) 690-6900  
FAX (503) 690-6906  
**Circle No. 306**

### LSI Logic Inc

1501 McCarthy Blvd  
Milpitas, CA 95035  
(408) 433-8000  
FAX (408) 434-6457  
**Circle No. 307**

### Motorola Inc

1300 N Almaschool Rd  
Chandler, AZ 85224  
(602) 821-4426  
FAX (602) 821-4850  
**Circle No. 308**

### Open Verilog International

1016 E El Camino Real  
Sunnyvale, CA 94087  
(408) 776-1684  
FAX (408) 776-0124  
**Circle No. 309**

### Synopsys Inc

700 E Middlefield Rd  
Mountain View, CA 94043  
(415) 962-5000  
FAX (415) 694-4255  
**Circle No. 310**

### Texas Instruments Inc

Semiconductor Group  
Military Products Div  
Box 60448, MS 3028  
Midland, TX 79711  
(915) 761-7293  
FAX (915) 561-6716  
**Circle No. 311**

### Vantage Analysis

**Systems Inc**  
42808 Christy St, Suite 200  
Fremont, CA 94538  
(510) 659-0901  
FAX (510) 659-0129  
**Circle No. 312**


### VLSI Technology Inc

1109 McKay Dr, MS 32  
San Jose, CA 95131  
(408) 434-7673  
FAX (408) 434-7931  
**Circle No. 313**



You're zooming up a single shot 10 ns spike, an event you simply cannot see on any \$3,000 digital scope. Unless it's the new TDS 320 with its incredible over sampling. Truly the world's first affordable 100MHz digital real-time scope.

At 500 Megasamples/sec, our new TDS 320 combines the storage and data manipulation benefits of digital with the signal fidelity of analog real-time. So you can make precise, confident measurements quickly. What's more, its intuitive user interface means you'll actually spend more time working with this digital scope than learning how to use it. And finally, we consider its price tag (a mere \$2,795) yet another spike the competition can't catch. So call your authorized Tektronix distributor today. Or call us at (800) 426-2200, ext. TDS3 to place your order.

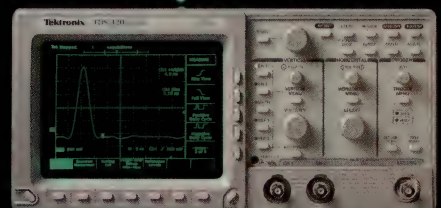

**Tektronix**



Acquire it...

# Develop it...with LabWindows®!



LabWindows for DOS accelerates the development of your data acquisition, instrument control, and data analysis programs with software tools based on proven industry standards.

## Flexibility

With LabWindows, you can design and control custom graphical user interfaces (GUIs) with graphs, strip charts, push-buttons, menu bars, and more. And, to acquire your data, you can select from over 290 instrument drivers for IEEE 488, RS-232, and VXIbus instruments, or from a wide range of analog and digital plug-in data acquisition boards. Add in over 150 functions from the LabWindows Advanced Analysis Library for all of your signal processing.

## Standard Programming Languages

LabWindows libraries are compatible with Microsoft C, BASIC, Professional BASIC, Visual Basic for DOS, Borland C++, and Turbo C++ compilers. With LabWindows, you can acquire, analyze, and present your data while maintaining the flexibility of standard C and BASIC programming languages.



**Call for FREE Demo Disk**  
**(800) 433-3488**  
**(U.S. and Canada)**



**NATIONAL INSTRUMENTS®**  
*The Software is the Instrument®*

6504 Bridge Point Parkway  
Austin, TX 78730-5039  
Tel: (512) 794-0100  
95 (800) 010 0793 (Mexico)  
Fax: (512) 794-8411

## Branch Offices

Australia 03 879 9422 • Belgium 02 757 00 20 • Canada 519 622 9310 • Denmark 45 76 26 00  
Finland 90 527 2321 • France 1 48 65 33 70 • Germany 089 7 14 50 93 • Italy 02 48301892  
Japan 03 3788 1921 • Netherlands 01720 45761 • Norway 03 846866 • Spain 91 896 0675  
Sweden 08 984970 • Switzerland 056 27 00 20 • U.K. 0635 523545

© Copyright 1993 National Instruments Corporation. All rights reserved. Product and company names listed are trademarks or trade names of their respective companies.

CIRCLE NO. 99



# ICs provide control for sensorless dc motors

Dave Peters and Jeff Harth, Silicon Systems Inc

*The need for low-cost, highly reliable, miniature, brushless dc motors has given rise to a new class of devices—sensorless dc motors. These motors eliminate the need for Hall-effect sensors, which are currently built into most brushless dc motors for control purposes.*

As dc motors get smaller, there is less space for the Hall-effect sensors you normally use for motor control. As a result, miniature sensorless motors are becoming common. Eliminating the Hall-effect sensors removes the need for sensor-control signals, reduces the size of the connector, and eliminates connections. Hall-effect sensors are also sensitive to temperature variation, RFI, and other types of noise commonly experienced in motor applications. All of these factors reduce motor reliability. Finally, Hall-effect sensors increase motor cost and make the motors larger. As a result, the motors consume power—an undesirable trait in battery-driven applications.

While eliminating Hall-effect sensors obviously has its advantages, it also has some disadvantages. Without Hall-effect sensors, brushless dc motors are somewhat more difficult to start and control. Fortunately, a variety of semiconductor manufacturers now offer ICs that are specifically designed to control sensorless dc motors. These chips monitor the back-EMF the motors generate across specific sets of windings and appropriately adjust the amplitude and polarity of the voltages across the motor windings. In this manner, the ICs switch the motor from one commutation state to the next in a programmed manner, automatically setting and regulating the speed.

In addition to speed control, you should also consider the question of motor starting. Starting is a unique problem for the sensorless motor, because back-EMF exists only when the motor is already turning. For start up to occur, the motor must rotate in the proper direction and attain a speed that lets back-EMF sensing begin. Today's sensorless motor-controller chips switch the amplitude and polarity of the voltages across the motor windings so that the motor starts turning slowly and then accelerates, in a programmed manner, to a speed where back-EMF speed control can take over.

If start up always involves identical conditions, you can preprogram a single self-start acceleration profile

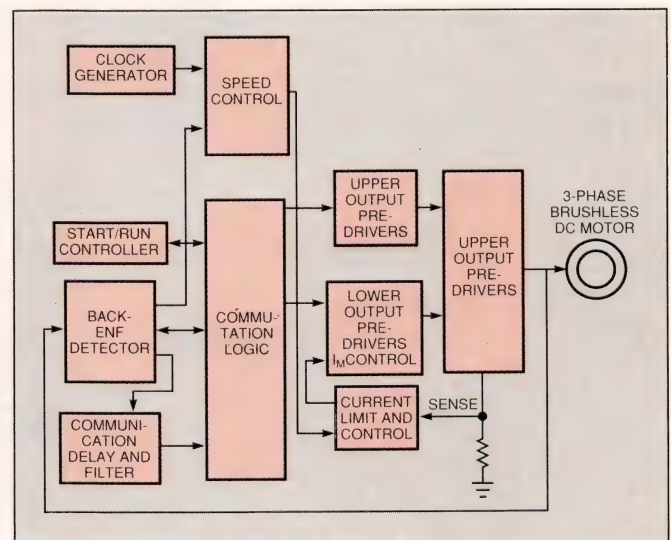


Fig 1—The speed-controller chips available today provide all the timing and control functions necessary to control speed, drive, and brake 3-phase, multipole brushless dc motors.



## MOTOR SPEED CONTROL

for the motor. If the load or other conditions will vary, start up may require adaptive microprocessor control. In this case, the  $\mu P$  will adjust the start profile to begin with the unknown load.

You can control motor speed by varying the current in the motor windings. You can vary the current in a linear fashion by varying the voltage applied to the windings, or you can use pulse-width modula-

tion (PWM) techniques and keep the voltage constant.

PWM-control techniques typically vary the duty cycle of the voltage applied to the motor windings to control the current in them. PWM control is most appropriate in applications where low power dissipation is very important. You vary the current to each winding by switching a power transistor on and off at a variable rate, or at a fixed rate with a variable duty

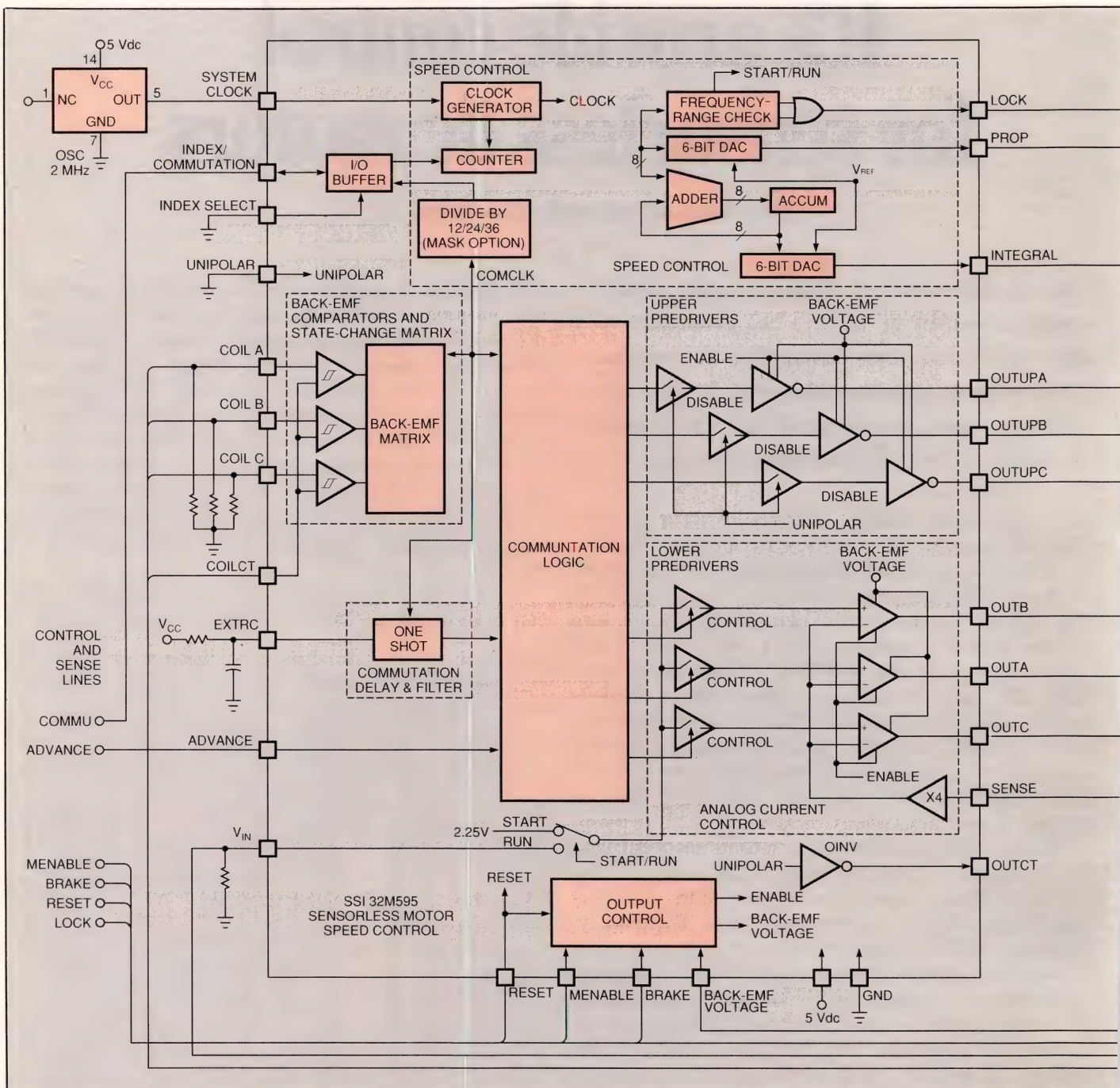


Fig 2—The current-limiting resistor  $R_{SENSE}$  is a key component in the sensorless motor-controller circuit. The resistor limits the start current to the motor windings and should be chosen to allow a start-up current about 10% higher than what is required.



cycle. Unfortunately, PWM-control schemes are more difficult to implement than linear schemes.

For either speed-control method to work, the controller must receive an index pulse, which indicates the start of a motor revolution. There are two ways to generate this index pulse. You can use an external optical shaft encoder to generate the pulse, or you can use the on-board speed controller or an external  $\mu$ P

to flag the start of a motor revolution by counting changes in commutation states. A 3-phase motor has six commutation states for each pair of poles. Once the  $\mu$ P knows how many pairs of poles the motor has, it can calculate the number of changes of commutation state in one revolution of the motor. It then simply counts changes of commutation state for each revolution and knows precisely when a new revolution is beginning.

**Fig 1** illustrates the basic system for brushless dc-motor control. This generalized system appears in two specific examples—one involves the control of a 12V bipolar motor and the second deals with a 24V unipolar motor. Both examples use the SSI32M595 sensorless motor-speed control chip—a device that contains on-board speed control. However, other products on the market can do a similar job.

The bipolar approach has the advantage of providing greater torque with the same motor design, while the unipolar scheme allows higher rpm, because all the voltage develops across a single winding. In addition, the unipolar design requires only one power transistor per terminal. However, it also requires a voltage divider circuit at each terminal to bring the voltage to the 12V range.


### Solving disk-drive problems

A disk-drive application using a sensorless motor as the spindle motor best typifies the task of 12V bipolar motor control. Assume that the drive has four 3½-in. disks and eight read/write heads. The disks rotate at 3600 rpm (377 rad/sec), and the spindle motor must get the disks up to the speed where the heads fly within 2 sec. The heads start in contact with the disk surfaces, yielding 15g of head load and a friction coefficient of about 1. At a speed of 1000 rpm, the heads start to fly.

Estimating the system inertia is the first step in the design. If you assume that motor inertia is small compared to disk inertia (a valid assumption in most cases), then system inertia will be equal to disk inertia. Assume that disk inertia equals 0.0075 oz-in.-sec<sup>2</sup> in this case. Calculating torque requirements is the next step. The acceleration rate ( $\alpha$ ) necessary to get up to 1000 rpm (104.7 rad/sec) in 2 sec equals the speed divided by the time to reach that speed, or  $104.7/2 = 52.35$  rad/sec<sup>2</sup>. The torque (T) required to accelerate the inertia equals the system inertia (estimated earlier to be 0.0075 oz-in.-sec<sup>2</sup>) multiplied by the acceleration rate  $\alpha$ , or

$$T = 0.0075 \times 52.35 = 0.393 \text{ oz-in.}$$

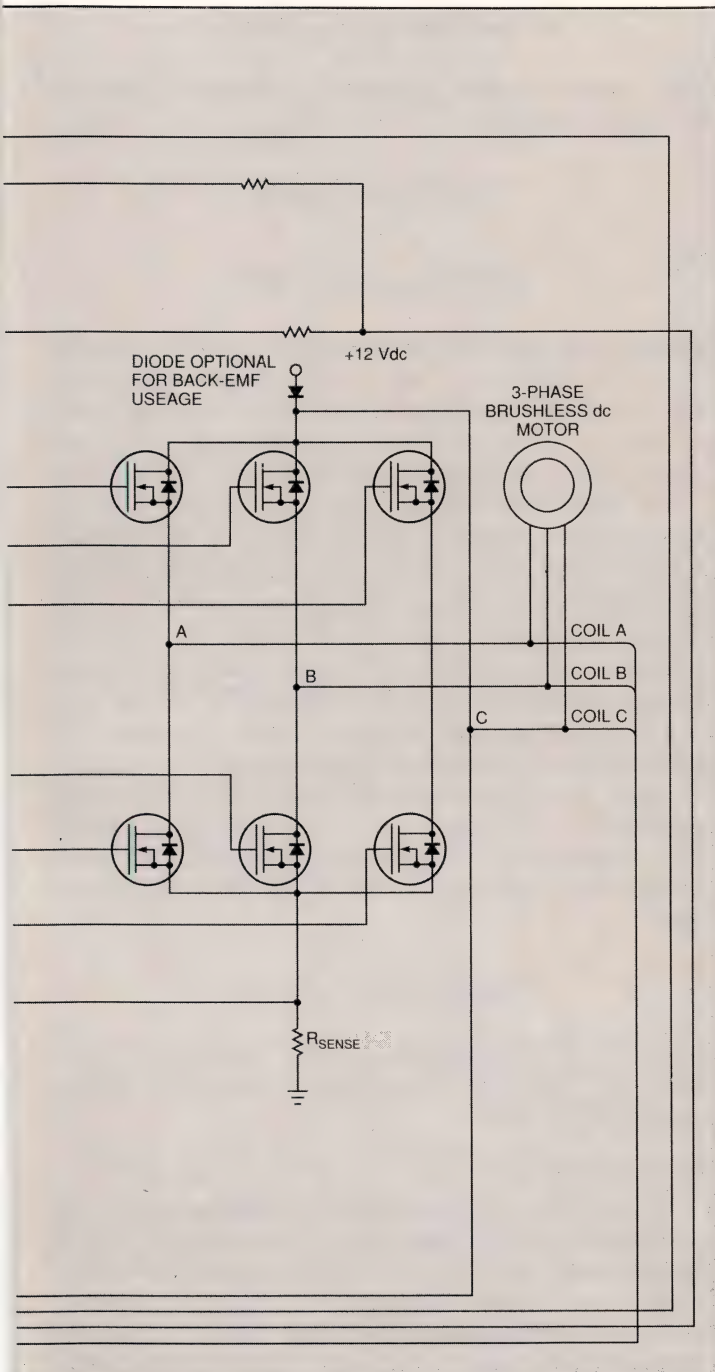To overcome the head friction at start-up, you must





## MOTOR SPEED CONTROL

add an additional torque element,  $T_F$ . Assuming a head-park radius (distance from center of the disk to the track location where the heads are parked) of 0.55 in., then  $T_F$  will equal

$$(15g/28.35)(8)(1)(0.55 \text{ in.}) = 2.3 \text{ oz-in.},$$

where 15g equals the head load, 28.35 equals the metric-to-English conversion factor, 8 equals the number of heads, 1 equals the coefficient of friction, and 0.55 equals the head-park radius. The total starting torque required is the sum of  $T$  and  $T_F$ , or 2.69 oz-in.

### Take a worst-case approach

To calculate the starting current for the motor windings, you must first calculate the motor-torque constant. To reflect worst-case conditions in a 12V system, assume a value of 10.8 for the low-line condition. Allowing 3V for head room to control speed means that the motor's back-EMF should be no more than 7V. Thus, the torque constant,  $K_T$ , will be

$$(7/377)141.6 = 2.63 \text{ oz-in./A},$$

where 377 equals the disk rotation in rad/sec and 141.6 is a factor that converts (volt-sec)/rad into oz-in./A. This is the probable upper limit to  $K_T$  and is meant to serve as a first approximation. Dividing the total starting torque ( $T + T_F$ ) by the torque constant gives the start-up current for the motor windings as  $2.69/2.63 = 1.02A$ .

Fig 2 details the control scheme for the 12V bipolar sensorless motor application. Note that the schematic includes a current-limiting resistor ( $R_{SENSE}$ ) that limits the start current to the motor windings. Select a value for  $R_{SENSE}$  that allows a start-up current about 10% higher than necessary. In this example, the current limit is equal to 2.25 (the chip's internal acceleration

voltage) divided by  $4R_{SENSE}$ . If  $R_{SENSE}$  is equal to  $0.5\Omega$ , the current limit works out to 1.125A.

At this point, you can calculate the elements of a start-up table. This table is a list of delay times between advances to the commutation state counter that allow time for the motor to rotate to the location where the next advance should occur. For a typical 3-phase, 8-pole motor, the angle of rotation per state is

$$\theta = 2\pi/(3)(8) = 0.262 \text{ rad/state.}$$

The amount of time required to complete a rotation of angle  $\theta$  is either

$$(\omega_{(N-1)} + \omega_N + \alpha T_N/2)/T_N,$$

or

$$(\alpha T_N^2)/2 + \omega_{(N-1)}T_N - \theta + 0,$$

where  $T_N$  is the time to move through an angle of  $\theta$  in a time period of  $N$ ;  $\omega_{(N-1)}$  is the angular velocity at the end of the last time period and at the start of the  $N$  time period;  $\omega_N$  is the angular velocity at the end of the  $N$  time period; and  $\alpha$  is the angular acceleration.

You must now calculate  $\alpha$  at the current limit  $I_M$ . The torque produced equals  $I_M K_T$ , which equals  $1.25A \times 2.63 \text{ oz-in./A} = 2.96 \text{ oz-in.}$  The amount of torque available for acceleration is the torque produced at the current limit less  $T_F$ , or  $2.96 - 2.3 + 0.66 \text{ oz-in.}$  The acceleration rate  $\alpha$  equals the torque available for acceleration divided by inertia, or  $0.66/0.00785 = 88 \text{ rad/sec}^2$ .

You can enter this value of  $\alpha$  into the quadratic equation for the amount of time to complete a rotation of angle  $\theta$  and then solve the equation to determine time per step. The first step, where the previous velocity is zero, is starting the motor from a dead stop. When solving the equation for  $N=1$  and  $\theta = 0.262 \text{ rad/state}$ ,

$$(88/2)T^2 + 0T - 0.262 = 0,$$

the time ( $T$ ) to complete the first step of  $\theta T$  equals 0.077 sec, and the instantaneous rotational velocity equals 6.79 rad/sec.

### Get a computer

You can use a simple computer program to run this calculation and generate a table. The number of steps in the start table must bring the motor above the speed where reliable commutation will occur. Then, the start cycle will end and self-commutation will take control. Assuming that the target speed is 500 rpm, a table for the design in Fig 2 will require only about 60 steps (Table 1).

The next task is to calculate the maximum motor re-

Table 1—Motor start up


Interval	T (msec)	T total (msec)	rpm
1	77.2	77.2	64
2	31.98	109.19	91
10	12.52	244.15	204
20	8.74	345.29	289
30	7.1	422.89	354
40	6.14	488.31	409
50	5.48	545.95	457
59	5.04	593.05	497
60	5.0	598.06	501
61	4.96	603.02	505
70	4.63	645.97	541




# TAKE UNFAIR ADVANTAGE OF YOUR COMPETITION.

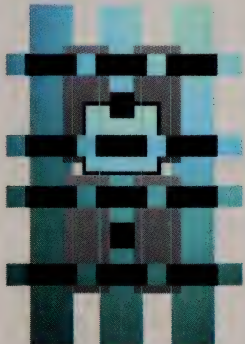**PAS 5500 steppers' smaller overlay tolerance provides IC Designers with a tremendous advantage to make smaller, faster and more powerful chips.**

Conventional stepper  
design rule tolerance,  $0.325\mu\text{m}$



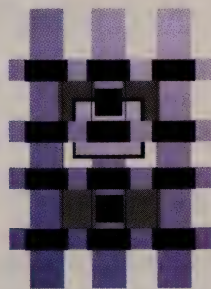
PAS 5500 stepper  
design rule tolerance,  $0.25\mu\text{m}$




The industry's smallest overlay tolerance,  $<70\text{nm}$ , allows PAS 5500 users to tighten design rules and reduce chip size while maintaining minimum feature size as shown here for a 16M EPROM Memory Cell.

16M EPROM  
Cell area  $3.6\mu\text{m}^2$

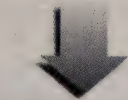16M EPROM  
Cell area  $2.9\mu\text{m}^2$



Chip area  $121.41\text{mm}^2$

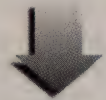

Chip area  $94.5\text{mm}^2$

Smaller chips mean higher speed, lower power, more competitive devices.

107  
16M EPROM  
die per  
150mm wafer

142  
16M EPROM  
die per  
150mm wafer

With more good die per wafer.

Smaller chips. Faster device speed. Lower power consumption. More good chips per wafer for more profit per wafer. *PAS 5500 stepper users have all the advantages.* Thanks to the industry's smallest overlay tolerance,  $<70\text{nm}$ , they can tighten design rules and reduce chip size while maintaining minimum feature size. ASM Lithography's patented PGA™ (phase grating alignment) system is the key. When you have PGA you can take unfair advantage of your competition. They can't match your chip size or device performance.



**So give us a call at 602-438-0559 and let us show you how our smaller overlay tolerance can give you all the advantages.**

**ASM Lithography**  
*Steppers for the decade ahead*

In U.S.A.: 2315 W. Fairmont Drive, Tempe, AZ 85282

Phone: (602) 438-0559, Fax: (602) 438-0793.

In Europe: De Run 1110, 5503 LA, Veldhoven, The Netherlands

Phone: (31) 40-580800, Fax: (31) 40-580333.

In Taiwan: Hermes-Epitek, 110 Ming Chuan Road, Hsinchu City, Taiwan, ROC

Phone (886) 35-339-131, Fax: (886) 35-330-110.

In Korea: Intraco, 31 Fl., M&B Building., 78-12, Banpo-Dong, Seouchu-Ku,

Seoul, 137-040 Korea Phone: (82) 2-595-7277, Fax: (82) 2-596-2711.

In Singapore: Hermes-Epitek Corp. PTE. Ltd., 510 Thomson Road #09-01,

SLF Building, Singapore 1129 Phone: (65) 353-3088, Fax: (65) 353-3011.

Phase grating alignment and PGA are trademarks of ASM Lithography.

©1993 ASM Lithography

CIRCLE NO. 100



## MOTOR SPEED CONTROL

sistance,  $R_M$ . The total available low-line power-supply voltage is impressed across three components—the driver transistors, the current-sample resistor, and the motor. The motor-terminal voltage is simply the back-EMF plus the IR drop across the motor resistance. There are two power transistors driving each motor winding in a bipolar application. Assume that the voltage drop will be the same across each transistor.

For a current of 1.125A (the current at start-up), the voltage drop across both transistors will be about 2V. The voltage drop due to motor resistance,  $V_{RM}$ , equals the low power-supply-voltage level minus the back-EMF (which is zero at start) minus the voltage drop across the driver transistors less the voltage drop across the sense resistor. Thus,  $V_{RM}$  works out to be  $10.8 - 0 - 2 - (1.125 \times 0.5) = 8.24V$ . Since  $V_{RM} = I \times R_M$ ,  $R_M$  will equal  $8.24/1.125 = 732\Omega$ .

The values for  $K_T$  and  $R_M$  are a good approximation for a design start. Having some values for  $K_T$  and  $R_M$  (two key motor specifications) lets you move on to the next step—setting the speed-control compensation. A 2-MHz system clock sets the internal speed control for 3600 rpm. External resistors (between the proportional-error DAC, the integral-error DAC and  $V_{IN}$ , and the summing resistor from  $V_{IN}$  to ground) provide the compensation for the speed-control loop.

You can determine the required values for the gain-control resistors needed to complete the speed-control compensation design by solving the loop-gain equations. The loop-gain control equation is

$$LG = (11.6K_I K_A K_T / js^2) + (0.775K_P K_A K_T / js),$$

where LG is the speed-control loop gain;  $K_I$  is the integral gain set by the external resistor ( $R_I$ ) in the network;  $K_P$  is the proportional gain set by the external resistor ( $R_P$ ) in the network;  $K_A$  is the current-control transconductance gain  $= 1/(4R_{SENSE}) = 0.5 A/V$ ;  $K_T$  is the motor torque constant  $= 2.63 \text{ oz-in./A}$ ;  $J$  is the iner-

tia  $= 0.0075 \text{ oz-in.-sec}^2$ ;  $s$  is the LaPlace Transform frequency variable, which  $j\omega$  can replace.

For  $45^\circ$  phase margin when the loop gain equals 1.0, the loop-gain in rectangular form is

$$-0.707 - j0.707 = (11.6K_I K_A K_T / j\omega^2) - j(0.775K_P K_A K_T / j\omega).$$

Assume you want a 1-Hz bandwidth, then you must solve the above equation when  $\omega = 2\pi(1 \text{ Hz})$ . Solving the real and imaginary parts separately for  $K_I$  and  $K_P$  yields values of  $K_I = 0.0132$  and  $K_P = 0.0327$ . Fig 3 shows the network that will produce these gains, where  $R_O = 10 \text{ k}\Omega$ , and  $R_P$  and  $R_I$  are the gain control resistors:

$$R_P = R_O(1 - K_I/K_P) - 1 = 291.6 \text{ k}\Omega$$

and

$$R_I = R_O(1 - K_P/K_I) - 1 = 695 \text{ k}\Omega.$$

This ends the design process for the circuit in Fig 2.

## Handling unipolar applications

To illustrate the design process for sensorless motor control in unipolar motor applications (Fig 4), consider the following design problem. The application here requires a variable speed control with an external speed sensor and controller, using a sensorless dc motor. The input for the speed control is the transconductance input  $V_{IN}$ . Load inertia plus motor inertia will be  $0.01 \text{ oz-in.-sec}^2$ , and speed control is required over a 1000-to-10,000-rpm range. Speed must be capable of changing from the low speed to the high speed in 1 sec. In this case, assume that you have negligible friction torque or viscous torque to deal with. Also, the motor is a 3-phase, 4-pole wye-connected motor, with center tap, as in the 12V bipolar example.

To operate in a unipolar fashion at greater than 12V, you must develop voltage divider networks for each of the motor's terminals, since the control chip should never have more than 15V on any input. In addition, you must bypass the motor-controller chip's internal low-rpm switch so that it will not switch motor current control away from  $V_{IN}$  to the internal acceleration voltage (2.25V). This circuitry provides full acceleration if the speed is very low compared to 3600 rpm (the nominal fixed motor speed used in disk-drive applications).

With a 2-MHz clock and an 8-pole motor, the low-rpm switch will activate if the rpm drops below 3492. To bypass the low-rpm switch, select a new clock frequency, which is a function of the number of poles in the motor and the motor's lowest operational control

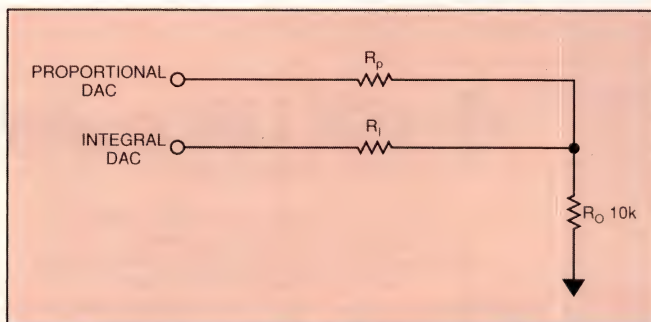


Fig 3—The compensation for the speed-control loop is done with external resistors between the proportional-error DAC, the integral-error DAC, and  $V_{IN}$ , with an additional summing resistor located between  $V_{IN}$  and ground.





# Mixed-Signal CBiCMOS Standard Cell ASIC's

**It's Here!** Raytheon's newest addition to its VRSA-Tile family of analog and mixed-signal ASICs is the RSC4000 Cell Library built on a high-performance 13V CBiCMOS process. The RSC4000 is ideal for integrating high-speed analog and mixed analog/digital functions. The process has 4 GHz NPN & 1.5 GHz PNP transistors and thin film resistors for high performance analog and digital ECL circuitry. The 2.5 $\mu$  CMOS integrates low power and high density logic and conversion functions.

The cell library contains analog, conversion, ECL and CMOS logic cells with many of them designed and characterized for 3.3V operation. A comprehensive design manual, proven CAD system and software libraries allow for fast, low risk customer (or Raytheon) designs.

For more information, give us a call at 1-800-722-7074.

In France: 01-46-3106-76

In Germany: 089-53-09-93-0

In Japan: 03-3280-4776

In the U.K.: 0279-421510

Raytheon Company, Semiconductor Division  
350 Ellis Street, Mountain View, CA 94043

## RSC4000 Sample Standard Cells

Current Feedback Op Amp	8-Bit Video ADC
Offset Voltage — 4 mV	Conversion Rate — 30 Msps
Bandwidth — 160 MHz	Power Consump. — 150 mW
Slew Rate — 700 V/ $\mu$ s	<b>8-Bit Video DAC</b>
<b>High Speed PLL</b>	Conversion Rate — 70 Msps
Max. Freq. — 120 MHz	Load — 37.5 or 75 $\Omega$
Lock Range — $\pm 15\%$	<b>ECL D Flip-Flop</b>
Supply Sensitivity — 0.2%/V	T <sub>PD</sub> — 1.5 ns
<b>Quadrature Modulator/ Demodulator</b>	Power Consump. — 13.5 mW
Wide Bandwidth — 250 MHz	<b>CMOS D Flip-Flop</b>
Large Differential Gain — 26 dB	T <sub>PD</sub> — 5.5 ns
Low Phase Error — $<2^\circ$ @ 150 MHz	Power Consump. — 50 $\mu$ W/MHz
	Supply Voltage — 3-5 V

## Raytheon

### WE THRIVE ON CHALLENGES



## MOTOR SPEED CONTROL


speed. The formula for the new clock frequency is

$$F_c = (\text{number of poles}/8)(\text{low rpm}/3492)(2 \text{ MHz}).$$

Because the number of poles is four and the low rpm is 1000, the new clock frequency will equal 286 kHz. The resistor-divider network, connected to the motor

windings, is shown in **Fig 5**. The maximum voltage at A, B, and C equals the supply voltage plus the back-EMF.

The acceleration rate necessary to reach full speed in 1 sec places a torque requirement on the motor. You can calculate this torque by multiplying the acceleration (from 1000 rpm to 10,000 rpm in 1 sec) by

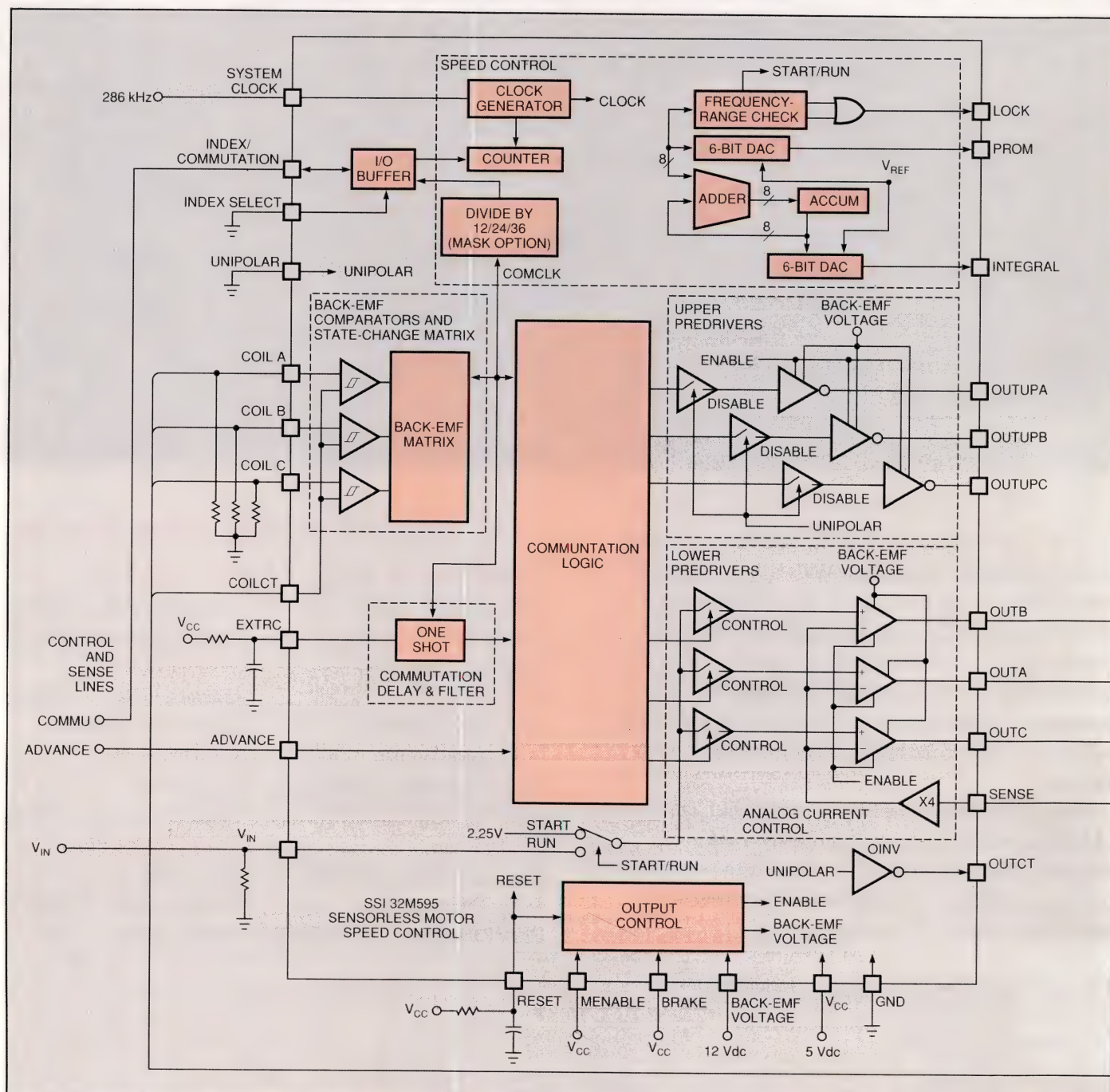

**Fig 4**—Speed control for this unipolar motor-control circuit is provided at the transconductance input,  $V_{IN}$ . In this case, the motor is again a 3-phase, 4-pole wye-connected unit with a center tap.



inertia. Because the acceleration required is  $942.5 \text{ rad/sec}^2$ , and the inertia is  $0.01 \text{ oz-in.-sec}^2$ , the torque required is  $9.425 \text{ oz-in.}$



Torque constant is a function of the amount of back-EMF the system can handle at maximum speed and the motor-winding resistance. The total voltage available is  $24\text{V}$ . This voltage drops across the back-EMF,

the driver transistor, and the motor winding. Maximum back-EMF occurs when the motor is spinning at  $10,000 \text{ rpm}$  ( $1047 \text{ rad/sec}$ ). Therefore, the back-EMF is related to the torque constant  $K_T$  by  $(K_T/141.6)(1047 \text{ rad/sec})$  and equals  $7.394K_T$ .

You can determine the IR drop in the motor windings ( $R_M$ ) and  $R_{\text{SENSE}}$  by dividing the motor torque by the torque constant and multiplying the result by the sum of the motor-winding resistance ( $R_M$ ) and  $R_{\text{SENSE}}$ . To calculate  $V_{\text{SAT}}$ , the voltage dropped across the driver transistor, divide the motor torque by the torque constant and multiply the result by the effective resistance ( $R_{\text{DS(on)}}$ ) of the driver transistor— $0.3\Omega$ , in this case.

The voltage applied across the motor terminals in Fig 4 is equal to the back-EMF ( $7.394K_T$ ) plus the IR drop in the motor windings  $(9.425/K_T)(R_M + R_{\text{SENSE}})$  plus  $V_{\text{SAT}}$   $(9.425/K_T)R_{\text{DS(on)}}$ . Therefore,  $24\text{V} - \text{back EMF} - \text{IR} - V_{\text{SAT}} = 0$  is a limit for  $K_T$  and  $R_M$ . Let  $R_T = R_M + R_{\text{SENSE}} + R_{\text{DS(on)}}$ . Therefore,

$$24 - 7.39K_T - (9.425/K_T)R_T = 0.$$

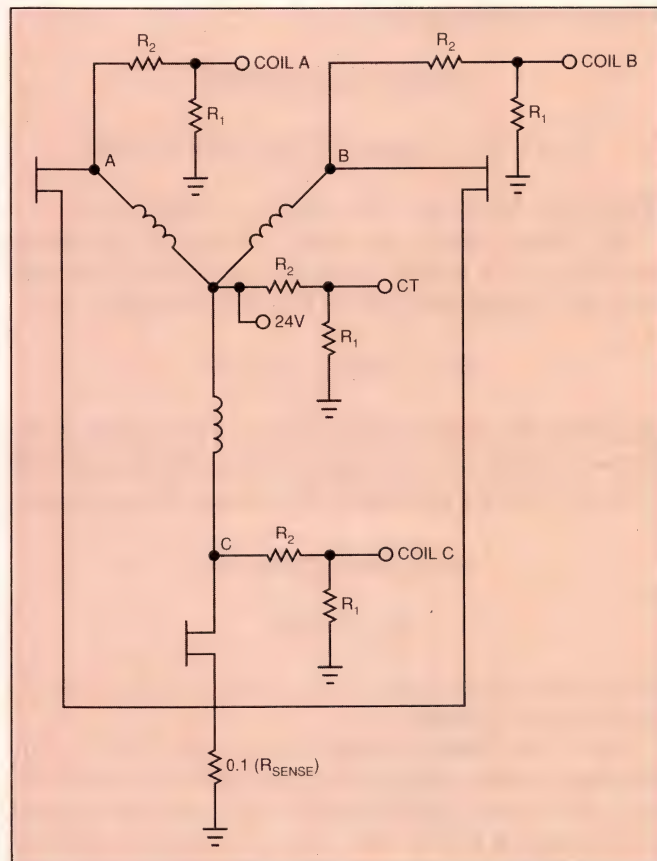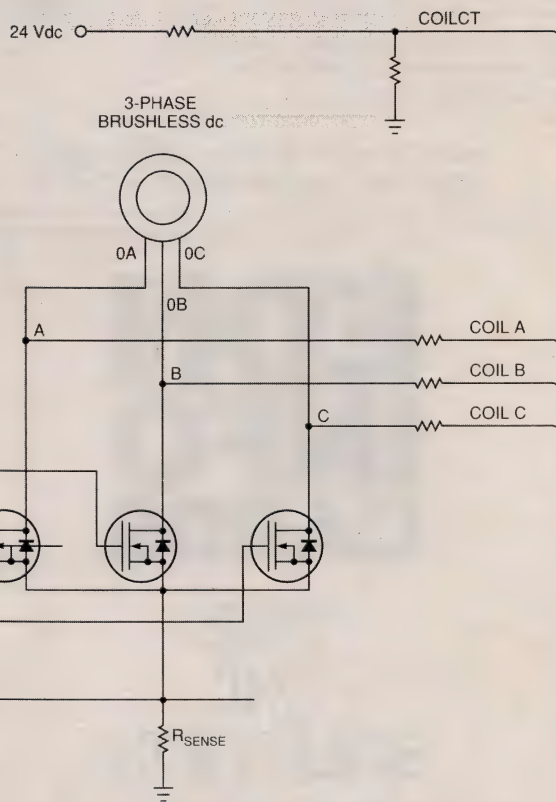

**Fig 5**—To operate in a unipolar fashion at voltage levels greater than  $12\text{V}$ , you must develop voltage-divider networks for each of the motor's terminals because the control chip should never have more than  $15\text{V}$  on any input.



## MOTOR SPEED CONTROL

Now you rewrite the equation to solve for  $K_T$  as

$$7.394 K_T^2 - 24K_T + 9.425R_T = 0.$$

You can assume a value for  $R_T$  and solve the quadratic equation  $K_T$ . If the roots are real,  $K_T$  can take the higher value and  $R_T$  can assume the trial value. To find the highest possible value for  $R_T$ , iterate to find the point where the roots for  $K_T$  are real and nearly equal to each other. The iteration yields an  $R_T$  of  $2.065\Omega$  and a  $K_T$  of 1.66:

$$R_T - R_{\text{DS(on)}} = R_M + R_{\text{SENSE}} = 2.065 - 0.3 = 1.765\Omega.$$

The current requirement through the motor windings will be equal to

$$9.425/K_T = 9.425/1.66 = 5.68A.$$

The value of  $R_{\text{SENSE}}$  will be equal to the voltage level at the current limit divided by the internal gain of the sense amplifier times the current requirement through the motor windings, or

$$2.25/(4 \times 5.68) = 0.099\Omega.$$

$$R_M = 1.765 - R_{\text{SENSE}} = 1.765 - 0.099 = 1.666\Omega.$$

Therefore,  $K_T = 1.66$  oz-in. and  $R_M = 1.666\Omega$  max.

For these values, the peak voltage at the motor terminals is the voltage drop across the motor windings plus the voltage drop across the driver resistor, or

$$24 + 7.394K_T = 36.274V.$$

To divide this peak voltage down to 12V or less at the motor winding, a you'll have to use a divider network such as that shown in Fig 5. You can use the expression

$$36.274(R_1/R_1 + R_2) = 12$$

or,

$$R_2 = 2.023R_1$$


to calculate  $R_1$  and  $R_2$ . If  $R_1$  equals 1.8 k $\Omega$ , then  $R_2$  would equal 3.64 k $\Omega$ .

$V_{\text{IN}}$  is the input to control speed and 2.25V is the maximum input voltage.  $V_{\text{IN}}$  controls the motor current, which can control speed. You need an external speed monitor in this case. The transconductance from  $V_{\text{IN}}$  to  $I_M$  is  $1/(4R_{\text{SENSE}})$  A/V. Having calculated values for the voltage divider and motor parameters  $K$  and  $R$ , you have completed the design of the 24V unipolar senseless dc motor controller.


EDN
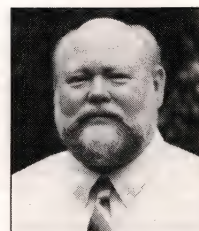
## Authors' biographies

*Dave Peters is a consultant at Silicon Systems Inc in Tustin, CA. He gives seminars and workshops in servo-system and speed-control design. He was also a member of the team that developed the speed-control chip used in the design examples in this article. Dave attended Brigham Young University in Provo, UT and National University in San Diego, CA.*



*Jeff Harth is a principal applications engineer at Silicon Systems Inc. In this position, he provides technical design support for servo- and motor-speed-control products. Jeff was also a member of the team that designed the speed-control chip used in this article. He holds a BSEE degree from California Polytechnic State University (San Luis Obispo, CA) and a Master's degree in system engineering from West Coast University (Los Angeles, CA).*

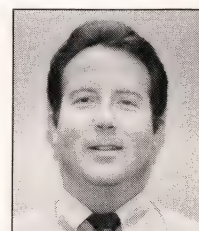

Article Interest Quotient (Circle One)  
High 503 Medium 504 Low 505

# EDN INFO CARDS

## THE 2¢ SOLUTION

to your marketing budget blues—the EDN Info Card Pack. At 2¢ per name, the EDN Info Card Pack can reach over 131,000 engineering specifiers affordably.

# EDN

A Partnership in Power and Prestige Worldwide



# We made our High Power Transformers smaller, lighter and ready to travel.

## Signal's new High Power International Transformers, 200VA to 3.5kVA, they're your passport to worldwide acceptance.

Our new MPI and HPI transformers share the same high performance and volumetric efficiency. Our unique insulating and construction techniques provide high isolation (4000V RMS Hipot), low leakage, and compliance with international safety standards. Here are other features that deserve a closer look:

- ★ Regulation: 7.5% or better (dependant on VA rating)
- ★ Low leakage current for medical applications
- ★ 5 mils thick copper Faraday shield reduces common mode noise
- ★ Shield terminated to handle high currents
- ★ MPI's—incorporate Faston/screw type shock proof terminals
- ★ HPI's—incorporate Euro style screw terminals
- ★ MPI's—operate at: 100V, 115V, 200V, 215V, 230V - 50/60 Hz
- ★ HPI's—operate at: 100V, 115V, 215V, 230V - 50/60 Hz
- ★ MPI's—approvals pending: UL 506, CSA 22.2 # 66 and VDE 0805 (IEC 950)
- ★ HPI's—approved to UL 506, CSA 22.2 # 66, and VDE 0550. Approval pending: TUV IEC 950
- ★ MPI's—constructed with Class B materials (130°C)
- ★ HPI's—constructed with Class H materials (180°C)

### ORDERING EXAMPLE:

MPI - 400 - 24

### MULTI-PURPOSE INT'L SERIES

VA SIZE (400VA)

OUTPUT VOLTAGE (SERIES CONNECTED)

AVAILABLE IN STANDARD VOLTAGES:

10V, 12V, 16V, 20V, 24V, 28V, 36V, 40V, 48V, 230V

FOR CUSTOM VARIATIONS CALL OUR ENGINEERING DEPARTMENT

Part No.	VA	Secondary		1-9 Pcs Price
		Series	Parallel	
MPI-200-10 THROUGH	200	10Vct. @ 20.0A	5V @ 40.0A	\$ 85.00
MPI-200-230	200	230Vct. @ 0.87A	115V @ 1.74A	
MPI-250-10 THROUGH	250	10Vct. @ 25.0A	5V @ 50.0A	90.00
MPI-250-230	250	230Vct. @ 1.1A	115V @ 2.2A	
MPI-300-10 THROUGH	300	10Vct. @ 30.0A	5V @ 60.0A	96.00
MPI-300-230	300	230Vct. @ 1.3A	115V @ 2.6A	
MPI-400-10 THROUGH	400	10Vct. @ 40.0A	5V @ 80.0A	111.00
MPI-400-230	400	230Vct. @ 1.74A	115V @ 3.48A	
MPI-650-10 THROUGH	650	10Vct. @ 65.0A	5V @ 130.0A	145.00
MPI-650-230	650	230Vct. @ 2.8A	115V @ 5.6A	
MPI-900-10 THROUGH	900	10Vct. @ 90.0A	5V @ 180.0A	162.00
MPI-900-230	900	230Vct. @ 3.9A	115V @ 7.8A	

### Mechanical Dimensions

Size	L	W	H	ML (mtg)*	MW (mtg)*	WGT
200VA	3.750"	4.203"	3.720"	3.250"	2.800"	6.22 lbs
	95.3 mm	106.6 mm	94.5 mm	82.6 mm	71.1 mm	2.82 kg
250VA	4.125"	3.898"	4.000"	3.625"	2.601"	6.76 lbs
	104.8 mm	99.0 mm	101.6 mm	92.1 mm	66.1 mm	3.07 kg
300VA	4.125"	4.223"	4.000"	3.625"	2.915"	7.80 lbs
	104.8 mm	107.3 mm	101.6 mm	92.1 mm	74.0 mm	3.54 kg
400VA	4.125"	4.805"	4.000"	3.625"	3.505"	9.82 lbs
	104.8 mm	122.0 mm	101.6 mm	92.1 mm	89.0 mm	4.46 kg
650VA	5.250"	4.430"	4.800"	4.500"	3.415"	14.83 lbs
	133.3 mm	112.5 mm	121.9 mm	114.3 mm	86.7 mm	6.73 kg
900VA	5.250"	5.197"	4.800"	4.500"	4.205"	19.84 lbs
	133.3 mm	132.0 mm	121.9 mm	114.3 mm	106.8 mm	9.01 kg

Part No.	VA	Secondary		1-9 Pcs Price
		Series	Parallel	
HPI-20	2000	230V @ 8.7A	115V @ 17.4A	\$ 368.00
HPI-27	2750	230V @ 12.0A	115V @ 24.0A	
HPI-35	3500	230V @ 15.2A	115V @ 30.4A	

### Mechanical Dimensions

Size	L	W	H	ML (mtg)*	MW (mtg)*	WGT
2000VA	7.500"	5.600"	6.560"	5.750"	4.350"	41.3 lbs
	190.5 mm	142.2 mm	166.6 mm	146.1 mm	110.5 mm	18.71 kg
2750VA	7.500"	6.230"	6.560"	5.750"	4.980"	48.0 lbs
	190.5 mm	158.2 mm	166.6 mm	146.1 mm	126.5 mm	21.77 kg
3500VA	7.500"	7.330"	6.560"	5.750"	6.080"	62.4 lbs
	190.5 mm	186.2 mm	166.6 mm	146.1 mm	154.4 mm	28.30 kg

**signal**  
TRANSFORMER

The American Original.™

BUY DIRECT: (516) 239-5777 ★ Fax: (516) 239-7208

Signal Transformer, 500 Bayview Ave., Inwood, NY 11696

\*For dimensional drawings, schematics, or any other additional questions you might have, please contact our Engineering Dept. CIRCLE NO. 106




What will Siliconix' new 3-V p-channel MOSFETs do  
to help shrink system size?
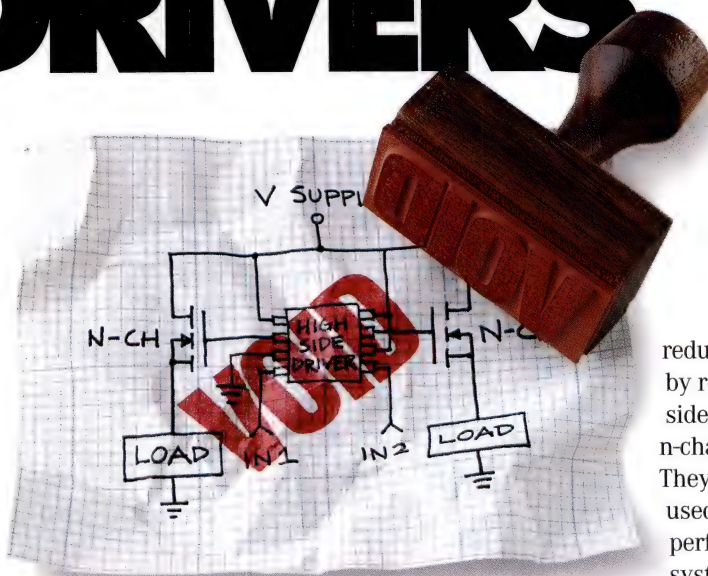
# STAMP OUT HIGH-SIDE DRIVERS


With leakage currents  
of only  $1\mu\text{A}$ , these new  
LITTLE FOOT® devices  
are the industry's most  
efficient 3-V solutions.

They're unequalled for  
design simplicity, power  
efficiency, small size, and  
cost effectiveness. And ideal for load switching in  
portable computers and cellular phones.



reduce part count  
by replacing a high-  
side driver IC and an  
n-channel MOSFET.  
They also can be  
used to enhance the  
performance of 5-V  
systems.

## LITTLE FOOT SO-8 POWER MOSFETs

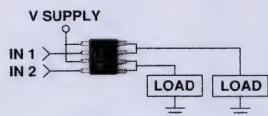

Device	Breakdown Voltage (V)	On- Resistance ( $\Omega$ )	Current (A)
Si9433DY	-12	0.075 @ $V_{GS} = -4.5\text{V}$	$\pm 5.1$
single p-ch	-12	0.110 @ $V_{GS} = -2.7\text{V}$	$\pm 4.0$
Si9933DY	-12	0.13 @ $V_{GS} = -4.5\text{V}$	$\pm 3.8$
dual p-ch	-12	0.21 @ $V_{GS} = -2.7\text{V}$	$\pm 3.0$

## Simplified load switching ... no high- side driver.

These new  
p-channel  
devices oper-  
ate directly  
from 3-V logic  
supplies or  
batteries.  
They simplify  
design and

## Increased efficiency ... and longer battery life.

Both the new surface-mount Si9433 and the Si9933  
draw far less power than the typical high-side driver/  
n-channel solution. And they have low voltage drop  
as well, so no heat sink is required.

## Designing small ... a big advantage.

These power dense SO-8 LITTLE FOOT devices  
significantly shrink system size. So, get small....  
contact your local TEMIC/Siliconix sales office.  
Or call our toll-free hot line now! **1-800-554-5565**,  
ext. 977. Ask for your "3-V LITTLE FOOT" Design Kit.

**Siliconix**  
A Member of the TEMIC Group



# ***A Dawn on a New Decade !***

## **The 30th Design Automation Conference**

See The Best In  
**Electronic Design Automation**  
Displayed To The World!

- Come hear what the Russians developed on an AT 286 PC with 640K RAM and a 20Meg Hard Drive, attend the session **"Russian CAE"**
- Over 115 exhibitors of EDA products
- Continuation of the successful user focused sessions, including a session on the probability of Windows/NT™ and the Intel Pentium™ processor becoming the next generation EDA platform
- Following the discussion by **Ralph D. Numberger** on the effect of the Clinton/Gore administration on EDA, an EDAC/DAC User Group will be organized during Session 20  
**Become a part of this new event**
- **Free Monday Exhibits-only passes** available for June 14, 1993  
Call 800-321-4573 or send a one line email message to: [freeday@dac.com](mailto:freeday@dac.com)
- Over 110 technical papers and panel presentations
- Full-day tutorials on cutting edge EDA topics
- Leading EDA vendors presenting their latest products, Monday, June 14, 1993
- For the first time at DAC, private Demo Suites will be conveniently located in the Dallas Convention Center and not in the hotels



**Dallas Convention Center • Dallas, Texas • June 14 - 18, 1993**

sponsored by:



Call: 800-321-4573 • fax: 303-530-4334 • 7490 Clubhouse Rd., Suite 102 Boulder, CO 80301 U.S.A. • email: [dacinfo@dac.com](mailto:dacinfo@dac.com)



## The little modem that could

Think of all the digital sorts of things that you'd like to do with your standard phone line: high-speed data communications, caller ID, and fax transmission and reception. Now envision these capabilities realized in a small, 1-in.-high aluminum box. What you see in your mind's eye is the 14.4-kbps Supra FAXModem V.32bis, a reliable workhorse for computer communications over the telephone. The external version of this product costs \$399.95. The company sells this product with DOS- or Windows-based communications and fax software for \$449.95, \$389.95 for an internal package, or \$479.95 for a similarly equipped Mac package.

I've owned a Supra 2400-bps modem for many years. It always operates reliably, even over noisy phone lines. The FAXModem V.32bis retains this critical feature, despite the way I'm using it. You see, in EDN's modern office environment, we have no archaic analog phone lines. Instead, we have modern AT&T digital PBX lines, incompatible with all conventional telephone equipment. Thus I must use a special phone coupler from Konexx (San Diego, CA) that taps into my digital phone's analog handset cord and provides a convenient RJ-11 jack for a modem. Despite the Konexx box, the PBX's digitization of the modem signal and conversion back to analog, and the usual telephone system noise, this modem had no problems communicating with modems across the country.

The FAXModem V.32bis operates at speeds to 14,400 bps when talking to a compatible modem. If you want to save \$100, you can buy the FAXModem V.32 for \$299.95. Using the FAXModem V.32bis's MNP 5 data compression, you can theoretically achieve 38,400-bps transmissions, and BTLZ compression can take you to 57,600 bps. I



never operated at those rates. You must be communicating with a compatible modem to use such high rates.

Beyond transmission rates, there's little you can say about a good modem; you plug it in, and it works. One unusual feature on this modem is a 2-character alphanumeric display that tells you what's happening with the modem. It tells you when the modem is dialing a number, when the remote modem connects with yours, and what transmission speed you're using. Being able to monitor this display is an excellent justification for having an external modem. The manual is clear, has several useful appendices, and includes a well-written troubleshooting chapter, on the off chance that you have problems.

Supra has updated the firmware in this modem twice since I received it. The first time was to expand the modem's fax capabilities. The product incorporates Rockwell's fax/modem chip set, so its capabilities are programmable. I tried the DOS-based fax software and easily was able to send a document to EDN's dumb fax machine but not to EDN's super smart "fax machine from hell" (EDN, October 1, 1992, pg 33). I didn't try to receive faxes using this

modem because the Konexx box doesn't allow the modem to answer the phone. However, the fax abilities are really determined by the fax software. Supra provides Fax-talk from Thought Communications (Santa Clara, CA) for DOS faxing and Winfax from Delrina Technology (San Jose, CA) for Windows users.

The second ROM upgrade added caller-ID abilities to the modem. You could use this feature to screen calls, assuming that you don't have a PBX that filters such information from your phone lines, but another suggested use really caught my eye. Bulletin boards conceivably can use caller ID for automatic log in. However, this feature isn't much help for road warriors with laptop computers who call in from the nearest pay phone.

In summary, this is a modem that performs well. It has good documentation, it has state-of-the-art capabilities, the vendor supports it well, and it doesn't cost as much as many of its competitors. If there's anything more you could possibly want in a modem, it will probably appear in the FAXModem's next ROM upgrade.—**Steven H Leibson**

Supra Corp, 7101 Supra Dr SW, Albany, OR 97321. Phone (503) 967-2400. FAX (503) 967-2401.



# Mmmmmmmn!

The perfect way to start your day.  
TOKIN high-performance mini-capacitors.



There's no question that TOKIN's new chip-type multilayer ceramic capacitors command a loyal following. Suddenly, you find them in the finest devices in town.

One reason is their large permittivity (capacitance). Another is size—1/5 that of conventional products. And to clinch the deal, they're very competitively priced.

What's more, these fresh capacitors are ideal for surface mounting and offer exceptional reliability.

TOKIN's unique roasting method involves firing two special materials with different temperature characteristics at a low temperature (less than 1,000°C). The result is increased capacitance and reduced costs.

An exciting breakthrough in capacitor technology!


TOKIN capacitors—the perfect blend for a wide range of applications from EMI/EMC filters to bypass capacitors.

Get an early start on your day. Give us a call and discover the true meaning of TOKIN performance.


## Characteristics [Y5U (Z5U)]

Cap.	Rated Voltage	
	25V	50V
10µF	IE106ZY5U-C205M IE106ZY5U-C205F IE106ZY5U-C304F	IH106ZY5U-C505F
	IE156ZY5U-C505F	—
	IE226ZY5U-C505F	—
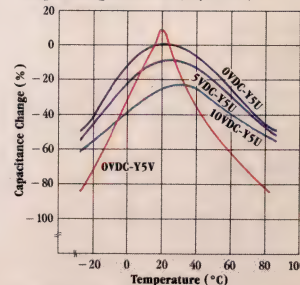
## Stability at Low and High Temperatures (10µF 25V)



## Frequency Characteristics (10µF 25V)

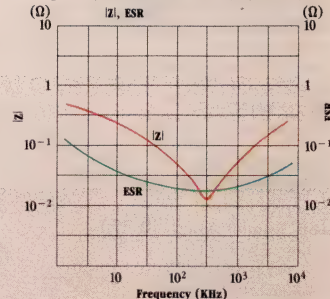


## New Multilayer Ceramic Capacitor

		10µF/25V		22µF/25V	
NEW	Y5U		2.7 × 5.7 × 2.5		5.0 × 5.7 × 2.5
	Y5U		6.3 × 10 × 3.0		8.0 × 12.5 × 4.0
Previous Models (No longer manufactured)	Y5V		4.0 × 8.0 × 3.0		6.3 × 10 × 3.0


## Dimensions

Shape	L	W	T (max)
C205	5.7 ± 0.4	2.7 ± 0.3	2.5
C304	4.5 ± 0.4	3.2 ± 0.3	2.5
C505	5.7 ± 0.4	5.0 ± 0.4	3.0

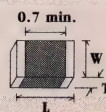

## Ceramic Capacitor End Termination (Reflow type)

Nickel/Tin Metal Termination	IE106ZY5U-C205M
Fired-on End Termination	All Case Code

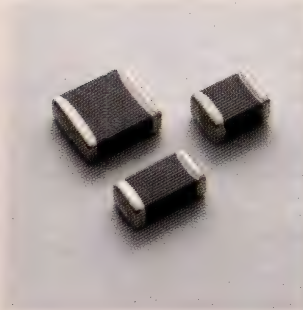

# TOKIN

## Tokin Corporation

Hazama Bldg., 5-8, Kita-Aoyama 2-chome, Minato-ku, Tokyo 107, Japan Phone: 03-3402-6166 Fax: 03-3497-9756

## Tokin America Inc.

155 Nicholson Lane, San Jose, California 95134, U.S.A. Phone: 408-432-8020 Fax: 408-434-0375

### Chicago Branch

9935 Capitol Drive, Wheeling, Illinois 60090, U.S.A. Phone: 708-215-8802 Fax: 708-215-8804

### Boston Branch

945 Concord Street, Framingham, Massachusetts 01701, U.S.A. Phone: 508-875-0389 Fax: 508-875-1479



**Business/Publishing Headquarters**  
**Cahners Building**  
**275 Washington St**  
**Newton, MA 02158**  
**Fax: (617) 558-4470**

**VP/Publisher**  
 Roy W Forsberg  
 (617) 558-4367  
 Darlene Fisher, Assistant  
 (617) 558-4363

**Advertising Sales Director**  
 Jeff Patterson  
 (617) 558-4454

**Marketing/Business Director**  
 Deborah Virtue  
 (617) 558-4779

**Director of Production/Manufacturing**  
 John R Sanders

**Production Staff**  
 Andrew A Jantz, Supervisor  
 Sheila Hamill, Manager  
 Lynn Morelli, Assistant

## NEW ENGLAND/NY

Chris Platt, Clint Baker  
 199 Wells Ave  
 Newton, MA 02159  
 Tel: (617) 964-3730  
 Fax: (617) 332-7128

## NEW YORK CITY/NEW JERSEY

Dan Rowland  
 249 W 17th St  
 New York, NY 10011  
 Tel: (212) 463-6419  
 Fax: (212) 463-6404

## SOUTHEAST CORRIDOR/PA

Steve Farkas  
 487 Devon Park Dr  
 Wayne, PA 19087  
 Tel: (215) 293-1212  
 Fax: (215) 293-0359

## IL, IN, KY, MI, OH, TN

Greg Anastos  
 Cahners Plaza  
 1350 E Touhy Ave, Box 5080  
 Des Plaines, IL 60018  
 Tel: (708) 635-8800  
 Fax: (708) 635-0929

## IL, MN, NE, IA, KS, ND, SD, WI, MO, AL, AR, OK, CANADA

Jack Johnson  
 Cahners Plaza  
 1350 E Touhy Ave, Box 5080  
 Des Plaines, IL 60018  
 Tel: (708) 635-8800  
 Fax: (708) 635-0929

## ARIZONA

Jim McErlan  
 44 Cook St  
 Denver, CO 80206  
 Tel: (303) 388-4511  
 Fax: (303) 394-4709

## COLORADO

Frank Granzeier  
 3031 Tisch Way, Suite 200  
 San Jose, CA 95128  
 Tel: (408) 243-8838  
 Fax: (408) 243-2144

## ORANGE/RIVERSIDE/SAN DIEGO COUNTIES

Jim McErlan  
 18818 Teller Ave, Suite 170  
 Irvine, CA 92715  
 Tel: (714) 851-9422  
 Fax: (714) 752-6867

## LOS ANGELES/SOUTHERN CA, NV

Susan N Green  
 18818 Teller Ave, Suite 170  
 Irvine, CA 92715  
 Tel: (714) 851-9422  
 Fax: (714) 752-6867

## NORTHERN CA/SILICON VALLEY

James W Graham, Frank Granzeier  
 Donnie Jones Adams  
 3031 Tisch Way, Suite 100  
 San Jose, CA 95128  
 Tel: (408) 243-8838  
 Fax: (408) 243-2144

## WASHINGTON, OREGON

Pat Dakin  
 1750 SW Skyline Blvd, Box 6  
 Portland, OR 97221  
 Tel: (503) 297-3382  
 Fax: (503) 297-4305

## TEXAS

Al Schmidt  
 2 Forest Plaza  
 12201 Merit Dr, Suite 730  
 Dallas, TX 75251  
 Tel: (214) 419-1825  
 Fax: (214) 419-1829

## European Operations Managing Director

Tully Giacomazzi  
 Cahners Publishing  
 Ortlerstrasse 8  
 Box 70 16 20  
 8000 Munich 70 Germany  
 Tel: 49 89 769 02 391  
 Fax: 49 89 769 02 144

## UK

John Waddell  
 Crystal Communications  
 Purland House  
 151 Nathan  
 London SE28 0AB  
 Tel: 44-81-312-4444  
 Fax: 44-81-312-1078

## ITALY

Gianni Soddu  
 International Advertising Network  
 Via Cassola 6  
 20122 Milano Italy  
 Tel: 39-2-583-15738  
 Fax: 39-2-546-2573

## SCANDINAVIA

Anders Josefson  
 ComPro Media AB  
 Box 1343  
 18125 Lidingo, Sweden  
 Tel: 46 87 65 7720  
 Fax: 46 87 65 3161

## FRANCE/BELGIUM

Laura Whiteman  
 14 Rue des Parisiens  
 92600 Asnieres sur Seine  
 France  
 Tel: 331-47900507  
 Fax: 331-47900643

## GERMANY—NIELSEN 4/BAVARIA

Margarethe Munchmeier  
 Verlagsvertretungen GmbH  
 Verlagsservice Mediaberatung  
 Neuturmstrasse 10  
 8000 Munchen 2 Germany  
 Tel: (49-89) 22 20 15  
 Fax: (49-89) 299 160

## SPAIN

Luis S Giner  
 Urbanizacion Santa Barbara  
 Edificio Cumbre, Apt 7B  
 08870 Sitges (Barcelona) Spain  
 Tel: 3-894-43-26  
 Fax: 3-894-88-37

## AUSTRIA

Sven Kollensperger  
 Permedia  
 Mozartstrasse 43  
 A-4020 Linz  
 Tel: 732-79-34-55  
 Fax: 732-79-34-58

## ISRAEL

Asa Talbar, Talbar Media  
 Box 22917  
 Tel Aviv 61228, Israel  
 Tel: 972-3-223-621  
 Fax: 972-3-524-2177

## SWITZERLAND

Peter Combaz, Roswitha N Briand  
 Exportwerbung AG  
 Kirchgasse 50, 8024 Zurich 1  
 Tel: 41 1 261 4690  
 Fax: 41 1 251 45 42

## NETHERLANDS/NORTHWEST GERMANY (NIELSEN 1,2)

Albert Ticheler  
 Dialtic  
 Busweg 46  
 5632 PN Eindhoven  
 Tel: 31-40-41-37-27  
 Fax: 31-40-42-04-30

## CENTRAL/SOUTHWEST GERMANY

Franz Fleischmann, MediaPac  
 Hanauer Landstrasse 294  
 D-6000 Frankfurt/Main 1  
 Germany; Tel: 4969 42 2951  
 Fax: 49 69 421288

## HONG KONG

Adonis Mak  
 Cahners Asia Limited  
 22nd fl, Lo Yang Court  
 Commercial Bldg  
 212-220 Lockhart Road  
 Wanchai, Hong Kong  
 Tel: 852-572-2037  
 Fax: 852-838-5912

## JAPAN

Kaoru Hara  
 Dynaco International Inc  
 Suite 1003, Sun-Palace Shinjuku  
 8-12-1 Nishishinjuku, Shinjuku-ku  
 Tokyo 160, Japan  
 Tel: 81-3-366-8301  
 Fax: 81-3-366-8302

## KOREA

Jeong-guon Seo  
 Media Network  
 CPO Box 6997  
 Seoul, Korea  
 Tel: 82-2-752-4392  
 Fax: 82-2-752-4394

## SINGAPORE/MALAYSIA

Hoo Siew Sai  
 Major Media Singapore PTE Ltd  
 52 Chin Swee Rd  
 #06-00 Resource Bldg  
 Singapore 0316  
 Tel: 65-738-0122  
 Fax: 65-738-2108

## AUSTRALIA

Alexandra Harris  
 World Media Singapore Pts Ltd  
 Level 1  
 Suite 5, 89 York St  
 Sydney, NSW 2000 Australia  
 Tel: 61-2-283-2788  
 Fax: 61-2-283-2035

## TAIWAN

Parson Lee  
 Acteam International Marketing Corp  
 ZF, No. 17, Alley 7, Lane 217, Sec. 3  
 Chung Hsiao E Rd  
 Box 82153, Taipei, Taiwan ROC  
 Tel: 886-2-7114833  
 Fax: 886-2-7415110

## PRODUCT MART

Joanne Dorian  
 249 W 17th St  
 New York, NY 10011  
 Tel: (212) 463-6415  
 Fax: (212) 463-6404

## INFO CARDS/LITERATURE LINK

Melissa Bachman  
 Tel: (617) 558-4282

## CAREER OPPORTUNITIES

Roberta Renard  
 National Sales Manager  
 Janet O Penn, Eastern Sales Manager  
 Nanci C Hilbert, Sales Coordinator  
 103 Eisenhower Pkwy  
 Roseland, NJ 07068  
 Tel: (201) 228-8602, 228-8610,  
 228-8608; fax: (201) 228-4622

Judy Telander  
 West Coast Sales Manager  
 12233 W Olympic Blvd, Suite 236  
 Los Angeles, CA 90064  
 Tel: (310) 826-5818  
 Fax: (310) 207-1067

Direct Mail Service: (708) 390-2361

Wendy A Casella, Mary Beth Cassidy,  
 Muriel Murphy  
 Advertising/Contracts Coordinators  
 (617) 964-3030

## Cahners Magazine Div

Robert Krakoff, President/Chief  
 Operating Officer  
 Cahners Publishing Co  
 Tom Dellamaria, Senior VP/Production  
 & Manufacturing


**Circulation:** Denver, CO  
 (303) 388-4511

Reprints of EDN articles are available on a custom printing basis at reasonable prices in quantities of 500 or more. For an exact quote, contact Andrea Marwitz, Cahners Reprint Service, Cahners Plaza, 1350 E Touhy Ave, Box 5080, Des Plaines, IL 60017. Phone (708) 390-2240.


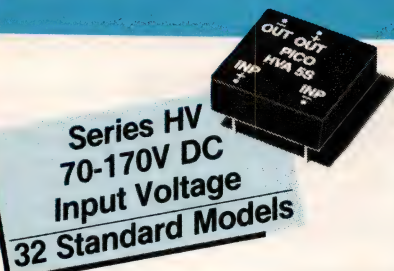
# PICO DC-DC INDUSTRIAL CONVERTERS

**Economical**  
**Wide Input Voltage**  
**36-170V DC**  
**Hi Reliability**



- Single and Dual Isolated Outputs
- Low Profile, .500" max. ht.
- Up to 15 Watts
- No External Components Required
- Fully Regulated
- Short Circuit Protection
- No Heat Sink or Electrical Derating Required
- -20°C to +70°C Operating Temp. Ambient



**Series LV**  
**36-80V DC**  
**Input Voltage**  
**36 Standard Models**

Delivery—  
stock to one week

**PICO**  
**Electronics, Inc.**

453 N. MacQuesten Pkwy. Mt. Vernon, N.Y. 10552

Call Toll Free **800-431-1064**

IN NEW YORK CALL **914-699-5514**  
FAX **914-699-5565**

See EEM  
or send direct for  
FREE PICO Catalog

## EDN-INTERNATIONAL ADVERTISERS INDEX

3M ITSD Vibration Control . . . . .	107	NCI . . . . .	167
AMP Inc . . . . .	28-29	NCR Corp . . . . .	30
ASM Lithography . . . . .	89	National Instruments . . . . .	84
AT&T Microelectronics . . . . .	131, 159-161	National Semiconductor, Inc . . . . .	22-23, 53-55, 71-73
Abbott Electronics Inc . . . . .	42	Nohau Corp . . . . .	69
Accel Technologies Inc . . . . .	157	Novatech U.S. Inc . . . . .	156
Advanced Micro Devices . . . . .	152	Omaton . . . . .	154
Advanced Microcomputer Systems Inc . . . . .	165	Omron Electronics Inc . . . . .	113
Advin Systems . . . . .	165	P-CAD/CADAM . . . . .	123-125
Allegro MicroSystems Inc . . . . .	C2	Pacific Softworks . . . . .	46
American Reliance Inc . . . . .	164	Philips Industrial Electronics . . . . .	125
Analogy . . . . .	167	Philips Key Modules . . . . .	70
Atlanta Signal Processors Inc . . . . .	52	Pico Electronics . . . . .	9, 172
BP Microsystems Inc . . . . .	164	Power-One Inc . . . . .	50
Bliley Electric Co . . . . .	152	Printrex . . . . .	155
Cactus . . . . .	166	Procom Technology . . . . .	144
Cahners CAPS . . . . .	149-151, 164	Quad Design . . . . .	34
Capilano . . . . .	167	Quality Semiconductor . . . . .	134
Ceibo . . . . .	164	Quatech . . . . .	166
Cirrus Logic . . . . .	32-33	Raltron Electronics Corp. . . . .	152
Coilcraft . . . . .	143	Roytheon Co . . . . .	91
Compcontrol Inc . . . . .	163	Router . . . . .	163
Condor . . . . .	165	Samsung Semiconductor . . . . .	12-13
Conversion Devices Inc . . . . .	48	Samtec Inc . . . . .	153
Cypress Semiconductor . . . . .	19	Scientific Endeavors . . . . .	165
Data/IO . . . . .	56, 167	Sierra Circuits . . . . .	163
Dale Electronics . . . . .	1	Signal Transformer Co . . . . .	C4
Datel Inc . . . . .	162, 178	Siliconix Inc . . . . .	C3
Design Automation Conference . . . . .	176	Silvaco International . . . . .	166
Digi-Key Corp . . . . .	2	Softaid . . . . .	164
EDN Caravan . . . . .	62-63	Star Semiconductor Corp . . . . .	67
ESL, A Subsidiary of TRW . . . . .	166	Switching Power Inc . . . . .	147
Elan . . . . .	167	Synergy Microsystems Inc . . . . .	24
FDK . . . . .	152	Tamarack . . . . .	166
Harris Semiconductor . . . . .	133	Tatum Labs Inc . . . . .	165
Hewlett-Packard Co. . . . .	16, 136-137	Tektronix Inc . . . . .	81-83
Hughes Microelectronics . . . . .	133	Texas Instruments . . . . .	10-11, 35-37
Hybridyne Inc . . . . .	60	Tokin Corp . . . . .	174
IEE . . . . .	38	Toshiba America Electronic Components . . . . .	14-15, 140
Incredible Technology . . . . .	163	Tribal Microsystems . . . . .	163
Independent Digital Consulting . . . . .	165	Universal Cross Assemblers . . . . .	167
Integrated Device Technology Inc . . . . .	40	Vicor Corp . . . . .	115-117
Integrated Motions . . . . .	164	Vishay Resistive Systems . . . . .	140A-B
Interpoint . . . . .	138	Westcor Corp . . . . .	6
Ironwood Electronics Inc . . . . .	167	WinSystems . . . . .	141
Kepeco Inc . . . . .	95-106	Wolfram Research Inc . . . . .	108
LeCroy . . . . .	64	Xeltek . . . . .	166
Leap . . . . .	166	Xicor Inc . . . . .	118
Linear Technology Corp . . . . .	126	Z-World . . . . .	163
Link Computer . . . . .	164	Zenith Electronics Corp. . . . .	158
Logical Devices . . . . .	165		
Maxim Integrated Products . . . . .	45, 47, 49		
Megapower Corp . . . . .	142		
Memory Protection Devices . . . . .	156		
Mental Automation . . . . .	167		
Mercury Computer Systems . . . . .	8		
Meta-Software Inc . . . . .	79		
Metalink Corp . . . . .	158, 165		
Micron Semiconductor Inc . . . . .	59		
Mini Circuits . . . . .	3, 4, 20-21, 26-27, 129		
Mizar Inc . . . . .	146		
Motorola Semiconductor Products Inc . . . . .	61		

**Recruitment Advertising 168-171**

This index is provided as an additional service. The publisher does not assume any liability for errors or omissions.





## DESKTOP VIDEO AND TELEPHONY PRODUCTS

GREAT VALLEY PRODUCTS

In just over four years GVP (Great Valley Products), located in King of Prussia, PA, has become the largest third party supplier in all key Commodore Amiga markets.

GVP is now building on the vision and exceptional functional expertise that has led to this phenomenal success. We are diversifying our products to other platforms. Specifically — development of high end professional desktop video solutions and telephone/fax/voice solutions for the PC platform.

We have multiple engineering openings for Directors thru Developers.

### Video Design Engineers

In depth knowledge of PAL and NTSC video applications a must. 3 plus years experience, Gate Array and PC hardware experience required.

### Modem Design Engineers

Requires 3 plus years DSP and/or Gate Array design, preferably in PC hardware design. Modem design for international applications a major plus.

### Software Engineers

Requires 3 plus years programming in C or Assembly; telephony or video background in PC environment preferred. Direct experience with drivers and MS Windows (GUI). DSP experience a plus.

In recognition of our achievements, GVP was listed in the Philadelphia Business Journal's 1991 and 1992 annual "Top 100 List" for privately held companies in the Greater Philadelphia/Delaware Valley Area.

### T. Williams Consulting GVP EXTERNAL RECRUITING OFFICE

P.O. Box 337, Collegeville, PA 19426

FAX: 215/489-4646

Equal Opportunity Employer

### IOWA MIDWEST COMMERCIAL UHF RADIO INDUSTRIAL CONTROL

4+ YRS. RF CIRCUIT DESIGN, DIGITAL INTERFACE, STEM INTEGRATION, TYPE APPROVAL TESTING, SOME INTERNATIONAL TRAVEL REQUIRED.

5+ YEARS. A-B PLC'S, LADDER LOGIC, 'C' PROGRAMMING, MOTION CONTROL, POWER ELECTRONICS, DATA ACQUISITION, DATA COMMUNICATION, MUST HAVE STRONG OBJECT MANAGEMENT EXPERIENCES.

DON GALLAGHER, MSEE, PRES.  
GALLAGHER & ASSOCIATES  
1145 LINN RIDGE RD.  
MOUNT VERNON, IA 52314  
(319) 895-8042 (319) 895-8455 FAX

### MIAMI, FLORIDA

B.S.E.E. EXPERIENCE IN DIGITAL & ANALOG ELECTRONICS. IN THE DESIGN OF MAGNETIC ELEMENTS (TRANSFORMERS, INDUCTORS, ETC.). THEORETICAL & PRACTICAL EXPERIENCE IN THE FIELDS OF DISCHARGE LIGHTING DEVICES. BASIC EXPERIENCE IN PLASMA PHYSICS AND A MINIMUM OF TWO YEARS WORK EXPERIENCE IN PLASMA PHYSICS AND A MINIMUM OF TWO YEARS WORK EXPERIENCE IN THE DEVELOPMENT AND DESIGN OF SWITCHMODE POWER ELECTRONICS OR A MINIMUM TWO YEARS OF WORK EXPERIENCE IN THE DESIGN AND DEVELOPMENT OF HIGH INTENSITY DISCHARGE ELECTRONIC BALLAST.

SUBMIT RESUME ONLY TO JOB SERVICE OF FLORIDA, 701 S.W. 27 AVENUE—ROOM 15, MIAMI, FL 33135. REF: JOB ORDER #FL 0785819.

E.O.E.

## It's Good To Be Well Connected In San Diego. NOKIA Proves It.

From Finland comes NOKIA Mobile Phones, Europe's largest—and the world's second largest mobile phone manufacturer. As part of the NOKIA group of high-technology companies with research and development centers worldwide, we have selected San Diego as the site for our latest R&D Center. Currently, we are seeking self-directed engineers to be the innovators of future generations of NOKIA hand-held portable digital cellular phones.

Start from the future by investigating the following opportunities:

**HARDWARE ENGINEER** Responsible for all hardware design aspects of a next-generation cellular telephone, including system and board design, prototype development and integration. Requires a BS/MS in EE or related science and 5+ years' experience developing hardware, board-level designs, systems, ASICs, PALs, FPGAs and Firmware. Must have demonstrated understanding of hardware, software and ASIC partitioning and completed at least two major designs from conception through high-volume production. Must also be able to design for EMI and mechanical considerations and have taken a product from conception to high-level production.

**CELLULAR SOFTWARE ENGINEERS** Responsible for designing, coding, debugging, integrating and testing software for next-generation cellular telephones. Requires BS/MS in CS, EE or related science, plus a minimum of 5+ years' software development experience in software design methodology, including Structured Analysis and design methods (CASE tools), and knowledge of network protocol software design. Unix or VMS operating systems and multi-tasking embedded systems also required.

**ANALOG/ASIC ENGINEER** Responsible for system-level definition, evaluation and testing of an analog CMOS integration circuit, including A/D's and D/A's; acting as liaison with vendors and supervising vendor's work; supporting other analog IC (Bipolar/Bi-CMOS) design projects. Will also design analog IC (Bipolar/Bi-CMOS) circuitry. Requires a BS/MS/Ph.D in a related discipline and a minimum of 5 years' experience in analog CMOS or Bi-CMOS integrated design. Familiarity with amplifiers, A/D and D/A converters and low power design, as well as knowledge and ability to use modern CAD tools in Apollo/HP environment also necessary.

**DIGITAL ASIC ENGINEERS** Requires a BS/MS in CS, EE or related science, plus a minimum of 5 years designing digital CMOS circuits. Must be familiar with digital signal processing in telecommunications applications, low power design methodologies, design for testability and FPGA prototyping techniques. Should have experience with modern design tools (VHDL, Mentor, Synopsys) for top down design simulation and verification.

**DSP ASIC ENGINEER** Responsible for specification, implementation and delivery of DSP ASIC parts. This includes specifying hardware requirements for algorithm and system functionality, writing detailed block-level specifications, writing and simulation of synthesizable VHDL models, VHDL synthesis, and gate-level simulation and timing verification. Requires previous experience in the following areas: **DSP algorithm implementation**, VHDL and Top Down Design Methodology, VHDL synthesis, low power logic design, gate array/std cell design implementation, testability, and state-of-the-art CAD/CAE tools. **Systems experience also required.**

**CELLULAR SYSTEMS ENGINEER** Requires 5+ years' cellular experience to include signaling protocols and development of cellular products for high-volume production. Also requires knowledge of the North American cellular market and related industry technologies. TIA experience is desirable. Must have strong technical leadership, communication, negotiating and presentation skills. Will be involved in setting the technical direction of the division by representing NOKIA in telecommunications organizations; direct involvement in negotiating and setting industry standards; and performing market and technology research. Some travel involved.

Discover the proven product lines and exciting opportunities that NOKIA is bringing to San Diego. Send your resume to: NOKIA Mobile Phones, Code 134, 9605 Scranton Rd., Ste. 303, San Diego, CA 92121, or fax it to: (619) 450-3168. No entry-level positions available. Principals only. No phone calls please.

**NOKIA**  
EEO/ADA Employer



## SENIOR SYSTEMS ENGINEERS

Loral Defense Systems-Akron, a division of the Loral Corporation, is seeking Senior Engineers with the following credentials:

- BSEE, 15+ years' experience in design, development, and integration of systems for simulator/trainer applications
- Extensive proposal experience
- Front-end requirement analysis
- Hardware/software systems integration
- Extensive knowledge pertaining to simulator methodology
- Good understanding of future technology paths in simulator/trainer arena
- Managerial experience

Also Programmer positions available—Junior and Senior; aircraft simulator background preferred.

We offer competitive compensation and benefits. Send resume to: Bill Turnbow; Loral Defense Systems-Akron; Dept. 131; 1210 Massillon Road; Akron, OH 44315-0001; or FAX to 216-796-6604.

Equal  
Opportunity  
Employer  
1X0200X

**LORAL**  
DEFENSE SYSTEMS-AKRON  
A DIVISION OF LORAL CORPORATION

### Attention - Data Processing Professionals

## A Special Career Event for Minority Professionals

Exhibit Hours: 12:30 to 6:00pm Free Career Seminars begin at 11:00am



Proudly Presents...

**AFFIRMATIVE ACTION**  
Career Conventions

FRIDAY, JUNE 11TH

**The NAACP Region VII**  
(MD, VA & WASHINGTON D.C.)

AT THE

**MCLEAN HILTON, TYSON'S CORNER**

7920 Jones Branch Drive  
McLean, VA 22102

TUESDAY, JUNE 29TH

**The NAACP Region V**  
(AL, FL, GA, MS, NC, SC & TN)

AT THE

**GEORGIA WORLD CONGRESS CENTER**

285 International Blvd., NW  
Atlanta, GA 30313

**AFFIRMATIVE ACTION**  
Diversity Job Fair

FOR MORE INFORMATION  
CALL 1-800-Job-Show  
(1-800-362-7469)

We are not an employment agency. No registration required. All companies are direct, Equal Opportunity Employers. Candidates with FBI/SSBI clearances are encouraged to attend. U.S. Citizenship required for some positions.

## AT&T Bell Laboratories

AT&T Bell Laboratories has the following positions available in its Power Systems Division located in Mesquite, TX, a suburb of Dallas.

### Power Electronics Engineer

Design state-of-the-art electronic power products for use in telecommunication and data systems. You will design switchmode power supplies for both internal customers and the commercial OEM market. State-of-the-art circuit design skills are required along with experience in magnetics, thermal, packaging, EMC, safety agency issues, and strong analytical abilities. An MS or PhD in Electrical Engineering with 5 years of experience is required.

### Mechanical Engineer

This position involves the physical design and development of electronic PWB assemblies and associated sheetmetal and plastic enclosures. As a member of an interdisciplinary product team, your responsibility will include thermal design, chassis design and PWB layout design. The successful candidate will have a BSME with at least 3 years of experience. Familiarity with UL, CSA, and VDE safety agency requirements a plus.

### Ferroresonant Power Engineer

Engineering support of ferroresonant product for use in telecommunication systems. You will provide sustaining engineering support for power supply product in full-scale production with continuous quality improvement and technical consultation with customers. Circuit design skills are required along with experience in magnetics, packaging, EMI, Bellcore requirements and strong analytical abilities. BSEE with 5 years of experience required.

### Electrical Test Engineer

Factory test creation for manufactured products including software, fixturing and documentation. Work closely with designers, manufacturing, and customer to ensure product quality and provide feedback for continuous product and process improvement. Lead effort to improve test process in cooperation with other test engineers. Understand statistical basis for test limits and apply to achieve target on all test parameters.

Interest and experience in test development including fixturing, documentation and software. experience with BASIC, C, UNIX, DOS, IEEE-488/HP1B and GenRad test equipment desired. Familiarity with power equipment and development desired. BS or MS degree in Electrical Engineering required.

For consideration, please send your resume, indicating position of interest, to: AT&T Bell Laboratories, Human Resources, 3000 Skyline Drive, Mesquite, TX 75149.

An equal opportunity employer.



**AT&T**

The right choice.



# INTERNETWORKING INTEROPERABILITY INTERFACES INTERPHASE

INTERPHASE CORPORATION, a rapidly growing, publicly held manufacturer of networking and mass storage products for UNIX and real-time systems, is expanding to include ATM, Fibre Channel, SONET, and extended area networks. We are currently seeking:

## **PRODUCT MARKETING MANAGERS**

Product Marketing Responsibility for network products, including Ethernet, Token-Ring, FDDI and ATM. Will be responsible for product direction, marketing communications coordination and key customer support. Minimum 5 years related product marketing experience in a computer related field. BS required; BSEE, MBA desirable.

## **ASSOCIATE PRINCIPLE ENGINEERS**

Minimum 10 years board level hardware, software and/or firmware design background. Two years group lead experience. BSCS, BSEE or equivalent.

**ATTN: Human Resources**  
**Department E193**  
**13800 Senlac Drive**  
**Dallas, Texas 75234-8823**  
**FAX: (214) 919-9200**  
**NO AGENCIES PLEASE**



***INTERPHASE***  
**CORPORATION**

*An Equal Opportunity Employer*



# DIGITAL DESIGN ENGINEERS IN SAN DIEGO

At QUALCOMM, we provide elegant solutions to the problems labeled unsolvable by giants, ranging from satellite communication, HDTV and cellular systems. You can be an effective force in forming the future of communications using your system level design expertise in addition to your low level design capabilities.

QUALCOMM is a leading innovator in the development of Code Division Multiple Access (CDMA) digital communications technology which improves the capacity of existing analog cellular telephone systems by more than tenfold. We're applying CDMA to cellular telephony and personal communication networks.

Consisting of more than 900 innovative individuals, QUALCOMM is located two miles from the University of California, San Diego and one mile from the Torrey Pines State Reserve and beach. Along with a highly stimulating work environment, you'll also enjoy a competitive salary, a full range of company-paid benefits that begin on date of hire, plus genuine opportunity for growth with a highly respected entrepreneurial communications company.

Our continuing success has generated a need for additional talented individuals to join our rapidly expanding research and development team in San Diego.

## SYSTEM ARCHITECTS

We are looking for individuals with a deep knowledge of all facets of design and implementation of highly reliable digital systems. These individuals will define the architecture of large and complex wireless digital communication networks, then migrate to a leading role responsible for the lower level design, implementation and integration of major subsystems. A BSEE or equivalent and a minimum of 5 years experience also required.

## SENIOR LEVEL DESIGNERS

We are seeking independent thinkers capable of high speed, high/low volume, board level designs using the latest in componentary and tools. Designs range from 10 to 500 ICs including tens of FPGAs and custom ASICs to multiples of the latest microprocessors and DSPs. A BSEE or equivalent and a minimum of 3 years experience also required.


## SPECIALIZED DIGITAL DESIGNERS

We are looking for engineers with the following specialized expertise: low power/battery operated, high speed digital circuits; parallel processing; VERY high speed digital design; backplane designers. A BSEE or equivalent and design experience in one of these specialized areas are required.
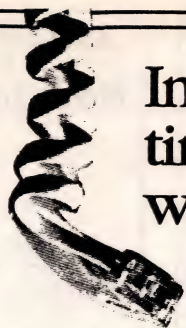
## DIGITAL SYSTEMS TEST ENGINEERS

We are seeking individuals versed with Testing and Reliability concepts. These individuals will develop functional test strategies and methods for complex digital systems and participate in all design phases.

Please send your resume by mail, fax or e-mail to: QUALCOMM, Attn: Human Resources, Dept. DS/EDN, 10555 Sorrento Valley Road, San Diego, CA 92121, FAX (619) 452-9096 or internet: jobops@qualcomm.com QUALCOMM is an Equal Opportunity Employer.



In these fast-paced times you don't want to be left hanging.

Yesterday's technology is — well, yesterday. And you want to put your name on advances in telecommunications you'll be reading about tomorrow.

PCSI has tomorrow's telecommunications headlines in the making. We're pioneering some of the most talked-about new technologies used in wireless computing and communications to make possible a new generation of personal and business products.

Founded in 1987, PCSI has grown with vision, energy, and success, enjoying sales growth averaging 100 percent per year. More than half of PCSI's employees are degreed engineers and computer scientists, and over half of them have advanced degrees. We're inviting additional individuals to apply the latest tools and techniques to product development that sets rather than follows the pace.

### Software Engineers

Senior, mid and junior level Designers/Implementers with experience in "C" and Assembler on DOS PC and/or embedded microprocessors for real-time applications. Experience with communications systems highly desirable. Minimum three years of experience.

### RF/Analog IC Design Engineers

Responsible for designing Wireless Digital Cellular Mixed Mode ASIC's. Minimum of 4 years Bipolar/CMOS/BiCMOS experience in the complete ASIC design process. Experience in the development of Synthesizers, Mixers, A/D's, D/A's, S/H's and Amplifiers. Knowledge of circuit design techniques in the frequency range from DC to 3 GHz, and top down design methodology using the latest in CAD tools. Experience designing for low power and low voltage highly desired, plus a record of successful design accomplishments.

### Design Verification Engineer

Responsible for system design verification of wired and wireless communications products for the portable computing market. Requires strong design and measurement background in voiceband wire-line modems and analog cellular voice implementations, including familiarity with EIA/TIA-496-A, 553, and IS-19-B standards. Experience with system-verification/engineering qualification plan and procedure development, as well as analog and RF measurement techniques, a plus. Seven years of experience.

### DSP Software Engineers

Mid-level Designer/Implementer experienced with the TMS320 processors. DSP functions and architecture, Assembly language and "C" a must. Voice processing experience highly desirable. Initial task to incorporate phone enhancement features into digital cellular telephone system.

PCSI enjoys a vigorous intellectual environment marked by collaboration, freedom and urgency. If this is the sort of environment that would bring out your best, send/fax or e-mail your resume, indicating position of interest, to: Professional Staffing, Pacific Communication Sciences, Inc., 10075 Barnes Canyon Road, San Diego, CA 92121. Fax: 619/535-9235. Internet Mailbox: careers@pcsi.com. As of February 1993, PCSI is a wholly-owned subsidiary of Cirrus Logic, Inc. of Fremont, California. Equal Opportunity Employer; Non-Smoking Environment.

**PCSI**  
The Clear Choice





## Schematic Capture for the Macintosh

### NEW DesignWorks™ 3.0!


Introducing a new generation of design tools for the Apple Macintosh. **DesignWorks 3.0 Schematic Features** Unlimited hierarchy • multi-level Undo/Redo • auto-packaging • spreadsheet-style attribute browser and much more. **Optional Digital Simulation Module** 13-state event driven simulation, fully interactive even on hierarchical designs • New interactive test vector panel **Schematic Libraries** New expanded libraries with over 13,000 parts, including all 74xx families, 75xx, 4000, ECL, processors, memories, etc. **Interfaces** Netlist outputs for SPICE, Douglas, McCAD, Cadnetix, OrCad, Tango, Rascal-Redac, etc. • Fully customizable reports

CALL (800) 444-9064 TODAY FOR YOUR FREE DEMONSTRATION KIT!

**CAPILANO COMPUTING**  
(604) 522-6200 Fax (604) 522-3972

CIRCLE NO. 263
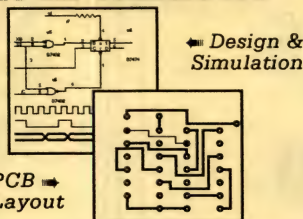
## Low Cost CAD Software for the IBM PC and Compatibles Now In Windows™



- ★ Easy to use schematic entry program for circuit diagrams (SuperCAD)—Only \$149.
- ★ Powerful, event-driven digital simulator (SuperSIM) starting at \$149.00. Includes models for TTL/CMOS parts.
- ★ Complete circuit board software package (Super PCB) including autorouter for only \$499. Handles multiple layers and surface mount. Printer and Gerber file output.

Write or call for free demo disks:


**MENTAL AUTOMATION, INC.**

5415 - 136th Place S.E.  
Bellevue, WA 98006  
(206) 641-2141



CIRCLE NO. 264

## SOIC TO DIP

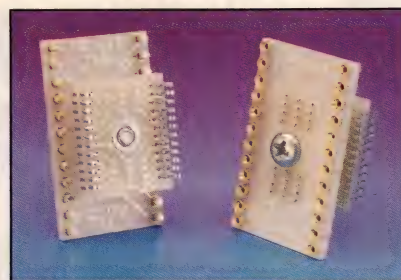


### WITH DIP/SOIC PACKAGE CONVERTER

- Convert surface mounted SOIC pattern to DIP.
- Solder to SOIC Land Pattern.
- Then plug DIP IC into DIP socket.
- DIP pins are gold plated machined pins.
- Recessed screw/nut for added strength
- Multiple sizes available

IRONWOOD ELECTRONICS  
P.O. BOX 21151, ST. PAUL, MN 55121  
(612) 431-7025; FAX (612) 432-8616  
CIRCLE NO. 265

The power of a consistent and colorful campaign can be yours with EDN's Product Mart Section.

### 48 Channel 50MHz Logic Analyzer

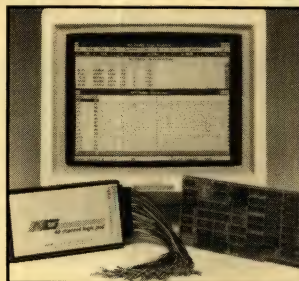

#### Complete System \$1895.00

New Windows 3.0 Compatible Software

- 48 Chnlns @ 50 MHz x 4K words deep
- 16 Trigger Words/16Level Trigger Sequence
- Storage and recall of traces/setups to disk
- Disassemblers available for: 68000, 8088, 8086, 6801, 6811, Z80, 8085, 6502, 6809, 6303, 8031

**NCI** 6438 UNIVERSITY DRIVE,  
HUNTSVILLE, AL 35806  
(205) 837-6667 FAX (205) 837-5221

CIRCLE NO. 267

### Device Programming Power!

#### PC-Based Universal System

- Supports PLDs, PALs, IFLs, FPLs, FPGAs, EPROMs, EEPROMs, Flash, Bipolar, CMOS, PROMs, Microcontrollers and more
- Universal PLCC socket for 20- to 84-pin devices
- Powerful editing facilities
- Fast data transfer over PC parallel port
- Self calibration and diagnostics
- One year warranty with free updates



Elan Model 6000-features latest pin driver technology to assure future device support.




**ELAN SYSTEMS, INC.**  
365 Woodview Ave.  
Morgan Hill, CA 95037

(800) 541-3526, FAX: (408) 778-2597

CALL NOW: 1-800-541-ELAN for your free device wall chart


CIRCLE NO. 268

### The ONLY Mixed-Signal Simulator

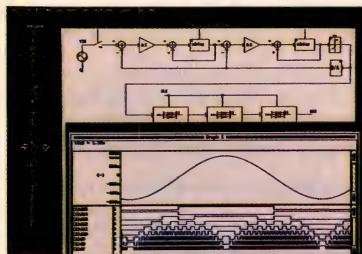
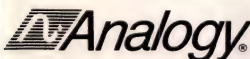
#### To Offer

- Native or Mixed-Simulator Options
- Concurrent IC and System Simulation
- MAST, Industry's de facto standard AHDL
- Largest Library of Parts
- Interfaces to Verilog-XL, CADAT, QuickSim II



**Analogy Inc.**  
P.O. Box 1669  
Beaverton, Oregon  
(503) 626-9700  
Fax (503) 643-3361

CIRCLE NO. 269

1802	6800	8041	COP400
3870	6801	8048	COP800
4004	6805	8051	SUPER8
6301	6809	8085	Z8
6502	68HC11	8096	Z80
64180	78C10	89700	MORE...

Cross-16 Meta-Assembler: US\$99 / CN\$119

XDASM Cross-Disassembler: US\$249/CN\$299

- Both MS-DOS products include support for ALL of the above processor families.
- EPROM emulators and Forth compilers too!
- Request our catalog.
- Credit cards are billed in Canadian dollars (CNS).
- Canadian residents please add 7% G.S.T.

#### Universal Cross-Assemblers

P.O. Box 6158  
Saint John, NB, Canada  
E2L 4R6  
Voice / Fax: (506) 847-0681



CIRCLE NO. 270

### FREE CATALOG



Affordable tools for programmable devices are just a phone call away.

- Unbeatable values on Data I/O® device programmers, software, updates, and accessories
- 30-day, money-back guarantee

Access to Data I/O's toll-free technical hotline and on-line bulletin board

To order your FREE catalog, call Data I/O Direct today.

**1-800-3-DataIO**  
(1-800-332-8246)


**DATA I/O**

CIRCLE NO. 271

To advertise in Product Mart, call Joanne Dorian, 212/463-6415



# SILVACO SmartSpice

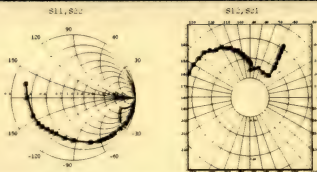

- Fastest, most accurate circuit simulator available
- Converges where ALL others don't
- Loaded with models and features
- Interactive with own schematic capture
- Cadence, Mentor, ViewLogic interface
- Comprehensive in-house Spice modeling service
- Very affordable for your DOS windows PC or UNIX workstation

SILVACO International  
4701 Patrick Henry Dr, #1, Santa Clara, CA 95054  
U.S. Ph: (408) 498-6000 Fax: (408) 498-6080  
Europe Ph: (49) 800-2120 Fax: (49) 800-2451

Make The Smart Move

CIRCLE NO. 254

## Universal Programmers

**SUPERPRO / EM \$399**

**SUPERPRO® \$549**

- Programs E(E)PROMs, Flash EPROMs to 8 Mbit, & Bipolar PROMs.
- Microcontrollers from INTEL, MOT, NSC, PIC, etc.
- PLD, GAL, MACH, MAX.... (not included in SUPERPRO / EM)
- Tests TTL/CMOS and Memory.
- New parts added upon customer request and free updates on BBS. (24 Hrs.)
- Online technical support & H/W warranty for 1 yr.

**ROM MASTER™ \$129**

- Universal E(E)PROM programmer to 4Mbit

**ROM MASTER/4 \$199**

- Universal E(E)PROM programmer 4 Gang Version

**XELTEK**

(408) 524-1929

757 N. Pastoria Avenue (408) 245-7084 FAX  
Sunnyvale, CA 94086 (408) 245 7082 BBS

CIRCLE NO. 257

## STAND-ALONE ALL-IN-ONE UNIVERSAL PROGRAMMER

LP-SU1 devices including EPROMs & EEPROMs, Flash EPROMs, Single Chip controller, PALs, GALs, EPLDs, PEELs, and IC test TTL, CMOS, DRAM, SRAM....etc.

- All-in-one design utilizes a single 40 pin socket
- The RAM buffer expand to 32 Mbits
- Can be operated from a PC using RS-232
- Dimensions: 240(L) x 176(W) x 65(H) mm




TAIPEI HSIEN RD.,  
SAN CHUNG CITY, TAIPEI HSIEN, TAIWAN, R.O.C.  
TEL: 886-2-9991860 FAX: 886-2-9990015

**LEAP ELECTRONIC CO., LTD.**

CIRCLE NO. 260

## WAVEFORM GENERATORS

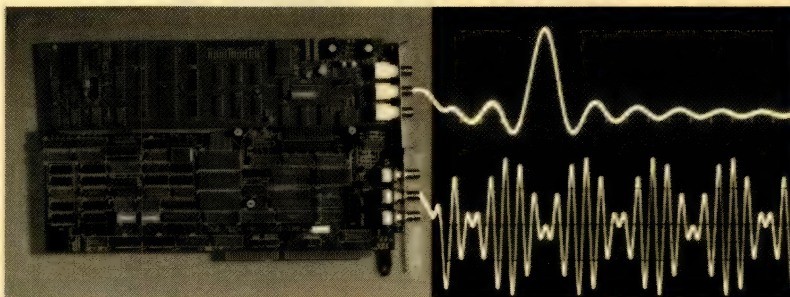

The WSB-10/WSB-100 Waveform Synthesizers provide generation of analog signals independent of the host computer, allowing full processor power to be used for other tasks, including calculation of waveform data. The WSB-10/WSB-100 is a useful laboratory tool used in reproduction or simulation of noise, audio signals, power line signals, and has many control applications.

Call for a free catalog  
**800-553-1170**

CIRCLE NO. 255

**QUATECH**

662 Wolf Ledges Pkwy-Akron, Ohio 44311

CIRCLE NO. 256


**8051/68HC11/Z80  
80C166\*/68000\*/683XX\***

**Integrated Debugging System**

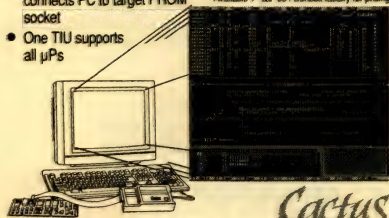**\$995 Includes:**

- Borland Turbo C like interface
- Multi-windowed editor
- Symbolic source or assembly debugging with 16K breakpoints
- CPU register, PSW, SFR memory, watch, output displays
- Target Interface Unit (TIU) connects PC to target PROM socket
- One TIU supports all  $\mu$ Ps
- Control program execution with Run, Stop, Run to Cursor, Reset, Step, Trace
- 128K ROM emulator built-in
- 8051, 68HC11 or Z80 target board included
- Supports many compilers

\*Available 1/2 or 1/3. Consult factory for pricing




180 North Vinedo Ave., Pasadena, CA 91107  
Tel: 800-847-1998 Fax: 818-796-6011

**Cactus**  
LOGIC

CIRCLE NO. 258
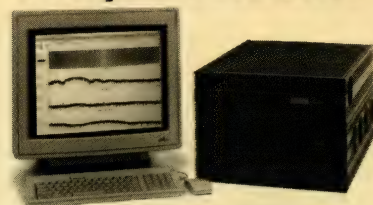
## Record, Playback, and Analyze at 500 MS/s



**With ESL's VP5000  
Signal Analysis System!**

- 32 to 256 MBytes real-time storage
- 200 MHz analog bandwidth
- Single and dual channel systems
- 10 KS/s to 500 MS/s digital I/O
- Embedded i860 processing and analysis
- Flexible acquisition and playback modes


High Throughput Solutions  
ESL, A Subsidiary of TRW  
495 Java Drive, P.O. Box 3510  
Sunnyvale, CA 94088-3510  
800.354.6195

**TRW**

CIRCLE NO. 259

A Single Module Solves Your Ethernet Connection Problem !

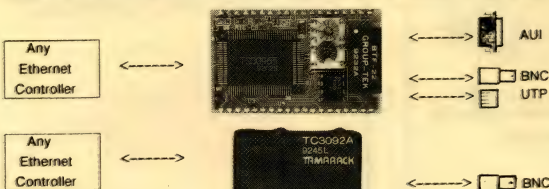No DC/DC Converters, No Pulse X'mers, No Mess-Ups, and No Procurement Problems !



**TC3095CT**

**ETHERNET 3-IN-1 TRANSCODER MODULE**

- \* Compatible with IEEE802.3 10BaseT/5/2
- \* Contains NS8391, NS8392, Pulse X'mer, DC/DC, AT&T 7220, & TP filter.
- \* Single +5V power supply. (No -9V required)
- \* Auto-detect/correct TP/Coax/AUI.
- \* Auto-polarity correction.
- \* Exceptional: Low power consumption(0.3W).

**TC3092A**

**ETHERNET COAX TRANSCIVER MODULE**

- \* Compatible with IEEE802.3 10Base5/2
- \* Contains NS8392, Pulse X'mer & DC/DC functions in one Hybrid module.
- \* Coax output short circuit protected.
- \* Single +5V power supply. (No -9V required)
- \* Exceptional: Low power consumption(0.3W).



**TAMARACK Microelectronics Inc.**

16F-4, No. 1, Fu-Hsing North Rd., Taipei, Taiwan, R.O.C.  
Fax: +886-2-776 0545 Telex: 17935 TAMARACK  
Tel: +886-2-772 7400

OEM &  
Agent Wanted !

Symbol of  
Excellence



IT'S VERY WELL  
MADE IN TAIWAN

The Only Electronic  
Component Awarded !

**CoBIT 93**  
HANNOVER  
24. - 31. 03. 1993

Hall 8 Booth #E01  
Tel/Fax: +49-511-89 504 55


CIRCLE NO. 261

CIRCLE NO. 262

To advertise in Product Mart, call Joanne Dorian, 212/463-6415



## ICE FOR THE 2105 DSP

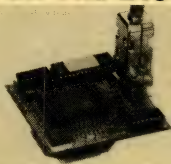

- Low cost in circuit emulator for the 2105 DSP comes with DOS user software.
- VGA color display allows viewing and editing target memory and registers.
- Pull-downs, menus, and soft keys are used in the mouse driven user interface.
- Your assembled files may be loaded, emulated, debugged, and printed with optional symbolic displays.
- Software breakpoints, step, trace, move, fill, and other functions are available.
- Designed for use in boot page mode.

Independent Digital Consulting, Inc.  
Box 1868, Akron, Ohio 44309  
Phone 216-753-0777 Fax 216-753-0772

CIRCLE NO. 245



### ADVIN versus DATA I/O

- **Data I/O and Model 2900:** reputable company, dependable equipment, supports 40-pins. Software updates: fair amount.
- **Advin and PILOT-U40:** reputable company, dependable equipment, supports 40-pins. Software updates: free via electronic BBS.

### ADVIN SYSTEMS INC.

Smaller Company, Better Service.  
800-627-2456, 408-243-7000, Fax 408-736-2503

CIRCLE NO. 246

Tatum CAE Software!  
from \$49 to \$4190

- ✓ **ECA-2** Analog Circuit Simulation
  - Interactive • Fast, Complete • Realtime Graphics
  - Interface to Mfr's Spice models • Expanded user function and conditions list • Model the unusual •
- ✓ **SpiceAge for Windows**
  - Analog Circuit Simulation • Thorough • Powerful
  - Easy to use • Loaded with helps • Super Plots •
- ✓ **GESECA** Schematic Graphic Entry
  - Emphasis on circuit design rather than PCB layout
  - Ideal front end for ECA-2 and SpiceAge • Libraries
  - Pleasure to use • Ports to Tango, Racal, etc. PCB
- ✓ **SAUNA** 3D Thermal Analysis
  - PCB's, heatsinks, enclosures, complex thermal designs • Menu driven • All modes: conduction, convection, radiation • Full thermal/mat'l's library
  - The 'must-have' software for the package designer
- ✓ **+ More!** CAE Software
  - Active filter synthesis, Logic ckt design, Tutorial, Curve fitting, and more • Call for demos/catalog •


**Tatum Labs, Inc.**  
1287 N. Silo Ridge Dr, Ann Arbor MI 48108  
Tel: 313 663-8810 Fax: 313 663-3640

CIRCLE NO. 247

The power of a  
*consistent*  
and *colorful*  
campaign can be  
yours with EDN's  
Product Mart  
Section.

CIRCLE NO. 248

## 8051 68HC11 COP8 68HC05

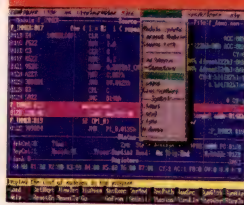

### iceMASTER Improved User Interface Features

- Easy to learn & use
- Windowed interface — user configurable
- FAST! Download — < 3 sec. typ. at 115KB
- Source level debug

- **A 4K frame trace buffer** with advanced searching capabilities.
- **iceMASTER** connects easily to your PC, requires no disassembly or expansion slots. Works on any PC (DOS or OS/2), MicroChannel or EISA. Even laptops!
- **Broad support of derivative devices.**
- **Rental and 10-day trials available.**
- **Now virtual memory and mouse support.**
- **Call today for free demo disk and ask about a free 8051 Macro Assembler! (800) 638-2423**




MetaLink Corporation P.O. Box 1329 Chandler, AZ 85244-1329  
Phone: (602) 926-0797 FAX: (602) 926-1170 TELEX: 499805METLIN

**NEW  
68HC05!**

CIRCLE NO. 249

## State Machine Design

For Complex & High Density PLDs

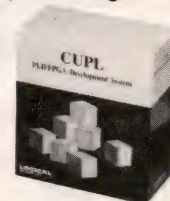


The most powerful PLD/FPGA CAE design software from \$495.00

**CUPL™ 4.2**

**1-800-331-7766 LOGICAL DEVICES, INC.**  
1-305-428-6868

CIRCLE NO. 250

## MEDICAL PC POWER SUPPLY

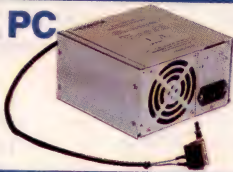


- 204-watt, medically approved, switching D.C. power supply
  - FCC Class B
  - 115/230 switch-selectable AC input
  - Fully enclosed with fan
  - UL544 certified (IEC 601 pending)
  - AC inlet
  - Flying lead AC on/off switch
  - Suitable for PC/AT, tower or file server
- Contact us today for complete information.



X-Med Systems Division of Condor D.C. Power Supplies, Inc.  
2311 Statham Parkway, Oxnard, CA 93033  
(805) 487-9465 • FAX (805) 487-9811

CIRCLE NO. 251

## Graphic Scientific Graphics

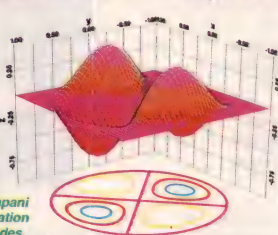

"All of the C language routines you need to write an impressive scientific graphing program of your own. Highly recommended."

PC Magazine 3/14/89

Windows ® and DOS versions now available.  
Licensed for personal use only.

### Scientific Endeavors

508 N. Kentucky Street, Kingston, TN 37763  
Orders: (800) 998-1571 FAX: (615) 376-1571

CIRCLE NO. 252

## Schematic Capture to Error Free PCB

**EZ-ROUTE Pro - \$995**  
**EZ-ROUTE Std - \$249**

EZ-ROUTE provides the most complete high performance solution for electronic design using personal computers. Available for DOS, WINDOWS, & SUN.

- 18,000+ Parts Library
- A through E sheet sizes
- DMD on both sides of board
- Netlist output comparable to: Futurusnet, PCAD, EDIF
- Output to penplotter, Gerber photoplotter & dot-matrix printer
- Design Rule Checker
- 256 board layers

For a **FREE** Evaluation call:  
**1-800-972-3733**

30 DAY NO-HASSLE MONEY BACK GUARANTEE


**ams** ADVANCED MICROCOMPUTER SYSTEMS, INC.  
1460 S.W. 3rd St., Suite B-8  
Pompano Beach, FL 33069  
(305) 784-0900 • FAX (305) 784-0904

CIRCLE NO. 253

To advertise in Product Mart, call Joanne Dorian, 212/463-6415



## 200Ms Digital Oscilloscope

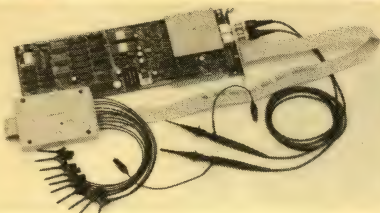

- 200 MSa/S Sampling Rate
- PC-BASED INSTRUMENT
- 2 Analog Channels
- 8 Digital Channels (8 Ch. Logic Analyzer)
- 100 MHz Analog Bandwidth
- 4K Samples/Channel (Analog & Digital)
- Powerful Software


\$1599 DSO-28100

\$1999 DSO-28200

Price is Complete  
Pods and Software  
included

## Universal Programmer

PAL EPROM FLASH  
GAL EEPROM MICRO

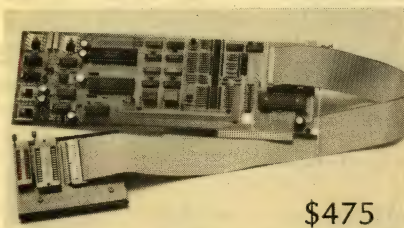


\$475

5ns PALs  
4 Meg EPROM (8 & 16 bit)  
22V10 & 26CV12 GALs  
Parts added at your request

Free software updates on BBS  
Powerful menu driven software

## 400 MHz Logic Analyzer

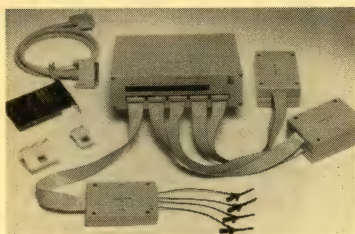

- Models Up To 128 Channels
- Models Up To 400 MHz
- Up To 16K Samples/Channel
- Variable Threshold Levels
- 8 External Clock Inputs
- 16 Level Sequential Triggering
- 100 MSa/s Pattern Generator (option)

\$799 LA12100 (100 MHz, 24 Ch)


\$1299 LA32200 (200 MHz, 32 Ch)

\$1899 LA32400 (400 MHz, 32 Ch)

Price is Complete  
Pods and Software  
included

**Call (201) 808-8990**  
**Link Computer Graphics, Inc.**  
369 Passaic Ave., # 100, Fairfield, NJ 07004 fax: 808-8786

CIRCLE NO. 242

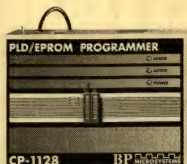

CP-1128

COMBINATION  
PROGRAMMER

\$1295.00

- PROGRAMS ALL AMD MACH EPLDs
- PROGRAMS ALL 22V10 PALs including BiCMOS PLDs
- SUPPORTS E/EPROMs UP TO 28 PINS
- SUPPORTS bipolar PROMs UP TO 28 PINS
- CALL 1-800-225-2102 FOR A LITERATURE PACK AND DEMO DISK
- LIFETIME FREE SOFTWARE UPDATES
- MANUFACTURER APPROVED
- MADE IN THE USA

**BP MICROSYSTEMS**

*The Engineer's Programmer™*

Houston, Texas 77043-3239 • (713) 461-9430 • (713) 461-7413

**1-800-225-2102**

CIRCLE NO. 237

## Programmable Power Supplies

3 Year  
Warranty



GPIB  
IEEE-488

... for the Price of Standard  
Linear Power Supplies

GPIB Interface Standard • Voltage/Current Programming and Readback via LCD Panel • Power-Off Memory • Voltage and Current Step-up/Step-down Function • Output Enable/Sisable • Superior Line/Load Regulation • Remote Sense Function • Programmable Overvoltage and Overcurrent Protection • Software Calibration • Voltage/Current Outputs Controllable with External Voltage (single output models only)

**American Reliance, Inc.**

9952 E. Baldwin Place, El Monte, CA 91731

(800) 654-9838 • Fax: (818) 575-0801

CIRCLE NO. 240

## A Complete Line of Development Boards, Programmers and In-Circuit Emulators



DS-51 - 8051 EMULATOR + TRACE + PROBE  
Supports 80C51/2/FA/FB, 8XC52/4, 8XC528, 8XC552, etc.

DB-51 CEIBO/SIGNETICS DEVELOPMENT BOARD  
Design board dedicated to Philips 80C51 family of  $\mu$ Cs.

MP-51  $\mu$ C, PLD AND EPROM PROGRAMMER  
Programs DIP, PLCC and QFP  $\mu$ Cs, Eeproms and PLDs.

DS-752 CEIBO/SIGNETICS EMULATOR  
Supports the 83C751/2 and 87C751/2 Philips/Signetics  $\mu$ Cs.

**CEIBO**

For more  
information,  
contact us today

1 BALLARD TERRACE LEXINGTON MA 02173

TEL: 617-863-9927 FAX: 617-863-9649

Ceibo Deutschland - Tel: 6151-9932-0 Fax: 6151-9932-99

Ceibo Israel - Tel: 972-52-555387 Fax: 972-52-553297

CIRCLE NO. 243

**80186  
Z180  
68HC16**



## In Circuit Emulators

✓ Source Level Debugger  
DOS & Windows!

✓ Real Time Trace

✓ Performance Analysis

✓ Memory Access Monitor

**Softaid**

**800-433-8812**

**(410)290-7760**

CIRCLE NO. 238

Now  
Networkable!

Facts about

**750,000**

**ICs and Semiconductors  
at Your Fingertips**

Cahners CAPS is the newest component search and selection tool for electronic design engineers:

- PC-driven, CD-ROM-based
- Includes unabridged manufacturers' technical documentation
- Represents more than 600 manufacturers worldwide


Call toll-free: 1-800-245-6696

CAHNER'S  
**CAPS**  
Computer Aided  
Product Selection

275 Washington Street  
Newton, MA 02158-1630  
Telephone: 508-692-4148  
Facsimile: 508-392-0603

CIRCLE NO. 241

**IMI**

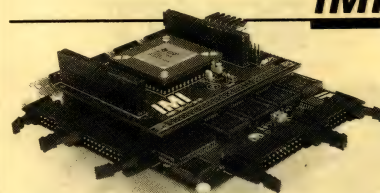

## EMBEDDED DSP

**MX31 Modular Embedded System**

TMS320C031 DSP: 32 bits, 33 Mflops • small footprint, low cost • comprehensive development tools

**I/O Daughterboards for:**

- signal processing • motion control • logic control
- image processing • data acquisition • prototyping

**Applications:**

- robotics • factory automation • vibration control
- automotive • industrial control • audio/speech

**INTEGRATED MOTIONS, INCORPORATED**

758 Gilman Street Berkeley, CA 94710

Tel: (510) 527-5810 Fax: (510) 527-7843

CIRCLE NO. 244

To advertise in Product Mart, call Joanne Dorian, 212/463-6415



# EDN PRODUCT MART

This advertising is for new and current products.

Please circle Reader Service number  
for additional information from manufacturers.

## EXPRESS

**Best Value in the World**  
Commercial & Milspec

**POLYIMIDE & FR4**  
**1 to 5 DAY TURN**  
1 to 12 Layers

PRINTED CIRCUIT PROTOTYPES


2 PIECE PRICES FOR FR4 .062 Th.

LAYERS	1	2	3&4	5&6	7&8
15	\$233	\$292	\$639	\$787	\$935
30	264	330	724	891	1059
60	311	389	853	1049	1137
90	358	448	980	1207	1434
120	385	486	1044	1311	1559

- 5 PIECES x 1.34
- 5 DAY PRICES ABOVE
- 10 PIECES x 1.67
- UL LISTED

### EXTRAS DISCOUNTS

- Photo Plotting
- Testing
- Gold Contacts - \$50
- 25% - Below 8 Mil/.020
- SMOBC & LPI - \$50

**10%**  **5%**  
COD CREDIT CARD SALES

FOR MORE INFORMATION CALL OR FAX

Ken Bahl

1108 W. Evelyn Ave., Sunnyvale, CA 94086

Phone (408) 735-7137 FAX (408) 735-1408 Modem (408) 735-9842

CIRCLE NO. 230

## DID YOU KNOW?

That to re-capture only *one* PCB design  
costs more than the price of an  
RSI-TRANSLATOR?

- Universal Netlist Translator \$ 395
- PCB-Translators for:
  - PADS, PCAD Redac, Tango, Protel and other. 995
  - Mentor, Cadence, other. 2,495

More than 150 DOS and UNIX Translators  
available.

For more information call  
(800) 766-1230



Router Solutions  
Incorporated

1800 Newport Center Drive  
Suite 180  
Newport Beach, CA 92660  
Tel.: (714) 721-1017  
Fax: (714) 721-1019

CIRCLE NO. 231

## OS-9 VMEbus Networking

Hardware and Software  
Solutions for:

- ARCnet
- Ethernet
- Tokenring
- Bitbus
- CAN
- RS-485

COMPCONTROL INC.


Phone (408) 356-3817

Fax (408) 356-1755

CIRCLE NO. 232

## ROM-IT™

EPROM EMULATION SYSTEM

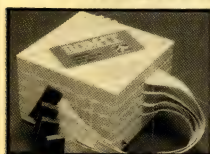

**The Most  
Flexible  
EPROM  
Emulator  
You Can Get  
Today!**

- Emulates up to 8 4-Megabit EPROMS through one standard serial port.
- Downloads 2-Megabit programs in less than 23 seconds.
- Allows you to examine and modify individual bytes or blocks.

- Accepts Intel Hex, Motorola S-Record and Binary files.
- Software available for IBM PC and compatibles.

- Base 27256 EPROM System \$395.00. Other configurations available.

ORDER TODAY—IT'S EASY  
CALL OR FAX FOR MORE INFORMATION



Incredible Technologies, Inc.  
(708) 870-7027  
(708) 870-0120 Fax  
Visa and MasterCard accepted.

CIRCLE NO. 233

## UNIVERSAL PROGRAMMERS & TESTERS

**FLEX-700 \$995**  
(CONNECTS VIA PRINTER PORT)

**TUP-400 \$745**  
**TUP-300 \$575**

- Program PLD (PAL, GAL, EPLD, PEEL, MAPL, MAX, MACH, ...) E (E) PROM (UP TO 16Mbit), BIPROM, SERIAL PROM, FLASH, MPU (87XX, 680XX, 68HC0XX, PIC16XX, TMS320XXX, Z8, PSD30X, HITACHI, NEC, ...)
- 40 pin DIP socket standard. Expandable to support PLCC, (T) SOP, SOIC, QFP, PGA, SIMM/ SIP, with up to 84 pins.
- Tests TTL74, CMOS 40/45, DRAM, and SRAM.
- Optional EPROM EMULATION capability.

## 8051 IN-CIRCUIT EMULATORS

**NICE-51 Systems from \$795**


- Support: 80(C)31/80(C)32 80C51FA/FB, 8344.80(C)51.80(C)52.80C851, 80C550.80C552.80C652/654...
- Features include: 128K emulation memory, symbol- and C source level debuggers, 16K deep and 48 bits wide real time trace recorder, pull down menu driven software, takes no space in user memory, I/O, interrupt, register, or stack.



Tribal Microsystems Inc.  
44308 S. GRIMMER BLVD. FREMONT, CA 94538  
TEL: (510) 623-8859  
FAX: (510) 623-9925

CIRCLE NO. 234

## NEW! Little PLC™ \$195

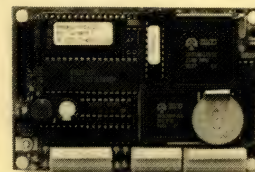

### Program It In C

Our new **Little PLC™** measures only 4.33 x 2.85 inches and can mount on standard DIN rail. This miniature controller costs only \$195, including 8 optically isolated inputs and 8 relay driver outputs. Low cost expansion cards allow you to add more inputs and outputs: digital and analog. It has dual RS-485 serial I/O, battery backed memory and time/date clock, programmable timers and a watchdog. Our easy to use and affordable **Dynamic C™** integrated development system also costs \$195. You can write simple programs in an hour, or you can develop major applications with 20,000 lines of C language.


### Z-World Engineering

1724 Picasso Ave., Davis, CA 95616  
(916) 757-3737 Fax: (916) 753-5141  
24 hr. Automatic Fax: (916) 753-0618  
(Call from your fax, request catalog #18)

CIRCLE NO. 235

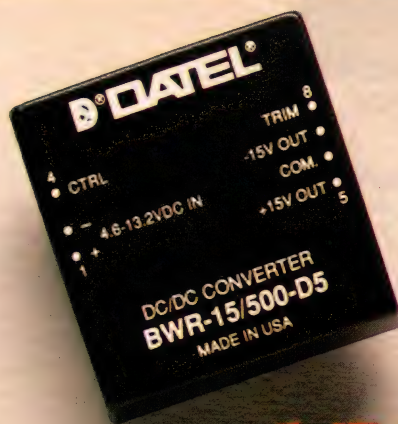To advertise in Product Mart, call Joanne Dorian, 212/463-6415






# XWR Series DC/DC Converters
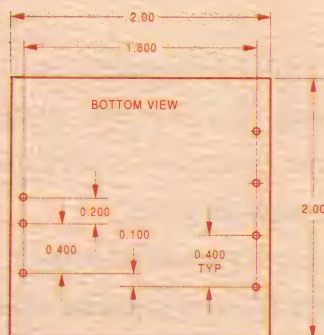
## 20Watt

DC/DC Converters  
Single/Dual/Triple  
34 New Models


- Inputs: 4.6-13.2V, 9-18V, 9-36V, 18-72V
- Typical Efficiencies to 84%+
- World's *ONLY* Wide Range 5V<sub>IN</sub>
- Extended Operating Temperature
- V<sub>OUT</sub> Adjustment Capability (TRIM)
- Insulated Case (will not short PC etch)
- TTL-compatible ON/OFF control
- Metal Case Shielding
- Single V<sub>OUT</sub>: 2.1, 3.3, 5, 12, 15V
- Dual V<sub>OUT</sub>:  $\pm 5$ ,  $\pm 9$ ,  $\pm 12$ ,  $\pm 15$ V
- Triple V<sub>OUT</sub>: 5,  $\pm 12$ V and 5,  $\pm 15$ V


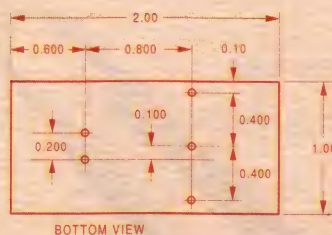
## 10Watt

DC/DC Converters  
Single/Dual/Triple  
25 New Models


- Inputs: 4.7-7V, 9-18V, 18-72V
- World's Smallest Commercial 10 W
- Lowest Profile: 0.37" tall
- Typical Efficiencies of 84%+
- Insulated Case (will not short PC etch)
- Metal Case Shielding
- World's *ONLY* Wide Range 5V<sub>IN</sub>
- Extended Operating Temperature
- Single V<sub>OUT</sub>: 3.3, 5, 12, 15V
- Dual V<sub>OUT</sub>:  $\pm 5$ ,  $\pm 12$ ,  $\pm 15$ V
- Triple V<sub>OUT</sub>: 5,  $\pm 12$ V and 5,  $\pm 15$ V


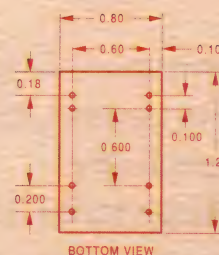
## 3 Watt

DC/DC Converters  
Single/Dual Output  
15 New Models

- Inputs: 4.5-9V, 9-18V, 18-72V
- Switching Frequency 200 KHz (typ)
- Black Plastic Case
- Pi-type Filter (L-type all -D48)
- Typical Efficiencies to 82%+
- Ideal for Telecomm/PCB applications
- Low Profile: 0.435" tall
- Excellent Line/Load Regulation
- 1000 Vdc Isolation (min)
- V<sub>OUT</sub>: 5, 12, 15,  $\pm 12$ ,  $\pm 15$



### General Specifications

- State-of-the-Art Thermal Management
- Continuous Short Circuit Protection
- Internal Input/Output filtering
- Overvoltage Protection
- 100% Burn-in @ Full Load
- Industry Standard Pinout & Packaging
- Very High Reliability
- Fully Encapsulated
- Delivery From Stock!



For complete data call or write today for a *free* new Power Supply catalog. DATEL, Inc., 11 Cabot Boulevard, Mansfield, MA 02048. Tel: (508)339-3000, FAX: (508)339-6356. For immediate assistance: all USA, EST business hours 1-800-233-2765.

**DATEL**  
INNOVATION and EXCELLENCE



JPEG coprocessor chip; it helps you develop application-specific designs based on the latest JPEG standard, DIS 10918-1. A development kit consists of a gate-level model, production test vectors, and behavioral model. The core is part of LSI Logic's CoreWare library. Price varies with the quantity of ASICs and the process technology used. **LSI Logic Corp.**, 1551 McCarthy Blvd, Milpitas, CA 95035. Phone (408) 433-8000.

Circle No. 462

**Image-browsing tool.** Kudo Image Browser handles cataloging, browsing, and retrieval of graphics files, scanned photos, Quicktime movies and Kodak Photo CD images. The tool is compatible with desktop publishing and multimedia packages such as Adobe Photoshop and Premier, Aldus Pagemaker, Quark XPress, and Macromedia Director. You can search using a scroll bar, a find command, or a riffle feature that displays images sequentially at about 10 frames/sec. For the Mac, \$295. **Impace Systems**, 4747 Morena Blvd, Suite 360, San Diego, CA 92117. Phone (800) 949-4555; (619) 272-2600, ext 4100; (619) 272-0593.

Circle No. 463

**User interface for analog simulation tools.** Easi (Environment for Analog Simulation) gives you one user interface to the maker's linear and nonlinear circuit-design tools called SuperCompact V3.0 and Microwave Harmonica V3.0. Using the X-Window system from MIT and the OSF-Motif standards, the interface simplifies entering and editing circuit netlists and using dialogue boxes to analyze, tune, and optimize your circuit. The software also helps you set up tabular and graphics plots of simulation data. For Sun, HP, and DEC workstations, US \$13,500 to \$23,700. **Compact Software Inc.**, 483 McLean Blvd, Paterson, NJ 07504. Phone (201) 881-1200.

Circle No. 464

**Tool for designing dc/dc converters.** SwitcherCAD lets you use a PC to design dc/dc converters based on the maker's switching regulator ICs. You input operating parameters such as input and output voltages, load current, output ripple, and isolation, and the program selects the appropriate circuit topology and offers a selection of ICs to implement it. The program also selects other components for the con-

verter such as input and output capacitors, inductor, diode and output filter, and calculates operating conditions for the selected components. The software lets you select either Experienced or Novice mode, depending on your background in power-supply design. \$20. **Linear Technology Corp.**, 1630 McCarthy Blvd, Milpitas, CA 95035. Phone (800) 637-5545; (408) 432-1900.

Circle No. 465

**Component information system.** The added features of CIS 1.1 to the previous version include a user-configurable interface for customizing search and results windows; enhanced integration with CAE tools for improved searches; operation with all features of military components; enhanced comparison of components; and better management of in-house data and documentation from third-party sources. CIS 1.1 runs in client-server mode on Unix workstations. \$50,000 to \$250,000, depending on number of authorized users. **Aspect Development Inc.**, 4410 El Camino Real, Suite 208, Los Altos, CA 94022. Phone (415) 941-2525. Fax (415) 941-9757.

Circle No. 466

## Perhaps there is something almost as reliable as our solid-state relays, after all.

AT&T's LH1500 family of Solid-State Relays offer more functionality for less money, while providing foolproof current limiting circuitry.


Reliably single-chip, our LH1500 devices ensure bounce-free operation, eliminate EMI, offer low power draw and enhanced surge protection.

Our LH1527/1537 (400V & 250V)

Relays are the first "true" Form C devices, with a single-

chip design that guarantees break-before-make operation.

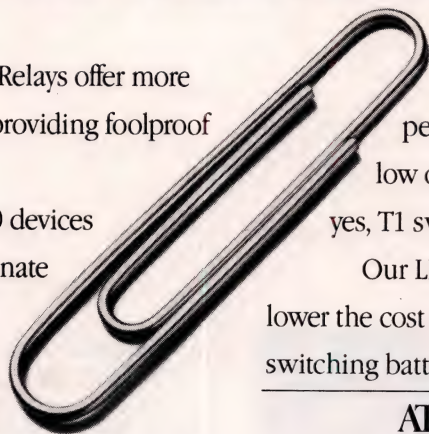The LH1571 is UL recognized, while the LH1514 and LH1527/1537 are UL recognized, CSA certified and BABT certified. (Shown actual size)




Our LH1514 Relay is the first to perform in high-frequency (up to 50 MHz) low on-resistance applications, proving that, yes, T1 switching can go solid-state.

Our LH1571 Protected Power Feed Relays lower the cost of providing UL safety protection while switching battery voltage to digital lines.

**AT&T Solid-State Relays.**  
**AT&T Reliable.**

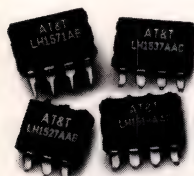For more about our state-of-the-art LH1500 family, just call AT&T Microelectronics 1 800 372-2447, ext. 912.





# Melts the Price of 8051 ICE



## Only \$851 for iceMASTER-PE

The world's most innovative emulator for members of the 8051 family is incredibly affordable. MetaLink's unique Advanced Emulation Technology (AET, patent pending) delivers the best possible emulator value for engineers, consultants and students.

AET is a revolutionary design architecture that provides more features with 75% fewer components, smaller board space and lower cost. Emulator and probe electronics are integrated in a single package only 3" by 4".

MetaLink also delivers leading-edge customer service, including a 30 day money back guarantee, 10 day trial for qualified customers, rental plans and free technical support.

- Up to 40 MHZ Operation
- 64K Emulation Code Memory
- 64K External Data Memory
- 128K Hardware Breakpoints
- 16K Trace Memory
- Transparent Trace (View Trace While Executing)
- Real Time & Nonintrusive
- Symbolic & Source-Level Debug
- Built-In Self-Test
- SUPPORTS 8031/8032'S
- SUPPORTS 8XC751/8XC752'S
- Windowed User Interface
- Serial Link to Any PC
- Macro Cross Assembler

**HOT NEW  
ICE!**

Call today for FREE DEMO DISK!

**(800) METAICE (800) 638-2423**


MetaLink Corporation P.O. Box 1329 Chandler, Az 85244-1329  
Phone: (602) 926-0797 FAX: (602) 926-1198



CIRCLE NO. 88
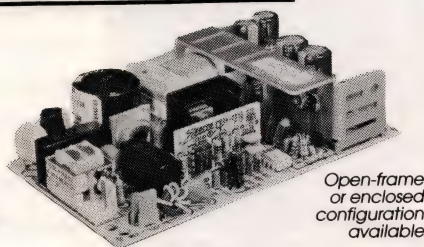
## ZENITH'S ZPS-30

**BIG 30 watt,  
universal input  
power supply in  
a small 3"x5" size**



Open-frame  
or enclosed  
configuration  
available

Zenith's small power supply is full of BIG surprises:

- Universal input with increased power density
- No minimum load requirements
- Automatically operates from any voltage between 90-265 VAC or 120-364 VDC
- Triple Output, + 5 and  $\pm$  12
- Single and dual output configurations also available
- UL, CSA, IEC and VDE/B approved
- UL 544 and IEC 601 applied for
- 1 year warranty from Zenith — a leading worldwide OEM supplier with over 70 years of electronics experience!

Zenith Model	Maximum Output Power (Watts)	Main Output		2nd Output		3rd Output	
		Volts DC (Nominal)	Amps (Min/Max)	Volts DC (Nominal)	Amps (Min/Max)	Volts DC (Nominal)	Amps (Min/Max)
ZPS-30	30	+ 5.0	0.0/3.0 PK 4.0	+ 12.0	0.0/2.0 PK 3.0	- 12.0	0.0/0.7

Inquire about our 45 watt, single, dual or triple output 3" x 5" power supply.

For more information call:  
**1-800-827-8720**

At Zenith, the quality goes in  
before the name goes on!®

**ZENITH**

**magnetics**

1000 Milwaukee Avenue  
Glenview, IL 60025-2493  
Fax: (708) 391-8569

U.S. and International Stocking Distributors

CIRCLE NO. 89

## EDN-NEW PRODUCTS

CAE & Software Development Tools

to assist with loading and testing CFI DR-compliant databases, and a development test for the DR-PI. Single-user license, \$6000; unlimited site license, \$30,000. **CAD Framework Initiative Inc.**, 4030 W Braker Lane, Suite 550, Austin, TX 78759. Phone (512) 338-3739. Fax (512) 338-3853. **Circle No. 458**

**Timing-driven crosstalk-analysis tool.** DF/Signal Integrity is a timing-driven crosstalk-analysis product for designers of multichip modules (MCMs) and pc boards. It does not assume, as other tools do, that adjacent signals switch simultaneously. The tool enhances the crosstalk-driven routing capabilities of Cadence's Allegro Physical Design System. It runs on Unix workstations from vendors that include DEC, HP, IBM, and Sun. \$21,000 to \$45,000, depending on configuration. **Cadence Design Systems Inc.**, 555 River Oaks Parkway, San Jose, CA 95134. Phone (408) 943-1234. Fax (408) 943-0513. **Circle No. 459**

**Real-time OS kernel.** Release 2.5 of the C Executive, a ROMable, multi-tasking OS kernel for real-time embedded systems, will run on 80386 and 80486  $\mu$ Ps. Control can pass from DOS to the C Executive, and from the C Executive to DOS, without rebooting. A standard PC can serve as a development system and a prototyping system. Price of the kernel depends on type and quantity of application. **JMI Software Consultants Inc.**, Box 481, 904 Sheble Lane, Spring House, PA 19477. Phone (215) 628-0840. Fax (215) 628-0353. **Circle No. 460**

**Image-development tools for Windows.** Glide, an image-analysis software-development package, includes a library of imaging functions plus prototyping and debugging tools. It lets you create prototypes, without programming, within a Windows application. It then generates C code to execute your prototype functions. The package includes Global Lab Image, an image-analysis application program, and a companion dynamic link library (DLL). \$3495. **Data Translation Inc.**, 100 Locke Dr, Marlboro, MA 01752. Phone (508) 481-3700. Fax (508) 481-8620. **Circle No. 461**

**JPEG image-compression ASIC core.** The CW702 JPEG image-compression core derives from LSI Logic's L64702



**PCB Design with TangoPRO™ for Windows® . . .**

# ***The Sky's the Limit***


All new TangoPRO, a premier line of PCB design tools developed for the engineering professional. Workstation-caliber performance and productivity on the PC plus Microsoft Windows' ease-of-use. TangoPRO integrates advanced PCB layout; fast, high-completion autorouting; and component library management. An outstanding tool for use on both digital and analog board designs.


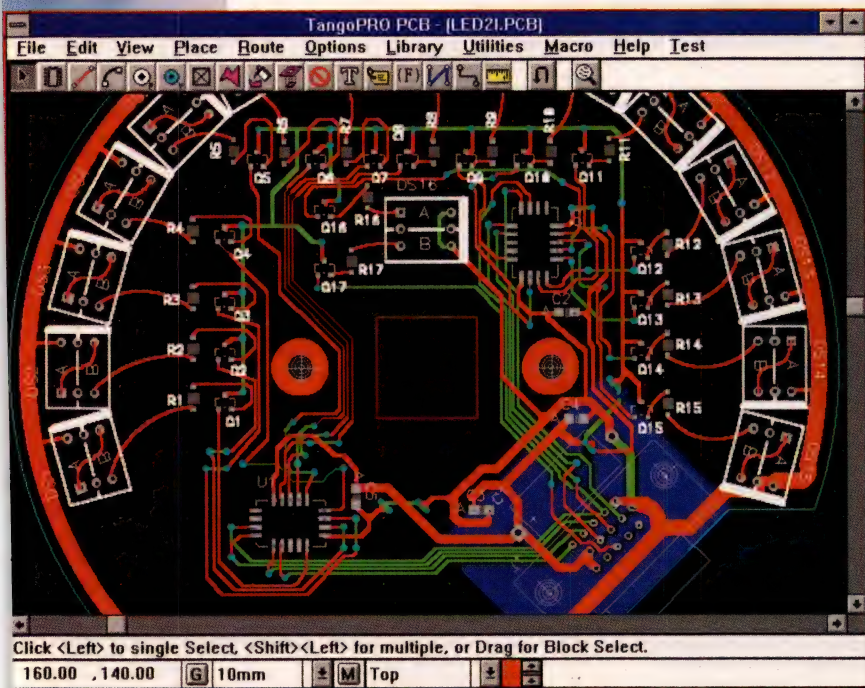
## ***Breeze Through Difficult PCB Designs with Powerful TangoPRO***

TangoPRO gives maximum flexibility, while making complex functions easy to use. TangoPRO highlights include:

- 32-bit architecture for optimum accuracy and performance plus unlimited components per design
- Sub-micron database with uniform and non-uniform grids down to .0001 inch or .01 mm
- Copper pour with backoff and "plowed" tracks
- Rotation of items down to .1 degree
- Pad stacks, blind/buried vias and curved tracks
- A world-class autorouter with unique "rip-up and reconstruct" algorithm for fast, 100% completion and manufacturable results



## ***See How TangoPRO Can Start Working for You***

Serious about printed circuit boards? TangoPRO provides solutions to your most complex design challenges. TangoPRO helps you create more polished and professional designs faster and easier than any other PCB tool set.

You'll see an immediate payback on your investment. And every Tango® product ships with the quality, service and support that have made ACCEL Technologies a leader in electronic design.

Find out for yourself why Tango is the fastest growing name in EDA. Call for a personal sales presentation or full-function evaluation package. TangoPRO for Windows or Tango for DOS – your choice for EDA solutions.

# ***Tango* PRO™**

**800 488-0680 for FREE EVAL**

ACCEL Technologies, Inc.  
6825 Flanders Drive  
San Diego, CA 92121-2986  
619/554-1000  
619/554-1019 Fax



# Uncommon sensor



The common sense choice for motion control is Novotechnik's **uncommon** sensor — the TR/TRS long-life position sensor.

The TR/TRS series features double bearing systems on both actuator shaft and spring, reducing side load errors and leading to independent linearities of up to 0.075%. Insensitive to shock and vibration, the sensor has a typical lifetime of  $100 \times 10^6$  operations with resolution better than 0.002mm.

The shaft of the TR/TRS is fitted with a special collar for use with automatic retraction systems; when fully retracted, the spring is completely protected by its DIN standard gauging head. The sensor is available with either a stress-relieved 3-conductor cable (TR) or plug-and-socket connection (TRS), and comes in four electrical stroke lengths: 25, 50, 75, and 100mm.

For Novotechnik's full line catalog of potentiometers, sensors and transducers, call or write:

**novotechnik**

Siedle Group

Novotechnik U.S. Inc.  
Transducers

237 Cedar Hill Street  
Marlborough, MA 01752  
Telephone: (508) 485-2244  
Fax: (508) 485-2430

CIRCLE NO. 86

## PCB MOUNTABLE 9V BATTERY HOLDER BH9V-PC

Mounts in any position  
battery always held securely in place.

Temp. range  
-40°C to +85°C

Resistant to most solvents

Male/female snap fastener terminals assures proper polarity.

Fits all 9V cells -alkaline, carbon zinc and carbon.

No need for snap-fit cables

Corner footpads

Nickel-plated spring steel PCB mountable contacts

Can be soldered on PCB

Space allows ease of flux solder wash

### For Memory Back-Up or Power Source

Use these handy BH9V-PC battery holders in microcomputer memory back-up systems, microprocessors, telecommunication equipment, etc.; or for power source in computer real time clocks, radios, smoke alarms and other appliances.


Black, high impact ABS plastic • Nickel-plated brass snap fastener terminals • Easy insertion and removal of batteries • Super efficient and economical • Custom holders available. • Now available with .110" quick fit/solder lugs.

For all the details, call or write today.



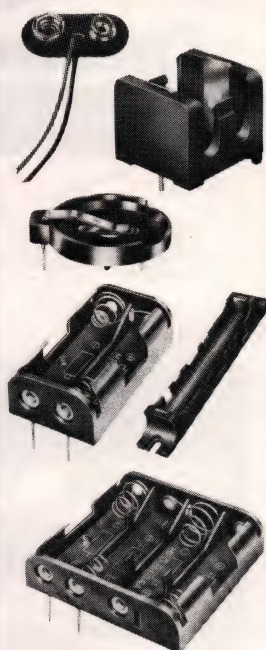**Memory Protection Devices Inc.™**

320 Broad Hollow Rd., Farmingdale, NY 11735  
(516) 293-5891 • FAX: (516) 752-1971



**A full range of  
battery products  
available from**



**Send for your  
free catalog today.**


## EDN-NEW PRODUCTS

CAE & Software Development Tools

### Equation editor for Windows.

Wiziword 3.0 is a WYSIWYG product that combines document processing, object-oriented drawing, plotting, equation editing, and both text and graphics filters. The equation editor is based on TeX, the markup language developed by Donald Knuth. The package is available for Windows, Macintosh computers, and most popular workstations. Windows version, \$595; Macintosh version, \$395; workstation versions, \$695.

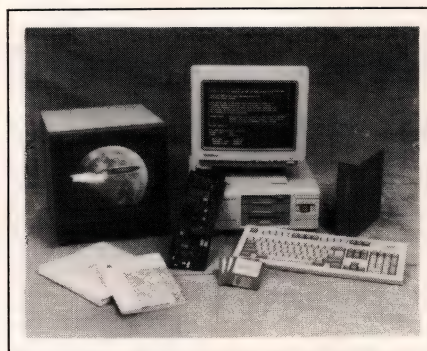**Microsystems Engineering Co.**, 2500 W Higgins Rd, Suite 950, Hoffman Estates, IL 60195. Phone (708) 882-0111. Fax (708) 882-8397. **Circle No. 456**



### Motion-picture file manager for OS/9, OS/9000.

The Motion Picture File Manager (MPFM) runs on OS/9 and OS/9000 and allows real-time playback of MPEG-encoded audio and video files. MPFM is available with video drivers for the Motorola MCD250 and the C-Cube CL450 MPEG video decoders. It is also available with audio drivers for the Motorola MCD260 and the Analog Devices ADSP2105 DSP chips. The software is compliant with the ISO 11172 standard. \$50,000. **Microware Systems Corp.**, 1900 NW 114th St, Des Moines, IA 50325. Phone (800) 475-9000. Fax (515) 224-1352. **Circle No. 457**

### CFI Design Representation toolkit.

The Design Representation (DR) 1.0 Toolkit provides a set of basic tools to assist understanding and using Release 1.0 of the CAD Framework Initiative's (CFI) Design Representation Standard. That standard provides an information model and a programming interface that an EDA tool or design database can use to share netlist information with other DR 1.0-compliant tools and design databases. The toolkit provides tools for developing and testing both applications tools and design databases. It contains a copy of the DR standard, an example implementation of the Design Representation Programming Interface (DR-PI), data for an example circuit, tools



## CAE & Software Development Tools

**COCOMO software cost-estimation tool.** Costar, an interactive tool for estimating the cost of software development, is based on the Constructive Cost Model (COCOMO) defined by Dr Barry Boehm in *Software Engineering Economics*. It produces estimates of a project's duration, staffing, and cost, so you can make trade offs and experiment with "what if" analyses to produce a project plan. You can use the tool during your project's definition phase to get early estimates and then produce more accurate forecasts as you refine your knowledge of the system you're developing. Versions are available for PC and VAX. Single copy, \$800; site license, \$3500. **Softstar Systems**, 28 Ponemah Rd, Amherst, NH 03031. Phone (603) 672-0987. **Circle No. 449**

**Signal-integrity tools.** The Aztec tools analyze signal integrity for ICs, MCMs, and pc boards. Different tools calculate parameters, simulate waveforms, and model ground planes. They run under X11R4 and OpenWindows on Sun workstations, and they are available with or without a Spice file generator. Individual tools from \$5000 to \$15,000; package, \$35,000. **Arizona Packaging Software Inc**, 1840 E River Rd, Suite 100, Tucson, AZ 85718. Phone (602) 577-8886. Fax (602) 577-0687. **Circle No. 450**

**Visual programming tools for Windows, NT.** New visual programming tools for Windows and Windows NT include the Visual C++ development system, the Delta version-control system, the Microsoft Developer Network (MSDN), and the Visual Control Pack. MSDN provides technical and strategic developer information; the Visual Control Pack is a collection of custom controls for the Visual C++ or the Visual Basic programming system. Visual C++, \$199 (standard version) and \$499 (professional version); Delta, \$499; MSDN, \$195 per year; Visual Control Pack, \$199. **Microsoft Corp**, 1 Microsoft Way, Redmond, WA 98052. Phone (206) 882-8080. **Circle No. 451**

**GUI tool and X-Base conversion tool.** GUI Assist helps you develop graphical user interfaces for OS/2 application programs, taking advantage of Microsoft's Visual Basic and Windows. In most cases, you can create Windows-like presentations for DOS programs without rewriting any of the original code. Another tool, X2c, lets you recom-

### FREE INFO, FREE POSTAGE

Use our postage-paid reader-service cards to get more information on any of these products.

pile X-Base application programs to C for OS/2. GUI Assist, \$125; X2c, \$995. **TSLI Inc**, Executive Court One, 2295 Corporate Blvd NW, Boca Raton, FL 33431. Phone (407) 994-4466. Fax (407) 994-6304. **Circle No. 452**

**Run-time error detection for C and C++.** Purify 2, for use with C and C++ on Unix systems, eliminates run-time memory-access errors and memory leaks. It includes an incremental linker and, for remote error reporting, a mail mode. The tool's features shorten build times and thus speed code testing. \$4000 per floating network license. **Pure Software Inc**, 1309 S Mary Ave, Sunnyvale, CA 94087. Phone (408) 720-1600. Fax (408) 720-9200. **Circle No. 453**



**VHDL libraries for ASICs.** Designers who use AT&T's 0.6- and 0.9- $\mu$ P CMOS cell libraries, with 3V and 5V options,

can now use Synopsys' VHDL System Simulator. The libraries have support for full timing and back-annotation, letting you specify and validate ASIC-based system designs and evaluate performance within the Synopsys design environment. The Synopsis simulator provides full support for IEEE-1076 VHDL. Price for library use depends on ASIC contract. **AT&T Microelectronics**, Dept AL-500404200, 555 Union Blvd, Allentown, PA 18103. Phone (800) 372-2447, ext 860; in Canada, (800) 553-2448, ext 860. Fax (215) 778-4106. **Circle No. 454**

**Data-acquisition and -analysis software for Windows.** Snap-Master 2.0 lets engineers and scientists acquire, display, analyze, and output data. It integrates sensors, transducers, and signal conditioning with a data-acquisition system. The new version includes support for Dynamic Data Exchange (DDE), zooming and panning for large files, multiple cursors, and event markers. \$1985. **HEM Data Corp**, 17336 Twelve Mile Rd, Southfield, MI 48076. Phone (313) 559-5607. Fax (313) 559-8008. **Circle No. 455**

## High Performance Thermal Line Printers
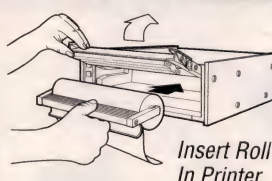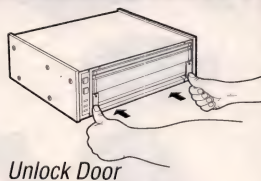
### LOAD PAPER WITHOUT THREADING OR ALIGNMENT



Printrex thermal line printers have an innovative paper handling system that allows the user to reload paper in seconds without any threading or alignment. The user simply inserts the paper carrier, closes the door and is ready to print.

The complete, integral paper handling system relieves the OEM of any need to design and fabricate any parts for paper handling.

Printing widths of 2 inches, 4 inches or 8 inches.

Printing speed up to 15 lines per second. 150 or 200 dots/inch.

# PRINTREX

2148 Bering Drive, San Jose, California 95131  
(408) 428-1877, Fax (408) 428-1899

CIRCLE NO. 85



# PICTURE YOURSELF BEHIND THE MOST POWERFUL SCHEMATIC SOFTWARE EVER.



## GET SCHEMAX™ FOR WINDOWS NOW AND SAVE \$250.

Introducing SCHEMAX - created by applying the philosophy of SCHEMA III, OMATION'S powerful schematic capture software to Windows, the most powerful software interface. The result offers you a universal schematic capture package that blows all other competitive programs away.

### SCHEMAX OUTPERFORMS OTHER SCHEMATIC CAPTURE PROGRAMS AND MAKES YOUR WORK EASIER WITH WINDOWS!

SCHEMAX offers you more than the ease and flexibility of a Windows interface. With SCHEMAX schematic capture you get more capabilities than with any other PC-based programs or workstations, with features like these:

- ▶ Autorouting signals around components
- ▶ Parts scaling
- ▶ Continuous zoom
- ▶ Combined parts select and browse
- ▶ Flexible regions - and more!

In addition, SCHEMAX lets you move your design to any PCB layout, PLD compiler or simulation program, as well as back annotate your ECOs from your competitive package to SCHEMAX. It's hard to picture a more powerful combination.

### TRY SCHEMAX FOR FREE! BUY SCHEMAX AND SAVE UP TO \$250.

Order your FREE demonstration disk from OMATION, and test drive SCHEMAX for Windows. Better yet, save \$250 off our already low \$595 price by trading your old schematic capture software - no matter what brand it is - when you buy new SCHEMAX from OMATION. Owners of SCHEMA schematic capture can upgrade to SCHEMAX for just \$149.

Any way you look at it, SCHEMAX for Windows is the most powerful schematic capture software ever. And at these rates, it's also the best value.

Call OMATION and order yours now!



OMATION, 801 PRESIDENTIAL DRIVE, RICHARDSON, TEXAS 75081

1-800-553-9119





2mm

# CONQUER SPACE WITH MICRO INTERCONNECTS

Arm yourself with Samtec  
2mm and .050" micro  
interconnects: the weapons you  
need to conquer surface mount  
and through-hole board  
space challenges.

Call 1-800-SAMTEC-9  
for our Space  
Wars Battle Kit,  
including new Full  
Line Solution Guide.



.050"


**samtec**



**IS SUDDEN SOLUTIONS**



## BLILEY CRYSTAL OSCILLATORS

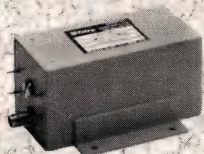

Our New NV15A is Small.  
It Has Good Frequency  
Stability and Phase Noise.

Look at the Specs.



Bliley Type NV15A OCXO	
Frequency:	5 MHz to 10 MHz
Frequency Stability:	$\pm 1 \times 10^{-8}$ 0°C to +50°C
Aging:	$5 \times 10^{-10}$ /day after 30 days
Output:	Sine Wave +13 dBm with 50 ohm load
Single Sideband Phase Noise:	10 Hz -125 dBc/Hz 100 Hz -145 dBc/Hz 1,000 Hz -150 dBc/Hz 100 KHz -150 dBc/Hz
Power Supply:	+12Vdc $\pm$ 10%
Size:	3.030" x 1.530" x 1.530"

See our new free catalog for details.

After all, we're the prime source for  
OCXO's, TCXO's, VCXO's, TCVCXO's and clocks.

BLILEY ELECTRIC COMPANY

**Bliley**

2545 West Grandview Blvd.  
P.O. Box 3428, Erie, PA 16508  
(814) 838-3571 • Fax: (814) 833-2712

CIRCLE NO. 81

## HIGH POWER FACTOR

Custom Switching Power Supplies  
for • Engineering work stations

- Computer main frames
- Computer peripheral equipment
- Business equipment
- Telecommunications
- etc.



- High power factor 0.99
- Design, manufacturing in Japan
- Repair center in U.S.A.

FDK also specializes in DC-DC converters, hybrid ICs, memory cards, ferrite cores, lithium batteries, stepper motors, optical isolators, etc.

**FDK** Your Best Strategic Partner  
**FDK AMERICA, INC.**

A Division of Fuji Electrochemical Co., Ltd.  
San Jose Office: 3099 North First Street, San Jose, CA 95134, U.S.A.  
TEL: 408-432-8331 FAX: 408-435-7478

Dallas TEL: 214-650-7742 FAX: 214-650-7792  
Boston TEL: 617-487-3198 FAX: 617-487-3199

CIRCLE NO. 82

Introducing Raltron's  
Surface Mount 32.768 KHz  
Tuning Fork Crystal.



**NEW!**  
**RSM-200**

Low profile  
Small plastic package  
Tape and reel  
High reliability

**Frequency:**  
32.768 KHz  
**Frequency Tolerance:**  
 $\pm 30$  ppm @ 25° C  
**Dimensions:**  
9.1mm length  
4.0mm width  
3.3mm height

**RALTRON**  
ELECTRONICS CORP.

2315 NW 107 AVENUE,  
MIAMI, FLORIDA 33172 U.S.A.  
FAX (305) 594-3973  
TELEX 441588 RALSEN  
(305) 593-6033

**ONLY RALTRON HAS IT ALL.**

Crystals / Crystal Oscillators  
Crystal Filters / Ceramic Resonators

CIRCLE NO. 83

## AMD 29K™ FAMILY SUPPORT

WITH AMD AND  
CORELIS

**RISC IS NO RISK!**

LOW-COST, NON-INTRUSIVE  
DEVELOPMENT TOOLS ARE  
AVAILABLE NOW FROM  
CORELIS FOR:

Am29000  
Am29050  
Am29030  
Am29200  
Am29205

**CORELIS TOOLS  
INCLUDE:**

- PRE-PROCESSORS FOR HP LOGIC ANALYZERS
- BOUNDARY SCAN EMULATORS
- COMPILERS, ASSEMBLERS, AND SOURCE-LEVEL DEBUGGERS

**CORELIS**

12607-H Hidden Creek Way  
Cerritos, California 90701

Tel: (310) 926-6727, Fax: (310) 404-6196

CIRCLE NO. 84



# CAPS<sup>®</sup> puts the whole world of PLD and FPGA devices in the palm of your hand for only \$495!



Since the beginning of time, people have been searching the world over to find ways to do things quicker, better, cheaper. Now, Cahners CAPS (Computer Aided Product Selection) introduces CAPS PLD, a CD-ROM-based database containing information on over 16,000 PLD and FPGA devices with more than 15,000 pages of technical documentation.

## KNOWLEDGE IS THE KEY TO SUCCESS


CAPS PLD takes the burden of researching PLD, complex PLD, and FPGA devices off your shoulders and puts knowledge into your hands. You receive a complete reference source of part numbers, parameters, alternate sourcing and technical documentation on one convenient CD-ROM disc all for the low cost of only \$495.\*

## SAVES TIME... INCREASES PRODUCTIVITY

CAPS PLD complements your PLD design tools by providing in-depth technical information and documentation from more than 40 of the leading PLD manufacturers to save you hours of research time. Now that's productivity!

\*Quarterly updates available for a nominal fee.

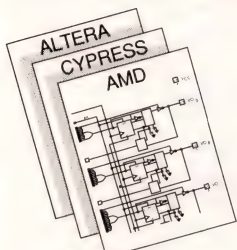*CAPS PLD™ ... A World of Knowledge in Your Hands*



CAPS PLD contains thousands of pages of Application Notes, Data Sheets and Technical Documentation

Available through:

**LOGICAL  
DEVICES, INC.**

Logical Devices, Inc.  
692 South Military Trail  
Deerfield Beach, FL 33442

CIRCLE NO. 103

CAHNERS  
**CAPS**  
Computer Aided  
Product Selection

Call 1-800-331-7766 ext. CAPS  
for your free demo disc



CAPS PLD Bundled  
with a Hitachi CD-ROM  
Drive for \$995.


EDN April 29, 1993 • 151



## Test & Measurement Instruments
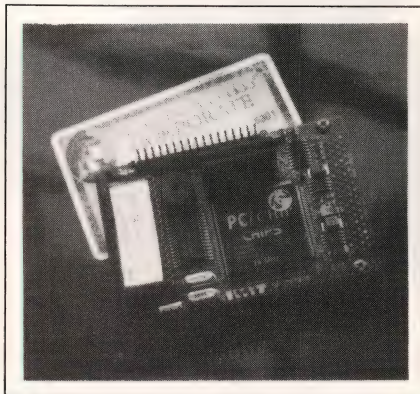
### 500M- to 2G-sample/sec DSOs.

Four new DSOs replace older members of the vendor's 54500 series. The new units have real-time sampling rates that range from 500M to 2G samples/sec, bandwidths from 125 to 500 MHz, two or four channels, prices from \$9500 to \$21,000, and delivery times from 6 to 16 weeks, ARO. Each scope features a 1.44-Mbyte MS-DOS-compatible floppy-disk drive and 32k points of memory per channel. The scopes trigger on 1-nsec glitches and perform FFTs. All units offer a sequential single-shot mode that allows segmentation of their memories into multiple records, enabling the storage of multiple events, even those that occur in rapid succession. A time-tag feature stores each event's time of occurrence. To prevent aliasing, the two 2G-sample/sec-max scopes offer a peak-detect mode in which they never take fewer than 1G samples/sec. To avoid overrunning their memories, the scopes store only the highest and lowest values acquired during the display interval and plot a vertical line between them. **Hewlett-Packard Co**, Box 58059, MS 51L-SJ, Santa Clara, CA 95051. Phone (800) 452-4844. **Circle No. 441**



**Credit-card-size data logger.** The GCAT2000/3000 card pair, which is based on the CT F8680 80386-compatible CPU, can boot from MS-DOS in ROM and drive a 640×200-pixel LCD or CRT. Each card measures 2.6×3.4 in. The unit includes a 6-channel, 13-bit ADC with 10-μsec conversion time. A FIFO memory stores series of ADC readings. Also included are floppy- and hard-disk controllers, a parallel port, two serial ports, a mouse port, a slot compatible with the Personal Computer Memory Card International Association standard, a clock/calendar, a negative-voltage generator for LCDs, 1 Mbyte of DRAM, and 512 kbytes of ROM. \$799. **Saelig Co**, 1193 Moseley Rd, Victor, NY 14564. Phone (716) 425-3753. Fax (716) 425-3835. **Circle No. 442**

### FREE INFO, FREE POSTAGE

Use our postage-paid reader-service cards to get more information on any of these products.

### 60- to 200-MHz, 2- and 4-channel analog scopes.

The TAS 400 series now includes true 4-channel units with 100- and 200-MHz bandwidth, in addition to the 2-channel 60- and 100-MHz units introduced last year. The new models (100-MHz, \$2395; 200-MHz, \$3495) offer user interfaces similar to those of the vendor's TDS series of DSOs. This similarity allows someone familiar with one series to immediately use scopes from the other. Although some competitive 4-channel scopes include only limited attenuators on two channels (so-called 2+2 models), these 4-channel units provide full attenuators on all channels. **Tektronix Inc**, Box 1520, Pittsfield, MA 01202. Phone (800) 426-2200. **Circle No. 443**

### Remote data-acquisition system.

Each DVT Series 50 unit has eight digital I/O lines and eight analog inputs. Each unit includes an RS-232C port, a printer port, and a modem. The intelligent modules can perform autocalibration, check inputs against limits, and provide alarm outputs. From less than \$500. **Dancer Communications Inc**, 114 Walnut St, Morton, PA 19070. Phone (215) 543-8066. Fax (215) 543-2151. **Circle No. 444**


### Dual-channel frequency synthesizers.

The PTS 620 provides two independent 1- to 620-MHz synthesizers in a single 5¼-in.-high, rack-mountable enclosure. The units, which you program by supplying parallel TTL, binary-coded-decimal inputs, provide 0.1-Hz resolution from 1 to 310 MHz and 0.2-Hz resolution above. In the decades from 100 kHz to 0.1 Hz, switching is phase continuous. The oven-controlled frequency standard is stable to 3 ppb/day and 1 ppm/year. \$12,725; delivery, 60 days, ARO. **Programmed Test Sources Inc**, Box 517, Littleton, MA 01460. Phone (508) 486-3008. Fax (508) 486-4495. **Circle No. 445**
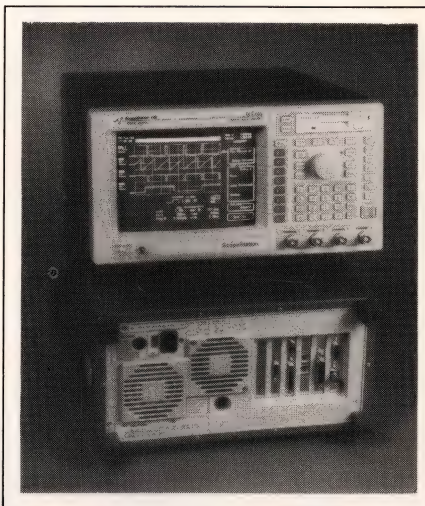
### 4-GHz-timing/1-GHz-state logic-analysis modules.

The 16515A, 16516A, 16517A, and 16518A are plug-in cards for the 16500A and B logic-analyzer mainframes. On eight channels per card, the plug-ins do timing analysis at 4G sample/sec and state analysis at

1G sample/sec. A mainframe accepts five cards, and you can add one expansion unit that accepts five more. Cutting the sampling rate in half doubles the number of channels per card. The master plug-in for state and timing analysis costs \$13,500; the slaves cost \$13,000 each. The master plug-in for timing analysis only costs \$9185; slaves cost \$8160 each. Delivery is 16 to 20 weeks, ARO. **Hewlett-Packard Co**, Box 58059, MS 51L-SJ, Santa Clara, CA 95051. Phone (800) 452-4844. **Circle No. 446**



### DSO with advanced communication capabilities.

The ScopeStation 140, a 100-MHz-bandwidth, 200M-sample/sec scope, can send faxes of waveforms. The 4-channel DSO features direct connection to Ethernet networks. To prevent aliasing, the scope—which includes a 3½-in. floppy-disk drive as well as RS-232C and Centronics ports—always digitizes at full speed. At lower sweep speeds, to avoid overrunning its 2k-sample per channel memory, it stores only the maximum and minimum values in each sampling interval and connects them on the screen with a solid vertical line. Less than \$5000. **LeCroy Corp**, 700 Chestnut Ridge Rd, Chestnut Ridge, NY 10977. Phone (914) 578-6035. Fax (914) 425-8967. **Circle No. 447**

### Programmer for PIC16C71 18-pin μP.

The \$144.95 Picquick programmer, which connects to the parallel port of an MS-DOS PC, programs both the EPROM and one-time-programmable versions of the low-cost microcontroller. The programming algorithm is the one suggested by the IC manufacturer. **Eltronics Ltd**, 704-33 Orchardview Blvd, Toronto, Ont Canada M4R 2E9. Phone (416) 483-7678. Fax (416) 483-2406. **Circle No. 448**



# Switching Power Delivers

LOW PROFILE 300-500-800 Watts COMPACT SIZES

- Universal Input
- Current Share
- Cost Effective
- Up to Five Outputs
- SELV Construction
- Up to 120 Amps
- Isolated Outputs
- EMI, VDE A / FCC A
- Soft Start
- Thermal Shutdown
- Fully Regulated
- Short Circuit Proof
- High Efficiency
- Power Good Signal
- 50° C. Full Power
- N+1 Parallelable
- Standard-proven Product
- System or SELF Cooling Option

## OFSX 500 SF

500 Watts

5" wide x 2.6" high x 11.75" long

5 VDC @ 75 Amps  
12 VDC @ 10 Amps  
2 VDC @ 20 Amps  
12 VDC @ 3 Amps

## OFSX 800 SF

800 Watts

5" wide x 2.6" high x 13.5" long


5 VDC @ 110 Amps  
12 VDC @ 20 Amps  
12 VDC @ 10 Amps  
24 VDC @ 5 Amps

## OFSX 300 SF

300 Watts

5" wide x 2.6" high x 8.5" long

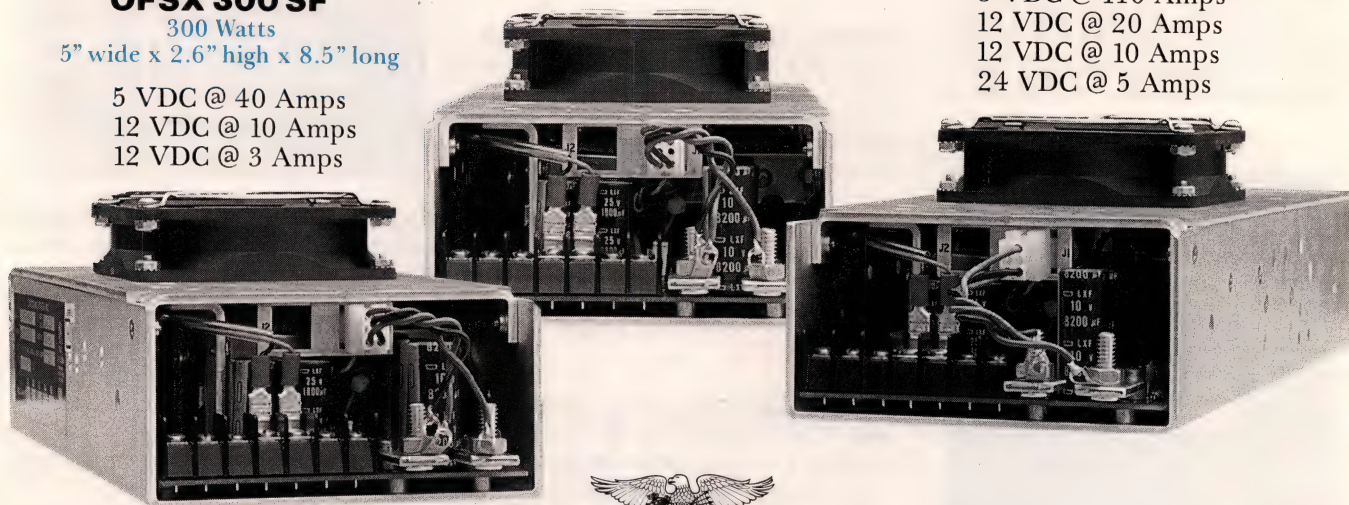5 VDC @ 40 Amps  
12 VDC @ 10 Amps  
12 VDC @ 3 Amps



★UL★CSA★TUV★BABT★

Telecommunications, Imaging, Medical and Computer Systems

*Call or write for our free Catalog-*

## Switching Power Inc.

3601 VETERANS HIGHWAY, RONKONKOMA, NEW YORK 11779

TEL. 516-981-7231, 1-800-456-8118

FAX 516-981-7266

SUNNYVALE, CALIFORNIA SALES OFFICE


TEL. 408-732-1230, FAX 408-732-5712

CIRCLE NO. 93

EDN April 29, 1993 • 147



## Computers & Peripherals

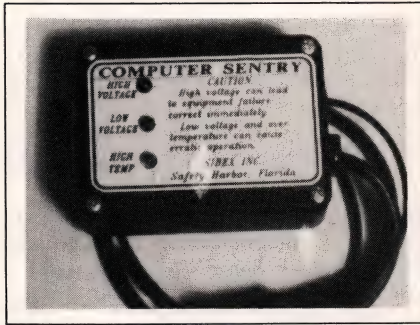

enclosure and does not require you to open the PC for installation. It connects in-line with the keyboard cable; a small temperature probe extends into the PC through any opening on the rear of the PC. \$49.95. **Sibex Inc.**, 1040 Harbor Lake Dr, Safety Harbor, FL 34695. Phone (813) 726-4343. **Circle No. 476**

**Rack-card short-range modem.** Model 1080RC 2U rack-card short-

range modem provides RS-232C data rates to 19.2 kbps over one or two unconditioned twisted pairs. The modem works with both software (X-On/X-Off) and hardware (RTS/CTS) handshaking and has built-in V.54 loopback test and V.52 bit-error-rate test. Transmissions as far as 10 mi are possible over #24 AWG twisted-pair wire. \$279. **Patton Electronics Co.**, 7958 Cessna Ave, Gaithersburg, MD 20879. Phone (301) 975-1000. Fax (301) 869-9293. **Circle No. 477**

**VME SCIM expansion board.** The VSIP 6U slave VME board accepts as many as four standard or custom modules that comply with specifications of the Standard Computer Interface Module (SCIM) bus. Modules for the open-architecture SCIM mezzanine bus provide analog and digital I/O, memory, graphics, and communications functions. Use of the modules reduces the board count of most VMEbus systems by at least one. \$450; SCIM modules, from \$120. **Arcom Control Systems Inc.**, 13510 S Oak St, Kansas City, MO 64145. **Circle No. 478**

**Image-processing modules.** The TIM-40 CFG frame grabber and the TIM-40 CD color-display boards adhere to the TIM-40 industry standard. The boards allow data transfers at 20 Mbytes/sec to other TIM-40 modules for distributed image processing. The products support the 3L Parallel C compiler and the Helios operating system. Each board uses a TMS320C40 parallel DSP chip. CFG, £4000; CD, £4500. **NEL**, East Kilbride, Glasgow G75 0QU, Scotland. Phone (44)(41) 607-272-4417. Fax (44)(41) 607-277-2200. **Circle No. 479**

**Industrial computer with SVGA.** The Model 8540-RV rack-mount industrial computer includes a 14-in. Super VGA monitor with a 13-in. diagonal viewing area. The unit's front panel conforms to NEMA specifications; a lockable door on the panel conceals controls and connectors for security. The unit measures 19 × 12.22 × 24 in. and includes a 250W power supply. \$3995. **Industrial Computer Source**, 10180 Scripps Ranch Blvd, San Diego, CA 92131. Phone (619) 271-9340. Fax (619) 271-9666. **Circle No. 480**



**(DSP)<sup>4</sup>=Quad 'C40**  
Any Way You Figure, Mizar's  
DSP Engine Is The Solution.

MIPS, MegaFLOPS, BOPS, bandwidth. They all indicate an aspect of DSP performance in one way or another. But when you consider what matters most, Mizar's MZ 7770 Quad 'C40 DSP Engine is the best solution for your embedded VME application.

Mizar, with its history of innovation in VME, has partnered with Texas Instruments, the leader in DSP technology, to bring this TI-designed product to the military and commercial markets.

The high throughput of the Quad 'C40 DSP Engine is achieved by four TI TMS320C40 DSP chips interconnected on a single VME card for a total of 200 MegaFLOPS. Coupled with this powerful architecture is a wealth of software tools like SPOX, C, OS/9, VxWorks

and Ada. And no other DSP board has TI's Network Operating System (NOS) for Ada multiprocessing applications. The MZ 7770 gives you a powerful DSP engine you can put to work now. That's what matters most.

Call today for more information on the MZ 7770 Quad 'C40 DSP Engine, on our 68K, SPARC and MIPS-based SBCs, or on any of our data acquisition and I/O products.

**1-800-635-0200**

**MIZAR**

**Your Source for Solutions**

2410 Luna Road  
Carrollton, TX 75006  
(214) 277-4600 (214) 277-4666 FAX


Mizar is a registered trademark of Mizar Digital Systems, Inc.  
Other names are trademarks of their respective manufacturers. ©1993 Mizar Digital Systems, Inc.



## Computers & Peripherals
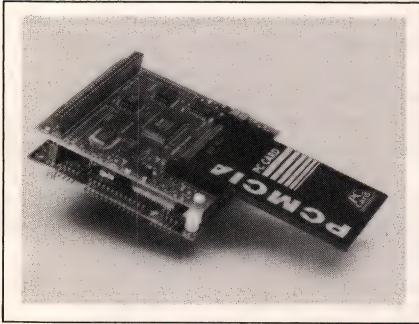
### FREE INFO, FREE POSTAGE

Use our postage-paid reader-service cards to get more information on any of these products.



#### PC/104-based PCMCIA card drive.

Card Drive P104, which operates in PC/104 embedded systems, reads and writes PCMCIA (Version 2.0) and JEIDA cards. It supports both I/O cards, such as fax/modems and LAN cards, and memory cards. Supported memory cards include SRAM and flash cards; flash technology support includes devices from AMD, Intel (Series 1 and Series 2), and Sundisk. The card drive stacks in a PC/104 configuration. The complete package includes the drive, device drivers, utility programs, and documentation. \$275 (1 to 9 units). **Adtron Corp.**, 3050 S Country Club Dr., Suite 24, Mesa, AZ 85210. Phone (602) 926-9324. Fax (602) 926-9359.

Circle No. 467

#### Self-refreshed DRAM cards.

Four new 88-pin JEIDA/JEDEC DRAM cards contain their own refresh circuitry, allowing you to shut down all system-refresh circuitry, including  $\mu$ Ps. Two cards hold 2 Mbytes of data ( $512k \times 32$  and  $512k \times 36$  bits); two other versions hold 4 Mbytes ( $1M \times 32$  and  $1M \times 36$ ). The cards require a single 5V supply and are available with access times of 70 and 80 nsec. The 80-nsec, 4-Mbyte card, \$240 (100). **Hitachi America Ltd.**, 2000 Sierra Point Pkwy, MS-080, Brisbane, CA 94005. Phone (800) 285-1601, ext 16; (415) 589-8300. Fax (415) 583-4207. Request literature package M16P009.

Circle No. 468

**Flat-panel terminal.** The INX5000T flat-panel display terminal provides monochrome VGA-compatible graphics on an 11.3-in. screen. It accepts either RS-232C or RS-485 input and includes ANSI 3.64 and VT100 terminal emulation. The unit is less than 2 in. deep and has a NEMA 4/12 front panel and a sealed 40-position membrane keypad. \$1295. **Ann Arbor Technologies Corp.**, Box 3083, Ann Arbor, MI 48106. Phone (313) 995-1360. Fax (313) 662-3707.

Circle No. 469

**JPEG evaluation board.** The JView board, designed around the manufacturer's JPEG processor IC, allows you to evaluate that chip and JPEG software-development tools. The PC/AT ISA card demonstrates multimedia functions for still images and live video. It records images to a hard disk and plays them back to a video window overlaid on standard VGA. Supplied software demonstrates full-motion video compression and decompression. \$3900, including application software. **LSI Logic Corp.**, 1551 McCarthy Blvd, Milpitas, CA 95035. Phone (408) 433-8000.

Circle No. 470

**PC-to-mainframe adapter.** The IRMA Pocket 3270 adapter connects portable and desktop PCs to mainframe 3270 computers. The device connects to a PC's parallel port and a 3270 controller via coaxial or twisted-pair cable. It comes with a power supply and software. \$695. **Digital Communications Associates Inc.**, 1000 Alderman Dr., Alpharetta, GA 30202. Phone (800) 348-3221. Fax (404) 442-4364.

Circle No. 471

**Printer servers.** Two Pocket Print Servers, models ESI-2848A and ESI-2831A, allow parallel-port printers to connect to Token Ring and TCP/IP Ethernet networks, respectively. Printers connect directly to the networks; chaining a printer to a file server or a workstation isn't necessary. The products use flash memory to store network software, so software upgrades will be easy. ESI-2848A, \$795; ESI-2831A, \$495. **Extended Systems**, 5777 N Meeker Ave, Boise, ID 83704. Phone (800) 235-7576; (406) 587-7575. Fax (208) 377-1906. In Europe, phone (49) 7034-27326. Fax (49) 7034-27364.

Circle No. 472


**VME RISC board.** The 38-10A VMEbus computer board includes a 40-MHz R3000 RISC processor, Ethernet and SCSI-2 interfaces, four serial ports, and as much as 16 Mbytes of DRAM. The RISC processor is an IDT 3081E  $\mu$ P, which includes an R3010 floating-point accelerator and 20 kbytes of configurable on-chip instruction- and data-cache memory. Board memory is a 32-bit-

wide, interleaved DRAM array that is closely coupled with the processor. \$4495. Delivery, eight weeks ARO. **Radstone Technology**, 20 Craig Rd, Montvale, NJ 07645. Phone (800) 368-2738. Fax (201) 391-2899.

Circle No. 473

**VME SCSI module.** The CXM-SCSI extends the control, address, and data lines of a VME board's  $\mu$ P and provides a SCSI connection on a VMEbus mezzanine. The module conforms to the public-domain Controller eXtension Connector specification. With its 3U form factor, it's about one-third the size of a full-height VME board. \$290. **PEP Modular Computers**, 750 Holiday Dr, Bldg 9, Pittsburgh, PA 15220. Phone (800) 228-1737; (412) 921-3322. Fax (412) 921-3356.

Circle No. 474

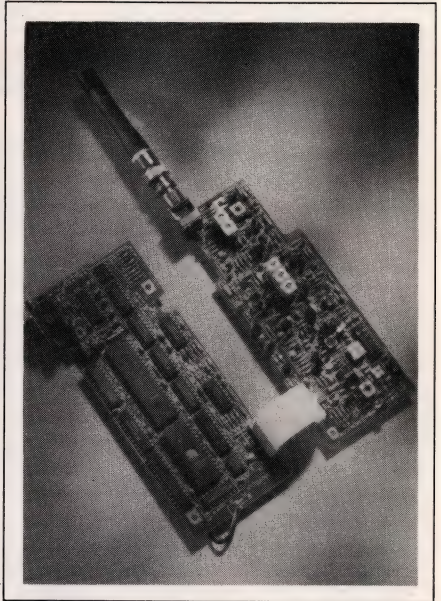


**Radio-modem board set.** The System 200 radio-modem board set for PCs communicates RS-232C data via FM signals between 450 and 470 MHz. One board is a transceiver, and the other is a modem. The base-station antenna is a quarter-wave whip; peripheral nodes use a heliflex. Transmission levels range from 1 mW to 2W; at 2W, line-of-sight connectivity is 2 mi or more. \$465 (1000). Delivery, 90 days ARO. **Moni-cor Electronic Corp.**, 2964 NW 60th St, Fort Lauderdale, FL 33309. Phone (305) 979-1907. Fax (305) 979-2611.

Circle No. 475

**PC-condition monitor.** Computer Sentry monitors voltages and temperature in a PC and warns against harmful conditions. The module mounts on the PC



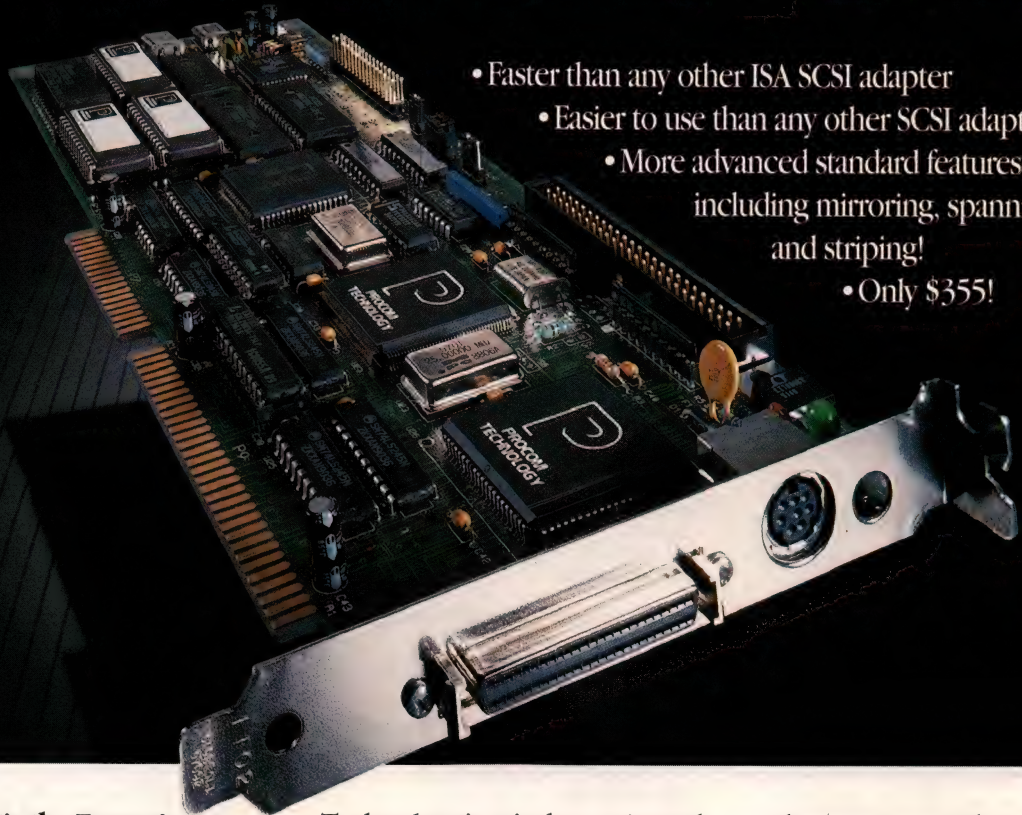
# ISA Xelerator.<sup>TM</sup> The New Standard For SCSI Host Adapters.



- Faster than any other ISA SCSI adapter
- Easier to use than any other SCSI adapter!
- More advanced standard features including mirroring, spanning and striping!
- Only \$355!
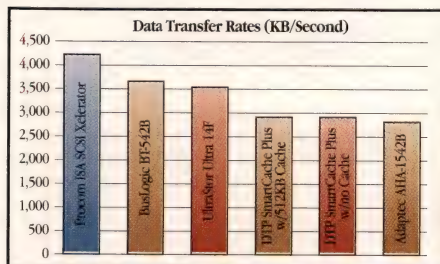
## It's the Fastest!

The Xelerator gives you a FAST SCSI-2, 10 megabytes per second data transfer rate. Our fast 16MHz processor reduces request processing time and you can fine tune the transfer rate to optimize the performance of CD-ROMs, DAT drives, MODs, scanners, removable media or any SCSI device.



## It's the Easiest to Use!

Configuring a disk system has always been a chore, but not with the Xelerator! With Procom

Technology's window-oriented setup and configuration screens, you'll be configured and ready to operate in minutes—not hours. Instead of 20 to 50 configuration jumpers, the Xelerator has five. Maintenance and re-configuration are just as simple. The Xelerator is easy enough for a beginner, yet still has the performance and features the advanced user needs.

## More Advanced Standard Features!

No other SCSI host adapter offers more standard features—**built-in disk mirroring, spanning and striping**, automatic configuration, 10-user power-on password security system, error logging and statistical data recording, programmable boot drive, disk and partition write protection to name just a few. And you can mirror, stripe and span all at

the same time with up to three levels of mirroring, striping and spanning.

But the best news is you can get the Xelerator at no more cost than ordinary SCSI host adapters—it retails for just \$355.

There's so much more we want to tell you about the Xelerator, including how you can get one. For more information, or the location of a dealer in your area, just call Procom Technology at 1-800-800-8600.



2181 Dupont Drive, Irvine, CA 92715  
714-852-1000; FAX: 714-852-1221  
International FAX: 714-261-7456



# In the race to market, we offer you a few shortcuts.



**If you need magnetics for your prototype, our Designers Kits can get you off and running fast!**

Each assortment puts a wide range of values right at your fingertips. So there's no need to waste hours calling around for samples or winding your own.

And when you're ready for production, you'll find we stock just about all the parts in our kits at low, factory-direct prices.

Call today and you can have your kit tomorrow! To order phone 800/322-2645.

## Surface Mount Kits

### 1008 Surface Mount Inductors

Inductance: 4.7 nH - 10  $\mu$ H  
42 values (10 of each) **Kit C100 \$125**

### 0805 Surface Mount Inductors

Inductance: 3.3 nH - 220 nH  
19 values (10 of each) **Kit C103 \$60**

### "Spring" Surface Mount Air Core Inductors

Inductance: 2.5 nH - 43 nH  
10 values (12 of each) **Kit C102 \$60**

## RF Inductor Kits

### "Unicoil" 7/10 mm Tuneable Inductors

Inductance: .0435  $\mu$ H - 1.5  $\mu$ H  
49 shielded, 49 unshielded (2 of each)  
**Kit M102 \$60**

### "Unicoil" 5 mm Tuneable Inductors

Inductance: 9 nH - 281 nH  
19 Shielded, 19 unshielded (2 of each)  
**Kit M105 \$60**

### "Slot Ten" 10 mm Tuneable Inductors

Inductance: 0.7  $\mu$ H - 1143  $\mu$ H  
18 shielded, 18 unshielded (3 of each)  
**Kit M100 \$60**

### "Slot Seven" 7 mm Tuneable Inductors

Inductance: 0.094  $\mu$ H - 275  $\mu$ H  
39 values (3 of each) **Kit M106 \$60**

### Axial Lead Chokes

Inductance: 0.1  $\mu$ H - 1000  $\mu$ H  
25 values (5 of each) **Kit F102 \$50**

### Horizontal Mount Inductors

Tuneable and fixed  
Inductance: 31.5 nH - 720 nH  
33 values (3 of each) **Kit M104 \$60**

## EMI/RFI Filter Kits

### Common Mode Data Line EMI Filters

Attenuation: 15 dBm, 1.5 - 300 MHz  
DC current capacity: 100 mA  
2, 3, 4, 8 line, surface mount and leaded (4 each)  
**Kit D103 \$75**

### Common Mode Line Chokes

Current: .25 - 9 Amps rms  
Inductance: 508  $\mu$ H - 10.5 mH  
8 styles (2 of each) **Kit P202 \$100**

## Power Magnetics Kits

### Current Sensors

Sensing range: 0.5 - 35 Amps  
Freq. resp.: 1 - 100 kHz, 50 - 400 kHz  
Transformer and sensor-only versions  
8 styles (15 total pieces) **Kit P203 \$50**

### Base/Gate Driver Transformers

Inductance: 1.5 mH Min. Freq: 10 - 250 kHz  
2 single, 2 double section (2 of each)  
**Kit P204 \$50**

### Mag Amp Toroids

Current: 1.5 Amps  
Volt-time product: 42 - 372 V -  $\mu$ sec  
6 styles (2 of each) **Kit P206 \$100**

### Power Filter Chokes

Current: 3, 5, 10 Amps Inductance: 5 - 300  $\mu$ H  
18 styles (48 total pieces) **Kit P205 \$75**

### Axial Lead Power Chokes

Current: .04 - 4.3 AC Amps  
Inductance: 3.9  $\mu$ H - 82  $\mu$ H  
30 values (2 of each) **Kit P209 \$150**

## Other Magnetics Kits

### Low Pass LC Filters

Poles: 3, 5 and 7 Cutoff frequency: 17 MHz  
Impedance: 50 Ohms  
3 filters (4 each) **Kit D102 \$60**


**Coilcraft**

**eem/electronic engineers master** See our catalog in Vol. A, Section 1800



connectors, or automatic-bus-grant connectors. \$1095 for a 21-slot unit with standard DIN connectors. **Hybricon Corp.**, 12 Willow Rd, Ayer, MA 01432. Phone (508) 772-5422. Fax (508) 772-2963. **Circle No. 435**

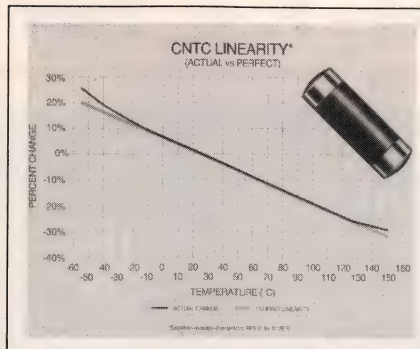**Thermistors.** The CNTC1/8 features a 1% max linearity deviation over a -10 to +130°C range. The cylindrical thick-film device is rated for 400 mW at 25°C and is available in resistance values of



500Ω to 10 kΩ. Resistance tolerance equals 2%; the negative temperature coefficient of resistance measures -2500 ppm/°C. The unit fits an industry-standard 1206 footprint for surface-mount applications. From \$0.65 (1000). **IRC Inc.**, 305 Greenway Rd, Boone, NC 28607. Phone (704) 264-8861. Fax (704) 264-8865. **Circle No. 436**

**Small-signal transistors.** The LT4217A and LT4239A small-signal transistors feature typical cutoff frequencies of 6 GHz, gain of 19 dB at 300 MHz, 2-dB noise figures at 300 MHz, and a maximum current rating of 400 mA. The 4217A is housed in a 0.28-in. stud package; the 4239A is housed in a conventional TO-39 package. LT4217A, \$7.30; LT4239A, \$2.70. **Motorola Inc.**, 5005 E McDowell Rd, Phoenix, AZ 85008. Phone (602) 244-3818. Fax (602) 244-4597. **Circle No. 437**

**Futurebus+ backplanes.** These Futurebus+ backplanes have an 8-layer design. The 14-slot units suit applications that involve 128 data bits, 64 address bits, and 80 I/O pins per slot. Features include a 52Ω impedance, active terminations, and 224A bus bars for 5V, 3.3V, and ground. From \$3000. **Electronic Solutions**, 6790 Flanders Dr, San Diego, CA 92121. Phone (800) 854-7086; (619) 452-9333. Fax (619) 452-9464. **Circle No. 438**

**Keyswitches.** ML Series keyswitches feature a full 3-mm travel and have a rated life of 10 million actuations min. The devices are supplied ready for pc-board mounting and require no special tooling. The single-pole NO units are rated for 12V and 10 mA max. Contact force measures 0.353 to 1.2324 oz. **Cherry Electrical Products**, 3600 Sunset Ave, Waukegan, IL 60087. Phone (708) 360-3599. **Circle No. 439**

**Touch screen.** The Quikpoint GX140 is a plug-and-play touch screen that snaps onto the front of any 13- or 14-in. monitor. The unit's controller card easily installs on the PC bus or it can reside in a stand-alone chassis that connects to the computer's serial port. The system has a 1024×1024 touch-point resolution and records a touch within 15 msec of finger contact. \$695. **Micro-touch Systems Inc.**, 55 Jonspin Rd, Wilmington, MA 01887. Phone (508) 694-9900. FAX (508) 694-9980. **Circle No. 440**

# ACT WORLDLY



## Our ISO9001 commitment gives you power supplies with international appeal.

With proven Megapower power systems, you also get the world-wide acceptance of quality earned by our pending ISO9001 certification.\* It's the measure of our total dedication to customer satisfaction, along with:

- ◆ Custom evaluation units fully agency approved in as little as a week.
- ◆ Power densities up to 8.5W/in<sup>3</sup>.
- ◆ Power conversion utilizing proven MHz zero current switching topology.
- ◆ Extensive manufacturing experience in high density MHz power systems.
- ◆ .99 active power factor correction available.

Call us today and find out more about Megapower's unsurpassed power densities and wide range of design options. We can quickly meet your new system requirements anywhere in the world. Phone: 408-370-8900 or FAX: 408-376-3672



1355 Dell Avenue, Campbell, CA 95008

\* Certification to ISO 9001 scheduled for Sept. 1993.



# Very Small, Very Fast, Very Smart



The Universe of high-performance, affordable, embedded system design expands with WinSystem's SBCs. Select 386/486 CPUs for standalone use. Or expand with the STD or PC/104 Bus. Unparalleled flexibility for space and budget-limited applications requiring PC performance and compatibility in harsh or remote environments.

Call or write for a *free* Catalog and Poster.

## **WinSystems®**

**THE EMBEDDED AUTHORITY™**

715 Stadium Drive • Arlington, Texas 76011 • Phone 817/274-7553 • FAX 817/548-1358



# EDN-NEW PRODUCTS

## Components & Power Supplies

The MJTP1230 through-hole version, \$0.094 (10,000). **MORS/ASC**, 134 Water St, Wakefield, MA 01880. Phone (617) 246-1007. Fax (617) 245-4531.

Circle No. 430

**DC/DC converters.** Series 1600 16W converters are available in 1-, 2-, and 3-output versions. All are approved to the latest revisions of UL 1950 and CSA 22.2. The 24 models in the series operate from 9 to 72V and output combina-



tions of 5, 12, 15,  $\pm 5$ ,  $\pm 12$ , or  $\pm 15$ V. I/O isolation equals 500V dc, and output accuracy measures  $\pm 1\%$ . All models include remote on-off control inputs and an input pi filter to reduce reflected ripple current. \$73.50 to \$87.50 (100). **Conversion Devices Inc.**, 15 Jonathan Dr, Brockton, MA 02401. Phone (508) 559-0880. Fax (508) 559-9288. Circle No. 431

**Rocker switches.** Series 8090 switches snap into 22 x 30-mm panel cutouts. The units are rated for 16A at 125V ac, 10A at 250V ac, and 16A at 28V dc. The devices are available in spst and dpst versions. The switches are UL recognized, CSA certified, and VDE approved. \$0.91 (1000). Delivery, 8 to 10 weeks ARO. **Eaton Corp.**, 4201 N 27th St, Milwaukee, WI 53216. Phone (414) 449-7483. Circle No. 432

**Coaxial attenuators.** LAV Series continuously variable coaxial attenuators span the dc to 800-MHz range and feature 0-to 20-dB attenuation. The units are available in 50 and 75 $\Omega$  versions. AV Series units are designed for narrow, octave, or multioctave service over the 0.95- to 26-GHz range. They feature 0-to 35-dB attenuation, 0.3-dB insertion loss, 1.3:1 VSWR, and 5W power ratings. From \$125. Delivery, stock to eight weeks ARO. **RLC Electronics Inc.**, 83 Radio Circle, Mount Kisco, NY 10549. Phone (914) 241-1334. Fax (914) 241-1753. Circle No. 433

**External power supplies.** TPES20, TPES40, and TPES60 Series universal-input supplies include 36 models with single, dual, and triple outputs. Power ratings range to 60W. All models have 2% load and 0.2% cross regulation on the main output. Cases have impact-resistant thermoplastic, which carries a 94V-1 UL rating and a 94V-0 CSA rating. Operating range spans 0 to 40°C. \$70 (100). Delivery, 8 to 10 weeks ARO. **Total Power International Inc.**, 418 Bridge St, Lowell, MA 01850. Phone (508) 453-7272. Fax (508) 453-7395. Circle No. 434

**VME-system backplanes.** HP Series 10-layer backplanes are designed for VME systems. Available in versions with 3 to 21 slots, the units feature a stripline construction. The units have in-board terminations, shrouds on all connectors, and several power options. The backplanes come with standard 3-row DIN connectors, enhanced DIN

## books that work the way you work

New edition!

### Operational Amplifiers, 2e

**Jiri Dostál, Research Institute for Mathematical Machines, Czechoslovakia**

This updated edition is an unusually practical and highly authoritative volume that examines design-philosophy, theory, practice, and the newest technologies.

April 1993 360pp. cloth 0 7506 9317 7 \$49.95 (£46.00)

Specific design examples of circuits!

### Radio Frequency Transistors: Principles and Practical Applications

**Norman E. Dye and Helge O. Granberg, Motorola**

Written by two experienced RF design engineers, this new book discusses the selection of solid state devices for specific applications.

January 1993 228pp. cloth 0 7506 9059 3 \$39.95 (£40.00)

Achieve acceptable EMC performance at minimal cost!

### EMC for Product Designers

**Tim Williams**

Electromagnetic compatibility is becoming increasingly important in the design of electronic products. In the absence of comprehensive U.S. standards, this book examines the European Commission's standards on EMC and, most importantly, outlines how EMC design principles need to be incorporated from the beginning to avoid cost and performance penalties.

1992 272 pp cloth 0 7506 9464 5 \$42.95 (£24.95)

### The EDN Series for Design Engineers

In the U.S.  
for more information  
or to place an order call  
**1-800-366-2665**  
M-F 8:30-4:30 E.T.  
Fax **617-438-1479**

In Europe, order from:  
Reed Book Services Ltd.  
Special Sales Department  
P.O. Box 5, Rushden  
Northants NN10 9YZ U.K.  
TEL. 0933 58521 FAX 0933 50284  
Please quote "Cahners 13.89"

**BUTTERWORTH-HEINEMANN**

80 Montvale Ave., Stoneham, MA 02180



SS089

CAHNERS 13.89



## Components & Power Supplies

### FREE INFO, FREE POSTAGE

Use our postage-paid reader-service cards to get more information on any of these products.

**Voltage dividers.** These 3-terminal dividers are available in gigohm values with ratios in the thousands and tolerances to 1%. Other specifications include a 10-ppm/°C temperature coefficient of resistance tracking, 0.1-ppm/°C voltage linearity, and 30,000V working voltage rating. Standard units are available in 100- and 1000-MΩ values. \$5.75 (100). **Ohmcraft**, 3800 Monroe Ave, Pittsford, NY 14534. Phone (716) 586-0823. Fax (716) 586-0015. **Circle No. 420**

**DC/DC converter.** The MHF+2805D converter outputs 15W from a 1.12×1.45×0.33-in. case—a 30W/in.<sup>3</sup> power density. The units develop a ±5V output from a 28V input. Line and load regulation equals 15 mV typ, and



input ripple is 25 mA p-p. Audio rejection equals 50 dB; efficiency ranges to 82%. Operating range spans -55 to +125°C. From \$353 (100). Delivery, eight weeks ARO. **Interpoint Corp.**, Box 97005, Redmond, WA 98073. Phone (206) 882-3100. Fax (206) 882-1990.

**Circle No. 421**

**Lightning suppressors.** The Model 29 single-stage DB-9 lightning suppressor comes in two versions: The 29 accommodates RS-232C levels, and the 29-1 works with RS-422 levels. The unit installs between the serial data cable and the DB-9 data port on a 386- or 486-based PC, laptop, or similar device. The unit employs avalanche diodes as suppression devices. Reaction time equals 2 nsec max. The 29-1 also accommodates EIA-530 interfaces and MIL-STD-188-114. \$44. **Telebyte Technology Inc.**, 270 E Pulaski Rd, Greenlawn, NY 11740. Phone (800) 835-3298; (516) 423-3232. Fax (516) 385-8184. **Circle No. 422**

**DIN connectors.** These 2-part connectors meet DIN 41612, VG 95324, and IEC 130/14 standards. The line includes a 48-position Form F unit rated for 4A that comes with or without polarization keys; 11- and 15-position Form H15

units rated for 15A; Form H15 devices with 7 or 10 contacts rated for 15A and 2 or 4 contacts rated at 50A; and mixed versions. \$3 to \$30. **Bicc-Vero Electronics Inc.**, 1000 Sherman Ave, Hamden, CT 06514. Phone (800) 242-2863. Fax (203) 287-0062. **Circle No. 423**

**Surge suppressors.** These devices can withstand a 24.5V jump-start for five minutes. The line includes three units—the 3J V18AUMLA1210, the 10J V18AUMLA1812, and the 25J V18AUMLA2220. All units have an 18V rating. V18AUMLA1210, \$0.41; V18AUMLA1812, \$0.70; V18AUMLA2220, \$1.15 (1000). **Harris Semiconductor**, Box 883, Melbourne, FL 32901. Phone (800) 442-7747. **Circle No. 424**


**Coaxial switches.** These failsafe coaxial switches are available in two lines: SS Series units, which operate over a dc to 18-GHz range, and HS Series devices, which have a dc to 12.4-GHz operating range. The spdt units switch in 20 msec. The SS units are available with SMA connectors. From \$215. **Alan Industries Inc.**, 745 Greenway Dr, Columbus, IN 47202. Phone (800) 423-5190. Fax (812) 372-5909. **Circle No. 425**

**DC/DC converters.** DC2-40 40W dual-output, open-frame converters operate from 36 to 72V inputs. The four models in the line output combinations of 5 and 12, 15, 24, or 25V. Key features include soft start, current limiting, short-circuit/overvoltage protection, and 3000V I/O isolation. The units include EMI/RFI suppression filters. \$40 (OEM qty). **Nidec/Power General**, 152 Will Dr, Canton, MA 02021. Phone (617) 828-6216. Fax (617) 828-3215. **Circle No. 426**

**LED pc-board mount.** The PCH 175 right-angle mount accommodates both bilead and trilead LEDs. The mount forms the bileads to meet conventional 0.1-in. pad spacings and forms the trileads in a triangular pattern, which staggers the leads for easier pc-board insertion. Its housing material carries a 94V-0 UL rating. \$0.04 (10,000). **Visual Communications Co Inc.**, 7920-G Arjons Dr, San Diego, CA 92126. Phone (619) 549-6900. **Circle No. 427**

**Trimmers.** G4S trimmer potentiometers are side-adjust, surface-mountable devices. Resistance values range from 10Ω to 2 MΩ, and tolerance equals ±20%. The 5×5.7×4.55-mm units are available in two versions: The A version has J-hook leads, and the B version has gull-wing terminals. Power rating equals 250 mW; operating range spans -55 to +125°C. The sealed devices are designed to accommodate flow and reflow soldering processes. \$1.06 (1000). Delivery, six to eight weeks ARO. **Tocos America**, 565 W Golf Rd, Arlington Heights, IL 60005. Phone (708) 364-7277. Fax (708) 364-7317. **Circle No. 428**

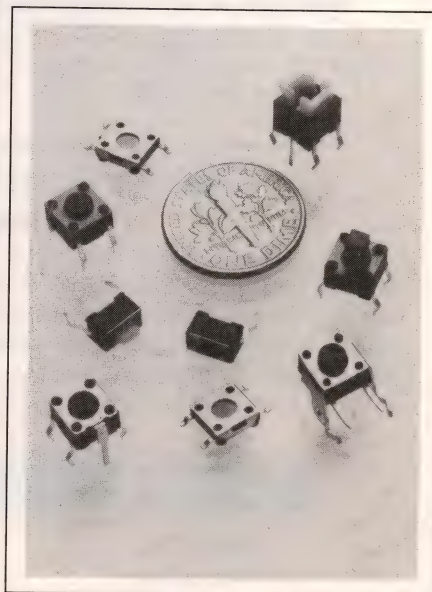**Linear power supply.** The Model 1.10.750's 10V output is suitable for driving transducer bridges. The 350-mA output can excite as many as 12 350Ω bridges. Line and load regulation equals ±0.1%, and noise and ripple figures measure 1 mV rms. Operating range spans -25 to +50°C. Versions operate from either 115 or 230V ac inputs. Foldback current limiting allows the units to be shorted indefinitely without damage. \$110. **Calex Mfg Co Inc.**, 2401 Stanwell Dr, Concord, CA 94520. Phone (800) 542-3355. Fax (510) 687-3333. **Circle No. 429**



**Miniature switches.** Series MJTP snap-dome miniature switches are available in through-hole and surface-mount versions. The single-pole, momentary-action units have contacts rated for 12V dc at 50 mA. Life is rated at 50,000 to 100,000 cycles. Various body styles have red, yellow, or green LEDs. The surface-mount units are compatible with most pick-and-place equipment.



# Our newest line of defense against heat.

DESC/QML QUALIFIED  
SMD MODELS AVAILABLE



MHF+ Series: 15 W, 125° C.

MHD Series: 20 W, 125° C.

MTR Series: 30 W, 125° C.

MFL Series: 65–200 W, 125° C.

## Insist on Interpoint.

### A full line of high-temperature DC-DC converters from the industry leader.

Get the hottest technology in board-mounted power supplies. Full military temperature range. Unsurpassed reliability. The lowest profiles. You can get it all with Interpoint's new line of DC-DC converters.

From arctic blasts to desert storms, Interpoint's new generation DC-DC converters stand up to the toughest military environments. They deliver full power over the entire -55° to +125° C. temperature range. And over an unprecedented power range, too. Interpoint can now offer you an off-the-shelf hybrid power supply for any power level from 2 to 285 watts.

For more than a decade, Interpoint DC-DC converters have proven their reliability in many of the world's most


MSA Series: 5 W, 125° C.

Interpoint's new line of DC-DC converters features constant PWM switching frequencies from 500 to 700kHz. Built-in sync. Parallel operation. Up to 50 dB audio rejection. Line and load regulation as low as 0.1%. And full MIL-STD-704 input for 28- and 270-volt systems.

advanced weapons systems — including mission-critical electronics on the Leopard II Tank and Harrier Aircraft, the Bradley Fighting Vehicle and F/A-18 aircraft. Our new generation converters are the most reliable yet. Each of them was designed with the specific intent of being qualified to the full performance and reliability standards of MIL-STD-883.

And Interpoint continues to lead the way in power supply miniaturization. With power densities as high as 70 watts per cubic inch and package heights as low as 6.8 mm, this new generation of converters is built for the tightly packed boards in today's military and commercial avionics, ground vehicles and portable equipment.

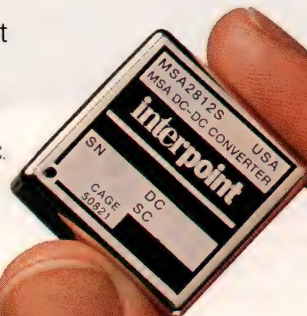It's the hottest new technology in DC-DC converters. And it's available only from Interpoint. For more information, call 44 (0) -276-26832.



CIRCLE NO. 67

## interpoint

10301 Willows Road P.O. Box 97005  
Redmond, WA 98073-9705



## EDN-NEW PRODUCTS

### Integrated Circuits

ceive side. The chips are pin-compatible with Crystal Semiconductor's CS61535A and CS61574A devices. Applications include DSX-1 cross-connect switches, line interfaces for PCM multiplexers, digital switches, data service units, and channel service units. \$9.70 (10,000). **VLSI Technology Inc.**, 8375 S River Pkwy, Tempe, AZ 85284. Phone (602) 752-8574. Fax (602) 752-6000.

Circle No. 415

**10-bit RAM-DACs.** Combining three 10-bit video RAM-DACs and a color-palette RAM in one package, ADV7150 family chips can simultaneously display 16.7 million colors. Features of the 170-MHz devices include 24-bit true color and 30-bit gamma-corrected operation. \$83 to \$148 (1000). **Analog Devices Inc.**, 181 Ballardvale St, Wilmington, MA 01887. Phone (617) 937-1428. Fax (617) 821-4273.

Circle No. 416

**FPGA.** The QL8x12A is a faster and less-expensive version of the QL8x12 FPGA. The 1000-gate device reduces

the internal logic-cell delay from 3.4 to 2.4 nsec; an optimized layout reduces the die size by 20%. A dedicated clock network has a clock skew of 500 psec across the chip. The FPGA is available in a 100-pin, 1.4-mm-high quad flatpack for use in PCMCIA cards. The QL8-



12A-2PL68C costs \$37.60 (1000). **Quicklogic Corp.**, 2933 Bunker Hill Lane, Santa Clara, CA 95054. Phone (408) 987-2000. FAX (408) 987-2012.

Circle No. 417

**SCSI bus terminator.** The TL2218-285 active SCSI-bus current-mode terminator is compatible with the 27 channels of the proposed Fast SCSI III standard.


The device terminates nine SCSI lines. The terminator is also compatible with active negation drivers, which are often used in high-speed SCSI systems. Besides operating in wide and fast SCSI III systems, the device can be used for single-ended active SCSI terminations. The output capacitance is 6 pF. \$1.75 (1000). **Texas Instruments Inc.**, Semiconductor Group, Literature Response Center, Box 17222, Denver, CO 80217. Phone (800) 477-8924, ext 3437.

Circle No. 418

**Multichip modules.** The MMS-D300 series multichip modules come in small form factors. The modules operate at 10 MHz to 1 GHz. Features include die attachment using wirebond process, silicon-to-package area ratios of 40% to 80%, and a direct thermal path from silicon to a heat sink. Packaging options include QFPs, PLCCs, and thin QFPs conforming to JEDEC standards. Packages are as thin as 1.2 mm. Typical modules house between 2 and 10 CMOS ICs in die form. \$10 to \$50 (10,000). **Micro-module Systems Inc.**, 10500 Ridgeview Ct, Cupertino, CA 95014. Phone (408) 864-7437.

Circle No. 419
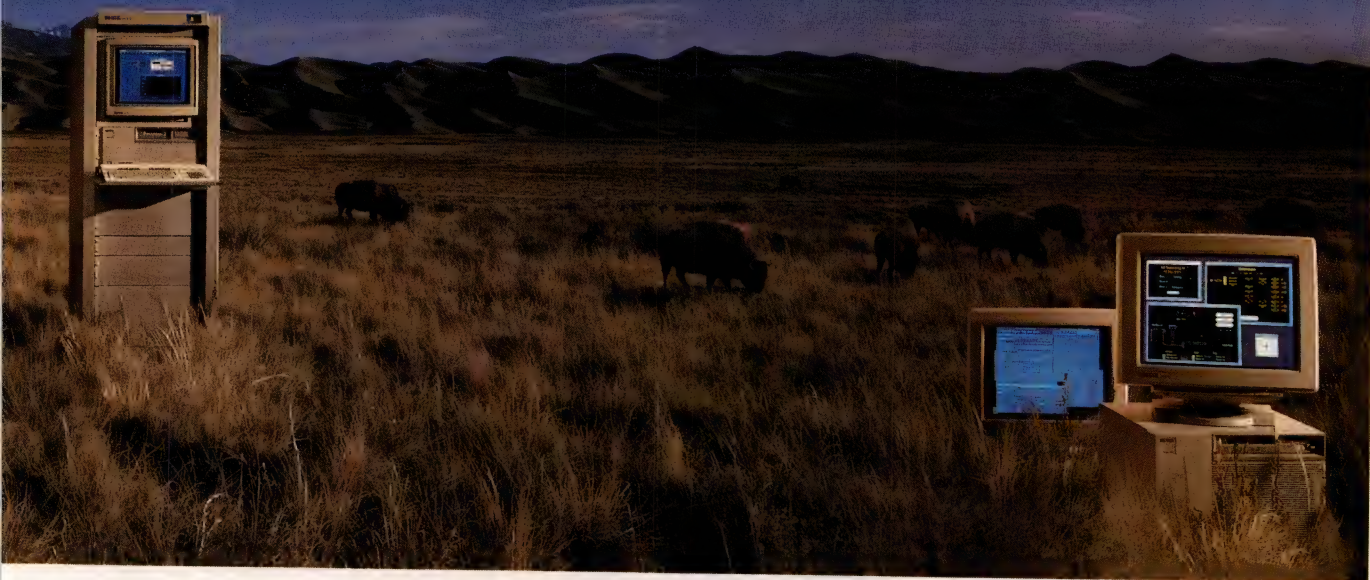
## Real-time industrial computer systems.



From factory floor to data center, HP has over 18,000 other products, ranging from board computers to instruments and computer systems. We also offer OEM and special support

services, with 10-year product support.

Call 1-800-729-8634, Ext. 783B for a free demonstration video and more information. It'll make your future look wide open.



**HEWLETT  
PACKARD**

UNIX is a registered trademark of UNIX System Laboratories Inc. in the U.S.A. and other countries. \*Based on 1992 UNIX revenue, UNIXWORLD Annual Report, 1992. Extended service and support agreements available at additional cost. ©1993 Hewlett-Packard Company. MCSY 9304.



## EDN-NEW PRODUCTS

### Integrated Circuits

**Switching regulators.** The LTC1148 and LTC1149 step-down switching regulators have typical efficiencies of 95% when operating at no load current and a 200- $\mu$ A supply current. The LTC1148 operates from input voltages of 4 to 16V; the LTC1149 operates from input voltages up to 48V. Both devices feature burst-mode switching, during which the chips switch external complementary power MOSFETs at up to 250 kHz. Both devices also have short-circuit protection. LTC1148 in 14-lead SOIC, \$4.25; LTC1149, \$5.20 (100). **Linear Technology Corp.**, 1630 McCarthy Blvd, Milpitas, CA 95035. Phone (408) 432-1900. Fax (408) 434-0507.

Circle No. 411

**ISA bus controller.** The VL82C481 single-chip ISA bus controller has write-back control logic for 486-based systems. The chip fits into Intel's Overdrive Ready upgrade strategy. The chip's memory controller addresses 64 Mbytes of system memory, which can be 256-kbit or 1- or 4-Mbit DRAMs. The memory controller provides page-mode DRAM access and burst reads and writes. The direct-mapped write-back

cache-control logic runs with 32 kbytes to 1 Mbyte of cache RAM. Power-on reset is optional. \$22 (10,000). **VLSI Technology Inquiries**, 200 Parkside Dr, San Fernando, CA 91340. Phone (602) 752-6202.

Circle No. 412

**Graphics accelerator.** The TGUI9420 graphics accelerator has both VL and ISA bus interfaces. The accelerator



linearly addresses 2 Mbytes of DRAM. The chip operates with 256k $\times$ 4-, 512k $\times$ 8-, or 256k $\times$ 16-bit DRAMs. The operations the graphics engine performs include pixel bit block transfer (bitblt), line draw, short-stroke vector draw, area fill, and image transfer. Ex-

tended graphics modes include 640 $\times$ 480 pixels with 32k, 64k, or 16.8M colors and 1024 $\times$ 768 pixels with 256 colors. \$31.50 (1000). **Trident Microsystems Inc.**, 205 Ravendale Dr, Mountain View, CA 94043. Phone (415) 691-9211. Fax (415) 691-9260.

Circle No. 413

**Analog switches.** Three CMOS analog switches have a maximum on-resistance of 35 $\Omega$ . The DG417 is a SPST normally open (NO) switch, the DG418 is a SPST normally closed (NC) switch, and the DG419 is a SPDT NO/NC switch. The devices have a breakdown voltage of 44V, a maximum turn-on time of 175 nsec, and a maximum turn-off time of 145 nsec. DG417 and DG418, from \$1.19; DG419, from \$1.63 (1000). **Maxim Integrated Products**, 120 San Gabriel Dr, Sunnyvale, CA 94086. Phone (408) 737-7600, ext 6087.

Circle No. 414

**T1/E1 line-interface units.** The VP14335 and VP14574 chips can synthesize DSX-1 and CCITT G.703 pulses. The VP14335 provides jitter attenuation on the transmit side; the VP14574 provides jitter attenuation on the re-

# HP now offers the widest range of UNIX and



**Our powerful, standards-based systems stand out from the herd.**

From board to system level. VME and EISA. HP-UX and HP-RT. We've got better products and services for your integration

needs than anyone else.

Our RISC-based systems offer binary compatibility with over 4,000 applications. And we're the #1 UNIX® systems vendor, leading the way with seamless

open systems client/server technology.\* Including HP RTAP/Plus UNIX-based application enabler software. And HP-RT, our POSIX compliant standards-based real-time OS.



## Integrated Circuits

### Full-duplex Ethernet controllers.


The 80C04 chip set has a full-duplex switching hub that lets 10Base-T nodes simultaneously transmit and receive data. Full-duplex data transfer effectively doubles the network bandwidth to 20 Mbps. The packet delay, which equals the central-switch delay, is predictable. The chip set employs a 33-MHz bus clock and has byte-swap control. It also has address and hash filters for sorting multicast addresses. \$13 (10,000). **SEEQ Technology Inc.**, 47131 Bayside Pkwy, Fremont, CA 94538. Phone (510) 226-7400. Fax (510) 657-2837.

Circle No. 401

### Programmable filter/equalizer.

The ML6017 filter/equalizer suits products having variable-speed data streams. You can tune the chip to track data streams of 9 to 48 MHz. A serial interface programs the chip on the fly. The chip contains two programmable filters: a lowpass filter, which removes high-frequency noise, and a bandpass filter, which removes low-frequency noise and high-frequency overtones. A programmable equalizer overcomes intersymbol interference. In a 20-pin super-small-outline package, \$5.95 (100,000). **Micro Linear Corp.**, 2092 Concourse Dr, San Jose, CA 95131. Phone (408) 433-5200.

Circle No. 402

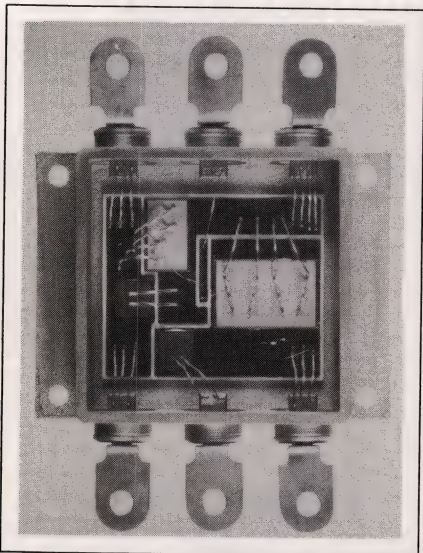

**High-power IGBTs, MOSFETs, and rectifiers.** The Power Block series is a packaging technology for high-power IGBTs (insulated-gate bipolar transistors), MOSFETs, and rectifiers. The IGBTs are rated for 30 to 60A and 600 to 1200V. The MOSFETs are rated for 8 to 120A and 50 to 1000V. Fast rectifiers, soft-recovery rectifiers, and Schot-

### FREE INFO, FREE POSTAGE

Use our postage-paid reader-service cards to get more information on any of these products.

tky rectifiers are rated for 100A and 50 to 1200V. \$219 to \$304 (100). **Omni-rel Corp.**, 205 Crawford St, Leominster, MA 01453. Phone (508) 534-5776. Fax (508) 537-4246.

Circle No. 403

**3.3V PLD.** The XC7236A is a 0.8- $\mu$ m complex PLD having I/O interfaces compatible with 3.3V logic. The core logic for the chip operates at 5V to provide high speed, and the I/O interfaces run at 3.3V. The chip also operates from 5V only. The clock-to-output delay is 10 nsec, and the maximum operating frequency is 60 MHz. 50-MHz device, \$16; 60-MHz device, \$19.50 (1000). **Xi-linx Inc.**, 2100 Logic Dr, San Jose, CA 95124. Phone (408) 559-7778. Fax (408) 559-7114.

Circle No. 404

**LCD-driver  $\mu$ Cs.** The L-Series consists of 10 new versions of the 68HC05 family of 8-bit  $\mu$ Cs. Each member contains an LCD driver and low-power-operation features. Drivers control LCDs having resolutions from 45 to 154k pixels. Prices start at \$3 (50,000). Development boards start at \$68. **Motorola Inc.**, 6501 William Cannon Dr W, Austin, TX 78735. Phone (512) 891-2035.

Circle No. 405

**Field-memory ICs.** The MSM518221 and MSM518222 2-Mbit memories can hold one field of a conventional NTSC TV screen. The 512  $\times$  512  $\times$  8-bit DRAMs provide FIFO operation and do not need external refreshing. You can cascade multiple ICs to increase storage depth. Each 8-bit plane has separate read and write ports. \$9.50 (10,000). Delivery 60 to 90 days ARO. **Oki Semiconductor**, 785 N Mary Ave, Sunnyvale, CA 94086. Phone (408) 720-1900. FAX (408) 720-1918.

Circle No. 406


**Futurebus+ controllers.** Three chips control different aspects of the IEEE-896 Futurebus+. The TFB2010 arbitration bus controller handles both central and distributed arbitration messages. The TFB2022 data-path unit stores and transfers 64-bit data and addresses. The TFB2002 I/O controller synchronizes the Futurebus+ protocols with the local bus. The chips handle both compelled- and packet-mode transfers.

TFB2010PJM, \$34; TFB2022MFP, \$380; TFB2002PPM, \$105. **Texas Instruments Inc.**, Semiconductor Group, Literature Response Center, Box 17222, Denver, CO 80217. Phone (800) 477-8924, ext 3015.

Circle No. 407

**Analog multiplexers.** Alternate-source versions of the industry-standard DG408 and DG409 analog multiplexers have a maximum on-resistance of 100 $\Omega$ . The breakdown voltage is 44V max, and the switching time is 250 nsec max. The chips operate from a 12 to 30V supply or from  $\pm 4.5$  to  $\pm 20$ V dual supplies. The ICs come in 16-pin DIPs and narrow SO packages. From \$3.45 (1000). **Maxim Integrated Products**, 120 San Gabriel Dr, Sunnyvale, CA 94086. Phone (408) 737-7600, ext 6087.

Circle No. 408

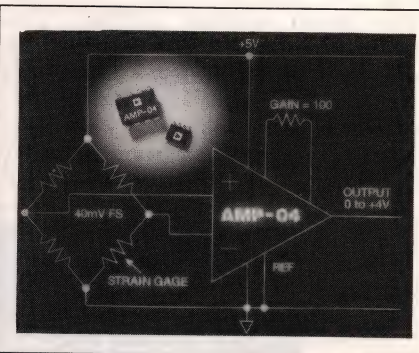

**Instrumentation amplifier.** The AMP-04 instrumentation amplifier operates from +5 to  $\pm 15$ V supplies. Specifications include a CMRR of 105 dB at a gain of 1000; maximum offset drift of 3  $\mu$ V/ $^{\circ}$ C; maximum offset voltage of 150  $\mu$ V; and maximum gain non-linearity of 0.005%. Selecting a resistor programs the gain from 1 to 1000. From \$4.55 (1000). **Analog Devices Inc.**, 181 Ballardvale St, Wilmington, MA 01887. Phone (617) 937-1428. Fax (617) 821-4273.

Circle No. 409

**Isolation amplifier.** The ISO122U isolation amplifier comes in a surface-mount package. The amplifier has an isolation voltage of 1500V rms min and is 100% tested for voltage breakdown at 2400V rms. Isolation mode rejection is 140 dB typ at 60 Hz, and the barrier leakage is 0.5  $\mu$ A max at 240V and 60 Hz. Gain is 1V/V, and the gain error is  $\pm 0.05\%$  of the full-scale reading (FSR). The nonlinearity is  $\pm 0.008\%$  FSR. \$7.95 (1000). **Burr-Brown Corp.**, Box 11400, Tucson, AZ 85734. Phone (602) 746-1111. Fax (602) 889-1510.

Circle No. 410



世界で一番早い  
La más rápida del mundo!

اسرع ما في العالم  
La plus rapide du monde!

Der schnellste auf der Welt!

世界上取快速  
Il più veloce nel mondo!

# IN ANY LANGUAGE, QUALITY SEMICONDUCTOR FIFOS ARE THE FASTEST IN THE WORLD!

Call and find out why... (408) 450-8019

## FIRST IN Engineering

Once again Quality Semiconductor is First In Engineering and product design! QSI consistently creates revolutionary devices that allow you to engineer innovative, leading edge products. When you need to be *Faster, Cleaner, and Quieter*, you need Quality Semiconductor.

## FIRST OUT with Delivery

Product design is where it starts, but delivery is what counts. Now QSI is ready to deliver the fastest family of asynchronous FIFOs in the world, as well as the next generation 66 MHz QS7223 and QS7224 clocked FIFOs. These products feature depths to 4k words and access times to 10 ns. Our new FIFOs



provide performance and innovation for the highest performance system designs possible. These FIFOs are available in DIP, PLCC, SOJ, SOIC, and even ZIP packages. Once again Quality Semiconductor provides the design flexibility that allows you to create products that lead the pack.

## Quality Engineering, Quality Products

Of course, that's what QSI does best! With record breaking innovations in FCT Logic, 250 pS QuickSwitch products, and SRAMs, we now feature the world's fastest FIFOs in a virtually unlimited range of packaging options. The new Quality FIFOs are available and ready to ship.

Quality Semiconductor, Inc.



### Quality Products The FIFO series

QS7201	512 x 9	12ns access
QS7202	1K x 9	12ns access
QS7203	2K x 9	10ns access
QS7204	4K x 9	10ns access
QS7223	2K x 9	66MHz Clocked Interface
QS7224	4K x 9	66MHz Clocked Interface



# A S I C

*T h e O p t i m u m C h o i c e*

## APPLICATIONS

*Electronic Tags  
Security (Access Control)  
Fuses (Smart Munitions)  
Automotive  
Telecommunications  
Medical  
Military*

## THREE TECHNOLOGY SOLUTION


*Hughes Microelectronics Europa Ltd. offer the capability of incorporating Analogue, Digital and Non-Volatile circuitry on the same piece of silicon. We offer full custom design, cell based design or wafer foundry business. With over 30 different processes on offer.*

## RELIABILITY

*We have been designing and processing full custom non volatile based designs for more than 12 years at our Glenrothes facility, offering superior reliability with > 1M endurance cycles/cell and > 100 years retention as standard.*
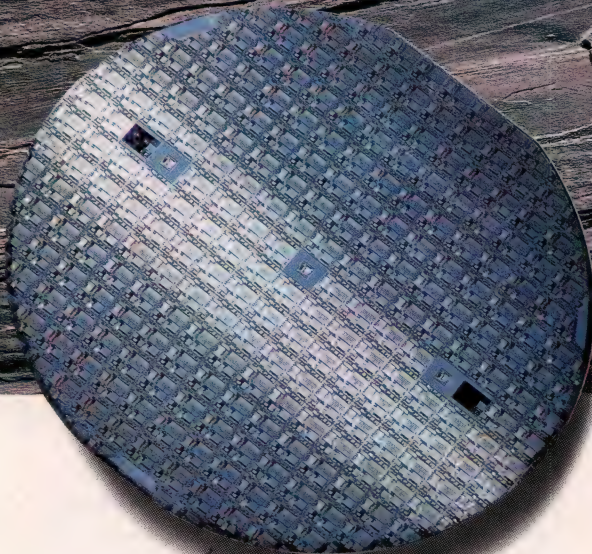
## VERY LOW OPERATIONAL VOLTAGE

*Our process capabilities and design experience allow us to design circuits which operate over wide voltage ranges. From circuits for identification tags operating down to 1.0v, to circuits suitable for the harsh automotive environment. We have the process to match your requirements.*



### HUGHES

**Hughes Microelectronics Europa Ltd.**  
Subsidiary of Hughes Aircraft Company

*Headquarters:  
Hughes Microelectronics Europa Ltd.  
Queensway Industrial Estate  
Glenrothes, Fife  
KY7 5PY, Scotland  
Tel: (0592) 754311  
Fax: (0592) 759775*

*Hughes Microelectronics Europa  
(Deutschland)  
Landsberger Str 398  
D-8000 Munchen 60  
Deutschland  
Tel: (089) 580 83 64  
Fax: (089) 580 82 61*

*Hughes Microelectronics Europa  
España  
C/DARRO, 13 El Viño  
28002 Madrid, España  
Tel: (34-1) 561 62 08  
Fax: (34-1) 561 92 90*

*Hughes Microelectronics Europa  
España S.A.  
Parque Tecnológico de Andalucía -  
Parcela P-1  
Carretera MA-401, Km. 11, Campanillas  
Apartado de Correos, 73 - 29590  
Málaga, España  
Tel: (52) 24.92.00  
Fax: (52) 24.92.47*



## Design Entry Blank

**\$100 Cash Award for all entries selected by editors. An additional \$100 Cash Award for the winning design of each issue, determined by vote of readers. Additional \$1500 Cash Award for annual Grand Prize Design, selected among biweekly winners by vote of editors.**

To: Design Ideas Editor, EDN Magazine  
Cahners Publishing Co  
275 Washington St, Newton, MA 02158

I hereby submit my Design Ideas entry.

Name \_\_\_\_\_

Title \_\_\_\_\_ Phone \_\_\_\_\_

Company \_\_\_\_\_

Division (if any) \_\_\_\_\_

Street \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

Country \_\_\_\_\_ Zip \_\_\_\_\_

Design Title \_\_\_\_\_

Home Address \_\_\_\_\_

Social Security Number \_\_\_\_\_  
(US authors only)

### Entry blank must accompany all entries.

Design entered must be submitted exclusively to EDN, must not be patented, and must have no patent pending. Design must be original with author(s), must not have been previously published (limited-distribution house organs excepted), and must have been constructed and tested. Fully annotate all circuit diagrams. Please submit software listings and all other computer-readable documentation on a 5¼-in. IBM PC disk in plain ASCII.

Exclusive publishing rights remain with Cahners Publishing Co unless entry is returned to author, or editor gives written permission for publication elsewhere.

In submitting my entry, I agree to abide by the rules of the Design Ideas Program.

Signed \_\_\_\_\_

Date \_\_\_\_\_

### ISSUE WINNER

The winning Design Idea for the October 1, 1992, issue is entitled "Differential amplifier reduces parts count," submitted by Irwin Cohen of Hewlett-Packard (Waltham, MA).

The winning Design Idea for the October 15, 1992, issue is entitled "1.5 to 5V converter supplies 200 mA," submitted by Jim Williams of Linear Technology Corp (Milpitas, CA).

## Reset trap locates system errors

Ed Thompson, Micro Computer Control, Hopewell, NJ

Unexpected system resets during development can often lead to much finger pointing between hardware and software team members. A simple technique can isolate the problem to either hardware or software, reduce frustrations, and speed debugging. The technique relies on the fact that a hardware reset sets processor registers to a known initial state, and software then initializes those same registers to another state. By testing the state of a register before software initialization, you can detect the cause of the reset. The solution presented here is for an 8051-based system, but could easily be adapted to a variety of system architectures.

### Listing 1—Startup code to trap reset cause

```
#define TMOD 0x03 /* Timer0 = 16-bit */

bit sw_reset; /* TRUE on Software Reset */

main()
{
    sw_reset = (tmmod == TMOD); /* Test Reset */
    tmmod = TMOD; /* Software Initialization */
    .
    .
    .
}
```

Listing 1 shows a sample section of C code to handle startup and initialization of the 8051 TMOD register. A hardware reset initializes this register to zero (00H). The code tests the state of this register against the software initialized value, and records the test result for later examination. You can write additional code to send this result to a spare I/O pin or output it to the UART upon receiving an appropriate inquiry. It's worthwhile to leave this code as a permanent part of the system to help explain unexpected reset events that could occur at later stages of system development and testing. **EDN BBS /DL\_SIG #1213** **EDN**

To Vote For This Design, Circle No. 395



# If 150 watts in a 50 watt package sounds like an overpromise... call us on it.

AT&T's next generation of Board

Mounted Power  
Modules (miniature DC/DC converters) is ready

to answer your call for small form factor 50 to 150 watt power devices.

AT&T Bell Laboratories designers have packed 150 watts (2:1 input voltage, 5 volts output) into the same 2.4 x 2.28 x 0.5 inch package that others get only 50 watts into.

This saves you board space. And speeds and simplifies your design-in.



Three times the power  
in a 50 watt space

than was ever available before: 54.8 watts per cubic inch power density.

While others may talk high power density, their devices demand a "skyscraper-high heatsink" for effective thermal management. That means

your space-saving board arrangements

go up, up, up  
in the air.

As for  
reliability, the

same AT&T quality design process that developed power modules with demonstrated MTBF >5 million hours was used for this next generation.

With AT&T power modules, you're also assured very competitive prices, plus the broadest offering: 0.5 to 200 watt products.

Call us at the number above. From technical support to creative power solutions, we'll give you real reasons to make AT&T your power resource.

---

## AT&T Power Systems. The power to do more.

---

For other power literature or power information, call 1 800 372-2447, ext. 911.



1-800-526-7819

Plus, our new  
84% efficient  
modules give  
you more  
useable power




You can separate the  $V_{CC}$  of the LM10 and the load. The  $V_{CC}$  for the LM10 must stay within the gate thresh-

**EDN**

---

— 25 —

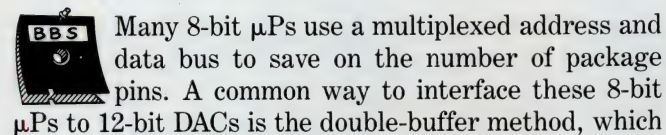

```


mov  a,high_byte      ; assume xxxxDddd DDDDDDDD as 12-bit
                        ; word 1-high-11-low-1
mov  dpl,a             ; high order 4 bits to low data pointer
mov  dph,#7fh          ; set a15=0
mov  a,low_byte        ; low order 8-bit to accumulator
movx @dptr,a           ; output 12-bit word to 12-bit DAC
                        ; in one instruction

```

The circuit in **Fig 1** can transfer the same 12-bit word, but doesn't require an external data latch. The circuit uses the address latch, IC<sub>1</sub>, and a short software routine (**Listing 1**) to transfer the four high-order bits of a 12-bit word to the address latch first, and to transfer the low-order 8 bits using one instruction. **EDN**

**BBS /DI-SIG #1239** **EDN**

---

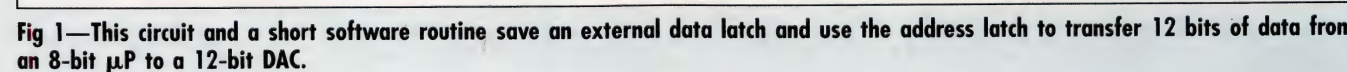




# RF TRANSFORMERS

*Over 80 off-the-shelf models...*

*3KHz-1500MHz from \$1<sup>95</sup>*

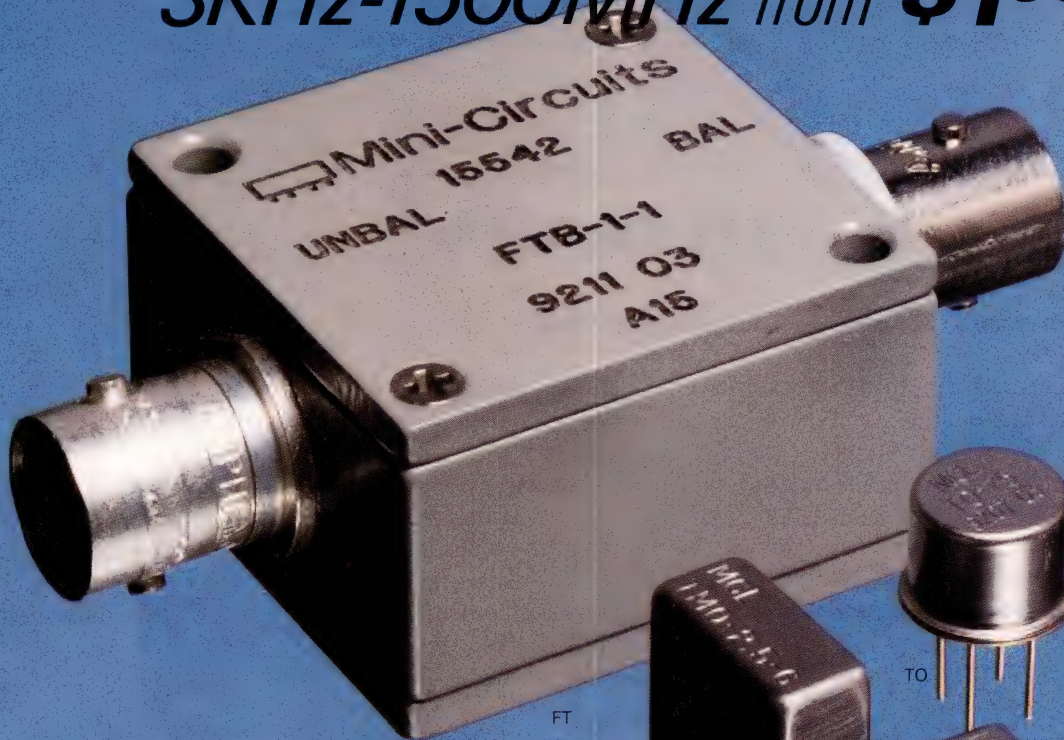


Having difficulty locating RF or pulse transformers with low droop, fast risetime or a particular impedance ratio over a specified frequency range?... Mini-Circuits offers a solution.

Choose impedance ratios from 1:1 to 36:1, in connector, TO-, flatpack, surface-mount, or pin versions (plastic or metal case built to meet MIL-T-21038 and MIL-T-55831 requirements\*). Coaxial connector models are offered with 50 and 75 ohm impedance; BNC standard, other types on request.

Ultra-wideband response achieves low droop and fast risetime for pulse applications. Ratings up to 1000M ohms insulation resistance and up to 1000V dielectric voltage. For wide dynamic range applications involving up to 100mA primary current, use the T-H series. Fully detailed data appear in our 740-pg RF/IF Designer's Handbook.

Need units in a hurry?... all models are covered by our exclusive one-week shipment guarantee. Only from Mini-Circuits.

\*units are not QPL listed.

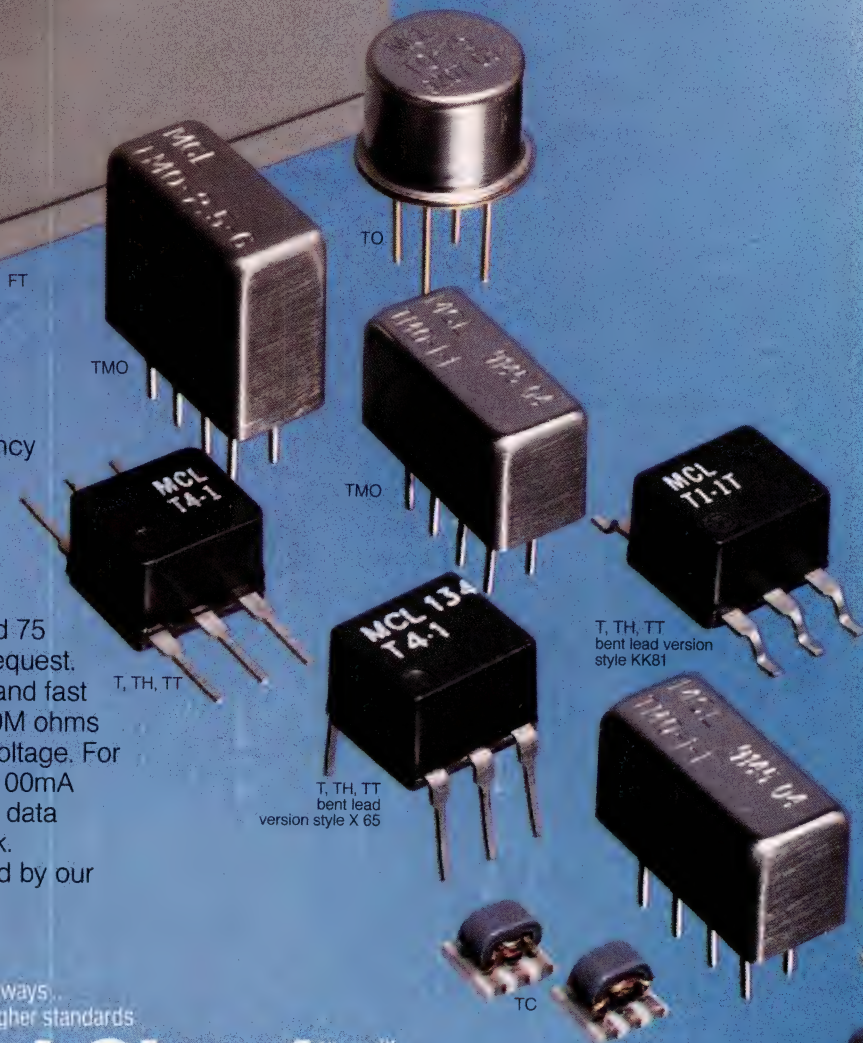

*finding new ways...  
setting higher standards*



**Mini-Circuits**

WE ACCEPT AMERICAN EXPRESS AND VISA

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718) 332-4661

Distribution Centers/NORTH AMERICA 800-654-7949 • 417-335-5935 Fax 417-335-5945 EUROPE 44-252-835094 Fax 44-252-837010

or detailed specs on all Mini-Circuits products refer to • THOMAS REGISTER Vol. 23 • MICROWAVES PRODUCT DIRECTORY • EEM • MINI-CIRCUITS' 740-pg HANDBOOK.



significant distortion occurs during the flat portions between peaks. The compensated waveform (trace D) recovers the low-frequency information and the peak current level.

Any spreadsheet can also implement the compensator. You need to import the ac current probe's waveform values from the scope, and you must know the sampling interval or time between points. The only trick is to implement the integration function (Table 1). If you put the waveform value,  $x(t)$ , in column A, then you should create a second column, B, that represents the integral of  $x(t)$ . Force the first cell to be 0, then each successive value is simply the previous value

**Table 1—Spreadsheet for ac-current-probe compensation**

	A	B	C
1	x(1)	0	= A1 + 450*B1
2	x(2)	= B1 + A2*25E-6	= A2 + 450*B2
3	x(3)	= B2 + A3*25E-6	= A3 + 450*B3
4	x(4)	= B3 + A4*25E-6	= A4 + 450*B4
5	etc	etc	etc

plus the present  $x(t)$  value times the sampling interval. Finally, create a third column, C, which sums the first column and  $\omega$  times the second column. For Table 1, the sampling interval was 25  $\mu\text{sec}$  and  $\omega = 450$ .

Although the integration function is the key to this technique, it is also its greatest limitation. If your scope has a dc offset error, then the integrator will cause the compensated waveform to ramp up or down depending on the sign of the offset. You can correct for this by subtracting the offset from each  $x(t)$  value before computing the result. Experiment with the correction value until the ramp disappears. This technique works because you're constraining the constant of integration to 0 by measuring only start-up conditions and by correcting for dc offsets in the instrumentation.

When using this technique, use your probe within its operating limits. The magnetic properties of many ac current probes limit the amount of dc and pulsed currents that you can apply. This technique only compensates for the probe's low-frequency roll off. Correcting for magnetic saturation effects is a much more complicated problem. EDN BBS /DI\_SIG #1236

EDN


To Vote For This Design, Circle No. 392

## Solid-state fuse resets itself

Isaac Eng, ESTCO Battery, Ottawa, Canada

The solid-state fuse in Fig 1 automatically resets once current has returned to normal after an overcurrent condition. The circuit draws less than 350  $\mu\text{A}$  with the fuse blown ( $Q_1$  off) or not blown ( $Q_1$  on). The circuit allows load currents up to 1A to flow, but drops into strobe mode with load currents that exceed 1A.

The LM10 op amp buffers the voltage of the current-sense resistor ( $R_1$ ) to charge  $C_1$  through a forward-biased  $D_1$ . Pin 8 of the LM10 compares  $C_1$ 's voltage to the LM10's internal 0.2V reference. When  $C_1$ 's voltage is less than 0.2V, the comparator output (pin 1) is high and keeps  $Q_1$  turned on and conducting load current. When the load current exceeds 1A, the voltage across  $C_1$  exceeds 0.2V. The comparator output goes low,  $Q_1$  turns off, and load current is cut off.  $C_1$  then discharges through the 3.3-M $\Omega$  resistor. When the voltage decreases below 0.2V,  $Q_1$  turns on again

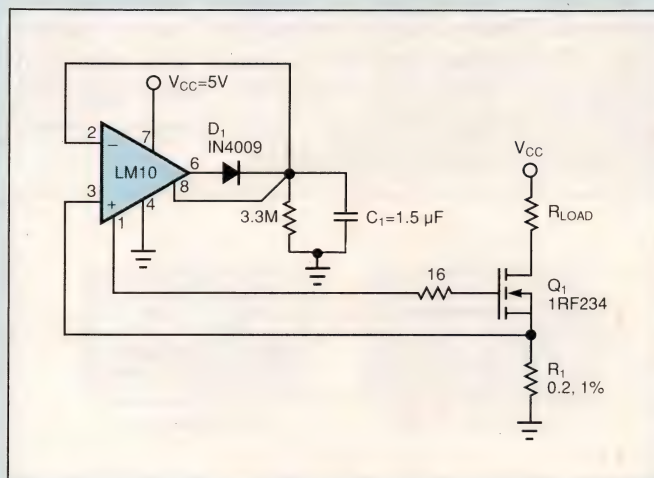

**Fig 1—Based on the charge on  $C_1$ , the LM10's internal comparator determines the state of pin 1, which shuts off  $Q_1$  if load current exceeds 1A.**



## Software extends ac current probe's range

Stan Sasaki, Tektronix, Beaverton, OR

AC current probes based on current transformers don't pass dc information. This limitation typically forces you to use more expensive dc current probes to analyze asymmetrical start-up waveforms such as turn-on or inrush currents. However, you can use ac current probes by taking advantage of the zero initial value of start-up events to recover low-frequency information. The required processing software is available in some digital oscilloscopes and all PC spreadsheets.

An ac current probe has a conversion factor of kV/A (Fig 1). The probe's frequency response rolls off at its low-frequency pole,  $\omega$ , set by the probe's transformer L/R time-constant or droop factor. An ideal compensator has a transfer function with a zero at  $\omega$  and a pole at dc. You can implement this compensator using the following equation:

$$y(t) = x(t) + \omega \cdot \int x(t) \quad (1)$$

Thus, if the ac current probe's waveform is  $x(t)$ , then compute the compensated output by adding  $x(t)$  to  $\omega$  times the integral of  $x(t)$ . The only parameter you need is  $\omega$ . Some ac current probes specify the roll-off frequency in Hz ( $\omega = 2\pi f$ ), but it's best to measure the value. Simply apply a dc current step and measure the decay time,  $\tau$ , or the time it takes for the probe's output to fall to 37% of its peak value. Then,  $\omega = 1/\tau$ .

Some digital scopes have a built-in integration function that let you define a new waveform that directly implements the compensator. Fig 2 shows voltage and current waveforms (traces A and B, respectively) on a disk drive's 5V supply. A dc current probe is the reference. Trace C is the output from an ac current probe. The probe's roll-off frequency was measured as just above 70 Hz, so  $\omega = 450$ . The scope calculated trace D using Eq 1. Notice how the compensator recovers the low-frequency information.

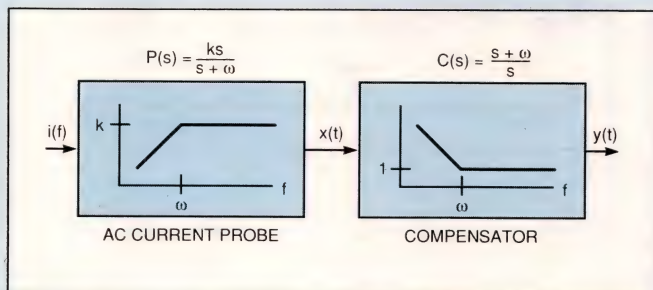


Fig 1—An ac current probe's response falls off at low frequencies, but a compensator with a pole at dc and zero at the probe's low-frequency cut off can theoretically extend the response to dc.

Fig 3 shows the start-up waveforms of a switching power supply. The dc current probe shows a peak current of  $-10A$  (trace B). The uncompensated ac current probe's reading (trace C) is low due to droop, and

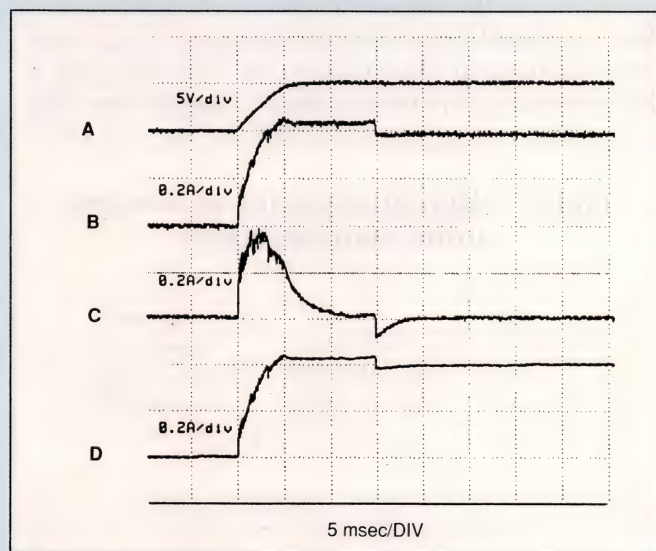


Fig 2—A dc-probe's measurements of a disk-drive's 5V start-up voltage and current (traces A and B, respectively) don't match the measurements of an ac current probe (trace C) until the compensation is included (trace D).



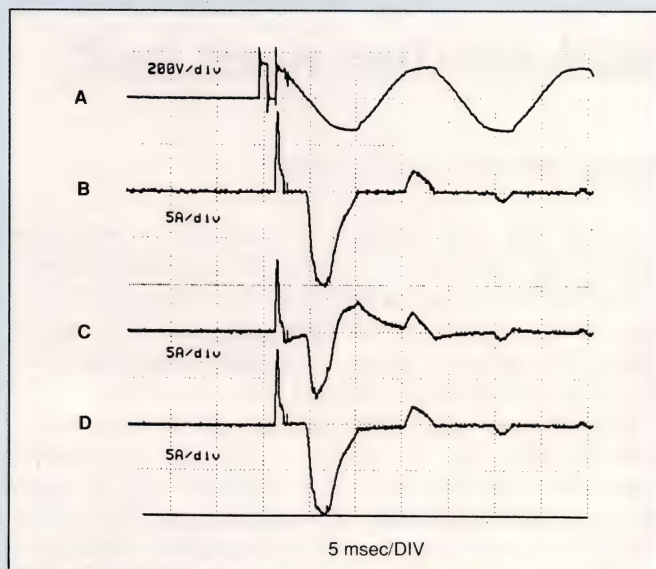


Fig 3—The compensated ac-current-probe measurement of a switching power supply's power-line voltage and current (trace D) improves upon the uncompensated ac measurement (trace C) by showing the true negative peak current level and removing the distortion. Traces A and B are the dc-probe measurements of voltage and current, respectively.

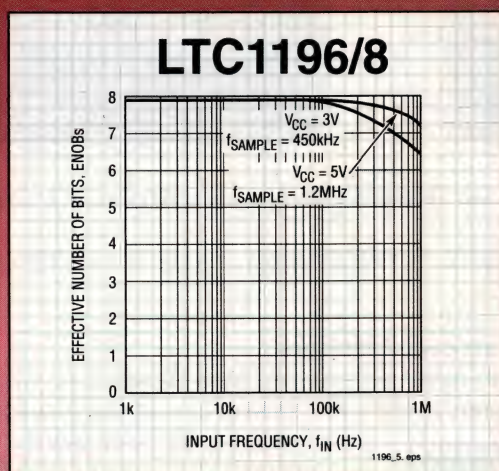


# NEW SO-8 ADCs 1 MSPS or 3V-3 $\mu$ A

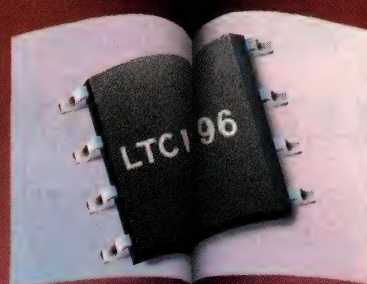

For high speed or micropower applications, Linear Technology provides the highest performance, most compact sampling 8-bit A/D converters at the lowest cost.

The high speed LTC1196/8, 600nsec 8-bit ADCs are designed and specified for 3V and 5V systems and squeezed into tiny SO-8 packages. Their high speed serial ports ease signal wiring and can transfer data at 12MHz bit rates to ASICs and PLDs. (Application assistance for interfacing to common PLDs is available.) Sampling at up to 1MSPS, their high impedance inputs digitize 1MHz signals to an accuracy of greater than 7 effective bits.

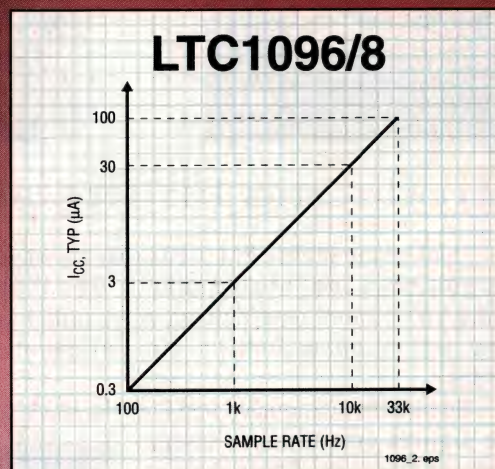The LTC1196 has a differential input while the LTC1198 digitizes 2 input channels and automatically powers down to 1nA between conversions. With a typical power dissipation of 50mW at 5V and 10mW at 3V, the LTC1196/8 provide the best combination of performance, power, board space and cost available.



For micropower applications, the LTC1096/8 has extremely low supply currents which automatically scale to the sample rate. The typical current drain from a 3V or 5V supply varies linearly from 3 $\mu$ A at 1KSPS to 100 $\mu$ A at 33KSPS. The ADCs also automatically power down between conversions.

The 2.7V minimum supply and SO-8 package are ideal for battery powered, hand held instruments and equipment. The serial I/O reduces opto-isolation cost and is compatible with SPI, Microwire, and other common serial formats.

Whether you are looking for high speed or micropower 8-bit sampling ADCs, you won't find higher performance, more compact, lower cost solutions anywhere.

Pricing in 1000 up quantities for LTC1196 starts at \$2.37 and \$2.85 for LTC1096. For more details, contact Linear Technology Corporation, 1630 McCarthy Boulevard, Milpitas, California 95035/408-432-1900. For literature only, call 800-637-5545.






TOUGH PRODUCTS  
FOR TOUGH APPLICATIONS.


CIRCLE NO. 51



# Real life simulation.

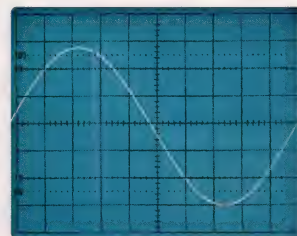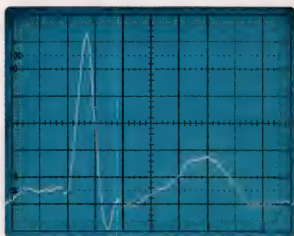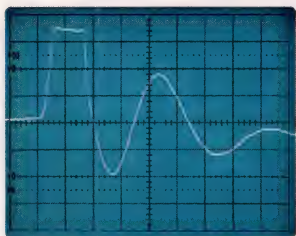

# Without doing this.

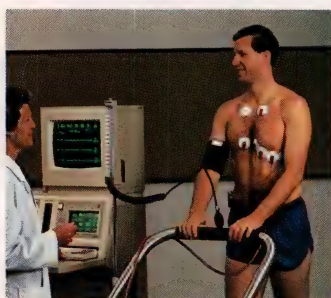

## Introducing Philips arbitrary waveform generator.

Think of the Philips PM 5150 arbitrary waveform generator as a real life simulator. One that can simulate any desired user-defined waveform. In other words: unlimited waveform simulation at your fingertips.

No need for expensive test models. It will match those signals encountered under actual operating conditions. All at half the price and twice the performance of other waveform generators. Sounds too good to be true?

### Just look at the specs.

Digital waveform synthesis with 12 bit amplitude resolution and 32K of waveform memory allows you to create, store and edit the most complex waveforms. All this at a maximum speed of 20MS/s. A choice of

20 standard waveforms gives access to common test signals.

### Build your own waveforms.

If, however, you run these 20 standard waveforms through the math, scaling and editing functions, over 1 million tailor-made waveforms are available. Waveform editing is extremely easy via the front panel or optional mouse.



### Optional sequence generator.

For unprecedented versatility, the optional sequence generator

will repeat and link waveforms in any order.

More memory. More speed. The new Philips PM 5150 arbitrary waveform generator. Real life simulation at a real low price.

## You'll measure better performance

For literature or a demonstration call:

Austria (0222) 60101-1772, Belgium (02) 5256692/94, Denmark (32) 882100, Finland (90) 5026371, France (1) 49428080, Germany (0561) 501466, Great Britain (0923) 240511, Ireland (061) 330333, Italy (039) 2036519, Netherlands (040) 503100, Norway (22) 748381, Portugal (1) 683121, Spain (1) 4042200, Sweden (08) 7821300, Switzerland (01) 7452244.  
For countries not listed, write to: Philips Test & Measurement, Building TQIII-3 5600 MD Eindhoven, The Netherlands.



# PHILIPS



## DIGITAL-NOISE GENERATION

oped DSP-based waveform synthesizer to incorporate the DNG algorithm. Thus, we had a composite real-time signal consisting of MF tones plus Gaussian noise to use as a source. We used an already existing user interface to vary the levels of the tones and noise.

Table 1 shows the results of the MF decoder performance for the DNG versus the GenRad 1390B, which is a commercially available random noise generator. In all cases, we used nominal MF frequencies, and the level of each tone was set to  $-22$  dBm at  $600\Omega$ . The MF tone-switching rate was 70-msec ON and 70-msec OFF.

Both noise sources performed equally well for a noise level of  $-30$  dBm, which actually exceeds the LSSGR requirements. We then raised the noise level to cause the MF decoder to fail (ie, miss digits). The two noise sources differ by 8.5% for the noise level required to produce the same MF decoder-error rate. After accounting for variations in the hardware test configurations, approximately a 5% difference remains between the DNG and 1390B noise levels. The internal structural differences of the noise sources themselves appear to be the cause of this difference. For this test case, the MF decoder appears to tolerate a slightly higher level of Gaussian noise from the DNG than the 1390B, for a given detection error rate.

The 16-bit, fixed-point DNG real-time performance compared favorably to that of a commercially available noise generator for moderate DSP sample rates. The fixed-point DNG performance is probably adequate for those applications where the accuracy of the random distribution is not of paramount importance. The DNG algorithms can offer a flexible and cost-effective solution for random noise generation, especially in those applications where you are already using DSP techniques.

You could increase the DNG's noise bandwidth if you increased the sample rate. However, this increase impacts hardware cost, especially for the DAC and the output lowpass filter needed. The commercial unit used for comparison here can generate noise up to 5 MHz in bandwidth.

A major deficiency of the fixed-point DNG is the relatively small word length. Ref 1, for example, recommends that the word length be at least 30 bits. Another deficiency has to do with the dynamic range (overflow and scaling considerations). You could address both of these deficiencies by using a 32-bit, floating-point DSP chip. However, floating-point DSP devices are typically slower and more expensive than their fixed-point counterparts.

Increasing the batch size would improve the distribution of the Gaussian sequence at the expense of increased computational load. The tradeoff is between

Table 1—DNG output sequence values

Iteration, n	Uniform x(n)		Gaussian g(n)	
	Hex Value	Decimal Value	Hex Value	Decimal Value
1	66B7	26295	347F	13439
2	1588	5512	340F	13327
3	1D75	7541	379F	14239
4	2C8E	11406	372F	14127
5	5EA3	24227	4ABF	19135

the accuracy of the output distribution and the DSP chip's speed. This tradeoff ultimately limits the bandwidth of the resultant noise signal. **EDN**

## References

1. Knuth, D E, "The Art of Computer Programming, Volume 2 / Seminumerical Algorithms," Addison-Wesley, 1981 Second Edition, pgs 9-24 and 170-173.
2. Law, A M, and W D Kelton, "Simulation Modeling and Analysis," McGraw-Hill, 1991 Second Edition, pgs 424 to 427.
3. Davenport, W B, and W L Root, "An Introduction to the Theory of Random Signals and Noise," IEEE Press, 1987, chapter 5.
4. Brown, A D E, "Generate Gaussian Noise with a DSP Chip," *EDN*, June 23, 1988, pgs 183-184.
5. Park, S K and K W Miller, "Random Number Generators: Good Ones are Hard to Find," *Communications of the ACM*, Volume 31, Number 10, October 1988, pgs 1192-1201.
6. Bell Communications Research, TR-TSY-000064 LSSGR, Revision 2, June 1985, Section 6.4.

## Acknowledgment

The author would like to express appreciation to Dr Ken Boudwin of Exxon Research and Engineering, Florham Park, NJ, for his help in understanding the statistical tests for randomness, and to Sherrie Gumienny, English Department Head for Life Center Academy, Burlington, NJ, for her review and helpful comments of the article.

## Author's biography

Bill Salibrici is a Principal Member of the Technical Staff of TeleSciences Co Systems, Moorestown, NJ, a supplier of operation-support systems for telephone companies worldwide. For the past five years, he has been responsible for development of DSP software for real-time, voice-band applications. Bill has a BSEE from Pennsylvania State University, University Park, PA, and has taken graduate studies from the University of Pennsylvania, Philadelphia, PA.

Article Interest Quotient (Circle One)  
High 494 Medium 495 Low 496




However, the MSB cycles with a full period. Therefore, the sequence **Eq 3** generates has a full period of length  $m$  (ie, the sequence repeats after  $m$  values).


**Fig 2** shows the algorithm used to implement **Eq 3** for uniformly distributed pseudo random numbers. Notice that **Eq 3** is partitioned so that  $[a \times x(n)] \bmod m$  is calculated first, and then the modulo  $m$  addition to  $c$  is done. **Fig 3** shows the algorithm used to implement **Eq 2** for Gaussian-distributed pseudorandom numbers. The batch size for Gaussian noise was 16, and the uniformly distributed random numbers come from **Eq 3**. Notice here that each element of the summation is divided by the batch size before adding it to the running sum. You do this to prevent overflow errors. You can easily apply these algorithms to other single-chip DSP devices with perhaps minor changes due to architectural differences.

**Listing 1** shows the source code used to implement the Uniform algorithm on the 77P25. **Listing 2** shows the source code used to implement the Gaussian algorithm. The **Listing Table** shows the first five numbers, in integer format, of the Uniform and Gaussian output sequences. (Both **Listings** and the **Listing Table** are located on the EDN BBS.)

Evaluating the results of several simulation programs addressed the question of how random the DNG is. These simulations showed that the raw DNG noise distributions have the expected shape. The results of two statistical tests for proper fit indicate that the hypothesis of normality for the Gaussian case is accu-

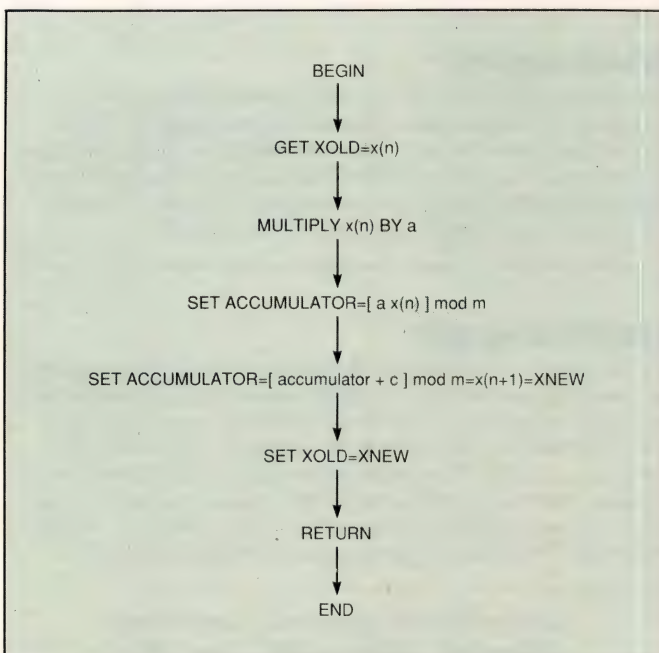

**Fig 2**—You can generate uniformly distributed, pseudorandom numbers with the program illustrated here.

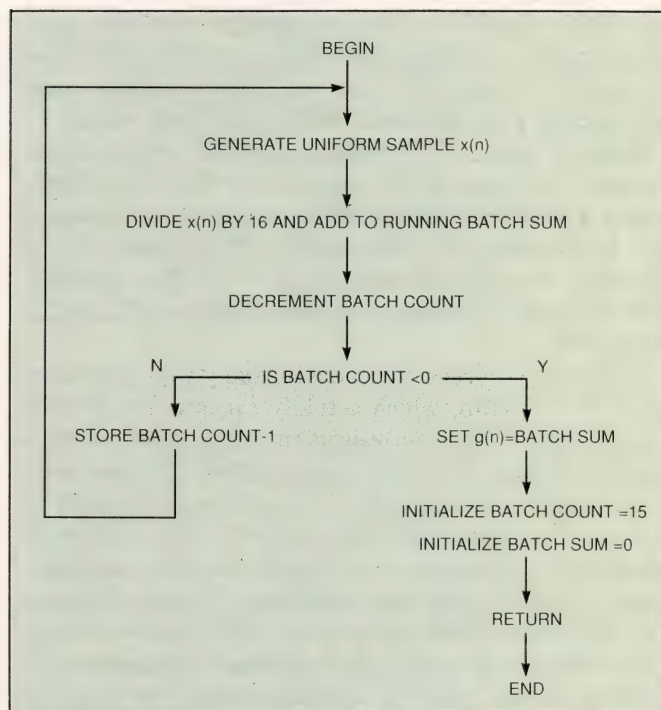

**Fig 3**—You can generate Gaussian-distributed, pseudorandom numbers by taking the output of the uniform algorithm described in **Fig 2** and following this flowchart.

rate. The autocorrelation function of the DNG compared to the drand48 function (a function Sun Microsystems Inc's C Library provides) are slightly different, but not radically so.

We performed further tests using the hardware design shown in **Fig 1**. We scaled the internal DNG random numbers for a zero mean by subtracting  $\frac{1}{2}$  and expanded them to full scale by multiplying by 2 so that the DSP chip's output range was between  $-1$  and  $+1$ . In order to use the codec DAC, we performed a linear-to- $\mu$ law software conversion before outputting the noise sample. A lowpass filter inside the codec band limits the analog noise output signal to approximately 3 kHz. The codec output has a full-scale excursion of  $\pm 3V$ , which introduces a voltage gain factor of 3 between the DSP chip's output and the final analog output.

These lab tests showed that the measured values for the mean and variance are close to theoretical values. Also, the Gaussian frequency spectrum of the DNG compares well to that of a commercially available noise generator for the 3-kHz band-limited case.

We needed the Gaussian noise source in order to test the detection of multifrequency (MF) tones in the presence of Gaussian noise. The Bell Communication Research LSSGR (**Ref 6**) defines the required MF decoder performance. We modified our internally devel-



## DIGITAL-NOISE GENERATION

(least significant bits) of  $X$ . For example,  $(a \times X) \bmod m$  is simply the product  $(a \times X)$  truncated to  $m$  LSBs.

One method to generate a Gaussian (or normal) distributed random-number sequence is to apply the Central Limit Theorem to batches of uniformly distributed random-numbers (Refs 3 and 4). You can mathematically express this idea as follows:

$$g(n) = \frac{1}{B} \sum_{i=0}^{B-1} x(i), \quad (2)$$

where the  $x(i)$  are uniformly distributed, independent random numbers;  $B$  is the batch size; and  $g(n)$  is a member of a set of random numbers approximately Gaussian distributed.

This algorithm produces a pseudorandom sequence whose distribution is close to Gaussian, provided that the batch size  $B$  is greater than 10. If you choose a power of 2 as your batch size, then you can use a shift-right operation to simplify the required division within the DSP chip.

The data representation internal to the 77P25 is the 16 bit, two's-complement, fractional format. This means that the most significant bit (MSB) is the sign bit followed by an implied binary point. The remaining 15 bits contain the fraction magnitude. You can represent the range of numbers  $-1.0$  to  $(1-2^{-15})$  in this format, or you can express them with hexadecimal numbers as 8000H to 7FFFH.

To apply the linear congruential generator in this

case, we used  $m=2^{15}$ , which is the size of the fraction magnitude. Then Eq 1 will generate positive integers between 0 and 32768.

However, the interpretation of these integers is  $x(n)/m$ , so that the end result will be a sequence of numbers that lie between 0 and 1. Refs 1, 2, and 5 discuss some criteria for choosing the four constants of Eq 1. The modulus  $m$  should be as large as possible so that the sequence it generates has a long period. The multiplier  $a$  should lie between  $0.01$  and  $0.99$   $m$ , such that  $a \bmod 8 \neq 5$ . For example, a value of  $a=9821$  satisfies this criteria. The increment  $c$  is immaterial when  $a$  is a good multiplier, except that it must have no factor in common with  $m$ . For example, a value of  $c=6925$  satisfies this criteria.

You may arbitrarily choose the seed value  $x(0)$ . Notice that a given seed value will exactly reproduce the same stream of random numbers. This feature may be useful in those applications where identical random numbers would yield a more precise comparison of the performance of different systems. For most of this article's data, 11186 is the seed value, although several other values were also tested. The linear congruential generator now becomes:

$$x(n+1) = [9821 \times x(n) + 6925] \bmod 2^{15}. \quad (3)$$

The LSBs of the numbers Eq 3 generates are not very random, but cycle with regular patterns. This nonrandom behavior is characteristic of all generators of Eq 1's form, where  $m$  is some integer power of 2.

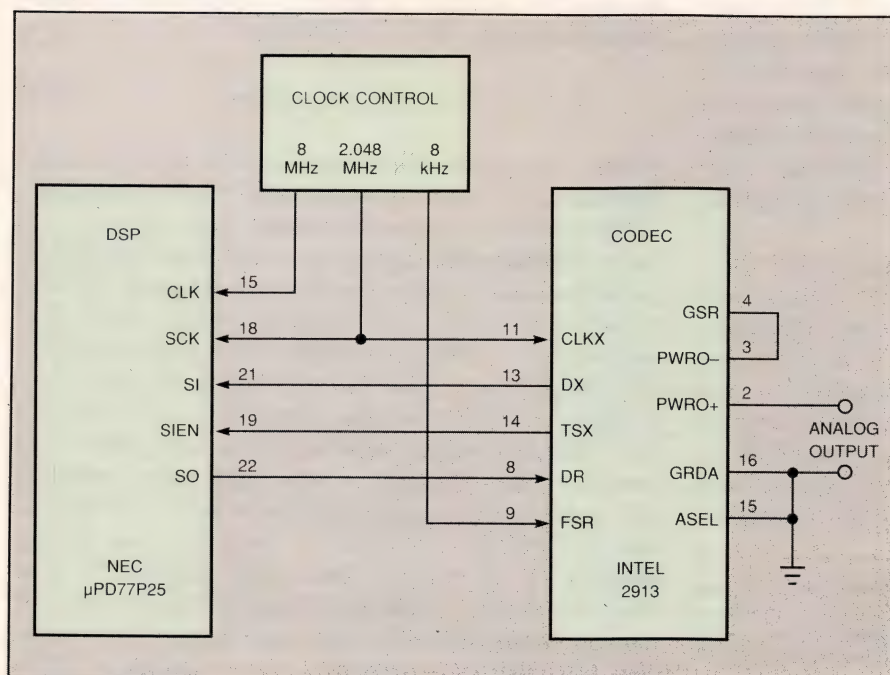


Fig 1—To test the noise produced by the DNG algorithm, we used an existing platform that included the DSP and codec.



# Fixed-point DSP chip can generate real-time random noise

Bill Salibrici, TeleSciences Co Systems

***An inexpensive, 16-bit, fixed-point DSP chip can generate real-time pseudorandom noise signals for testing the performance of telephony systems in the presence of noise.***

As device costs drop and development support grows, DSP chips are finding use in diverse applications, such as in real-time digital waveform synthesis. Increased DSP use raises two questions: Can you exploit the fast multiply-accumulate capability of single-chip DSP devices to generate real-time random noise samples, and, if so, how would the performance compare to a commercially available noise generator? To answer those questions, we wrote and tested a DSP application. This application required a signal plus random noise, as is often needed in testing digital filters used to implement tone detection. We developed the digital noise generator (DNG) algorithm to generate real-time, pseudorandom, uniformly or Gaussian-distributed signals.

We used the  $\mu$ PD77P25, a 16-bit fixed-point DSP chip from NEC Electronics, to test the DNG algorithm. The chip is a second-generation, medium-speed, single-chip device. We chose the chip out of convenience; the hardware platform from an existing application was already available. However, the concepts presented in this article are applicable to other fixed-point, as well as floating-point, DSP chips. Fig 1 shows a block diagram of the hardware used to test the algorithm.

The  $\mu$ PD77P25 has a serial output port that can interface to a simple, low-cost codec, which we used as a DAC.

The codec also contains internal antialiasing filters, which further simplifies the hardware. Other fixed-point DSP chips that include a serial output port are the Analog Devices ADSP-2101, AT&T DSP16, Motorola DSP56000, and Texas Instruments TMS320C25. The sample rate used here is 8 kHz, which means that the highest frequency component contained in any synthesized output waveform must be band limited to 4 kHz or less to prevent aliasing errors.

The linear congruential generator (Refs 1 and 2) was used to generate a uniformly distributed random-number sequence given as follows:

$$x(n+1) = [a \times x(n) + c] \bmod m, \quad (1)$$

where  $a$ ,  $c$ , and  $m$  are constants;  $\bmod$  is the modulus operator;  $n \geq 0$ ; and  $x(0)$  is the seed or starting value.

For properly chosen constants and a given seed value, this algorithm produces a uniformly distributed, pseudorandom sequence of positive integers between 0 and  $m$ . The term pseudorandom simply means that you use a deterministic method to generate a sequence of numbers that appear to be independent draws from a uniform distribution. Eq 1 basically states that you can obtain the next value in the sequence from the previous value through several operations, including the multiply-add combination for which DSP devices are well suited. The modulus operator gives the remainder of one number divided by another. If  $m$  is chosen to be the word size of the DSP chip, then the modulo  $m$  operation becomes quite simple. The operation  $(X) \bmod m$  is accomplished by taking  $m$  LSBs



Software listings for this article are available on EDN's computer bulletin-board system (BBS). Phone (617) 558-4241 with modem setting 300/1200/2400 8,N,1. Access /freeware SIG and specify (r)ead option followed by (k)eyword search for "MS #530".



# Design Engineers Bulletin


New Product and Applications Information for Design Engineers

## New 25ns, 5V, E<sup>2</sup>PROM is world's fastest!

**Turbocharge your DSP and high speed microprocessor design**

**X**icor's new X28TC256 is the first E<sup>2</sup>PROM with access time compatible with Digital Signal Processing (DSP) circuits, and many high-speed microprocessors. The fast access time of the X28TC256 reduces system chip count by eliminating high-speed static RAMs previously required as fast read buffer memories. Sixty-four bytes of data may be read at high-speed before an automatic wait signal indicates the end of sequence. Page-to-page latency time is 150ns after which the 25ns per byte data rate resumes. Full memory read is achieved at TAA (effective) of less than 27ns per byte. The 5-volt X28TC256 does not require the complex write algorithm common to flash-type devices. Internal write cycle controls are fully automatic. User friendly features such as Software Data Protect (SDP) and end of write cycle indication (Data polling) are also standard. The X28TC256 is available in 32-pin DIP or surface mount packages.

The 5-volt X28TC256 Read Access Timing

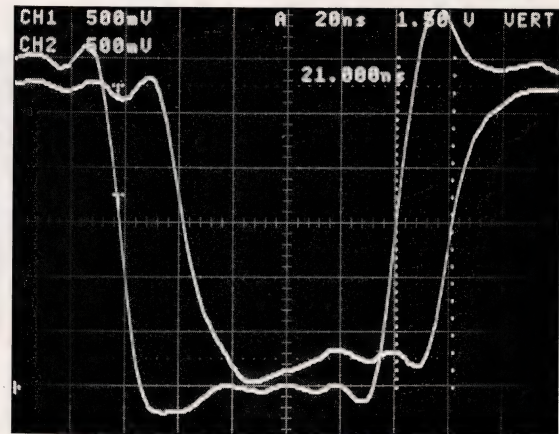


*The X28TC256 improves system chip count by eliminating high-speed static RAM's.*

## Finally, the perfect memory!

**35ns RAM never forgets data on power down**


**T**he AUTOSTORE feature of the X20C17 2K X 8 High Speed Static RAM prevents loss of important data during power-down periods without requiring additional circuitry or components. When the system voltage falls below

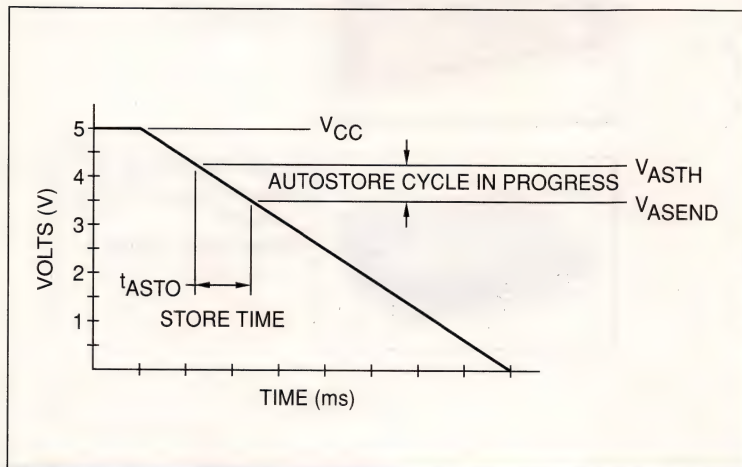4.0 Volts, the X20C17 will automatically capture the data currently in its RAM and store it in E<sup>2</sup>PROM. The store operation is complete in a maximum of 2.5 msec. Once the data is stored in this manner it cannot be forgotten. Data retention is guaranteed to be in excess of 100 years, even at high temperatures. On power-up, the device will recall data from the E<sup>2</sup>PROM into the RAM. In this way, any data that is written into the X20C17 will remain valid until altered by the system regardless of the status of the system supply voltage. The X20C17's fast access time (35 nsec) allows it to be interfaced directly to high speed buses, eliminating the need for external buffering circuitry or wait states.



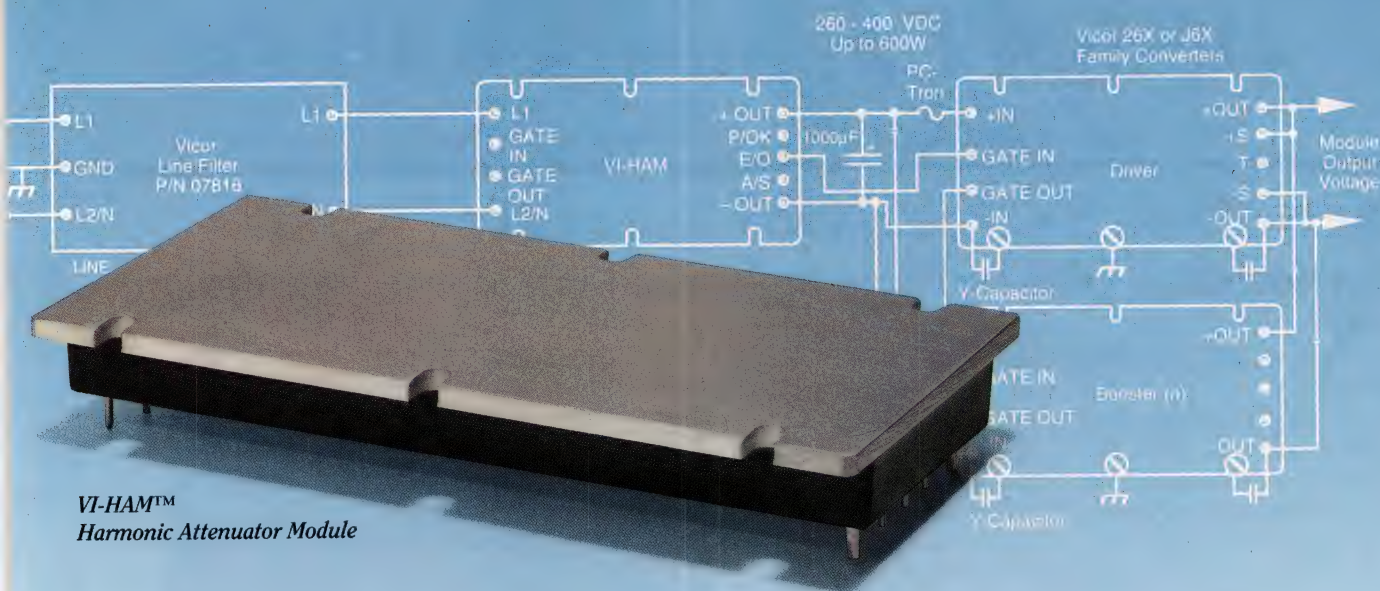*The X20C17 automatically captures data to E<sup>2</sup>PROM cells when system power levels decrease to 4.0V.*





# Unity Power Factor


- Universal Input: 85-264 VAC, 50/60 Hz
- Up to 600 Watts of Power
- Booster Versions Available
- Meets IEC 555
- High Efficiency
- Adaptive Output Voltage Control (Pat. Pend.)
- Input Surge Current Limiting
- Short-Circuit Protection
- Module Enable and Power OK
- Size: 4.6" x 2.4" x 0.5"

Use VI-HAM modules with Vicor VI-26X or VI-J6X MiniMod™ DC-DC converters in booster-expandable arrays to satisfy a wide range of power demands. And when your system has to meet international standards for EMI/RFI emissions, choose the Vicor filter that fits your need.

Build new flexibility into *your* power system designs with the VI-HAM module.  
Call today for details.



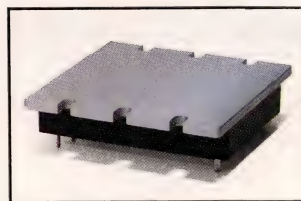**VI-26X DC-DC Converter**  
Output voltages available:  
1-95 VDC  
Output power available:  
50-200 watts



**VI-J6X MiniMod DC-DC Converter**  
Output voltages available:  
1-95 VDC  
Output power available:  
10-100 watts

## Component Solutions For Your Power System

**Vicor Corporation**, 23 Frontage Road, Andover, MA 01810 (508) 470-2900 or (800) 735-6200

Vicor GmbH • Germany • Tel: +49-89-329-2763 • Fax: +49-89-329-2767 Vicor Far East • Taiwan • Tel: +886-2-9188240 • Fax: +886-2-9132982







**AVAILABLE FROM STOCK!**  
**Universal Input & Unity Power Factor**
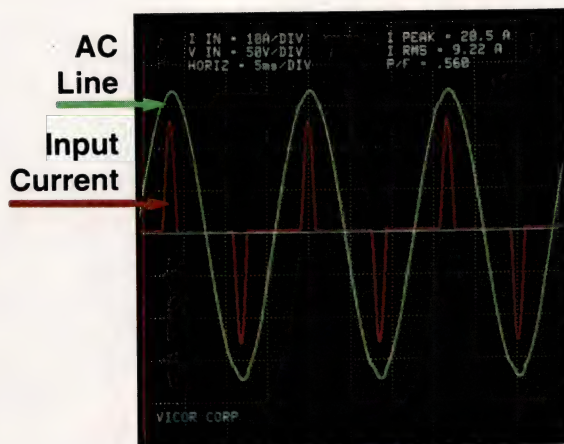
# Component Power Solution

The pressure is on to wring more and more usable power from a standard AC outlet—safely and economically. And to pack the necessary power-processing capability into ever-smaller spaces, preferably at the point of load. Needed: a board-mounted module that offers up to 600 watts of power...power factor of better than 0.99...and power density greater than 100 watts/in<sup>3</sup>.




**No Power Factor Correction**

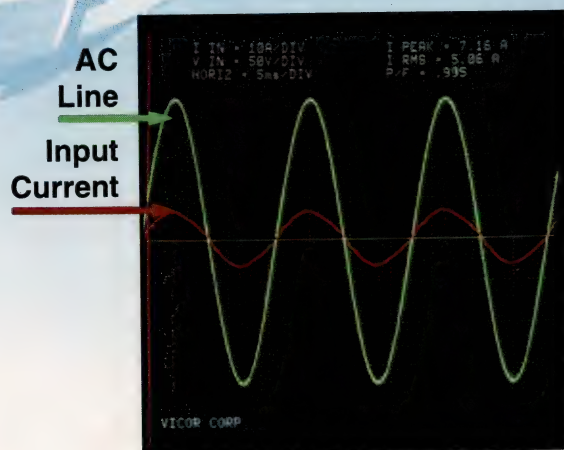

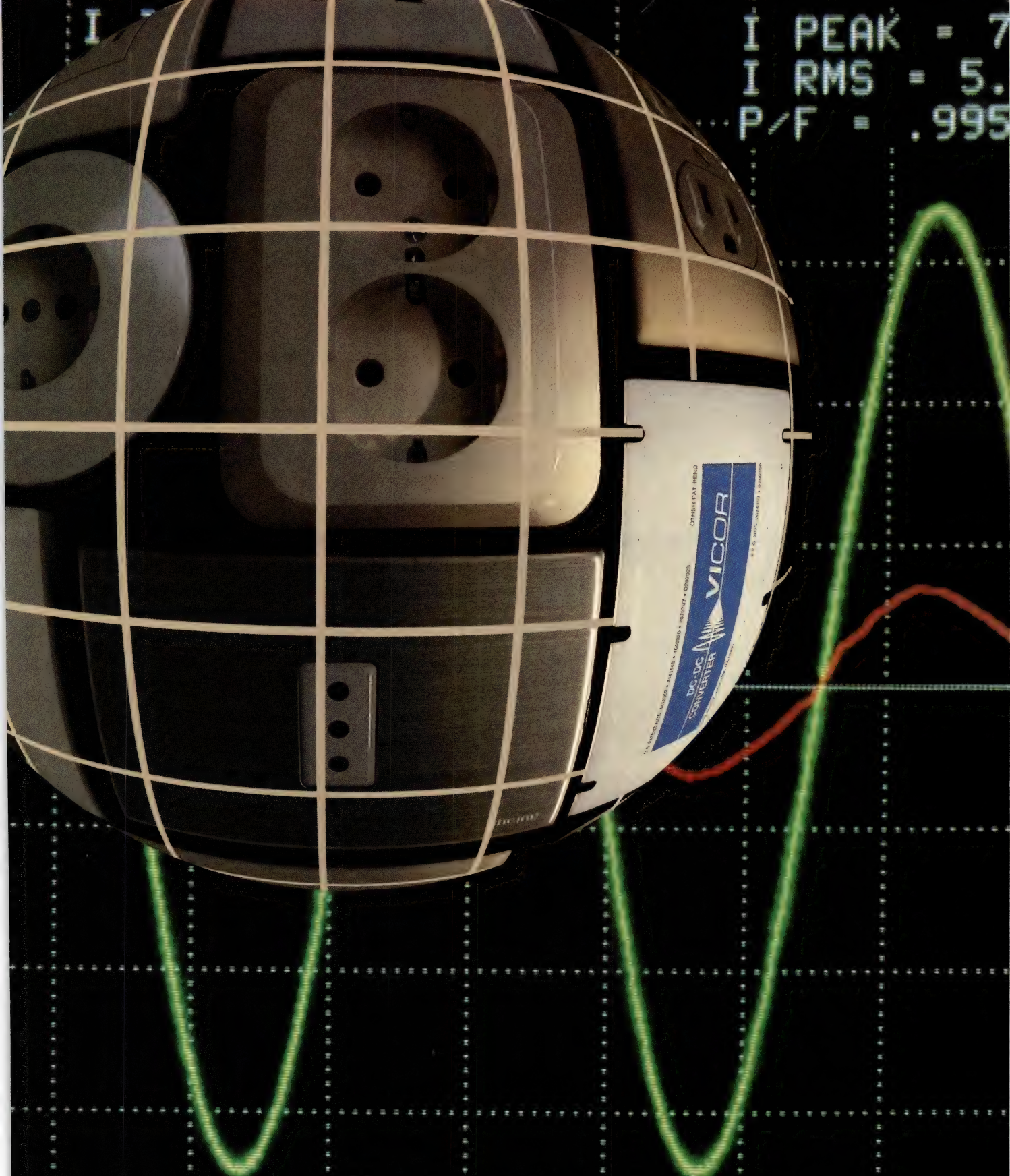**Power Factor Correction with VI-HAM**

Solution: the VI-HAM Harmonic Attenuator Module. This component-level front end—in the industry standard package—provides unity power factor for line powered systems anywhere in the world. Vicor DC-DC converters and VI-HAM modules together create a universal input, off-line switching power supply for systems requiring from hundreds of watts to kilowatts of total power, with any number of outputs, from 1 to 95 VDC.





I PEAK = 7  
I RMS = 5.  
P/F = .995

OTHER DAT. REQ.  
VICOR  
DC-DC CONVERTER  
W. G. MOULDER, INC.

# Universal Input Unity Power Factor

CIRCLE NO. 117

COR CORP



## SIMULATING COMPONENT VARIATIONS WITH SPICE

shows an 8-pole, lowpass Butterworth filter constructed with four Sallen and Key (Refs 4 and 5) low-pass filters. A common perception is that multiple-pole filters produced in volume will not perform reliably because of component variation. The concern is that component variation will distort a filter's performance; poles will shift so much that the filter will no longer be a true Butterworth filter. Monte Carlo analysis can investigate this concern.

Listing 2 models Fig 4's filter circuit using 10% capacitors and 1% resistors, both with uniform distribu-

### Listing 2—Simulation model for an 8-pole Butterworth filter

```

V1 1 0 AC 1.0V ;Input signal is 1 volt

R1 1 2 ONE_PERCENT_R 31.6K ;Sallen and Key Filter #1
R2 2 3 ONE_PERCENT_R 14.3K
C1 2 4 TEN_PERCENT_C 0.082UF
C2 3 0 TEN_PERCENT_C 0.068UF
E1 4 0 (3, 4) 1000K

R3 4 5 ONE_PERCENT_R 22.1K ;Sallen and Key Filter #2
R4 5 6 ONE_PERCENT_R 16.9K
C3 5 7 TEN_PERCENT_C 0.1UF
C4 6 0 TEN_PERCENT_C 0.068UF
E2 7 0 (6, 7) 1000K

R5 7 8 ONE_PERCENT_R 31.6K ;Sallen and Key Filter #3
R6 8 9 ONE_PERCENT_R 13.7K
C5 8 10 TEN_PERCENT_C 0.15UF
C6 9 0 TEN_PERCENT_C 0.039UF
E3 10 0 (9, 10) 1000K

R7 10 11 ONE_PERCENT_R 37.4K ;Sallen and Key Filter #4
R8 11 12 ONE_PERCENT_R 14.7K
C7 11 13 TEN_PERCENT_C 0.39UF
C8 12 0 TEN_PERCENT_C 0.012UF
E4 13 0 (12, 13) 1000K

.MODEL ONE_PERCENT_R RES(R=1 DEV=1%) ;1% uniform distribution
.MODEL TEN_PERCENT_C CAP(C=1 DEV=10%) ;10% uniform distribution

.AC DEC 50 30 300 ;50 points/decade, 30 to 300 Hz
.MC 50 AC V(13) YMAX LIST OUTPUT ALL ;50 runs. Monitor V(13) using
; YMAX collating function

.PROBE V(13) ;Specify PSpice "oscilloscope"

.END

```

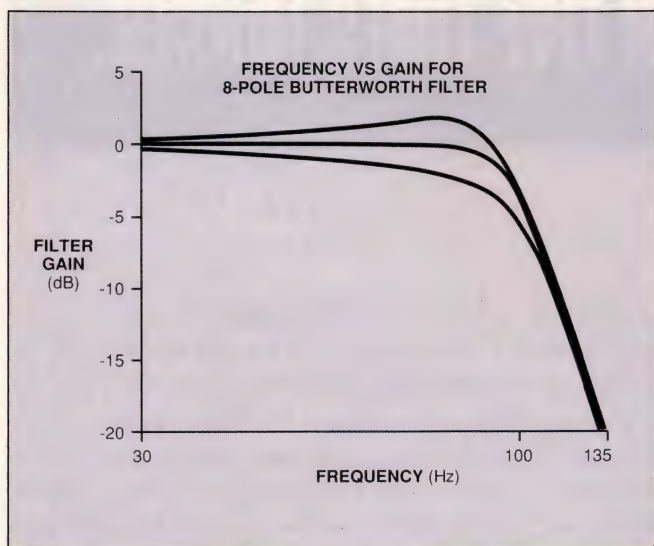


Fig 5—The simulated gain for Fig 4's circuit shows that the circuit does, as intended, behave like a Butterworth filter. The plot shows the results from three of the 25 simulation runs: the run with nominal component values, the run with the lowest gain, and the run with the highest gain.

tions. Again, high-gain voltage-controlled voltage sources replace op amps to simplify the PSpice model. The .AC directive specifies the frequency domain, which is well suited for analyzing filters. The .PROBE directive specifies PSpice's graphical output.

The filter's simulated gain appears in Fig 5. The curves are from three of 25 simulation runs: the run with nominal component values, the run with the lowest gain, and the run with the highest gain. Although the cut-off frequency varies, the filter appears to behave like a Butterworth filter.

Monte Carlo analysis helps you understand the effects of component tolerances on circuits without having to rely on rules of thumb or guesses. Because you'll understand these effects before a circuit goes into production, you can correct many problems in the design phase. And depending on the version of Spice you use, your current circuit models should require only a few changes to let you analyze performance using Monte Carlo techniques.


EDN

### References

1. *The Design Center User's Guide and Reference Manual*, Version 5.1, Microsim Corp, Irvine, CA, 1992.
2. Tuinenga, P W, *Spice: A Guide to Circuit Simulation and Analysis Using PSpice*, Prentice-Hall, Englewood Cliffs, NJ, 1988.
3. Kalos, Malvin H and Paula A Whitlock, *Monte Carlo Methods, Volume 1: Basics*, John Wiley and Sons, New York, NY, 1986.
4. Daryanani, G, *Principles of Active Network Synthesis and Design*, John Wiley and Sons, New York, NY, 1976.
5. Sallen, R P, and E L Key, "A Practical Method of Designing RC Active Filters," *IRE Transactions on Circuit Theory*, CT-2, May 1955, pgs 74-85.
6. Rubinstein, Reuven Y, *Simulation and the Monte Carlo Method*, John Wiley and Sons, New York, NY, 1981.
7. Walpole, Ronald E and Raymond H Myers, *Probability and Statistics for Engineers and Scientists*, Macmillan Publishing Co Inc, New York, NY, 1978.
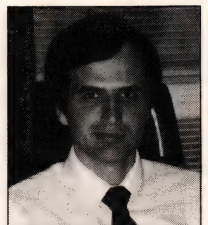
### Author's biography

George Ellis is manager of new product engineering at Kaydon Corp in Blacksburg, VA, where he concentrates on developing data-acquisition systems. George is the author of *Control System Design Guide* (Academic Press Inc, Orlando, FL, 1991). He has BSEE and MSEE degrees from Virginia Polytechnic Institute and State University (Blacksburg, VA).



Article Interest Quotient (Circle One)  
High 506 Medium 507 Low 508





# WITH OMRON SWITCHES, YOUR MOUSE CAN NOW EXPECT TO RUN FIVE TIMES LONGER.



When computer mouse manufacturers needed a tiny, yet highly reliable snap action switch that could stand up to rough, high-frequency switching, they turned to Omron. To meet the challenge, Omron developed the model D2F subminiature switch. With its remarkably small size and incredible life of 5 million operations, the advanced switch really "clicked" with the industry. For advanced switching solutions for the office automation, computer peripheral, appliance and consumer electronics industries, Omron provides the performance you need in basic switches. Choose standard, micro, miniature and subminiature styles in a wide variety of contact configurations, amp ratings, terminal types or actuator styles. With highly automated production and 100% performance testing with zero defects. And with our switch you need — fast. So, if you're find the right switch, call Omron at

**OMRON**  
WE HAVE THE FUTURE IN CONTROL.  
CIRCLE NO. 92

you get consistently high quality large local inventories, you get the tired of running around in circles to 1-800-62-OMRON.

EDN April 29, 1993 • 113



## SIMULATING COMPONENT VARIATIONS WITH SPICE

To compare the many simulations mathematically, Monte Carlo methods use collating functions. Spice programs let you choose a collating function according to the measure of performance you consider most important. For example, if you're simulating a switching circuit, you might want to know when a rising edge occurs. In this case, you can specify that the time of the edge be recorded for each simulation. Different versions of Spice offer different collating functions; for example, PSpice has five to choose from. However, you can choose only one function for per Monte Carlo analysis.

The following examples use an intuitive collating function, called YMAX, which compares simulations. The first simulation run uses nominal values for each component; subsequent runs use random numbers to generate values for all components and their tolerances. The value of YMAX results from comparing the output waveform of each run to that of the first, or nominal, run. The YMAX value is the point of greatest difference between the two waveforms.

### Analyzing circuits

Two examples illustrate Monte Carlo analysis. The first considers the effects of cascaded gain stages; the second examines the effects of component variation in a high-pole-count analog lowpass filter.

A common question among engineers concerns a cascaded op-amp circuit such as the one in Fig 3: If each of the six resistors has 1% tolerance, how much should you expect the overall gain to vary? The easy answer is to assume the worst case:  $\pm 6\%$ . This would occur if R1, R3, and R5 were 1% low, and R2, R4, and R6 were 1% high. It is unlikely that this combination would ever occur, but how much variation would be likely to occur? Monte Carlo analysis answers just such questions.

Listing 1 contains a model for the Monte Carlo analysis of the circuit in Fig 3. Note that high-gain voltage-controlled voltage sources replace the op amps in order

### Listing 1—Simulation model for cascaded op amps

```
V1 1 0 1.00 ;Input signal is 1 volt D.C.
R1 1 2 ONE_PERCENT_R 1K ;Gain stage #1
R2 2 3 ONE_PERCENT_R 1K
E1 3 0 (0, 2) 1000K
R3 3 4 ONE_PERCENT_R 1K ;Gain stage #2
R4 4 5 ONE_PERCENT_R 1K
E2 5 0 (0, 4) 1000K
R5 5 6 ONE_PERCENT_R 1K ;Gain stage #3
R6 6 7 ONE_PERCENT_R 1K
E3 7 0 (0, 6) 1000K
.MODEL ONE_PERCENT_R RES(R=1 DEV=1%) ;1% uniform distribution
.DC V1 0.0 1.0 1.0 ;D.C. analysis at 0 and 1 volt
.MC 250 DC V(7) YMAX LIST OUTPUT ALL ;250 runs. Monitor V(7) using
;YMAX collating function
.END
```

to simplify the PSpice model. Note also that only a few lines make up the Monte Carlo model: an .MC line specifying 250 simulations and the YMAX collating function, and a .MODEL line specifying uniformly distributed  $\pm 1\%$  resistors.

Simulations using this model show that circuit gain varies much more than  $\pm 1\%$ . The greatest variation over 250 simulations is  $+3.9\%$ , and the gain from seven simulations (of 250) varied more than  $\pm 3\%$ .

The results are very different, however, when the circuit's resistors have a normal, rather than uniform, distribution. To change the distribution, you need only modify the .MODEL line to

```
.MODEL ONE_PERCENT_R RES(R=1
DEV/GAUSS=0.25%)
```

With this change, the greatest variation in circuit gain over 250 simulation runs is  $+1.8\%$ , and only 21 runs show gains that vary more than  $\pm 1\%$ .

Simulating the effects of component variation in a filter is another use for Monte Carlo analysis. Fig 4

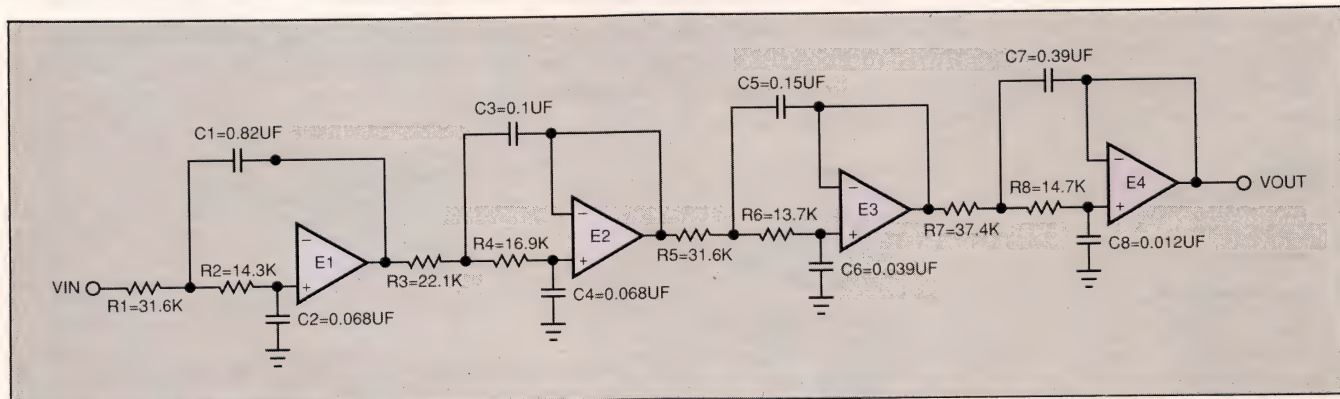


Fig 4—For this 8-pole, lowpass Butterworth filter, Monte Carlo analysis can help determine if the filter's poles will shift so much that the circuit will no longer be a true Butterworth filter.



large volume, you would probably specify a normal distribution. However, if you're using components that have been discriminately selected from a low-yield batch, the distribution will be closer to uniform.


For example, manufacturers may select capacitors with  $\pm 20\%$ ,  $\pm 10\%$ , and  $\pm 5\%$  tolerances from one manufacturing batch. The selected capacitors have a somewhat uniform distribution (Fig 2a); however, the remaining capacitors have a distribution with a "notch" (Fig 2b). To account for a distribution such as this, you have to specify the distribution yourself.

In PSpice, you can divide custom distributions into as many as 100 parts, each part being a section of the distribution curve. You specify the distribution with two  $x,y$  pairs for each part. For example, you can specify a 5-part distribution for  $\pm 20\%$  capacitors (Fig 2c) by using the following statements:

```
.MODEL TWENTY_PERCENT_C CAP(C=1
DEV/BI_MODAL 20%)
.OPTIONS DISTRIBUTION=BI_MODAL
.DISTRIBUTION BI_MODAL (-1, 0) (-0.5, 1) (-0.5, 0)
(0.5, 0) (0.5, 1) (1, 0)
```

One problem with statistical analysis is that component manufacturers usually don't provide distributions. One lot of 20% capacitors may contain a substantial number of 10% capacitors because the manufacturer produced more than enough 10% capacitors to fill orders; the next lot may not have any 10% capacitors.

If you don't know the distribution, you can take a guess; uniform distribution will usually provide reasonable results. If you're especially concerned about a component, you can contact the manufacturer, but

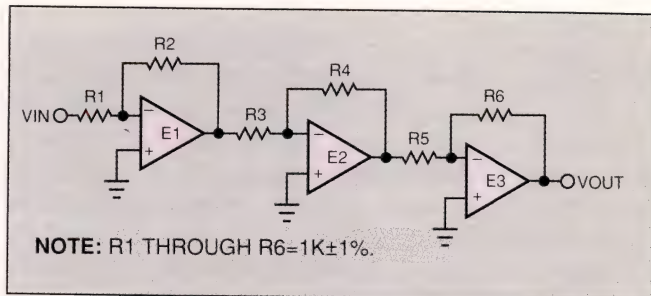

**Fig 3**—In a cascaded op-amp circuit, the tolerances of the resistors combine to affect the circuit's gain. In the worst case, the gain varies by  $\pm 6\%$ ; however, it's likely that the actual variation will be less.

don't expect much help. The manufacturer may provide guidance but probably won't make any commitments.

Spice programs such as PSpice use Monte Carlo analysis to investigate component variations. Monte Carlo analysis, as its name implies, is based on chance. It involves using random numbers in a calculation that has the structure of a statistical, not deterministic, process (Ref 3).

Monte Carlo methods often fall into two categories: solution and simulation. Solutions directly solve a problem, such as determining the numerical value of  $\pi$ . Monte Carlo methods for circuit analysis are in the second category—simulations.

The effects of component tolerances on circuit performance are statistical, and those effects can be characterized by simulating a circuit multiple times. Each time, the simulation generates random numbers to create new values for components with tolerances. The combination of many simulations predicts the range of performance you can expect from the circuit.

## Spice programs with Monte Carlo analysis

Spice programs that include Monte Carlo analysis are available from several vendors, and some programs are available in modestly priced evaluation versions. Evaluation versions let you experiment

before buying a complete package. They usually do everything, or almost everything, that production versions do, but they limit the size and complexity of circuits you can simulate.

For information about Spice programs that feature Monte Carlo analysis, contact the following companies:

**Intusoft**  
2525 S Western Ave, Suite 203  
San Pedro, CA 90732  
(301) 833-0710  
**Circle No. 351**

**Meta-Software Inc**  
1300 White Oaks Rd  
Campbell, CA 95008  
(800) 346-5953  
Fax (408) 371-5100  
**Circle No. 352**

**Microsim Corp**  
20 Fairbanks  
Irvine, CA 92718  
(800) 245-3022  
Fax (714) 770-3022  
**Circle No. 353**

**Spectrum Software**  
1021 S Wolfe Rd  
Sunnyvale, CA 94086  
(408) 738-4387  
**Circle No. 354**

**Tatum Labs Inc**  
3917 Research Park Dr, Suite B-1  
Ann Arbor, MI 48108  
(313) 663-8810  
**Circle No. 355**



## SIMULATING COMPONENT VARIATIONS WITH SPICE

any model by following the parameter with "DEV=nn%". For example, a transformer (K) can have a variable-effective air gap if you add the lines

```
K1 1 2 3 4 VARIABLE_AIR_GAP 100UH
.MODEL VARIABLE_AIR_GAP CORE
(GAP=0.1 DEV=5%)
```

Here, the air gap is 0.1 cm  $\pm 5\%$ .

Sometimes, parameters vary in groups. PSpice provides the LOT directive for these cases. For example, suppose you're using a resistor pack with eight resistors that you know have a tolerance of  $\pm 1\%$  and are matched to be within 0.2% of each other. The resistor model would be

```
.MODEL ONE_PERCENT_RPAK RES(R=1
DEV=.02%
LOT=.08%)
```

With this model, you can specify eight resistors in your circuit. (Actually, this same statement can specify any number of resistors in a pack.) The values of the eight will vary  $\pm 1\%$  from one run to the next, but on any given run, they will vary only  $\pm 0.2\%$  from each other. If the circuit has more than one resistor pack, you need a .MODEL directive for each one. These directives let the resistances of one pack vary from the resistances of a second pack by the full  $\pm 1\%$ .

A component's tolerance describes only the limits of variation. For a complete description, you must also know the statistical distribution—how likely a component is to take on a particular value. (Distribution is

actually the integral of density. However, it is common to refer to a graph of statistical density as a "distribution," and the examples used here follow that conventional usage.)

The simplest distribution is uniform (Fig 1a), in which components are equally likely to take on any value within the tolerance band. PSpice defaults to uniform distributions. PSpice also supports Gaussian, or normal, distributions (Fig 1b), which are the most common distributions in manufacturing.

Gaussian distributions are described by two parameters: the mean, or average (usually represented by  $\bar{x}$  or  $\mu$ ), and the standard deviation ( $\sigma$ ). Components with normal distributions are much more likely to take on values in the center of the tolerance band rather than at the outside edges.

You can specify a normal distribution for  $\pm 1\%$  resistors with the PSpice command

```
.MODEL ONE_PERCENT_GAUSS_R RES(R=1
DEV/GAUSS=0.25%)
```

Here, the resistor values have a normal distribution and  $\sigma = 0.25\%$ . PSpice limits values of normal distributions to  $\pm 4\sigma$ , so ONE\_PERCENT\_GAUSS\_R can vary  $\pm 1\%$ .

Manufacturing tolerances usually have normal distributions, so if you're using a component produced in

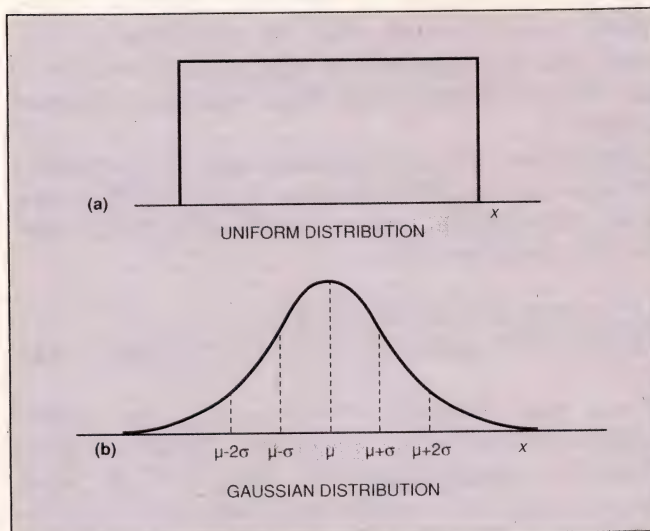


Fig 1—If the statistical distribution of components is uniform (a), then component values are equally likely to have any value within their tolerance band. The Gaussian, or normal, distribution (b) is the most common distribution in manufacturing, however.

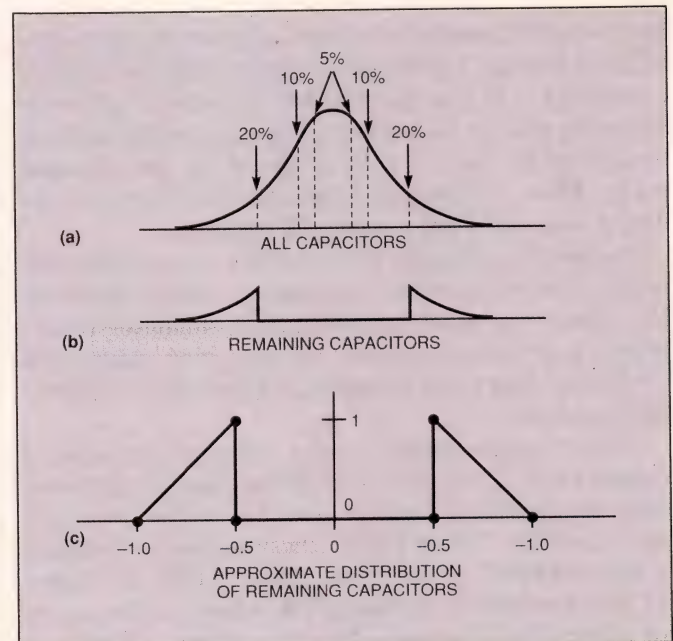


Fig 2—Capacitors with a specified tolerance may have a somewhat uniform distribution that doesn't include the Gaussian curve's "tails" (a). After those capacitors have been removed from a manufacturing batch, the remaining capacitors have a distribution with a "notch" in the middle (b). To account for distributions such as this one in Spice, you have to specify the distributions yourself (c).



# Mathematica

## THE DEFINITIVE SYSTEM FOR TECHNICAL COMPUTATION

**"Not merely a product but a revolution"**

— Macworld


**"The importance of the program cannot be overlooked"**

— New York Times


**Basic function:** Integrated environment for numerical, symbolic, graphical computation, interactive programming.

**Users:** Scientists, engineers, mathematicians, programmers, financial analysts, students. Over 150,000 worldwide. Includes all 50 largest U.S. universities.

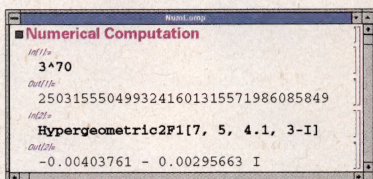**Numerical computation:** Arbitrary-precision arithmetic, complex numbers, special functions (hypergeometric, elliptic, etc.), combinatorial and integer functions. Matrix operations, root finding, function fitting, Fourier transforms, numerical integration, numerical solution of differential equations, function minimization, linear programming.




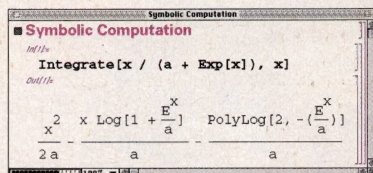**Symbolic computation:** Equation solving, symbolic integration, differentiation, power series, limits. Algebraic operations, polynomial expansion, factorization, simplification. Operations on matrices, tensors, lists, strings.




**Graphics and sound:** 2D, 3D plots of functions, data, geometrical objects. Contour, density plots. 3D rendering with intersecting surfaces, lighting models, symbolic descriptions. Color PostScript output, combining and labeling, publication quality graphics, animation (most versions). Sound from waveforms and data (most versions).

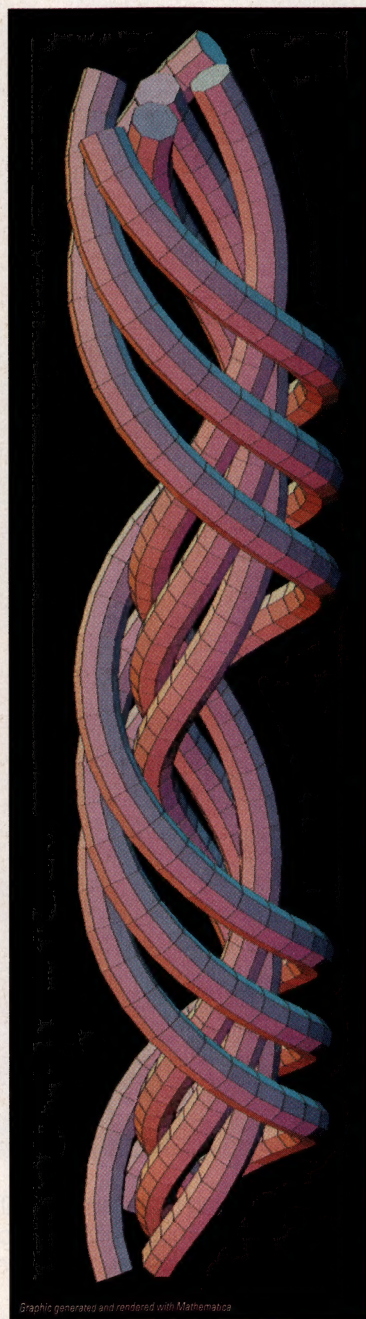**Programming:** High-level, interactive, symbolic language. Procedural and functional program-



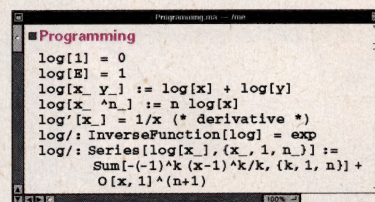ming constructs. Transformation rules and pattern matching. Fully compatible on all platforms. No built-in limitations on computation size.



**External interface:** Input of data (numbers, records, text) from files, programs. Output in TeX, C, Fortran, PostScript. Calling of external programs and functions. General *MathLink*® interprocess communication mechanism.

**User interface:** Electronic book interactive documents mixing text, graphics, animations, calculations. Graphics, animation, sound interapplication compatibility. Style sheets, hierarchical outlining. Computation kernel can run on remote computer (most versions).

**Additional material:** Journal, newsletters, more than 30 books. Add-on packages, free *MathSource*™ electronic resource.

**Versions:** Macintosh • Microsoft Windows • MS-DOS • NEC PC • DEC RISC, VAX • HP • IBM RISC • MIPS • NeXT • SGI • Sony • SPARC, Sun-3 • CONVEX and others • Network licensing available. Student versions. Now shipping Version 2.2.

For the latest information call Wolfram Research at:

**1-800-441-MATH**



### Wolfram Research

**Wolfram Research, Inc.**

100 Trade Center Drive, Champaign, IL 61820-7237, USA  
+1-217-398-0700; fax: +1-217-398-0747; email: info@wri.com

**Wolfram Research Europe Ltd.**

Evenlode Court, Main Road, Long Hanborough, Oxon OX8 2LA, UK  
+44-(0)993-883400; fax: +44-(0)993-883800; email: info-euro@wri.com

Representatives in over 30 countries; contact main office.

© 1993 Wolfram Research, Inc. Mathematica and MathLink are registered trademarks and MathSource is a trademark of Wolfram Research, Inc. Mathematica is not associated with Mathematica Inc., Mathematica Policy Research, Inc., or MathTech, Inc. All other product names mentioned are trademarks of their producers.

CIRCLE NO. 107



# Use Spice to analyze component variations in circuit designs

George Ellis, Kaydon Corp

***If you already use Spice to simulate circuits, you can easily use Monte Carlo methods to investigate the effects of component variation on circuit performance. Modifying your circuit models to do this analysis is only a matter of adding a few lines.***

In the hectic process of design, simulation, prototyping, and testing, it's easy to neglect variations in circuit components. If you do consider variations, you may add some margin to nominal component values and yet be guided by only a rule of thumb or an educated guess. Then, component tolerances can stack up the wrong way and yield unpleasant results.

It's possible, though, to accurately account for component tolerances without expending extraordinary effort. Spice, the most popular circuit simulator today, provides a variety of tools for analyzing component variations. The most powerful of these tools is Monte Carlo analysis.

Circuit performance varies because parameter values vary. The variations either can be deterministic or statistical. Deterministic variations are possible to predict. For example, the resistance of copper is deterministic: It increases about 0.39% for every °C of temperature increase. The effect is the same, for all practical purposes, from one piece of copper to the next.

It's not possible, however, to predict precisely the effects of statistical variations on any given component. Examples of statistical variations include manufacturing tolerance (the variation of values from one unit to

the next) and aging (the variation of values over time). Fortunately, you can analyze statistical variations with Spice.

If you're uncomfortable working with statistical variation, it may be because the analysis tools seem mysterious. However, if you already use Spice to simulate your circuits, you may be surprised to learn how easily Spice can simulate variations. In fact, you will probably need to make only a few modifications to your circuit models to investigate the most important sources of variation.

The examples presented here use PSpice (Refs 1 and 2), a version of Spice from Microsim Corp. The implementation of variation analysis differs among Spice versions, but the principles are the same. You should be able to apply this information to any version of Spice that offers statistical-variation analysis.

PSpice lets you add a tolerance value to any parameter by using the DEV directive in the .MODEL command. For example, you can specify a 1%, 20-k $\Omega$  resistor with these two lines:

```
R1 1 2 ONE_PERCENT_R 20K
.MODEL ONE_PERCENT_R RES(R=1 DEV=1%)
```

When you simulate the circuit, the "ONE\_PERCENT\_R" in the specification for R1 will point PSpice to a model named ONE\_PERCENT\_R, which shows that R, the resistance multiplier, has a 1% device tolerance. (Incidentally, the character string "ONE\_PERCENT\_R" has no meaning itself; any name would have worked.)

The DEV directive can apply to any parameter in



**.75 A or 1.5 A**

**45 V**

## THE POWER TO DRIVE 2 WINDINGS WITH ONE IC

### 2916, 2917, & 2918 Dual Full-Bridge PWM Motor Drivers

#### FEATURES

- For Bipolar Stepper Motors or For Two DC Motors
- $\pm 0.75$  A or  $\pm 1.5$  A Continuous Output Current
- 45 V Output Sustaining Voltage
- Internal PWM Current Control
- Internal Clamp Diodes
- Internal Thermal Shutdown

#### Circuitry Elegantly Engineered To Meet Your System Requirements

Containing two full bridges, the Allegro's 2916, 2917, & 2918 motor drivers are designed to drive both windings of a bipolar stepper motor or bidirectionally control two dc motors. Each bridge is capable of sustaining

45 V and includes internal pulse-width modulation (PWM) control of the output current to  $\pm 0.75$  A (2916) or  $\pm 1.5$  A (2917, 2918). Current is determined by the user's selection of a reference voltage and sensing resistor. Included on chip are ground clamp and flyback diodes for protection against inductive transients. Internally generated delays prevent cross-over currents when switching current direction. Thermal protection circuitry disables the outputs if the chip temperature exceeds safe operating limits.

#### Designed For Manufacturability

Allegro's ICs are "designed-for-manufacturability" under stringent standards of Total-Quality. Design/Production teams, under our

PACE (Product And Cycle-time Excellence) program, work closely with our customers to meet their time-to-market and quality/reliability objectives.

Headquartered in Worcester, Massachusetts, Allegro operates two Wafer-fabrication plants as well as assembly/test facilities. Design centers are located worldwide, sharing common cell libraries and design tools.

#### Take A Test-Drive... Call For Samples

Samples are available now. Just give us a call at 1•508•ALLEGRO and we'll have our Sample Pack in the mail to you the same day. After all, the measure of our success can only be *your total satisfaction*.

## THE PACE QUICKENS



Formerly Sprague Semiconductor Group

**CALL 1 • 508 • ALLEGRO**

115 Northeast Cutoff, Worcester, Massachusetts 01615

CIRCLE NO. 104



# To control vibration, get your hands on this brochure.

Improve product performance with  
**Scotchdamp™ brand Vibration Control Systems**



# 3M

Discover why more engineers are designing Scotchdamp™ brand Vibration Control Materials into electronic equipment. From disk drives and circuit boards, to video cameras, sensitive measuring devices and even jet engines, thin, light-

weight 3M damping materials efficiently dissipate vibrational energy. Mechanical fatigue, performance loss and unwanted noise are virtually eliminated.

For a free brochure loaded with application and technical information, circle

the number below, call 612-733-4076 or write: Vibration Control Systems, 3M Industrial Tape and Specialties Division, 3M Center Bldg. 220-8E-04, St. Paul, MN 55144-1000. Our FAX number is 612-733-0729.